

Sequential Design

ELEC 311


Digital Logic and Circuits

Dr. Ron Hayne

Images Courtesy of Cengage Learning



Sequential Circuits

 

Design Example

◆ 2-bit Variable Counter

X1	X0	Function	Ex. Sequence (Z1 Z0)
0	0	down	00, 11, 10, 01, 00, ...
0	1	up	00, 01, 10, 11, 00, ...
1	0	down, even	00, 10, 00, 10, 00, ...
1	1	up, odd	01, 11, 01, 11, 01, ...

State Assignment: $Q1\ Q0 = Z1\ Z0$

Transition Table (1)

	Inputs		PS		NS	
mt	X1	X0	Q1	Q0	Q1+	Q0+
0	0	0	0	0		
1	0	0	0	1		
2	0	0	1	0		
3	0	0	1	1		
4	0	1	0	0		
5	0	1	0	1		
6	0	1	1	0		
7	0	1	1	1		

Transition Table (1)

	Inputs		PS		NS	
mt	X1	X0	Q1	Q0	Q1+	Q0+
0	0	0	0	0	1	1
1	0	0	0	1	0	0
2	0	0	1	0	0	1
3	0	0	1	1	1	0
4	0	1	0	0		
5	0	1	0	1		
6	0	1	1	0		
7	0	1	1	1		

Transition Table (1)

	Inputs		PS		NS	
mt	X1	X0	Q1	Q0	Q1+	Q0+
0	0	0	0	0	1	1
1	0	0	0	1	0	0
2	0	0	1	0	0	1
3	0	0	1	1	1	0
4	0	1	0	0	0	1
5	0	1	0	1	1	0
6	0	1	1	0	1	1
7	0	1	1	1	0	0

Transition Table (2)

	Inputs		PS		NS	
mt	X1	X0	Q1	Q0	Q1+	Q0+
8	1	0	0	0		
9	1	0	0	1		
10	1	0	1	0		
11	1	0	1	1		
12	1	1	0	0		
13	1	1	0	1		
14	1	1	1	0		
15	1	1	1	1		

Transition Table (2)

	Inputs		PS		NS	
mt	X1	X0	Q1	Q0	Q1+	Q0+
8	1	0	0	0	1	0
9	1	0	0	1	0	0
10	1	0	1	0	0	0
11	1	0	1	1	1	0
12	1	1	0	0		
13	1	1	0	1		
14	1	1	1	0		
15	1	1	1	1		


Transition Table (2)

	Inputs		PS		NS	
mt	X1	X0	Q1	Q0	Q1+	Q0+
8	1	0	0	0	1	0
9	1	0	0	1	0	0
10	1	0	1	0	0	0
11	1	0	1	1	1	0
12	1	1	0	0	0	1
13	1	1	0	1	1	1
14	1	1	1	0	1	1
15	1	1	1	1	0	1


Next State (FF) Equations

- ♦ $D1(X1, X0, Q1, Q0) = Q1^+ = \Sigma m(0, 3, 5, 6, 8, 11, 13, 14)$
- ♦ $D0(X1, X0, Q1, Q0) = Q0^+ = \Sigma m(0, 2, 4, 6, 12, 13, 14, 15)$
- ♦ $D1 = (X0' \cdot Q1' \cdot Q0') + (X0 \cdot Q1' \cdot Q0) +$
 $(X0' \cdot Q1 \cdot Q0) + (X0 \cdot Q1 \cdot Q0')$
- ♦ $D0 = (X1' \cdot Q0') + (X1 \cdot X0)$

Xilinx CPLD Implementation

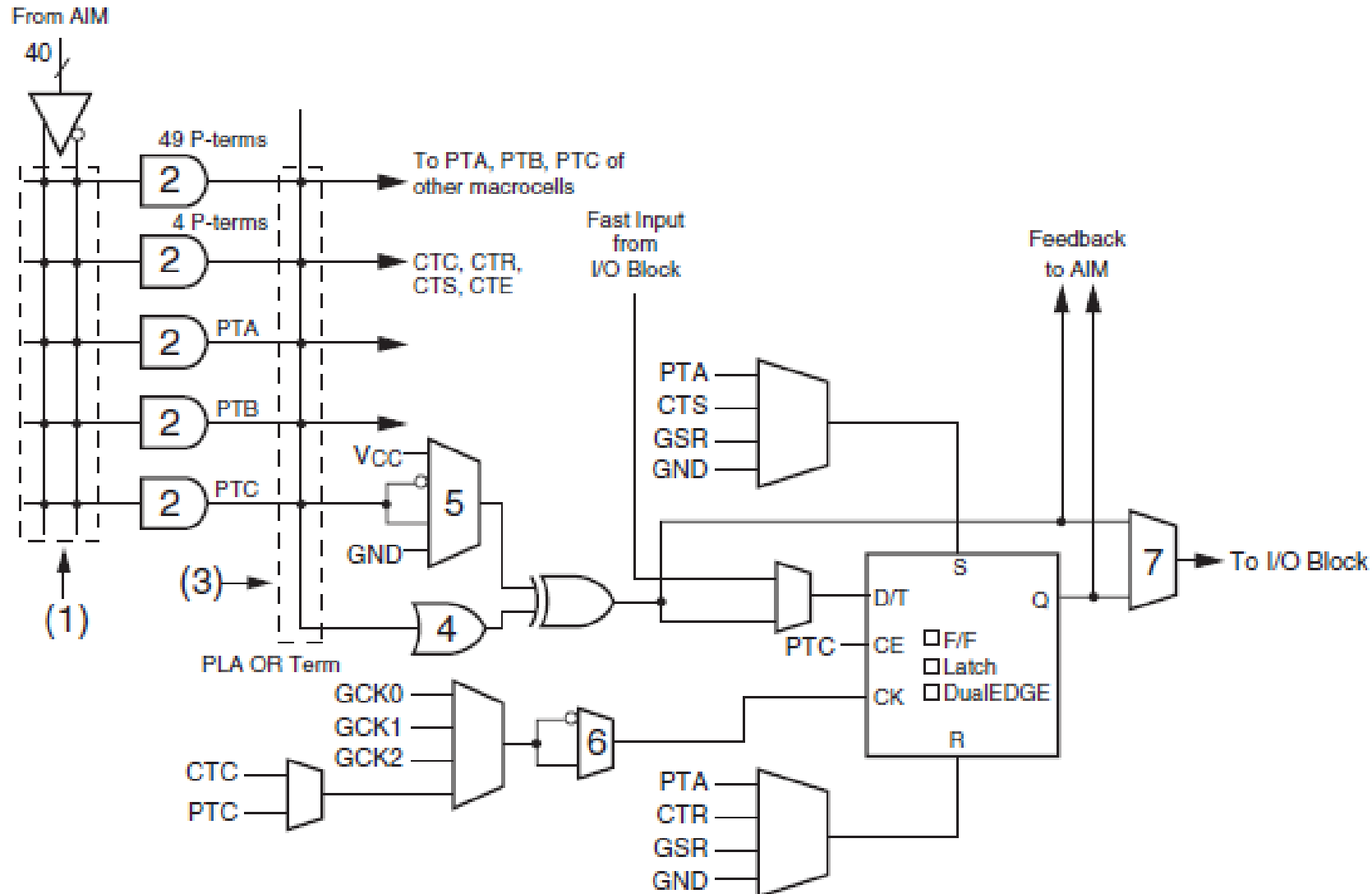

Xilinx FPGA Implementation

 


UNISIM Library Components

◆ FDC

- D Flip-Flop with Asynchronous Clear
 
```
component FDC
  port (Q : out STD_LOGIC;
        C : in STD_LOGIC;
        CLR : in STD_LOGIC;
        D : in STD_LOGIC);
end component;
```



VHDL Package

- ◆ project4_pkg.vhd
 - Clock Divider

```
component CLK_DIV
    port (CLK_IN   : in std_logic;
          CLK_OUT  : out std_logic );
end component;
```

VHDL Model

```
library UNISIM;
use UNISIM.VComponents.all;
use work.Project4_Pkg.all;

entity Counter is
    Port ( X : in std_logic_vector(1 downto 0);
          CLR : in std_logic;
          CLK : in std_logic;
          Z : out std_logic_vector(1 downto 0));
end Counter;

architecture DATAFLOW of Counter is
    signal D : std_logic_vector(1 downto 0);
    signal Q : std_logic_vector(1 downto 0);
    signal SLOW_CLK : std_logic;
```

VHDL Model

begin

```
D(1) <= (not X(0) and not Q(1) and not Q(0)) or  
        (X(0) and not Q(1) and Q(0)) or  
        (not X(0) and Q(1) and Q(0)) or  
        (X(0) and Q(1) and not Q(0));
```

```
D(0) <= (not X(1) and not Q(0)) or  
        (X(1) and X(0));
```

```
CDIV : CLK_DIV port map (CLK, SLOW_CLK);
```

```
FF1 : FDC port map (Q(1), SLOW_CLK, CLR, D(1));
```

```
FF0 : FDC port map (Q(0), SLOW_CLK, CLR, D(0));
```

```
Z <= Q;
```

end DATAFLOW;

Summary

- ◆ Design Example
 - Functional Description
 - Transition Table
 - Next State Equations
 - FPGA Implementation
 - VHDL Model