

ELEC-311
Project 3
Adder-Subtractor

Charles Pittman

October 29, 2013

1 Objective

- Design a combinational logic circuit that adds, or subtracts, two 4-bit 2's complement numbers
- Describe the circuit using VHDL

2 Discussion

The circuit to be constructed was a 2-bit comparator. A 2-bit comparator takes two 2-bit numbers, $P = P_1P_0$ and $Q = Q_1Q_0$, and produces an output, $GT = 1 \iff P > Q$. The truth table describing this function is shown in Table ???. This can be displayed more concisely as a summation of min-terms: $\sum_m(P_1, P_0, Q_1, Q_0) = (4, 8, 9, 12, 13, 14)$.

Using a Karnaugh map (Fig ??), a minimal form of the function was found: $GT = P_0Q_1Q_0 + P_1P_0Q_0 + P_1Q_1$. This function was then translated into the circuit shown in Fig ??.

The NAND gate is considered to be a functionally complete set because any logic function can be created with only NAND gates. This is demonstrated graphically in Figure ??. Using these conversions, the circuit was again translated into one using only NAND gates (Fig ??), and truth table verified (not shown).

3 Results

X	Y	X	Y	X + Y	X - Y
3	1	0011	0001	0100	0010
1	5	0001	0101	0110	1100
-2	3	1110	0011	0001	1011
-2	-4	1110	1100	1010	0010
4	6	0100	0110	01010	1110

Table 1: Test vectors and expected values.

4 VHDL

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;
use work.project3_gates.all;

entity circuit is
  port (X      : in  std_logic_vector(3 downto 0);
        Y      : in  std_logic_vector(3 downto 0);
```

```

        Z      : out std_logic_vector(3 downto 0);
        SEL    : in  std_logic;
        Cout   : out std_logic);
end circuit;

architecture Structural of circuit is

    signal C : std_logic_vector(2 downto 0);
    signal S : std_logic_vector(3 downto 0);

begin

    x3 : ExclusiveOR port map(SEL, Y(3), S(3));
    x2 : ExclusiveOR port map(SEL, Y(2), S(2));
    x1 : ExclusiveOR port map(SEL, Y(1), S(1));
    x0 : ExclusiveOR port map(SEL, Y(0), S(0));

    fa3 : FullAdder port map(X(3), S(3), C(2), Cout, Z(3));
    fa2 : FullAdder port map(X(2), S(2), C(1), C(2), Z(2));
    fa1 : FullAdder port map(X(1), S(1), C(0), C(1), Z(1));
    fa0 : FullAdder port map(X(0), S(0), SEL, C(0), Z(0));

end Structural;

```

 


Figure 1: 4-bit adder/subtractor.