
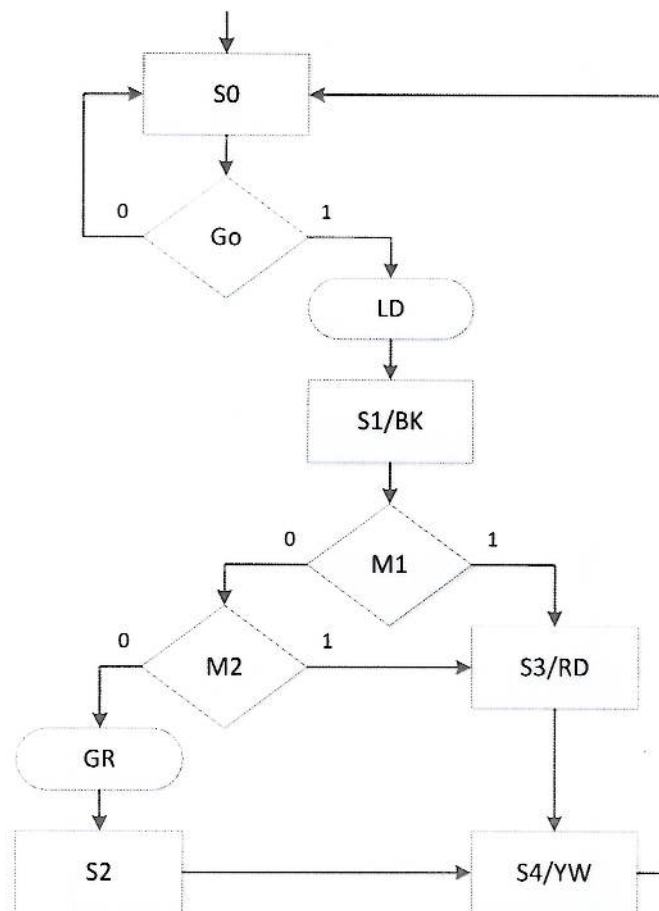


Given the following SM Chart:

 

1. Write a complete VHDL model (entity and behavioral architecture) for the controller. Use two processes for the combinational and sequential parts of the circuit.
2. Realize the controller using a two-address microprogram.
 - a) Convert the SM chart to proper form by adding a minimum number of states.
 - b) Write the microprogram required to implement the circuit.

①



entity Controller is

port (Go, CLK : in bit;

M : in bit-vector (1 to 2);

LD, BK, GR, RD, YW : out bit);

end Controller;

architecture Behave of Controller is

signal PS, NS : integer 0 to 4;

begin

process (Go, M, PS)

begin

LD <= '0'; BK <= '0'; GR <= '0'; RD <= '0'; YW <= '0';

case PS in

when 0 =>

if Go = '0' then

NS <= 0;

else

LD <= '1'; NS <= 1;

end if;

when 1 =>

BK <= '1';

if $m(1) = '0'$ then

if $m(2) = '0'$ then

$GR \leq '1'; NS \leq 2;$

else

$NS \leq 3;$

end if;

else

$NS \leq 3;$

end if;

when $2 \Rightarrow$

$NS \leq 4;$

when $3 \Rightarrow$

$RD \leq '1'; NS \leq 4;$

when $4 \Rightarrow$

$YW \leq '1'; NS \leq 0;$

end case

end process;

process (clk)

begin

if rising-edge (clk) then


$PS \leq NS;$

end if;

end process;

end Behavioral;

(2) a)

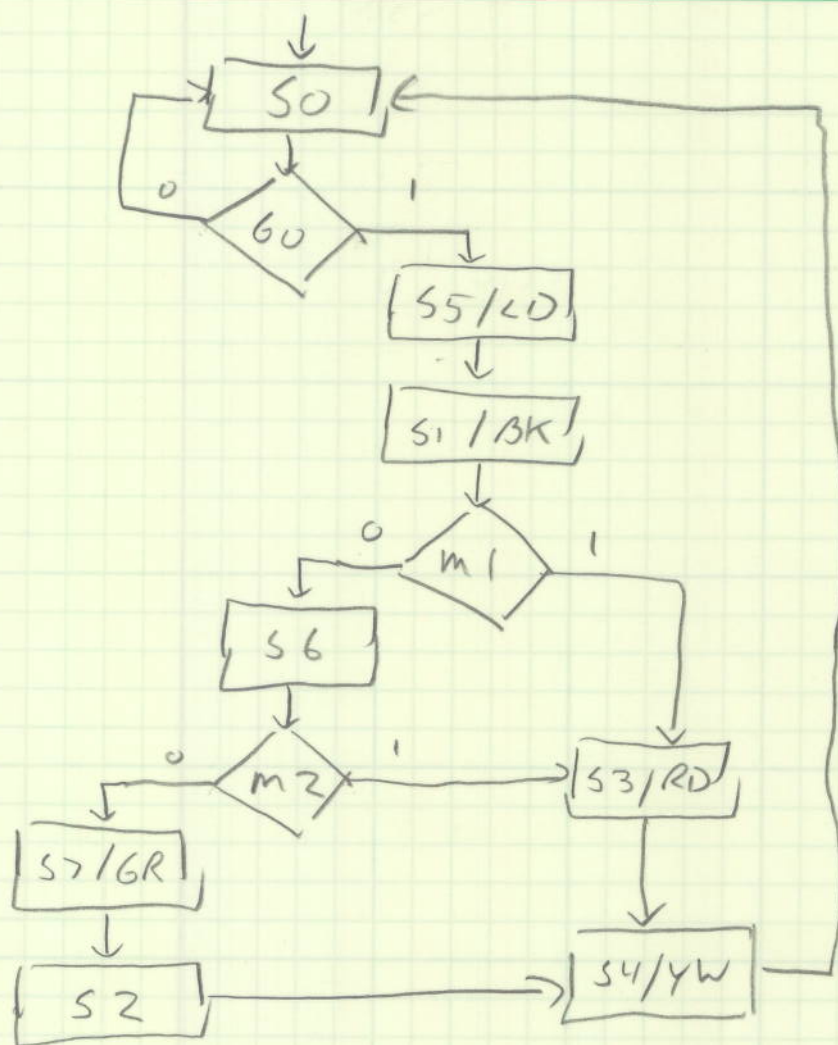

TEST	
00	G0
01	m1
10	m2
11	1

b)

STATE	APPR	TEST	NSF	NST	LD	BK	GR	RD	YW
S0	000	00	000	101	0	0	0	0	0
S1	001	01	110	011	0	1	0	0	0
S2	010	11	100	100	0	0	0	0	0
S3	011	11	100	100	0	0	0	1	0
S4	100	11	000	000	0	0	0	0	1
S5	101	11	001	001	1	0	0	0	0
S6	110	10	111	011	0	0	0	0	0
S7	111	11	100	100	0	0	1	0	0