

Sequential Design

ELEC 311

Digital Logic and Circuits


Dr. Ron Hayne

Images Courtesy of Cengage Learning




Sequence Detector

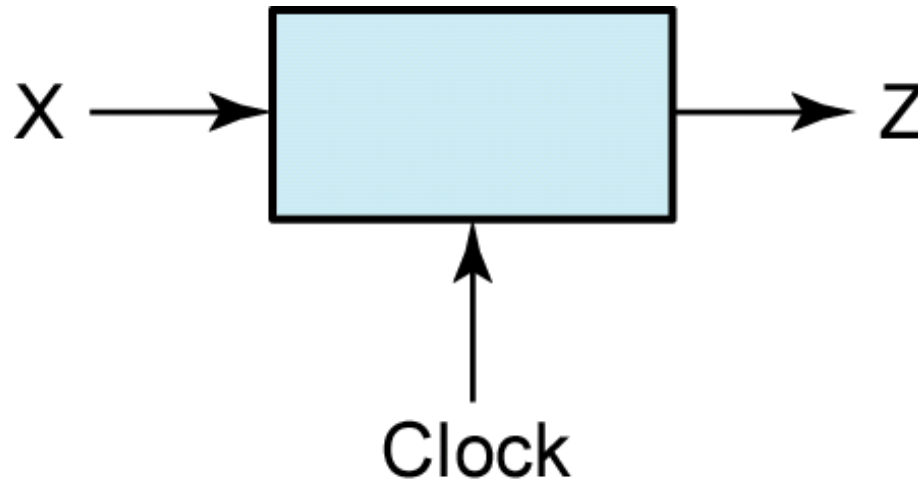
- ◆ Design a circuit that will produce an output $Z=1$ for any sequence (X) ending in 101
 - The circuit does not reset when a 1 output occurs



State Graph

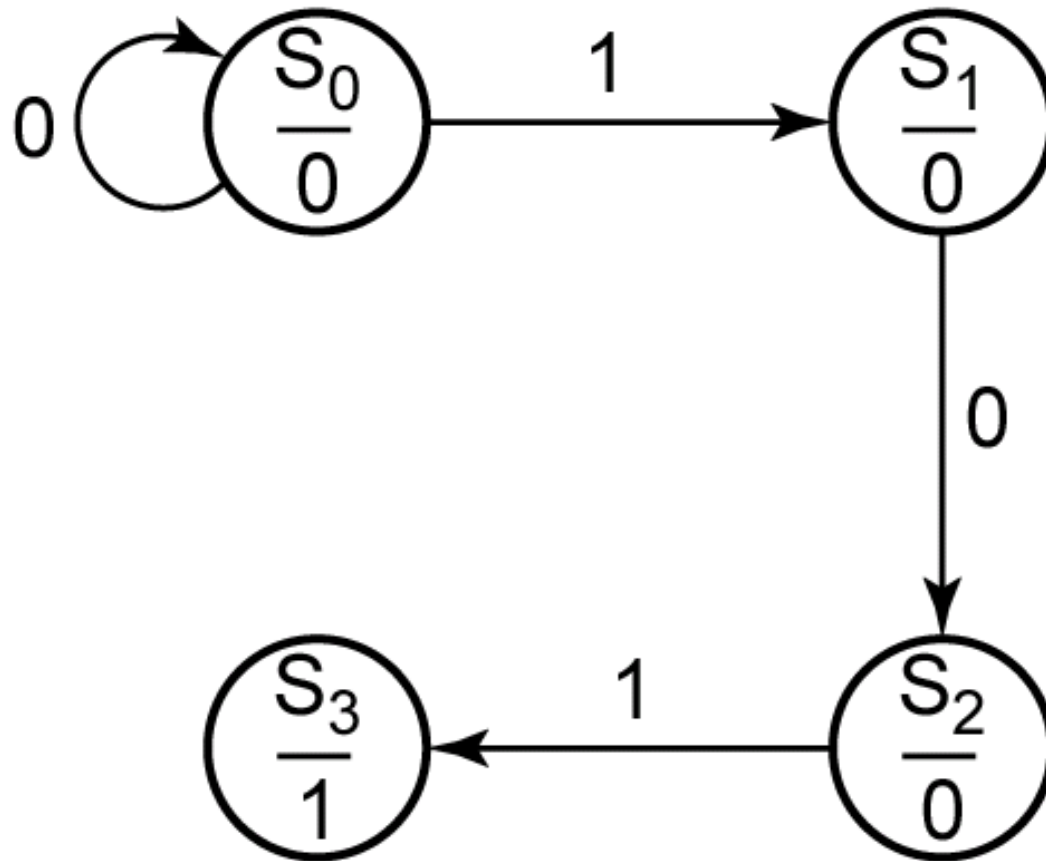


State Graph

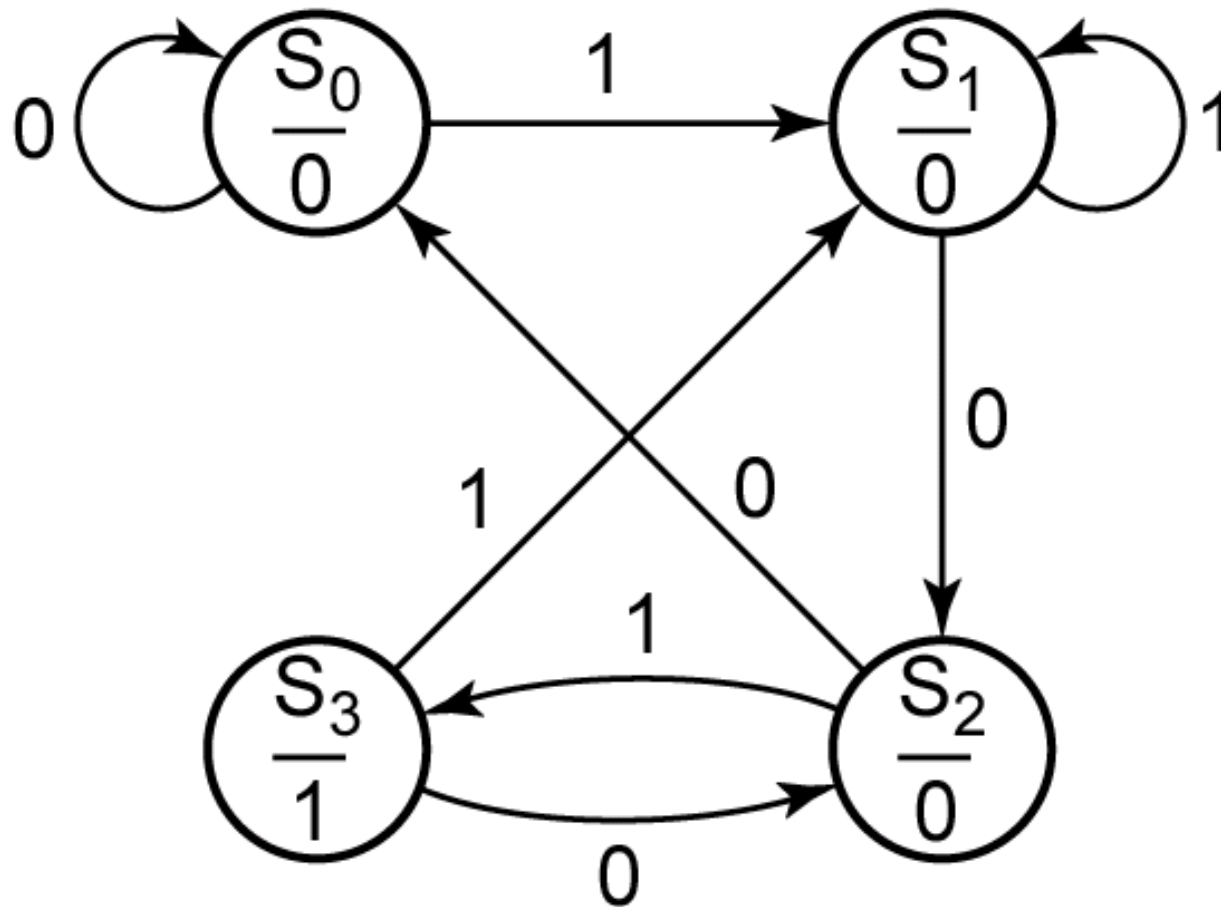

State Table

Present State	Next State		Present Output(Z)
	$X = 0$	$X = 1$	
S_0	S_0	S_1	0
S_1	S_2	S_1	0
S_2	S_0	S_3	0
S_3	S_2	S_1	1

Sequential Circuits

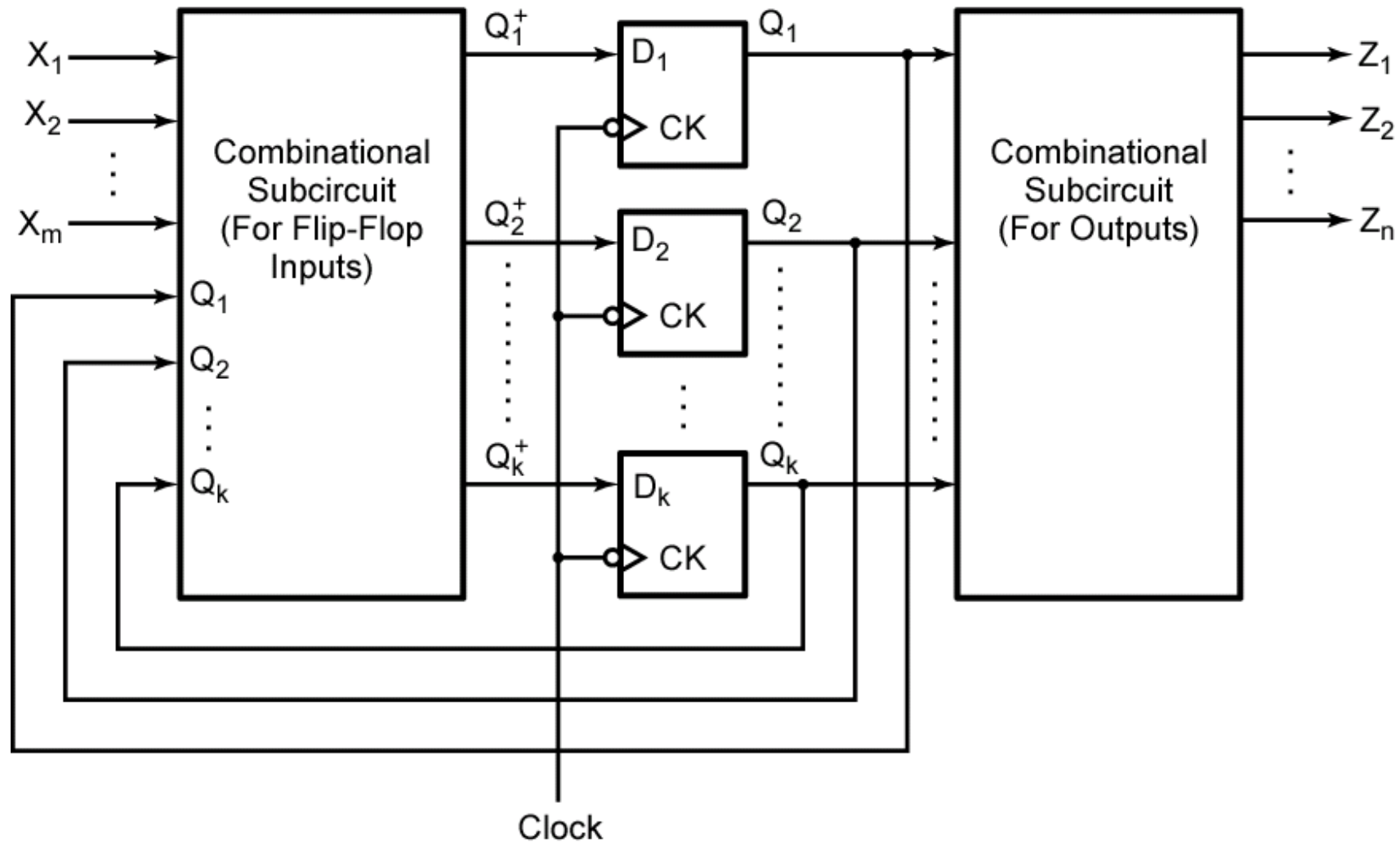


Serial Data Transmission


FIGURE 14-19

Serial Data
Transmission

© Cengage Learning 2014

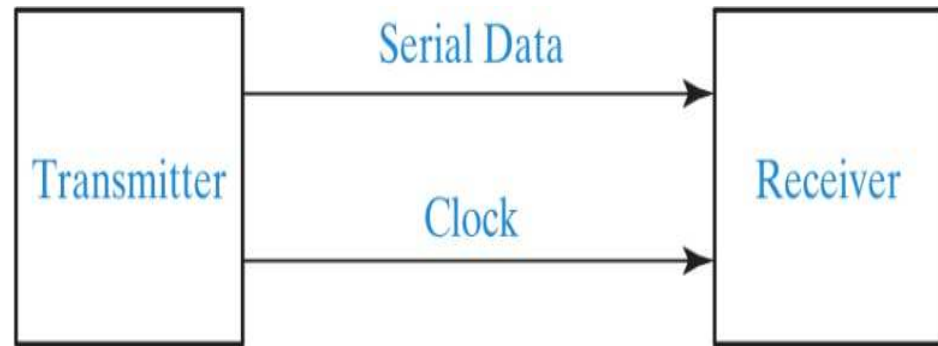

(a)

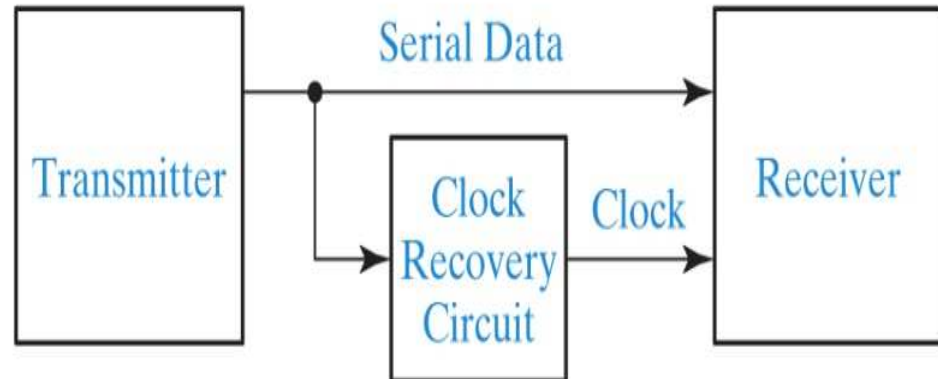


(b)

Serial Data Coding Schemes

FIGURE 14-20
Coding Schemes
for Serial Data
Transmission

© Cengage Learning 2014

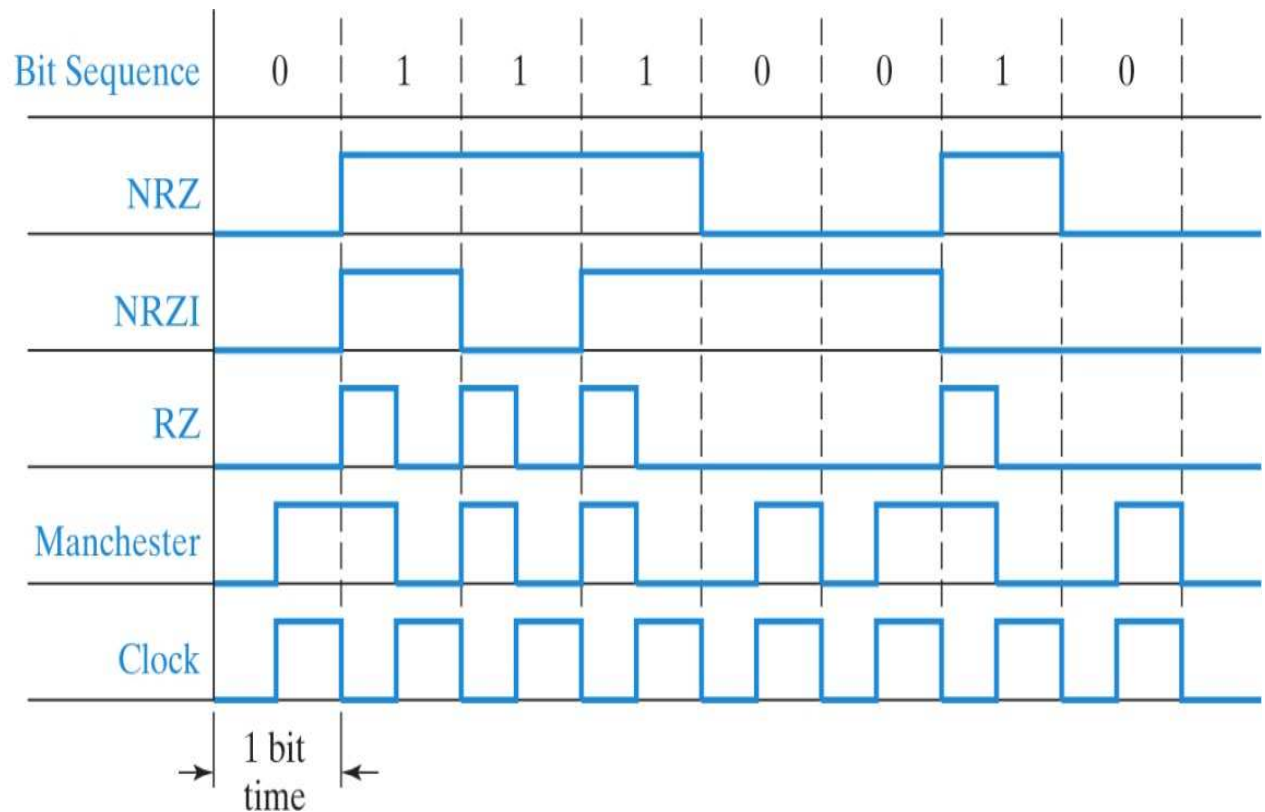

NRZ to Manchester Conversion



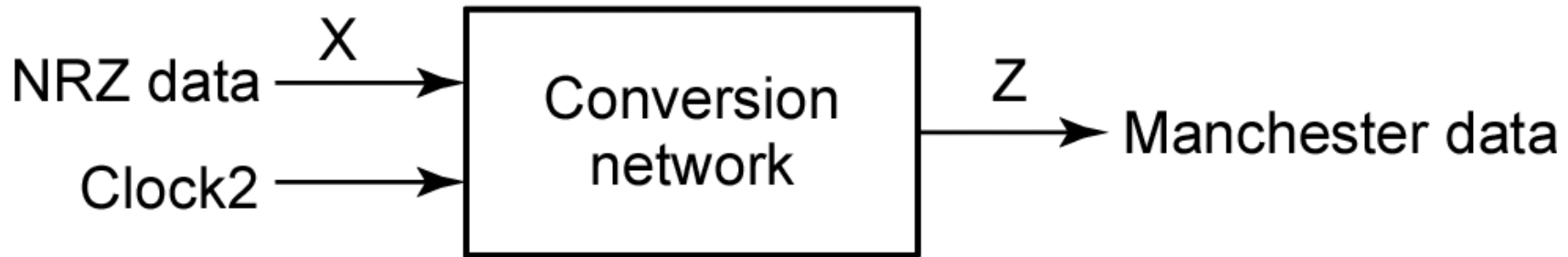


FIGURE 14-22
Moore Circuit for
NRZ to Manchester
Conversion
© Cengage Learning 2014

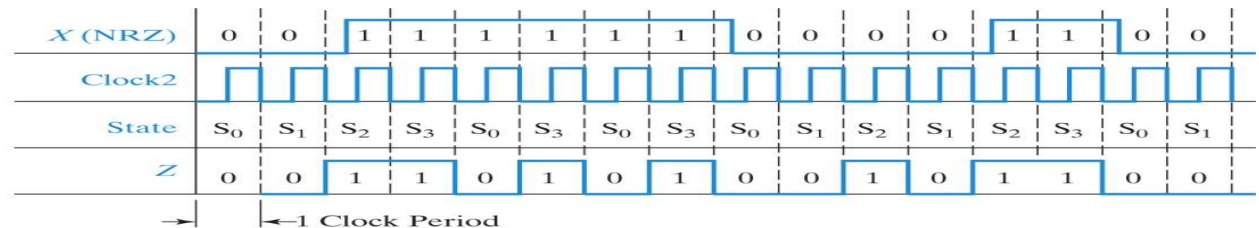

(a) Timing chart

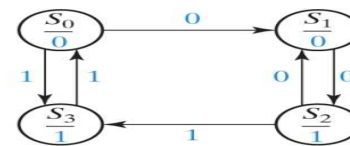


(b) State graph


Present State	Next State		Present Output (Z)
	X = 0	X = 1	
S_0	S_1	S_3	0
S_1	S_2	—	0
S_2	S_1	S_3	1
S_3	—	S_0	1

(c) State table

State Graphs

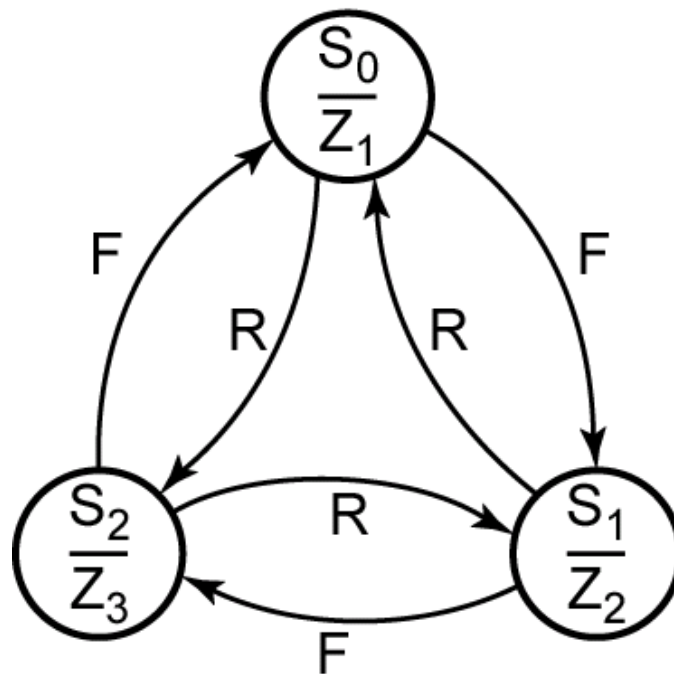

State Graphs

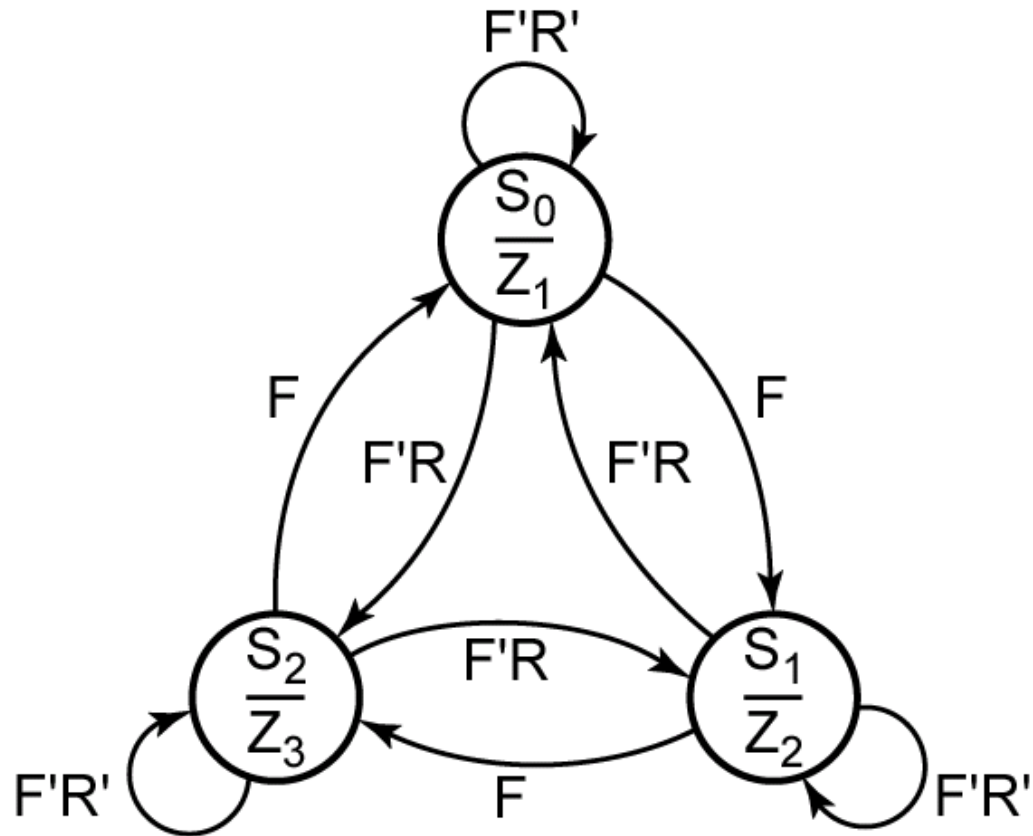

Summary

- ◆ Sequential Design
 - State Graph
 - State Table
 - Transition Table
 - Next State Maps
 - Sequential Circuit