

Additional VHDL


ELEC 418

Advanced Digital Systems


Dr. Ron Hayne

Images Courtesy of Thomson Engineering

Tristate Logic and Busses

 

<i>B</i>	<i>A</i>	<i>C</i>
0	0	Hi-Z
0	1	Hi-Z
1	0	0
1	1	1

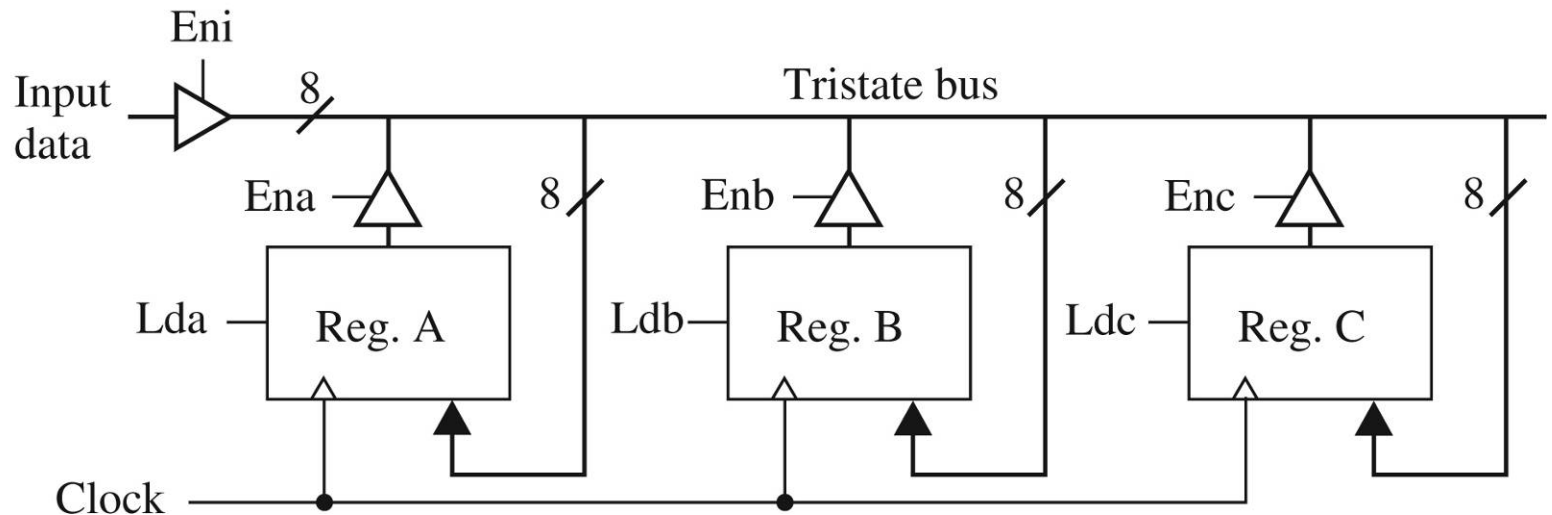


IEEE 1164 Standard Logic

◆ 9-Valued Logic System

- 'U' Uninitialized
- 'X' Forcing Unknown
- '0' Forcing 0
- '1' Forcing 1
- 'Z' High Impedance
- 'W' Weak Unknown
- 'L' Weak 0
- 'H' Weak 1
- '-' Don't Care

SRAM Model

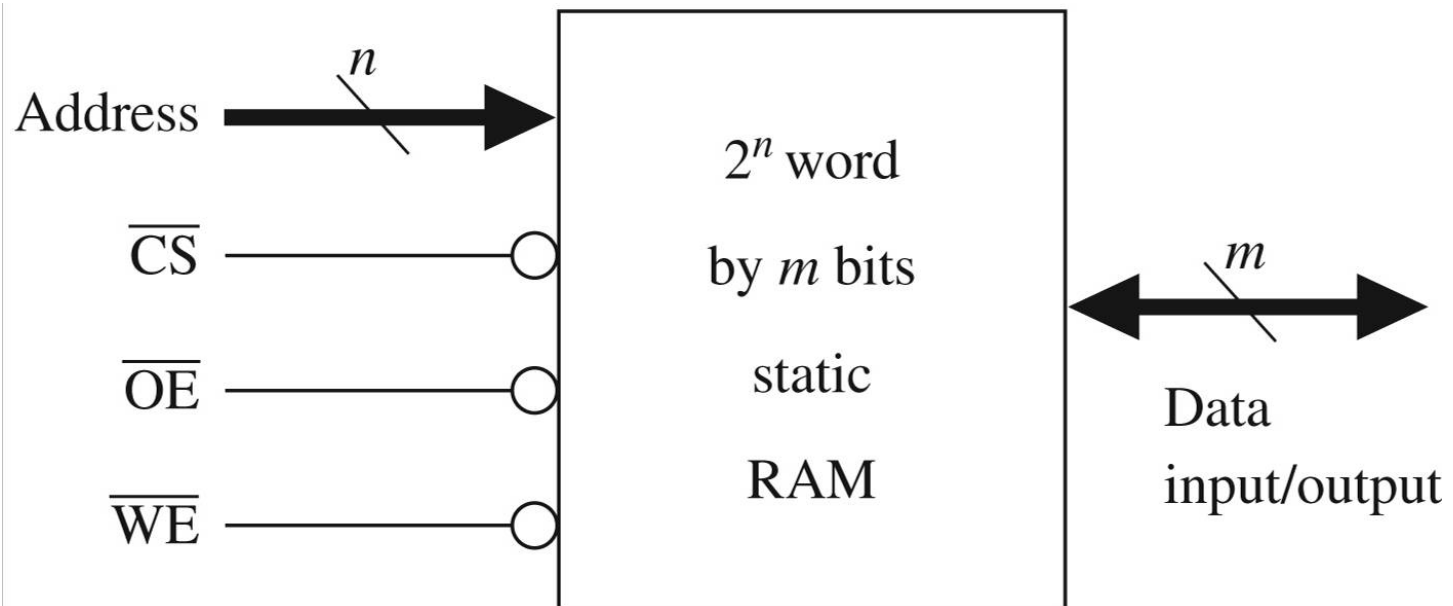

\overline{CS}	\overline{OE}	\overline{WE}	Mode	I/O pins
H	X	X	not selected	high-Z
L	H	H	output disabled	high-Z
L	L	H	read	data out
L	X	L	write	data in

VHDL Model

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;

entity RAM6116 is
    port(Cs_b, We_b, Oe_b: in std_logic;
          Address: in std_logic_vector(7 downto 0);
          IO: inout std_logic_vector(7 downto 0));
end RAM6116;
```

VHDL Model

```
architecture simple_ram of RAM6116 is
  type RAMtype is array(0 to 255) of
    std_logic_vector(7 downto 0);
  signal RAM1: RAMtype;
begin
    IO <= RAM1(conv_integer(Address)) when Cs_b = '0'
    and Oe_b = '0'
    and We_b = '1'
    else "ZZZZZZZZ";
```

VHDL Model

```
process (We_b, Cs_b)
begin
    if Cs_b = '0' and rising_edge(We_b) then
        RAM1(conv_integer(Address)) <= IO;
    end if;
end process;
end simple_ram;
```

Generics

```
library IEEE;
use IEEE.std_logic_1164.all;

entity Businv is
    generic(width: positive);
    port(x: in std_logic_vector(width-1 downto 0);
         y: out std_logic_vector(width-1 downto 0));
end Businv;

architecture Behave of Businv is
begin
    y <= not x;
end Behave;
```


Generic Instantiation

```
entity Businv_8 is
    port(in8: in std_logic_vector(7 downto 0);
          out8: out std_logic_vector(7 downto 0));
end Businv_8;

architecture Structure of Businv_8 is
    component Businv
        generic(width: positive);
        port(x: in std_logic_vector(width-1 downto 0);
              y: out std_logic_vector(width-1 downto 0));
    end component;
begin
    B1: Businv generic map(8) port map(in8, out8);
end Structure;
```

Time Modeling

```
library IEEE;
use IEEE.std_logic_1164.all;

entity xor2 is
    generic(gate_delay: time := 2 ns);
    port(in1, in2: in std_logic;
         z: out std_logic);
end xor2;

architecture behave of xor2 is
begin
    z <= in1 xor in2 after gate_delay;
end behave;
```


Named Association

```
component FA is
    port(X, Y, Cin: in std_logic;
          Cout, Sum: out std_logic);
end component;

FA0: FA port map(A(0), B(0), '0', open, S(0));

FA0: FA port map(Sum => S(0),
                  X    => A(0),
                  Y    => B(0),
                  Cin => '0');
```

Regular Structures (Generate)

 

entity Adder4 is

```
port(A, B: in std_logic_vector(3 downto 0);
```

```
  Ci: in std_logic;
```

```
  S: out std_logic_vector(3 downto 0);
```

```
  Co: out std_logic);
```

```
end Adder4;
```

Generate Statements

```
architecture Structure of Adder4 is
  component FullAdder
    port(X, Y, Cin: in std_logic;
         Cout, Sum: out std_logic);
  end component;
  signal C: std_logic_vector(4 downto 0);
begin
  C(0) <= Ci;
  Co <= C(4);
  FullAdd4: for i in 0 to 3 generate
  begin
    FAx: FullAdder port map (A(i), B(i), C(i),
                             C(i+1), S(i));
  end generate FullAdd4;
end Structure;
```

Summary

- ♦ IEEE 1164 Standard logic
- ♦ Generics
- ♦ Named Association
- ♦ Generate Statements