

ELEC-313  
Lab 8: Bipolar Junction Transistor  
Characterization

November 20, 2013

Date Performed: November 13, 2013  
Partners: Charles Pittman  
Stephen Wilson

## Contents

1	Objective	3
2	Equipment	3
3	Schematics	3
4	Procedure	3
5	Results	4
6	Conclusion	8
7	Equations	8

## List of Figures

1	Common-emitter transistor circuit	3
2	$V_{CE}$ vs. $I_C$	7

## List of Tables

1	$I_B = 20 \mu\text{A}$	4
2	$I_B = 50 \mu\text{A}$	5
3	$I_B = 80 \mu\text{A}$	5
4	$I_B = 100 \mu\text{A}$	6
5	Average values of $\beta$ per $I_B$	6
6	$V_{CE} = 5 \text{ V}$	6
7	$V_{CE} = 10 \text{ V}$	6
8	$V_{CE} = 15 \text{ V}$	7
9	Average values of $\beta$ per $V_{CE}$	7
10	$h_{oe}$ vs. $r_o$	7

## 1 Objective

The objective is to plot the output characteristic of a common-emitter transistor circuit, and use it to determine the current gain and output conductance.

## 2 Equipment

Transistor: 2N7000                      Power supply: HP E3631A  
Function generator: HP 33120      Multimeter: HP 34401A  
Oscilloscope: Agilent 54622D      Capacitors: 0.1  $\mu$ F  
Resistors: 100  $\Omega$ , 300  $\Omega$ , 470  $\Omega$ , 1 k $\Omega$  (x2) 33 k $\Omega$ , 100 k $\Omega$  (x2)

## 3 Schematics

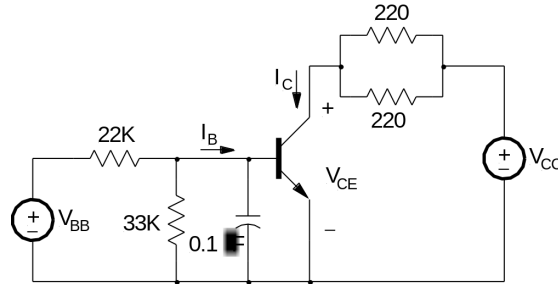


Figure 1: Common-emitter transistor circuit

## 4 Procedure

The following steps were observed to plot the output characteristic of a common emitter transistor circuit:

1. Construct the circuit of Figure 1. Use the +6 V power supply for  $V_{BB}$  and the +25 V supply for  $V_{CC}$ . Be sure to keep the connection distance between the capacitor and the transistor short. Use the HP multimeter to measure the base current ( $I_B$ ) on the source side of the capacitor and Fluke multimeters to measure the collector voltage and current ( $V_{CE}$  and  $I_C$ ).
2. Adjust  $V_{BB}$  so that base current ( $I_B$ ) is 20  $\mu$ A.
3. Adjust  $V_{CC}$  from 0.5 – 1.5 V in 0.25 V steps, then from 2 – 20 V in 2 V steps.

4. At each step measure the collector current,  $I_C$ , and the collector-to-emitter voltage,  $V_{CE}$ . If  $I_B$  has drifted, readjust  $V_{BB}$  before recording the values of  $I_C$  and  $V_{CE}$ .
5. Adjust  $V_{BB}$  for a base current of 50  $\mu\text{A}$ , 80  $\mu\text{A}$ , and 100  $\mu\text{A}$ . Repeat steps 3 and 4 at each  $I_B$  value.

## 5 Results

$V_{CC}$ (V)	$I_C$ (mA)	$V_{CE}$ (V)	$\beta$
0.50	0.232	0.454	11.60
0.75	0.233	0.705	11.65
1.00	0.234	0.954	11.70
1.25	0.237	1.204	11.85
1.50	0.237	1.454	11.85
2	0.242	1.954	12.10
4	0.25	3.95	12.30
6	0.25	5.95	12.60
8	0.26	7.95	12.75
10	0.26	9.96	12.85
12	0.26	11.95	13.10
14	0.27	13.94	13.30
16	0.27	15.95	13.40
18	0.27	17.95	13.50
20	0.27	19.95	13.70

Table 1:  $I_B = 20 \mu\text{A}$

$V_{CC}$ (V)	$I_C$ (mA)	$V_{CE}$ (V)	$\beta$
0.50	2.73	0.178	54.60
0.75	4.34	0.236	86.80
1.00	4.96	0.41	99.20
1.25	4.95	0.662	99.00
1.50	4.97	0.91	99.40
2	4.98	1.41	99.60
4	5.15	3.39	103.00
6	5.25	5.38	105.00
8	5.39	7.36	107.80
10	5.58	9.34	111.60
12	5.77	11.31	115.40
14	5.97	13.28	119.40
16	6.21	15.26	124.20
18	6.45	17.23	129.00
20	6.69	19.20	133.80

Table 2:  $I_B = 50 \mu\text{A}$

$V_{CC}$ (V)	$I_C$ (mA)	$V_{CE}$ (V)	$\beta$
0.50	3.08	0.135	38.50
0.75	4.95	0.163	61.88
1.00	6.8	0.191	85.00
1.25	8.58	0.229	107.25
1.50	9.1	0.421	113.75
2	9.4	0.881	117.50
4	10.79	2.71	134.88
6	11.03	4.68	137.88
8	11.45	6.63	143.13
10	11.99	8.56	149.88
12	12.72	10.47	159.00
14	13.41	12.39	167.63
16	14.20	14.29	177.50
18	15.05	16.20	188.13
20	15.85	18.10	198.13

Table 3:  $I_B = 80 \mu\text{A}$

$V_{CC}$ (V)	$I_C$ (mA)	$V_{CE}$ (V)	$\beta$
0.50	3.21	0.12	32.10
0.75	5.11	0.143	51.10
1.00	7.02	0.164	70.20
1.25	8.93	0.186	89.30
1.5	10.79	0.214	107.90
2	10.33	0.77	103.30
4	11.33	2.67	113.30
6	13.95	4.34	139.50
8	15.63	6.14	156.30
10	16.60	8.02	166.00
12	17.98	9.95	179.80
14	19.20	11.70	192.00
16	20.70	13.69	207.00
18	22.40	15.53	224.00
20	23.80	17.37	238.00

Table 4:  $I_B = 100 \mu\text{A}$

$I_B$ ( $\mu\text{A}$ )	$\beta_{avg}$
20	12.55
50	105.85
80	132.00
100	137.99

Table 5: Average values of  $\beta$  per  $I_B$

$I_B$ ( $\mu\text{A}$ )	$I_C$ (mA)	$\beta$
20	0.25	12.26
50	5.20	104.00
80	11.10	138.75
100	14.67	146.68

Table 6:  $V_{CE} = 5 \text{ V}$

$I_B$ ( $\mu\text{A}$ )	$I_C$ (mA)	$\beta$
20	0.26	12.97
50	5.64	112.84
80	12.47	155.88
100	18.00	180.00

Table 7:  $V_{CE} = 10 \text{ V}$

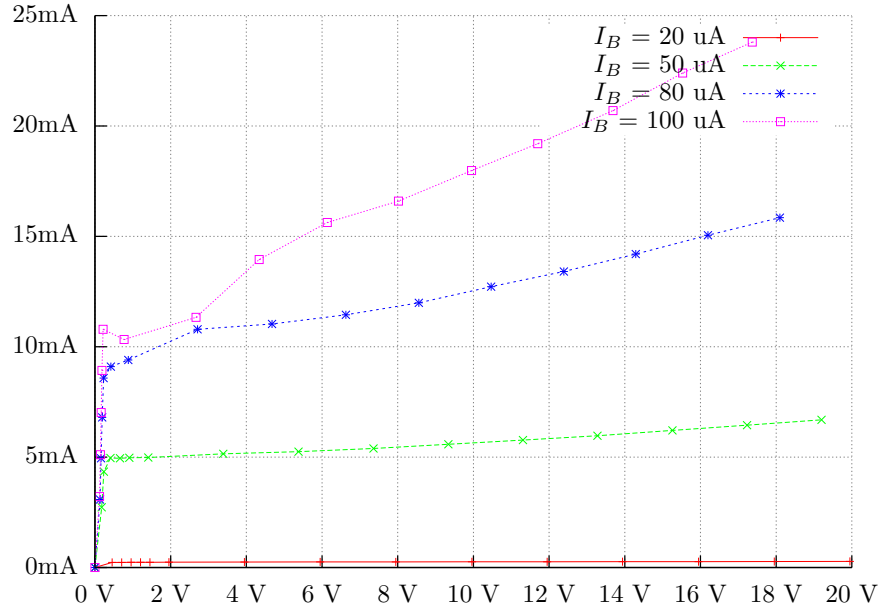


Figure 2:  $V_{CE}$  vs.  $I_C$

$I_B$ ( $\mu A$ )	$I_C$ (mA)	$\beta$
20	0.27	13.32
50	6.18	123.61
80	14.50	181.25
100	22.93	229.30

Table 8:  $V_{CE} = 15 V$

$V_{CE}$ (V)	$\beta_{avg}$
5	100.42
10	115.42
15	136.87

Table 9: Average values of  $\beta$  per  $V_{CE}$

$I_B$ ( $\mu A$ )	$h_{oe}$	$r_o$ ( $k\Omega$ )
20	1.700E-6	58.82
50	9.950E-5	10.10
80	3.669E-4	2.726
100	7.412E-4	1.349

Table 10:  $h_{oe}$  vs.  $r_o$

## 6 Conclusion

As shown in Figure 2, the family of curves associated with the four  $I_B$  currents loosely follow the typical plots of Bipolar Junction Transistors (BJTs). The mode of operation of the transistor transitions to the forward-active mode when  $V_{CE}$  is greater than approximately 0.2 V. Also, as  $I_B$  increases, the slope of the  $I_C$  to  $V_{CE}$  increases.

Tables 2b, 2a1, 2a2, and 2a3 show that as  $I_B$  increases, the ratio of  $I_C$  to  $I_B$  ( $\beta$  [also known as the current gain]) increases. But, this change in  $\beta$  seems to taper off as the  $I_B$  current (Table 2b) increases such that if one were to plot mean  $\beta$  vs.  $I_B$ , it would resemble logarithmic growth. For each of the values of  $I_B$ ; as  $I_C$  and  $V_{CE}$  increase,  $\beta$  increases as well (as shown in Table 2a). If one were to plot mean  $\beta$  vs.  $V_{CE}$ , I suspect it would resemble exponential growth though there is minimal evidence to prove this, considering only three data points are provided in Tables 2a1, 2a2, and 2a3.

Figure ?? shows the slope of each of the family of curves for  $V_{CE}$  values greater than 3 V. The output conductance  $h_{oe}$  was conducted with the slope of each of the four the trend line equations and the Equation ???. As  $I_B$  increased,  $h_{oe}$  increased. Therefore, as  $I_B$  increased, current gain  $\beta$  because the output resistance  $r_o$  decreased.

## 7 Equations

$$\beta = \frac{I_C}{I_B} \tag{1}$$

$$h_{oe} \approx \frac{1}{r_o} = \frac{\Delta I_C}{\Delta V_{CE}} \tag{2}$$