

ELEC-311
Project 4
Synchronous Design

Charles Pittman

December 5, 2013

Objective

- Design and test a synchronous sequential circuit which implements a 2-bit binary counter.
- Describe the circuit using VHDL.

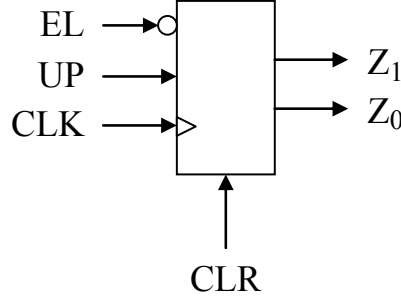


Figure 1: 2-bit binary counter

Discussion

Figure 1 shows a block diagram of the 2-bit binary counter to be implemented. It takes four inputs: E_L , U_P , C_{LK} , and C_{LR} ; and the present state is shown by a 2-bit binary number (Z_1Z_0). Since the output (which indicates present state) is only two bits, the circuit can have only four states. The U_P (active-high) control selects the counter's direction: count up when high; count down when low. E_L (active-low enable) and C_{LK} (rising-edge triggered) determine when state changes are normally permitted: only when C_{LK} changes low-high while $E_L = 0$. The only exception to this is C_{LR} (active-high asynchronous clear) signal, which immediately sets the count to 0.

The circuit's regular behavior (i.e. without the asynchronous clear signal) is shown in Table 1. The sums of minterms in columns Q_1^+ and Q_0^+ were then used to develop the next-state equations. Two Karnaugh maps were used (not pictured) to minimize the equations:

$$\begin{aligned}
 Q_1^+ &= \sum_m (0, 3, 5, 6, 10, 11, 14, 15) \\
 &= E_L' U_P' Q_1' Q_0' + U_P' Q_1 Q_0 + E_L' U_P Q_1' Q_0 + U_P Q_1 Q_0' + E_L Q_1 \quad (1)
 \end{aligned}$$

$$\begin{aligned}
 Q_0^+ &= \sum_m (0, 2, 4, 6, 9, 11, 13, 15) \\
 &= E_L' Q_0' + E_L Q_0 \quad (2)
 \end{aligned}$$

mt	Inputs		PS		NS		Outputs	
	E_L	U_P	Q_1	Q_0	Q_1^+	Q_0^+	Z_1	Z_0
0	0	0	0	0	1	1	0	0
1	0	0	0	1	0	0	0	1
2	0	0	1	0	0	1	1	0
3	0	0	1	1	1	0	1	1
4	0	1	0	0	0	1	0	0
5	0	1	0	1	1	0	0	1
6	0	1	1	0	1	1	1	0
7	0	1	1	1	0	0	1	1
8	1	0	0	0	0	0	0	0
9	1	0	0	1	0	1	0	1
10	1	0	1	0	1	0	1	0
11	1	0	1	1	1	1	1	1
12	1	1	0	0	0	0	0	0
13	1	1	0	1	0	1	0	1
14	1	1	1	0	1	0	1	0
15	1	1	1	1	1	1	1	1

Table 1: Transition Table for Figure 1

VHDL

```

library IEEE;
use IEEE.STD_LOGIC_1164.all;

library UNISIM;
use UNISIM.VComponents.all;

use work.project4_pkg.all;

entity counter is
    port (EL : in std_logic; -- Active-low enable
          UP : in std_logic; -- Active-high control (count up/down)
          CLK : in std_logic; -- Rising-edge trigger clock
          CLR : in std_logic; -- Active-high asynchronous clear
          Z : out std_logic_vector (1 downto 0)); -- 2-bit number
end counter;

architecture Dataflow of counter is
    signal d : std_logic_vector(1 downto 0);
    signal q : std_logic_vector(1 downto 0);
    signal slow_clk : std_logic;

begin

```

```

-- q next-state equations
d(1) <= (not EL and not UP and not q(1) and not q(0)) or
        (not UP and q(1) and q(0)) or
        (not EL and UP and not q(1) and q(0)) or
        (UP and q(1) and not q(0)) or
        (EL and q(1));
d(0) <= (not EL and not q(0)) or (EL and q(1));

-- Stretch the clock input for slow_clk
CDIV : CLK_DIV port map (CLK, slow_clk);

-- D flip-flops to do the actual switching
FF1 : FDC port map(q(1), slow_clk, CLR, d(1));
FF0 : FDC port map(q(0), slow_clk, CLR, d(0));

Z <= q; -- Give Z the present state (for output)
end Dataflow;

```