

Microelectronics Circuit Analysis and Design

Donald A. Neamen

Chapter 2

Diode Circuits

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 2-1

In this chapter, we will:


- Determine the operation and characteristics of diode rectifier circuits, which is the first stage of the process of converting an ac signal into a dc signal in the electronic power supply.
- Apply the characteristics of the Zener diode to a Zener diode voltage regulator circuit.
- Apply the nonlinear characteristics of diodes to create waveshaping circuits known as clippers and clampers.
- Examine the techniques used to analyze circuits that contain more than one diode.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 2-2

Block Diagram for ac to dc Converter

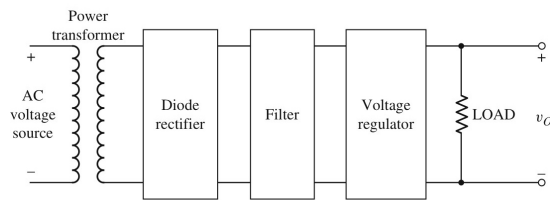

The diode rectifier, filter, and voltage regulator are diode circuits.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 2-3

Problem-Solving Technique: Diode Circuits


1. Determine the input voltage condition such that the diode is conducting (on).
 - a. Find the output signal for this condition.
2. Determine the input voltage condition such that the diode is not conducting (off).
 - a. Find the output signal for this condition.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 2-4

Half-Wave Rectifier

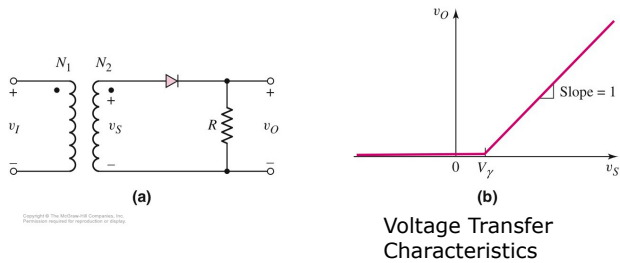


Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 2-5

Signals of Half Wave Rectifier

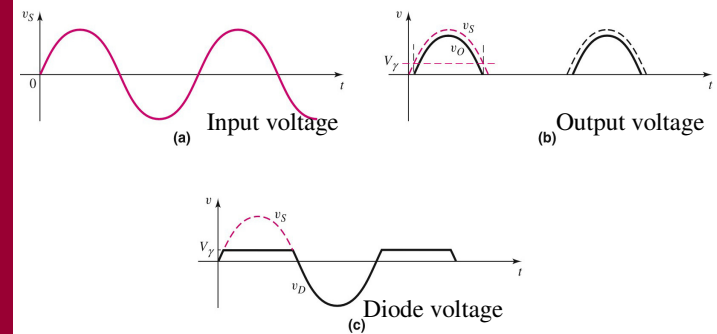


Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 2-6

Half-Wave Rectifier as Battery Charger

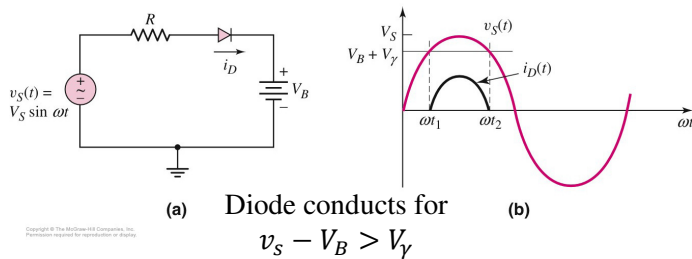

$$\omega t_1 = \sin^{-1}\left(\frac{V_B + V_\gamma}{V_S}\right) \quad \& \quad \omega t_2 = 180^\circ - \omega t_1$$


$$\text{Percent time} = \frac{\omega t_2 - \omega t_1}{360^\circ}$$

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 2-7

Half-Wave Rectifier with Filter

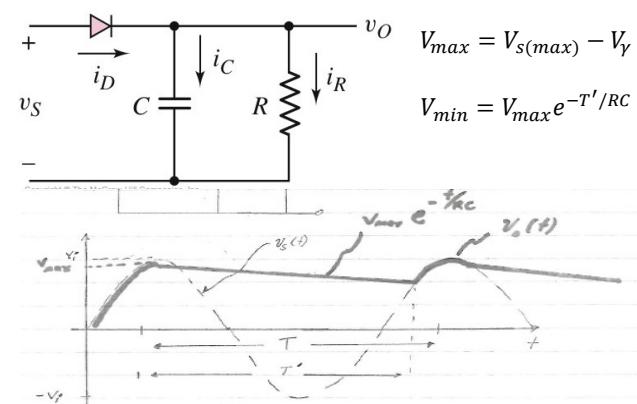

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 2-8

Half-Wave Rectifier with Filter

For $RC \gg T'$ and if $T' \cong T = 1/f$
Then

$$V_{min} = V_{max} e^{-T'/RC} \cong V_{max} \left(1 - \frac{1}{fRC}\right)$$

$$V_r = V_{max} - V_{min} = V_{max} \left(\frac{1}{fRC}\right)$$

$$\% \text{ Ripple} = \frac{V_{max} - V_{min}}{V_{max}} \times 100\%$$


$$\% \text{ Ripple} = \frac{1}{fRC} \times 100\%$$

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 2-9

Full-Wave Rectifier

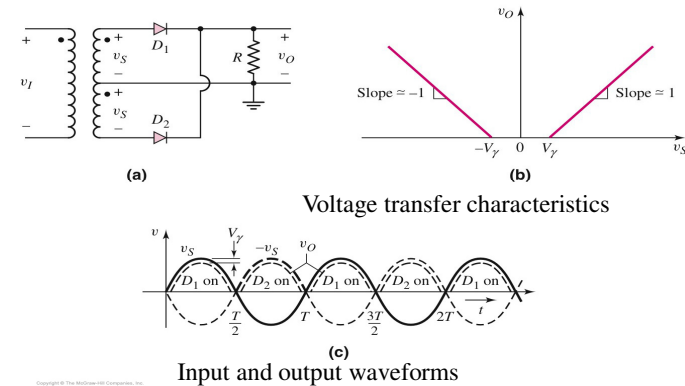


Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 2-10

Full-Wave Bridge Rectifier

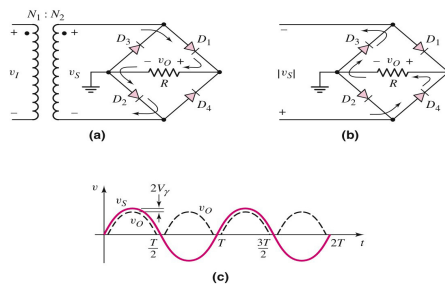

When v_S is positive, D_1 and D_2 are turned on (a). When v_S is negative, D_3 and D_4 are turned on (b).


In either case, current flows through R in the same direction, resulting in an output voltage, v_O , shown in (c).

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 2-11

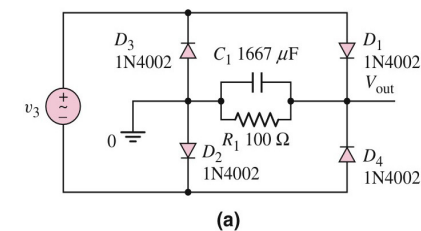Output Voltage of Full-Wave Rectifier with RC Filter




Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 2-12

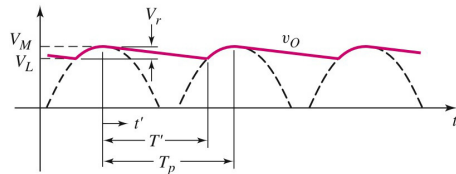Output Voltage of Full-Wave Rectifier with RC Filter



The ripple on the 'dc' output is $V_r = \frac{V_M}{2fRC}$ where $f = \frac{1}{2T_p}$


The average 'dc' output is $V_{avg} = \frac{1}{T'/2} \int_0^{T'/2} V_M \sin \omega t dt \cong \frac{2}{\pi} V_M$

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 2-13

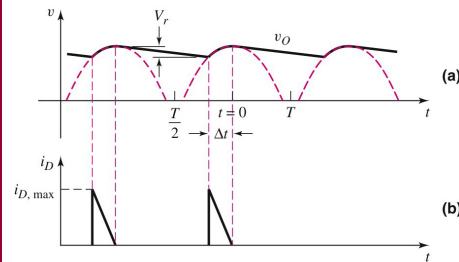Output Voltage of Full-Wave Rectifier with RC Filter




Diode conducts current for only a small portion of the period.

Neamen


Microelectronics, 4e
McGraw-Hill

Chapter 2-14


Demodulation of AM Signal

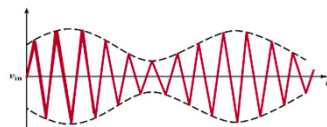

Modulated input signal

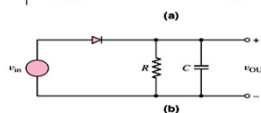

Detector circuit

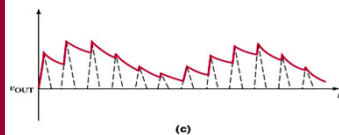


Demodulated output signal

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 2-15

Voltage Regulator

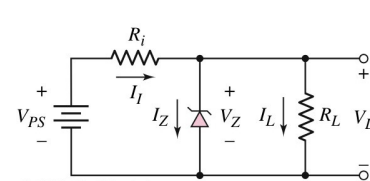

$$I_L = \frac{V_Z}{R_L}$$

$$I_i = \frac{V_{PS} - V_Z}{R_i}$$

$$I_Z = I_i - I_L$$


The characteristics of the Zener diode determines V_L .

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 2-16

Design DC Power Supply Circuit

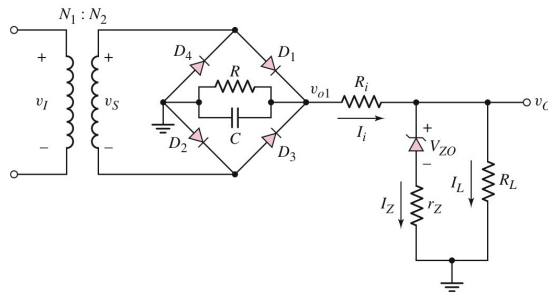


Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 2-17

Example

Select a diode and resistor to supply a steady 9 V to a radio which draws 0 to 0.1 A. The source is an unsteady 12V supply.

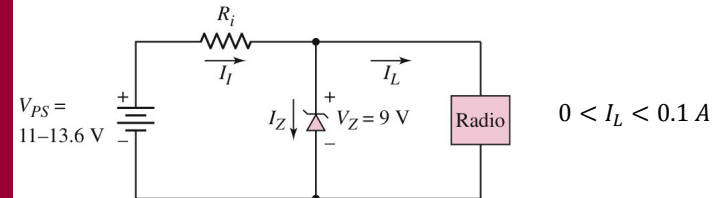
Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

Zener diode voltages range from 2.0 to 25 volts, at power rating from 0.3 to 5 watts.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 2-18

Example

1. Choose a zener diode voltage:

Select 9V zener for this example.

2. Determine max. circuit current:

The load requires 100mA, plus we need at least 10 mA for the zener diode. Since the supply is unstable, we can add 20-50% margin to obtain a safe value. Let's choose **Imax = 200mA**.

3. Select zener diode power rating:

$$P_z = V_z \cdot I_{max} = 9 \cdot 0.2 = 1.8W$$

=> select 1.8W or higher rated zener

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 2-19

Example

4. Select the resistor:

$$R_i = \frac{V_{PSmax} - V_z}{I_{max}} = \frac{13.6 - 9}{0.2} = 23\Omega$$

5. Select the resistor power rating:

$$P_r = V_r \cdot I_{max} = 3.6 \cdot 0.2 = 0.72W$$

=> select 0.72W or higher rated resistor.


Would the circuit be adequate if the source voltage varied up to 15.5V?

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 2-20

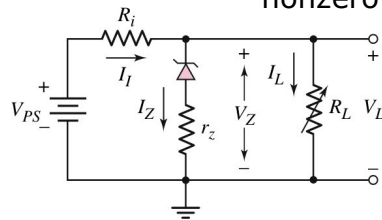Voltage Rectifier with nonzero Zener resistance



The Zener diode begins to conduct when $V_{PS} = V_Z$.

When $V_{PS} \geq V_Z$:

$$V_L = V_Z$$

$$I_L = V_Z/R_L, \text{ but } V_Z \neq \text{constant}$$

$$I_I = (V_{PS} - V_Z)/R_i$$


$$I_Z = I_I - I_L$$

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 2-21

Single Diode Clipper

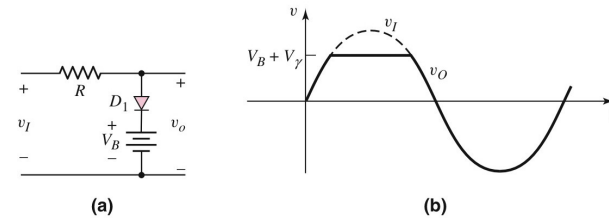

For $v_I < V_B + V_\gamma$ the diode is open and $v_O = 0$


For $v_I \geq V_B + V_\gamma$ the diode conducts and $v_O = v_I$

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 2-22

Additional Diode Clipper Circuits

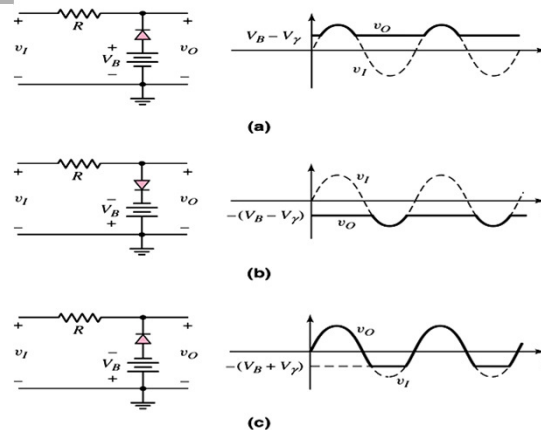


Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 2-23

Parallel-Based Diode Clipper Circuit

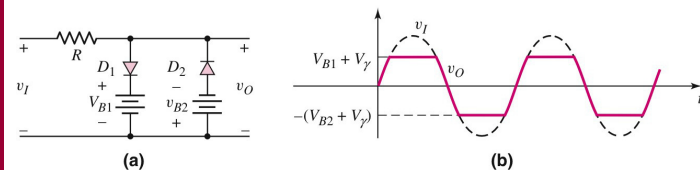


Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 2-24

Series-Based Diode Clipper Circuits

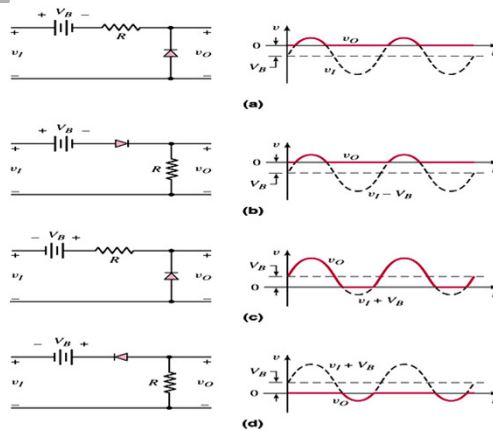


Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 2-25

Diode Clamper Circuit

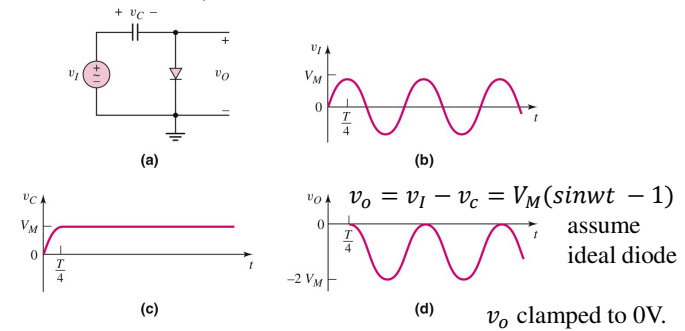The clamper circuit shifts the entire signal voltage by a DC level. v_o is clamped to V_γ . The output is a shifted replica of input.




Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 2-26

Diode Clamper Circuit with Voltage Source

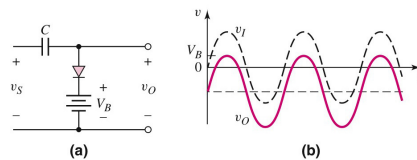The clamper circuit shifts the entire signal voltage by a DC level. v_o is clamped to $V_\gamma + V_B$ ($V_\gamma = 0$ shown).




v_C charges to $V_M - V_B$.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 2-27

2 Diode Circuit

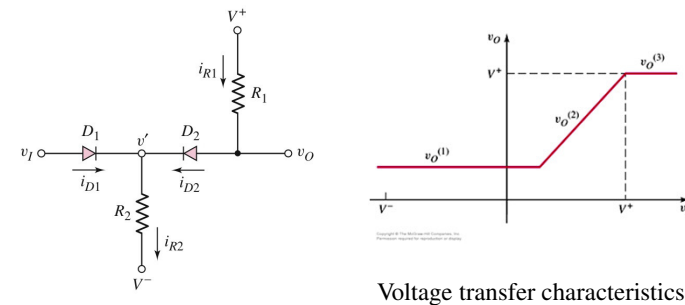

Voltage transfer characteristics

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 2-28

Problem-Solving Technique: Multiple Diode Circuits


1. Assume the state of the diode.
 - a. If assumed on, $V_D = V_\gamma$
 - b. If assumed off, $I_D = 0$.
2. Analyze the 'linear' circuit with assumed diode states.
3. Evaluate the resulting state of each diode.
4. If any initial assumptions are proven incorrect, make new assumption and return to Step 2.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 2-29

Exercise problem

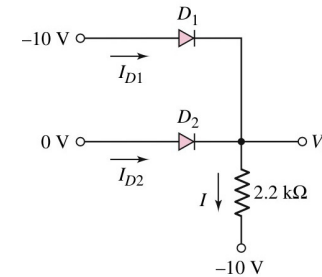
 D_1 is not on. D_2 is on.
This pins V_O to -0.6VCopyright © The McGraw-Hill Companies, Inc.
Permission is required for reproduction or display.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 2-30

Diode Logic Circuits: 2-Input OR Gate

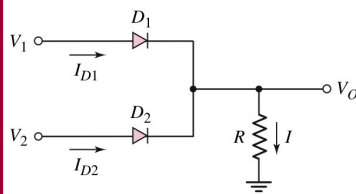Copyright © The McGraw-Hill Companies, Inc.
Permission is required for reproduction or display.

$$V_\gamma = 0.7V$$


V_1 (V)	V_2 (V)	V_O (V)
0	0	0
5	0	4.3
0	5	4.3
5	5	4.3

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 2-31

Diode Logic Circuits: 2-Input AND Gate

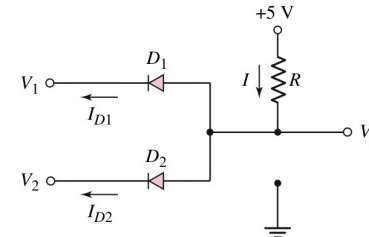Copyright © The McGraw-Hill Companies, Inc.
Permission is required for reproduction or display.

$$V_\gamma = 0.7V$$

V_1 (V)	V_2 (V)	V_O (V)
0	0	0
5	0	0
0	5	0
5	5	4.3

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 2-32