

ELEC 313 Lab 5

CMOS Circuits

REFERENCE: 1. Microelectronic Circuits, Sedra & Smith, Oxford University Press, Chapter 13
2. Fundamentals of Logic Design, Roth & Kinney, Cengage, Appendix A

OBJECTIVE: The objective of this experiment is to construct and observe the operation of a CMOS inverter and NAND gate.

EQUIPMENT: ALD1105 Dual N-channel and Dual P- channel matched pair MOSFET
Power Supply (Vdc)
Function Generator
Oscilloscope

PRIOR PREPARATION (Pre-Lab):

1. Download and review the specification sheet for the ALD1105 Dual N and P channel matched pair MOSFET.
2. Using your text or other resources review the circuit operation of CMOS Inverter and NAND gate circuits similar to those of figure 1 and figure 2.
3. Annotate a copy of both figure 1 and figure 2 with the appropriate pin numbers from the ALD1105 spec sheet, and place in your lab notebook.
4. Create a truth table for the expected outputs of the NAND gate.

EXPERIMENT

The following procedure will be used to evaluate the CMOS inverter.

- 1) Construct the circuit of figure 1.
- 2) Connect the V^+ terminal (Pin 11) to the + supply voltage.
- 3) Connect the V^- terminal (Pin 4) to the circuit ground.
- 4) Set V_{DD} to 5 volts using the HP source.
- 5) Use the function generator for input v_i . Set the function generator to a frequency of 20 kHz and select a triangle wave. Set the wave for 0 to 5 volts using the offset.
- 6) Connect CHANNEL 1 of the oscilloscope to the input and CHANNEL 2 to the output.
- 7) Use the x-y plot function of the scope to produce the transfer characteristic v_o vs. v_i . (Press the main key, then the xy softkey, then adjust the voltage scales as needed.)
- 8) Capture the v_o vs. v_i data, so you can recreate the plot for the lab report.
- 9) Adjust the amplitude and offset of the function generator for an input square wave of 0 to 5 V *as measured on the oscilloscope*.
- 10) Adjust the scope and capture both input and output on one screen for the report.
- 11) Measure the propagation delay times of the output waveform.

The following procedure will be used to evaluate the CMOS NAND gate.

- 1) Construct the circuit of figure 2.
- 2) Connect the V^+ terminal (Pin 11) to the + supply voltage.
- 3) Connect the V^- terminal (Pin 4) to the circuit ground.
- 4) Set the + supply voltage to 5 volts DC using the HP source.

- 5) Set input A to 0 volts.
- 6) Use the function generator for input B. Set the function generator to a frequency of 20 kHz and select a square wave. Set the square wave for 0 to 5 volts using the offset.
- 7) Connect CHANNEL 1 of the oscilloscope to the input and CHANNEL 2 to the output.
- 8) Adjust the scope and capture both input and output on one screen for the report.
- 9) Repeat step 8 with input A set to +5 volts.

LAB REPORT

Your report should be completed in the format requested by the instructor. The lab report should be in standard format and include the following additional items:

- 1) Using the transfer characteristic for the inverter, explain the circuit operation.
- 2) Discuss the operation of the NAND gate circuit and explain how it achieves its truth table.
- 3) Discuss how the screen capture relates to the truth tables for the NAND gate circuit.

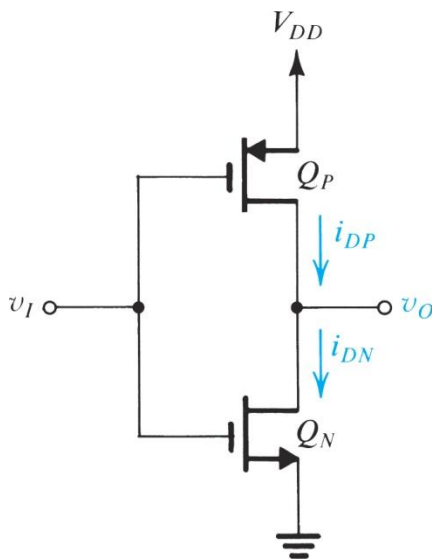


Figure 1: CMOS Inverter.

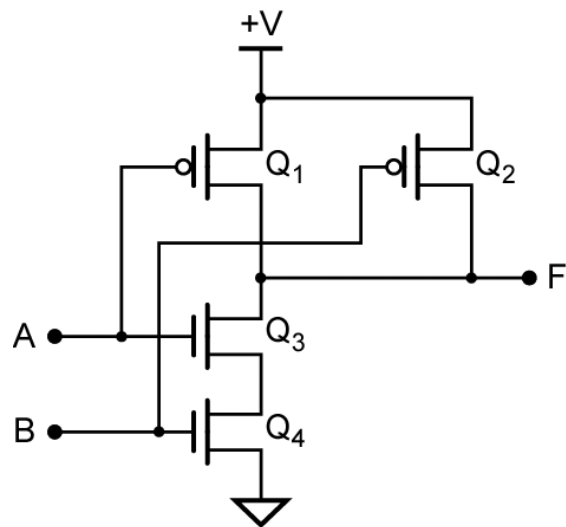


Figure 2: CMOS NAND Gate.