

ELEC-313
Lab 2: Diode Characterization

September 22, 2013

Date Performed: September 18, 2013
Partners: Charles Pittman
Stephen Wilson

1 Objective

The objective is to observe the operation of a diode, and its conformance to the Shockley equation:

$$I_D = I_S \left(e^{\frac{V_D}{V_T}} - 1 \right)$$

2 Schematics

Circuit Tested

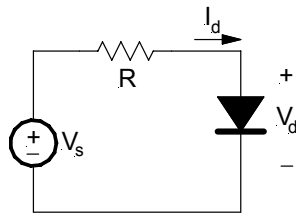


Figure 1: Circuit used for Part A and Part B.

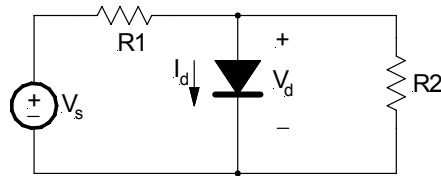


Figure 2: Circuit used for Part C.

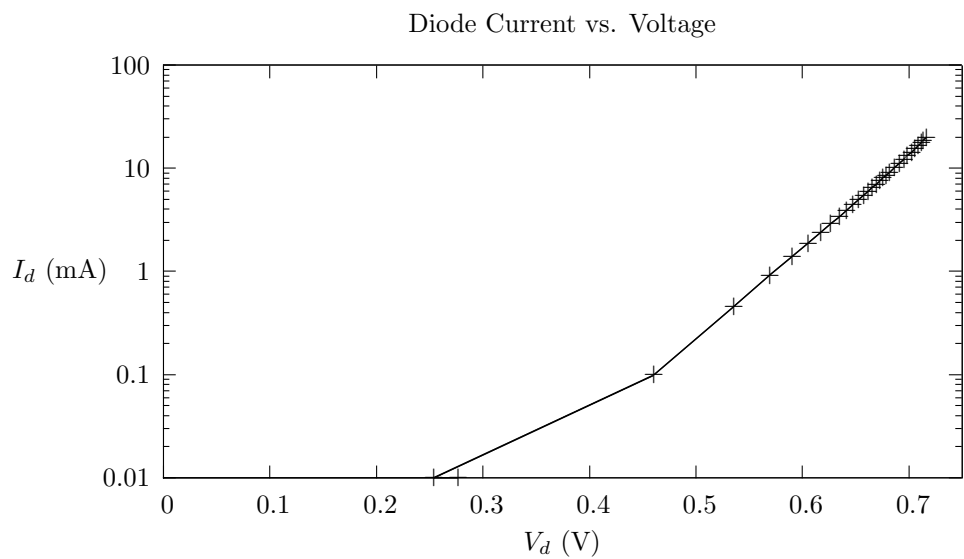


Figure 3: Diode characteristics measured in Part A.

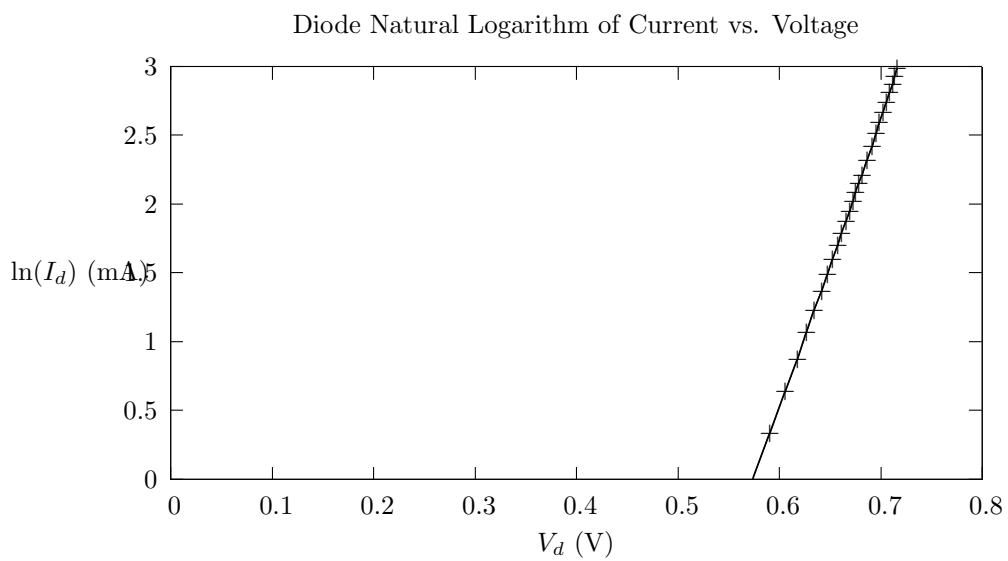


Figure 4: $\ln(I_d)$ vs. V_d .

R (Ω)	V_d (V)	I_d (mA)
200	0.751	46.00
500	0.713	18.60
1k	0.682	9.30
2k	0.650	4.70
5k	0.605	1.85
10k	0.571	0.94
20k	0.538	0.47
50k	0.494	0.19
100k	0.464	0.10

Table 1: Diode characteristics measured in Part B.

V_d (V)	I_d (mA)	V_{OC} (V)
0.712	27.2	6.70

Table 2: Diode characteristics measured in Part C.

3 Procedure

4 Results

4.1 Part A

4.2 Part B

5 Conclusion

6 Appendix

Equations