

1. Design a floating-point multiplier which uses the IEEE single precision floating-point format. Ignore special cases other than 0 and truncate the result.

- a) Draw a block diagram for the multiplier showing the necessary registers and control signals.
- b) Draw the SM Chart for the control circuit.
- c) Write a complete VHDL model for the multiplier (use two processes).
- d) Simulate for the following test data (using a testbench):

$$25.25 \times -2.5 = -63.125$$

$$0 \times 25.25 = ?$$

$$-7.5 \times -7.5 = ?$$

Hints:

- The controller needs to handle FZ, FV, and EV (but not Fnorm).
- The fractions are unsigned (not 2's complement) multiplication. The sign bits are handled separately.
- Use the + and * operators to implement the exponent adder and fraction multiplier
 - `addout <= ('0' & E1) + ('0' & E2) - bias;`
 - `multout <= ('1' & F1) * ('1' & F2);`