

ELEC-313
Lab 8: Bipolar Junction Transistor
Characterization

November 16, 2013

Date Performed: November 13, 2013
Partners: Charles Pittman
Stephen Wilson

1 Objective

The objective is to plot the output characteristic of a common-emitter transistor circuit, and use it to determine the current gain and output conductance.

2 Equipment

Transistor: 2N7000 Power supply: HP E3631A
Function generator: HP 33120 Multimeter: HP 34401A
Oscilloscope: Agilent 54622D Capacitors: 0.1 μ F
Resistors: 100 Ω , 300 Ω , 470 Ω , 1 k Ω (x2) 33 k Ω , 100 k Ω (x2)

3 Schematics

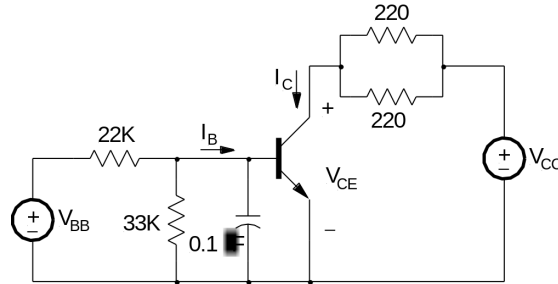


Figure 1: Common-emitter transistor circuit

4 Procedure

5 Results

6 Conclusion

7 Equations

$$h_{oe} \approx \frac{1}{r_o} = \frac{\Delta i_C}{\Delta v_{CE}} \quad (1)$$

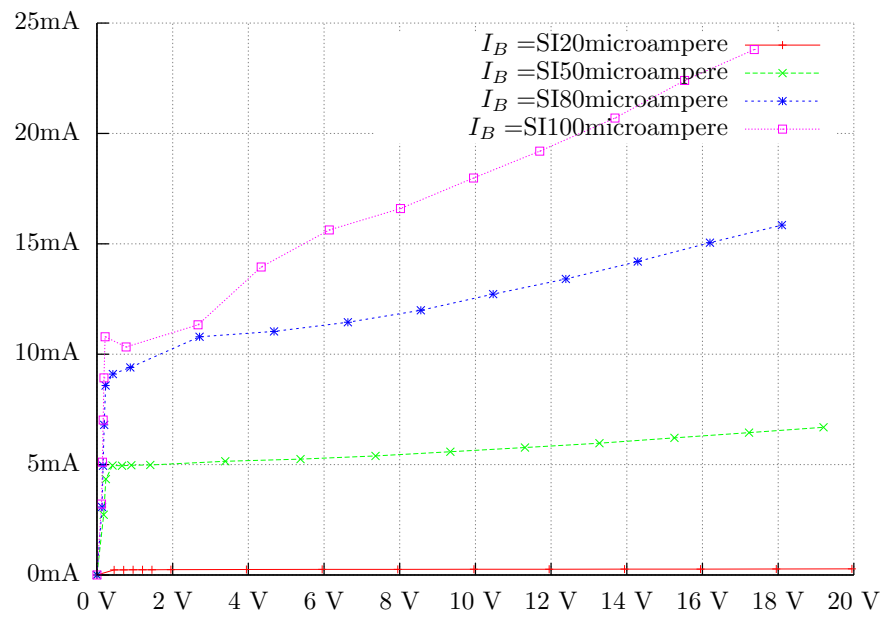


Figure 2: V_{CE} vs. I_C