

ELEC-313  
Lab 6: MOSFET Characterization

November 5, 2013

Date Performed: October 30, 2013  
Partners: Charles Pittman  
Stephen Wilson

## 1 Objective

The objective is to construct and observe the operation of a CMOS inverter and NAND gate.

## 2 Equipment

Transistor: 1N4007

Power supply: HP E3631A

Resistors:  $330\ \Omega$  (x3),  $2.2\ \text{k}\Omega$ ,  $33\ \text{k}\Omega$

Multimeters: Fluke 8010A (x2)

## 3 Schematics

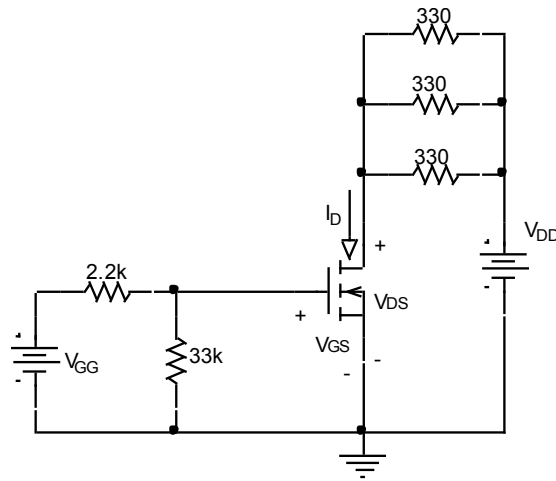


Figure 1: Circuit used in this lab.

## 4 Procedure

### 4.1 DC Characteristics

1. Obtain the 2N7000 MOSFET transistor and resistors needed to build the circuit shown.
2. Construct the circuit of figure 2. Use the HP multi-meter to measure the drain current,  $I_D$ , and the Fluke multi-meters to measure  $V_{DS}$  and  $V_{GS}$ . Use the  $+6\ \text{V}$  power supply for  $V_{GG}$  and the  $+25\ \text{V}$  supply for  $V_{DD}$ .
3. Set  $V_{GG}$  to  $0\ \text{V}$  and  $V_{DD}$  to  $5\ \text{V}$  and measure  $V_{DS}$  and  $I_D$ .

4. Slowly increase  $V_{GG}$  until the transistor just begins to conduct current as evidenced by a small drop in  $V_{DS}$ . Record the value of  $V_{GS}$  as the Gate Threshold Voltage,  $V_{TN}$ .
5. Adjust  $V_{GG}$  to increase  $V_{GS}$  by 0.2 V above the threshold. Readjust  $V_{DD}$  to return  $V_{DS}$  to 5 V, and then measure the drain current ( $I_D$ ). Record the value of  $V_{GS}$  in the first column of table1, and record the value of  $I_D$  in the second column (the  $V_{DS} = 5$  V column).
6. Continue to increase  $V_{GS}$  in steps of 0.2 V while maintaining  $V_{DS}$  at 5 V. Measure the drain current at each step. Record the values of  $V_{GS}$  and  $I_D$  in table 1. Stop this process when the drain current reaches approximately 80mA.
7. Complete the entries in table 1 by adjusting  $V_{DD}$  and  $V_{GG}$  to obtain the various required  $V_{DS}$  and  $V_{GS}$  values, then measuring  $I_D$  at each value. Do not exceed 80mA drain current.

## 4.2 Small-Signal Transconductance

1. Adjust  $V_{GG}$  and  $V_{DD}$  to obtain  $V_{DS} = 5$  V and  $I_D = 10$  mA.
2. Record the value of  $V_{GS}$  as  $V_{G1}$ .
3. Record the exact measured value of  $I_D$  and assign it to  $I_{D1}$ . Use the full resolution of the HP multimeter.
4. Increase  $V_{GS}$  by 10 mV and record it value as  $V_{G2}$ .
5. Measure  $I_D$ , recording it as  $I_{D2}$ .
6. Compute the small signal transconductance (Eq 1).

## 5 Results

The following table shows several  $V_{GS}$  values that are just slightly over the overdrive voltage  $V_{OV}$  and gives an idea of the amount of variation for values resulting from Equation 2.

$V_{TN} = 2.11$ V	$V_{DS} = 0.5$ V	$V_{DS} = 1$ V	$V_{DS} = 1.5$ V
$V_{GS} = 2.91$ V			0.1078
$V_{GS} = 2.71$ V		0.0931	
$V_{GS} = 2.51$ V	0.07688		

Table 1:  $k'_n$

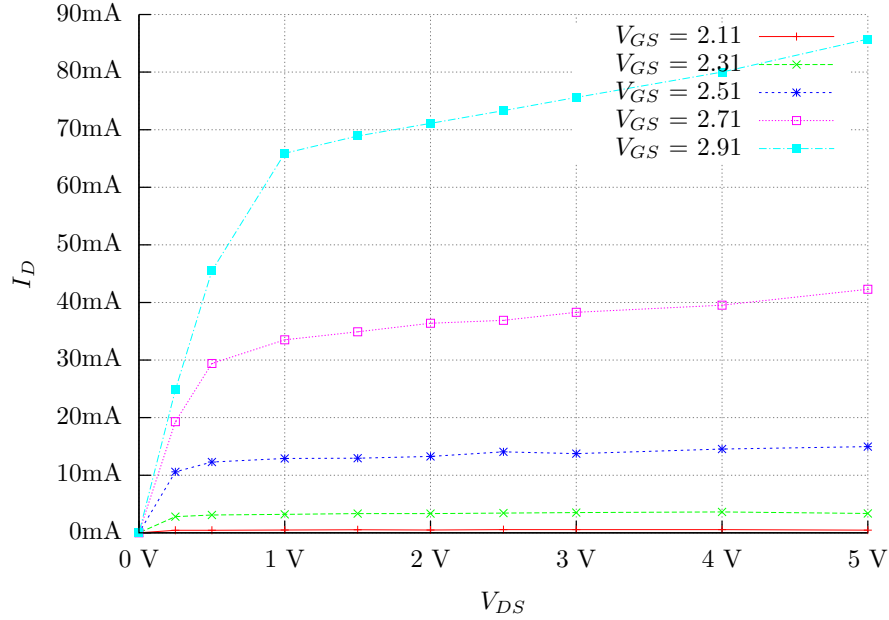


Figure 2: Graph

## 6 Conclusion

Its hard to compare the Figure 2 plot with the 2N7000 data sheet because the data sheets lowest  $V_{GS}$  curve is 3 V, which is still higher than the highest  $V_{GS}$  curve in Figure 2. However, it is still apparent that the  $V_{GS}$  curve of 2.91 V in Figure 2 is similar to the 3 V curve because the  $V_{OV}$  points are roughly the same with a  $V_{DS}$  value of 1–1.5 V. After the  $V_{OV}$  point, both curves taper off and have a very slight positive slope.

Its easier to compare Figure 2 plot with the PSpice simulation because the  $V_{GS}$  are closer to the values seen in Figure 2. Again the  $V_{OV}$  values are similar in both the plot and the simulation. But, the PSpice simulation curves are flat at points beyond the  $V_{OV}$  instead of sloped like it is in Figure 2.

The second PSpice simulation was more representative of the Figure 2 plots because the value of  $\lambda$  was changed from 0 (in the first simulation) to .06, which made the  $V_{GS}$  curves slope beyond the  $V_{OV}$ . Adding the  $\lambda$  also raised the  $I_D$  current for the individual  $V_{OV}$  points. This is because the  $\lambda$  value represents the slight resistance that is inherent to the transistor a low  $\lambda$  value is a higher resistance and a high  $\lambda$  is a lower resistance because the resistance is the inverse of the  $\lambda$ .

## 7 Equations

$$g_m = \frac{I_{D2} - I_{D1}}{V_{GS2} - V_{GS1}} \quad (1)$$

$$\frac{k'_n}{2} \cdot \frac{W}{L} = \frac{I_{D1}}{(V_{GS1} - V_{TN})^2} \quad (2)$$