

ELEC 316 Electromagnetic Energy Conversion


Power in Single Phase AC Circuits

Power in Single Phase AC Circuits

- Instantaneous Power
- Average Power and RMS Quantities
- Examples

Instantaneous Power $P(t)$

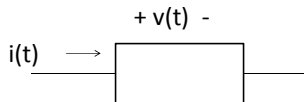- Power = $\frac{d}{dt}(\text{Energy})$
- Units = joules/sec = watts
- $P(t) = v(t) i(t)$



$P(t)$ for AC resistive load

$$P(t) = v(t)i(t) = V \cos(\omega t + \Phi_v) I \cos(\omega t + \Phi_v) \\ = V I \cos^2(\omega t + \Phi_v)$$

$$\text{Using } \cos^2(A) = \frac{1}{2} (1 + \cos 2A)$$

$$P(t) = \frac{1}{2} V I \{1 + \cos 2(\omega t + \Phi_v)\}$$

An average value = $\frac{1}{2} VI$, plus a double frequency term

$P(t)$ for AC Inductive load

$$P(t) = v(t)i(t) = V \cos(\omega t + \Phi_v) I \cos(\omega t + \Phi_v - 90) \\ = V I \cos(\omega t + \Phi_v) \cos(\omega t + \Phi_v - 90) \\ \text{where } I = V / \omega L$$

$$\text{Using } \cos(A) \cos(B) = \frac{1}{2} (\cos(A+B) + \cos(A-B))$$

$$P(t) = \frac{1}{2} V I \cos[2(\omega t + \Phi_v) - 90] \\ = \frac{1}{2} V I \sin[2(\omega t + \Phi_v)]$$

Double frequency term with an average value = 0.

$P(t)$ for AC Capacitive load

$$P(t) = v(t)i(t) = V \cos(\omega t + \Phi_v) I \cos(\omega t + \Phi_v + 90) \\ = V I \cos(\omega t + \Phi_v) \cos(\omega t + \Phi_v + 90) \\ \text{where } I = \omega C V$$

$$\text{Using } \cos(A) \cos(B) = \frac{1}{2} (\cos(A+B) + \cos(A-B))$$

$$P(t) = \frac{1}{2} V I \cos[2(\omega t + \Phi_v) + 90] \\ = -\frac{1}{2} V I \sin[2(\omega t + \Phi_v)]$$

Double frequency term with an average value = 0.

P(t) for general RLC Load

$$P(t) = v(t)i(t) = V \cos(\omega t + \Phi_v) I \cos(\omega t + \Phi_i)$$

$$= V I \cos(\omega t + \Phi_v) \cos(\omega t + \Phi_i)$$

$$\text{where } I = V/Z \text{ and } \Phi_i = \Phi_v - \angle Z$$

$$\text{Using } \cos(A) \cos(B) = \frac{1}{2} (\cos(A+B) + \cos(A-B))$$

$$P(t) = \frac{1}{2} V I \{ \cos(\Phi_v - \Phi_i) + \cos(2\omega t + \Phi_v + \Phi_i) \}$$

$$\text{Double frequency term with an average value} = \frac{1}{2} V I \cos(\Phi_v - \Phi_i)$$

Average Power

$$P_{avg} = \frac{1}{T} \int_0^T P(t) dt$$

$$T = \text{period of all forcing functions}$$

$$\text{Resistive case}$$

$$P_{avg} = \frac{1}{T} \int_0^T \frac{1}{2} V I \{ 1 + \cos(2\omega t + \Phi_v) \} dt = \frac{1}{T} \frac{VI}{2} T$$

$$= \frac{VI}{2}$$

Average Power

$$\text{General RLC case}$$


$$P_{avg} = \frac{1}{T} \int_0^T \frac{1}{2} V I \{ \cos(\Phi_v - \Phi_i) + \cos(2\omega t + \Phi_v + \Phi_i) \} dt$$

$$= \frac{1}{T} \frac{VI}{2} \cos(\Phi_v - \Phi_i) T$$


$$= \frac{VI}{2} \cos(\Phi_v - \Phi_i)$$

RMS Quantities

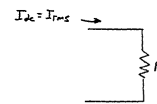- RMS Value: The RMS value of a periodic current is equal to the value of a dc current which flowing through a resistance R delivers the same average power to R as the periodic current does.



$$P_{avg} = I_{rms}^2 R$$

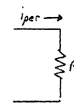

$$P_{avg} = \frac{1}{T} \int_0^T i_{per}^2 R dt$$

RMS Quantities

Setting the expressions equal and solving for I_{rms}

$$I_{rms} = \sqrt{\underbrace{\frac{1}{T} \int_0^T i_{per}^2 dt}_{\text{mean}}}_{\text{root}} \quad \text{RMS}$$

RMS Quantities

- For a sinusoid $i_{per} = I \cos(\omega t + \Phi_i)$

$$I_{rms} = \sqrt{\frac{1}{T} \int_0^T (I \cos(\omega t + \Phi_i))^2 dt}$$

- Using $\cos^2(A) = \frac{1}{2} (1 + \cos(2A))$

$$I_{rms} = \frac{1}{\sqrt{2}} I = 0.707 I$$

- It follows for $V_{per} = V \cos(\omega t + \Phi_v)$

$$V_{rms} = \frac{1}{\sqrt{2}} V = 0.707 V$$

RMS Quantities

- Note for a sinusoid in the General RLC case

$$P_{avg} = \frac{VI}{2} \cos(\Phi_v - \Phi_i) \\ = V_{rms} I_{rms} \cos(\Phi_v - \Phi_i)$$

- A general periodic function

$$I_{per} = I_1 \cos(\omega_1 t) + I_2 \cos(\omega_2 t) + I_3 \cos(\omega_3 t) + \dots$$

- Has average power

$$P_{avg} = \frac{1}{2} (I_1^2 + I_2^2 + I_3^2 + \dots) R = I_{rms}^2 R$$

- So

$$I_{rms} = \sqrt{\frac{1}{2} (I_1^2 + I_2^2 + I_3^2 + \dots)}$$

Example 1

Given that $i(t) = \sqrt{2} \cdot 5 \text{ A} \cos(377t + 45^\circ)$ flows through a 2Ω resistor, Calculate the average power.

$$P_{ave} = (I_{rms})^2 R = (5)^2 (2) = 50 \text{ W}$$

Or

$$P_{ave} = \frac{1}{2} (I_{peak})^2 R = \frac{1}{2} (5\sqrt{2})^2 (2) = 50 \text{ W}$$

Example 2

Given $i(t) = \sqrt{2} \cdot 5 \text{ A} \cos(377t + 45^\circ) + \sqrt{2} \cdot 3 \text{ A} \cos(754t + 60^\circ)$ flows through a 2Ω resistor. Calculate the average power.

$$I_{rms} = \sqrt{5^2 + 3^2} = \sqrt{34} \text{ A}$$

$$P_{ave} = (I_{rms})^2 R = (\sqrt{34})^2 (2) = 68 \text{ W}$$

Or

$$P_{ave} = \frac{1}{2} (I_{1peak})^2 R + \frac{1}{2} (I_{2peak})^2 R \\ = \frac{1}{2} (5\sqrt{2})^2 (2) + \frac{1}{2} (3\sqrt{2})^2 (2) = 68 \text{ W}$$

Example 3

Given $i(t) = \sqrt{2} \cdot 5 \text{ A} \cos(377t + 45^\circ) + \sqrt{2} \cdot 3 \text{ A} \cos(377t + 60^\circ)$ flows through a 2Ω resistor. Calculate the average power.

$$\tilde{I} = \sqrt{2} \cdot 5 \angle 45^\circ + \sqrt{2} \cdot 3 \angle 60^\circ$$

$$= 11.23 \angle 50.6^\circ = \sqrt{2} \cdot 7.94 \angle 50.6^\circ$$


$$P_{ave} = (I_{rms})^2 R = (7.94)^2 (2) = 126 \text{ W}$$

Note:

$$P_{ave} \neq (I_{1rms})^2 R + (I_{2rms})^2 R = (5)^2 (2) + (3)^2 (2) = 68 \text{ W}$$

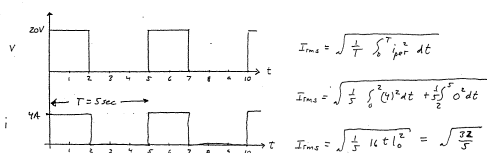Example 4


ex. 4. Determine the average power consumed by a 5Ω resistor when the following periodic voltage is applied across it:



$$P_{ave} = I_{rms}^2 R = \left(\frac{32}{5}\right)(5) = 32 \text{ W}$$


Example 5 and 6

ex. 5. Find the average power

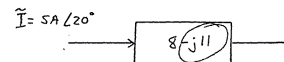

$$P_{ave} = \frac{1}{2} I_{pk}^2 R = \frac{1}{2} (5)^2 (8) = 100 \text{ W}$$


ex. 6. Find the average power

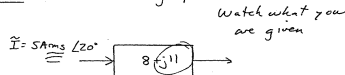

$$P_{ave} = I_{rms}^2 R = (5)^2 (8) = 200 \text{ W}$$

Example 7

ex. 7.

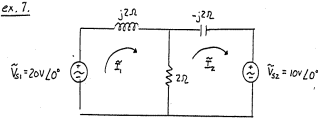

Find the average power absorbed by each component.

Step 1. Write the mesh equations

$$\text{Mesh 1: } -\tilde{V}_{s1} + \tilde{I}_1 j2 + (\tilde{I}_1 - \tilde{I}_2) 2 = 0$$

$$\text{Mesh 2: } (\tilde{I}_2 - \tilde{I}_1) 2 - \tilde{I}_2 j2 + \tilde{V}_{s2} = 0$$

Example 7 cont...

Step 2. Place into matrix form and solve with MATLAB

$$\begin{bmatrix} 2+j2 & -2 \\ -2 & 2-j2 \end{bmatrix} \begin{bmatrix} \tilde{I}_1 \\ \tilde{I}_2 \end{bmatrix} = \begin{bmatrix} \tilde{V}_{s1} \\ -\tilde{V}_{s2} \end{bmatrix}$$

$$\begin{bmatrix} \tilde{I}_1 \\ \tilde{I}_2 \end{bmatrix} = \begin{bmatrix} 11.18 \text{ A } \angle -63.45^\circ \\ 7.07 \angle -45^\circ \end{bmatrix}$$

Example 7 cont...

Step 3. Identify the required currents

Current into the + side of \tilde{V}_{s1} : $-\tilde{I}_1 = 11.18 \text{ A } \angle +116.55^\circ$

Current into the + side of \tilde{V}_{s2} : $\tilde{I}_2 = 7.07 \text{ A } \angle -45^\circ$

Current into 2Ω : $\tilde{I}_1 - \tilde{I}_2 = 5 \text{ A } \angle -90^\circ$

Step 4. Establish the average powers

$$P_{\text{ave},L} = 0$$

$$P_{\text{ave},C} = 0$$

$$P_{\text{ave},R} = \frac{1}{2} I_{R,pk}^2 R = \frac{1}{2} (5)^2 (2) = +25 \text{ W absorbed}$$

$$\begin{aligned} P_{\text{ave},s1} &= \frac{1}{2} V_{s1,pk} I_{s1,pk} \cos(\angle V_{s1} - \angle I_{s1}) \\ &= \frac{1}{2} (20\text{V}) (11.18 \text{ A}) \cos(0 - 116.55^\circ) \\ &= -50 \text{ W absorbed [THIS SOURCE DELIVERS POWER]} \end{aligned}$$

$$\begin{aligned} P_{\text{ave},s2} &= \frac{1}{2} V_{s2,pk} I_{s2,pk} \cos(\angle V_{s2} - \angle I_{s2}) \\ &= \frac{1}{2} (10\text{V}) (7.07 \text{ A}) \cos(0 - (-45^\circ)) \\ &= +25 \text{ W absorbed} \end{aligned}$$