

ELEC-313
Lab 3: Diode Circuits

September 29, 2013

Date Performed: September 25, 2013
Partners: Charles Pittman
Stephen Wilson

Contents

1	Objective	3
2	Equipment	3
3	Schematics	3
4	Procedure	3
4.1	Rectifier	3
4.2	Voltage Regulator	3
5	Results	3
6	Conclusion	5
7	Equations	5

List of Figures

1	Circuits used in this lab.	3
2	AC input vs. DC output of rectifier circuit, where $R_L = 10\text{ k}\Omega$	4

List of Tables

1	Percent difference of capacitor in rectifier circuit.	3
2	AC input vs. DC output of rectifier circuit, where $R_L = 10\text{ k}\Omega$	4
3	Effect of R_L on DC output in rectifier circuit.	4
4	Calculated values for voltage regulator circuit	4
5	Measured values for voltage regulator circuit	5
6	Comparison of values for voltage regulator circuit	5

1 Objective

The objective is to construct, measure, and observe the behavior of two common diode circuits: a voltage rectifier, and a voltage regulator.

2 Equipment

Diode: 1N4007

Zener diode: 1N5231

Resistors: $47\ \Omega$

Capacitor: $1\ \mu\text{F}$

Resistive decade box: HeathKit IN-3117

Power supply: HP E3631A

Function generator: HP 33120A

Multimeter: Fluke 8010A

Oscilloscope: Agilent 54622D

3 Schematics

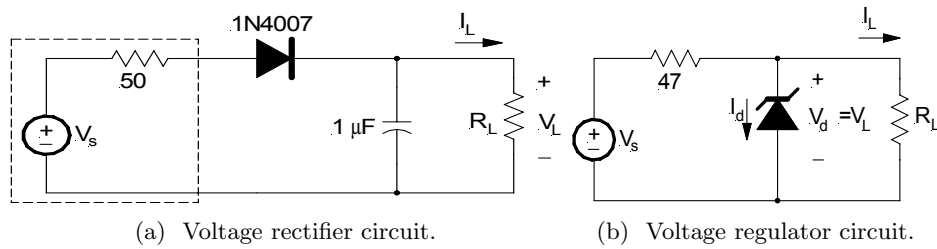


Figure 1: Circuits used in this lab.

4 Procedure

4.1 Rectifier

4.2 Voltage Regulator

5 Results

Nominal (μF)	Measured (μF)	Difference
1	0.938	6.2%

Table 1: Percent difference of capacitor in rectifier circuit.

V_S (V _{peak})	V_{max} (V)	V_{min} (V)	V_r (V)	V_{DC} (V)	Ripple
1	0.488	0.369	0.119	0.429	24.4%
2	1.41	1.10	0.310	1.26	22.0%
3	2.39	1.88	0.510	2.14	21.3%
4	3.31	2.38	0.930	2.85	28.1%
5	4.25	3.19	1.06	3.72	24.9%

Table 2: AC input vs. DC output of rectifier circuit, where $R_L = 10\text{ k}\Omega$.

R_L (Ω)	V_{max} (V)	V_{min} (V)	V_r (V)	V_{DC} (V)	Ripple
1k	4.13	0.440	3.69	2.29	89.3%
10k	4.25	3.19	1.06	3.72	24.9%
100k	4.321	4.193	0.128	4.257	2.962%

Table 3: Effect of R_L on DC output in rectifier circuit.

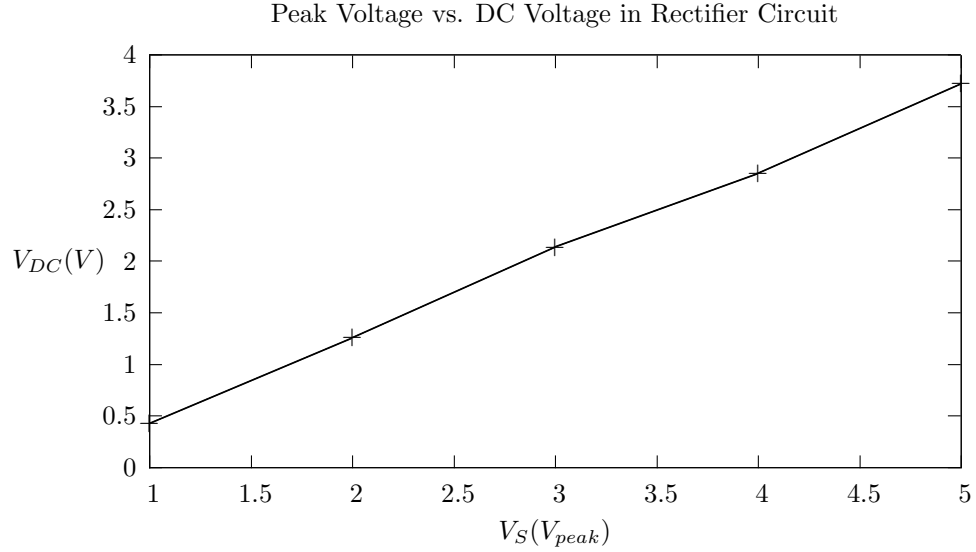


Figure 2: AC input vs. DC output of rectifier circuit, where $R_L = 10\text{ k}\Omega$

R_L (Ω)	V_{OC} (V)	V_S Drop (V)
100	6.12	7.5
330	7.88	5.8
1k	8.90	5.3

Table 4: Calculated values for voltage regulator circuit

R_L (Ω)	V_L (V)	I_L (mA)	V_{OC} (V)	V_S Drop (V)	Voltage Regulation
100	5.163	50.9	6.10	7.5	4.20%
330	5.318	15.62	7.87	5.9	1.17%
1k	5.11	5.27	8.60	5.3	5.28%
∞	5.38	—	—	—	—

Table 5: Measured values for voltage regulator circuit

R_L (Ω)	V_{OC} (% diff)	V_S Drop (% diff)
100	0.359%	0.0%
330	0.102%	1.7%
1k	3.327%	0.0%

Table 6: Comparison of values for voltage regulator circuit

6 Conclusion

7 Equations

$$\%_{diff} = \frac{|nominal - measured|}{nominal} \times 100\% \quad (1)$$

$$\%_{reg} = \frac{V_{load} - V_{noload}}{V_{noload}} \times 100\% \quad (2)$$