

Data Converters

ELEC 330

Digital Systems Engineering

Dr. Ron Hayne

Images Courtesy of Ramesh Gaonkar and Delmar Learning

Basic Concepts

- ◆ Analog Signals
 - Continuous
 - Infinite values in a given range
 - Example
 - Clock face with hands
- ◆ Digital Signals
 - Discrete values
 - On/Off
 - 1/0
 - Example
 - Digital clock

Basic Concepts

- ◆ Limitations of analog signals
 - Pick up noise as they are amplified
 - Difficult to store
- ◆ Advantages of digital signals
 - Noise margin
 - Easily stored in memory
- ◆ Limitations of digital signals
 - How accurately analog signals are represented
 - Quantization


Embedded System

- ◆ Typical analog/digital system
 - Transducer
 - Converts non-electrical signals into electrical signals
 - A/D converter
 - Converts analog signals into digital signals
 - Digital processor
 - Processes digital data
 - D/A converter
 - Converts digital signals into equivalent analog signals
 - Transducer
 - Converts electrical signals into non-electrical signals

Analog-to-Digital Conversion

- ◆ A/D, ADC, or A-to-D

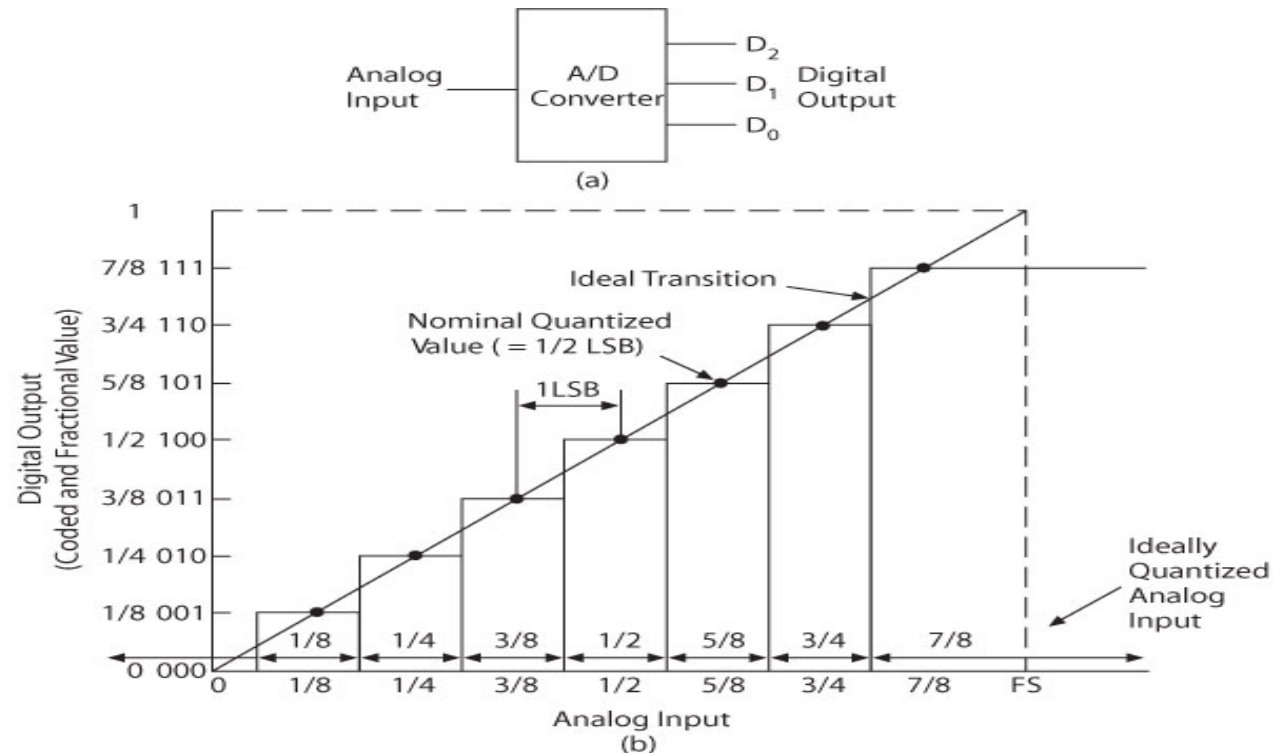- Converting a continuous varying signal, such as voltage or current, into discrete digital quantities that represent the magnitude of the signal compared to standard or reference




SOURCE: Analog Devices, Inc., Integrated Circuit Converters, Data Acquisition Systems, and Analog Signal Conditioning Components (Norwood, Mass.: Author, 1979), p. 1-18.

A/D Conversion

- ◆ Flash
 - Uses multiple comparators in parallel
 - High-speed, high cost
- ◆ Integrator
 - Charges a capacitor for a given amount of time
 - Slow, but high accuracy and low noise
- ◆ Successive Approximation
 - Effective compromise among resolution, speed, and cost
- ◆ Counter
 - Similar to successive approximation circuit
 - Slower, with variable conversion times


Successive Approximation

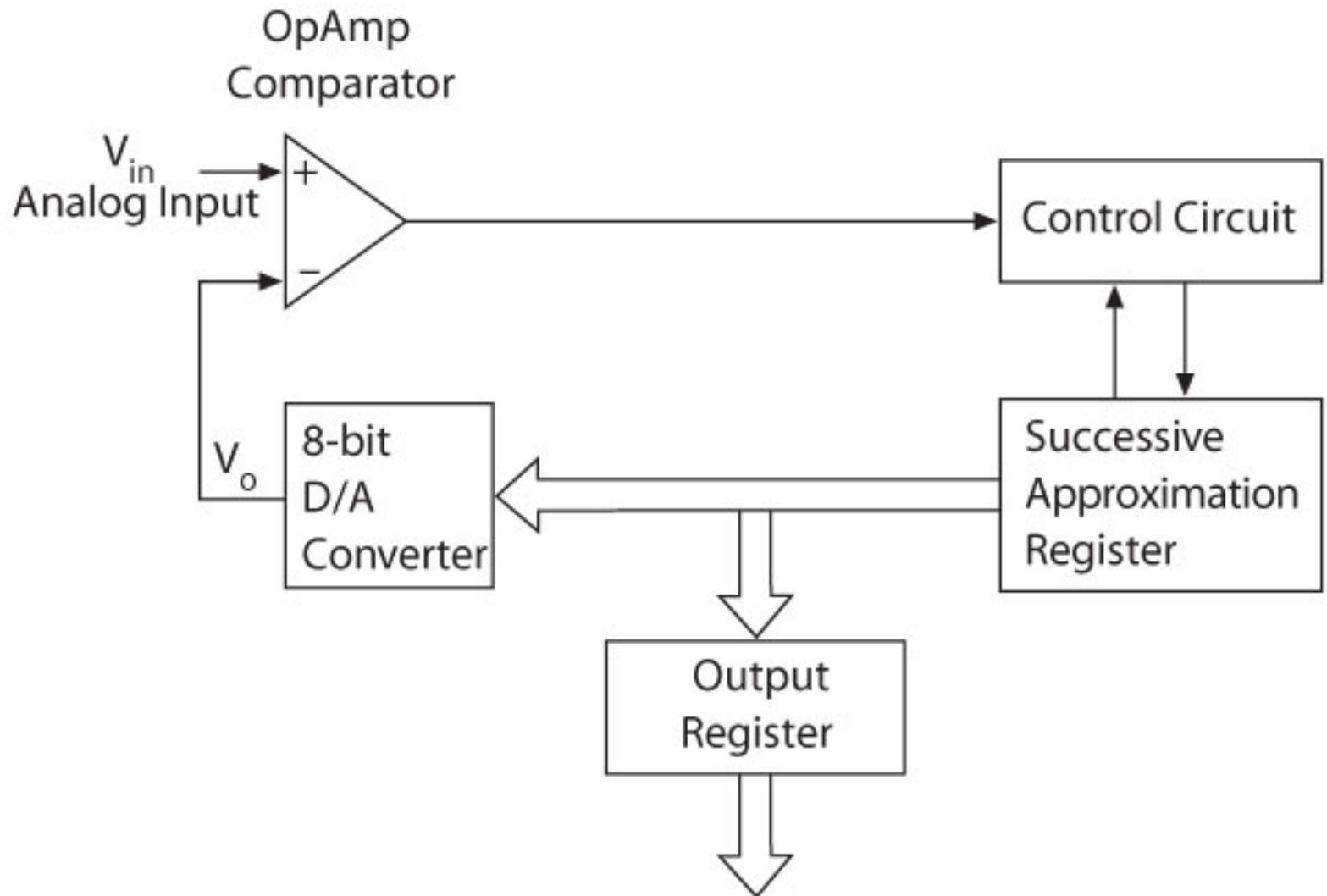

PIC18F A/D Converter Module

- ◆ The PIC18F4520
 - 10-bit A/D converter
 - 13 channels AN0 - AN12
 - Three control registers
 - ADCON0, ADCON1, and ADCON2
- ◆ The PIC18F452
 - 10-bit A/D converter
 - 8 channels AN0 - AN7
 - Two control registers
 - ADCON0 and ADCON1


PIC18F4520 A/D Converter

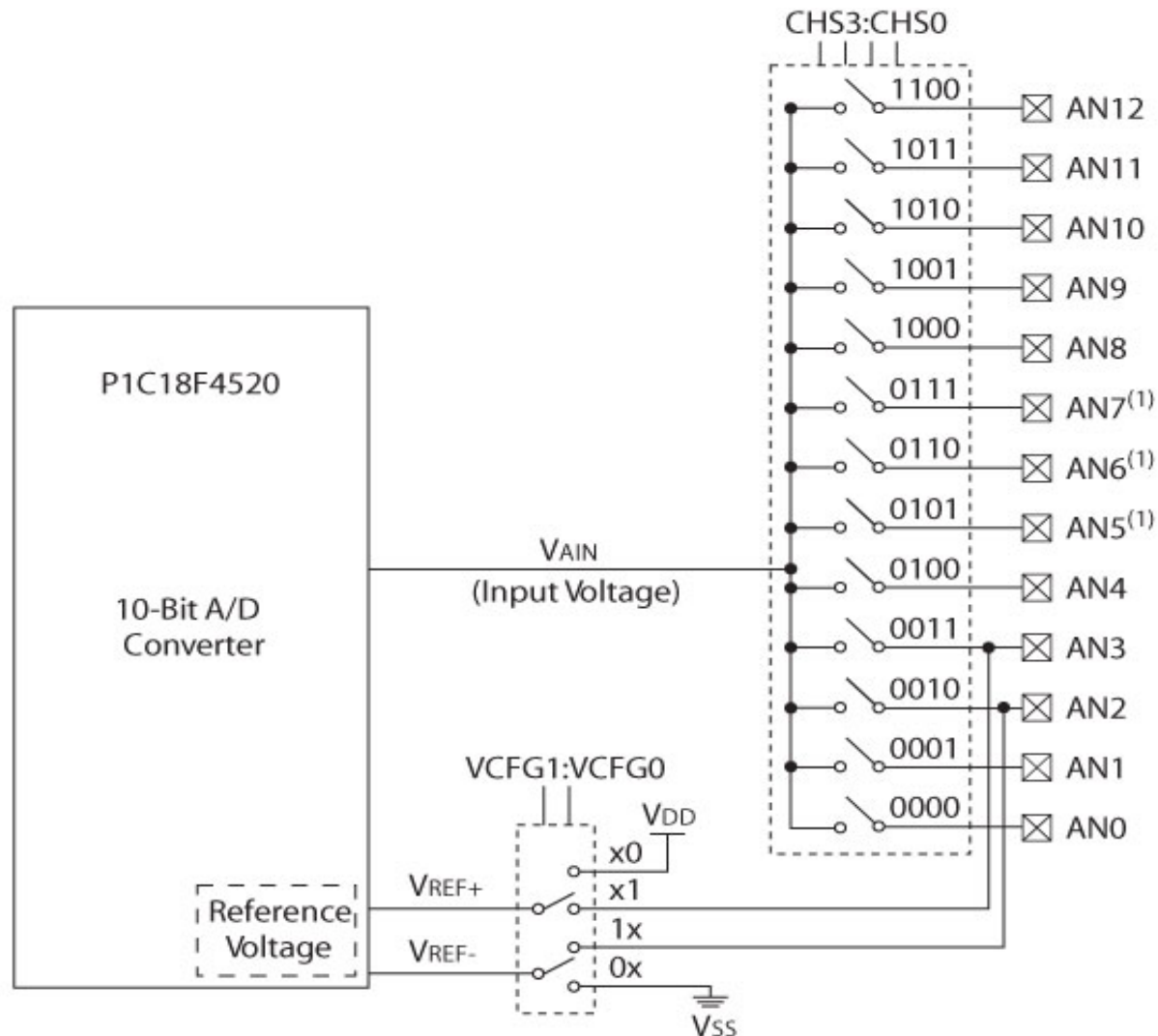

Note 1: Channels AN5 through AN7 are not available on 28-pin devices.
2: I/O pins have diode protection to V_{DD} and V_{SS}.


A/D Control Register0

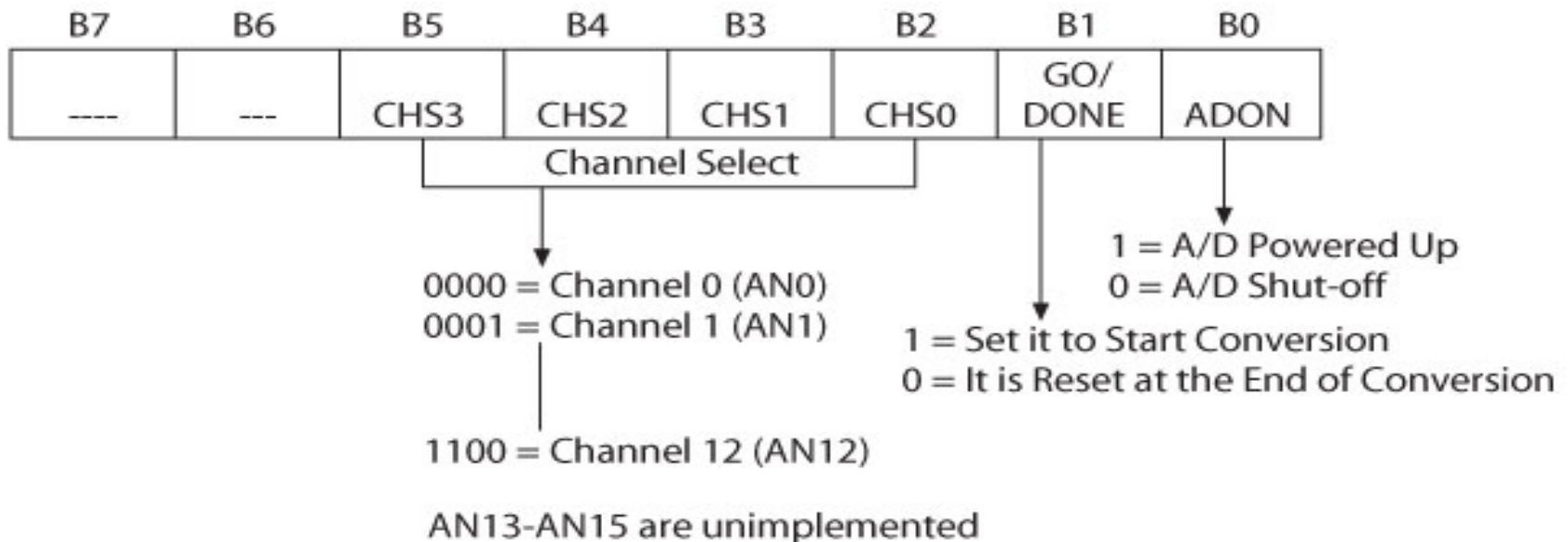- ◆ ADCON0 Register
 - Select channel for input analog signal
 - Start conversion
 - Indicate end of conversion



A/D Control Register1

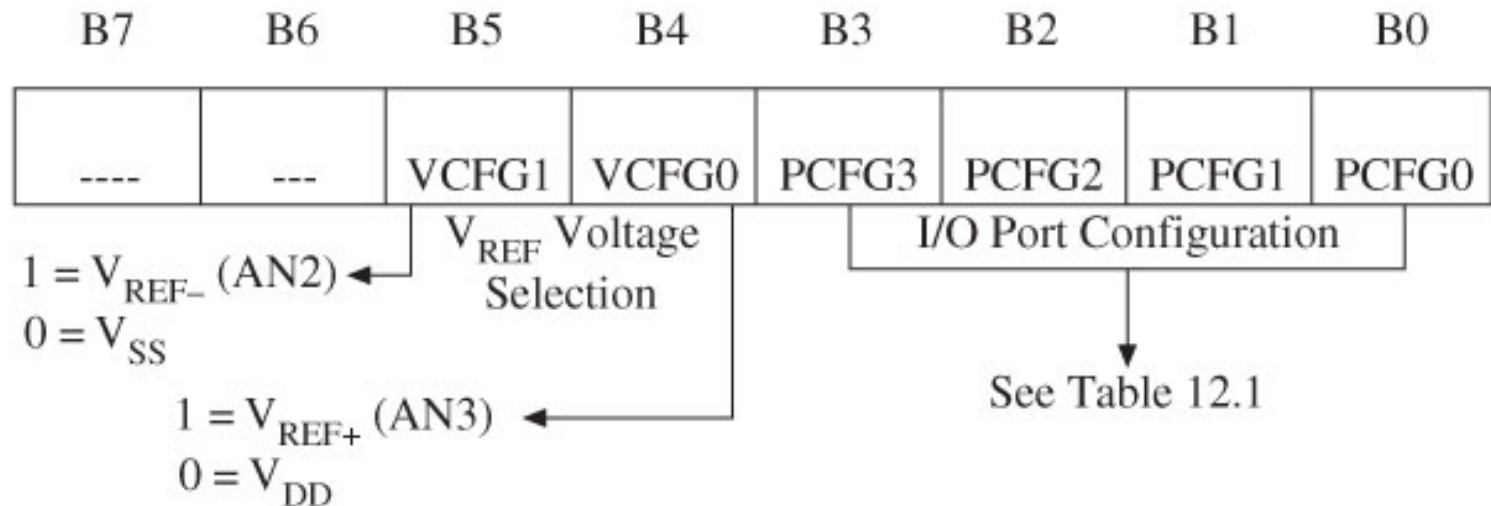
- ◆ ADCON1 Register
 - Set up I/O pins
 - Analog signal or digital signals
 - Select V_{REF} voltages



A/D Control Register2

◆ ADCON2 Register

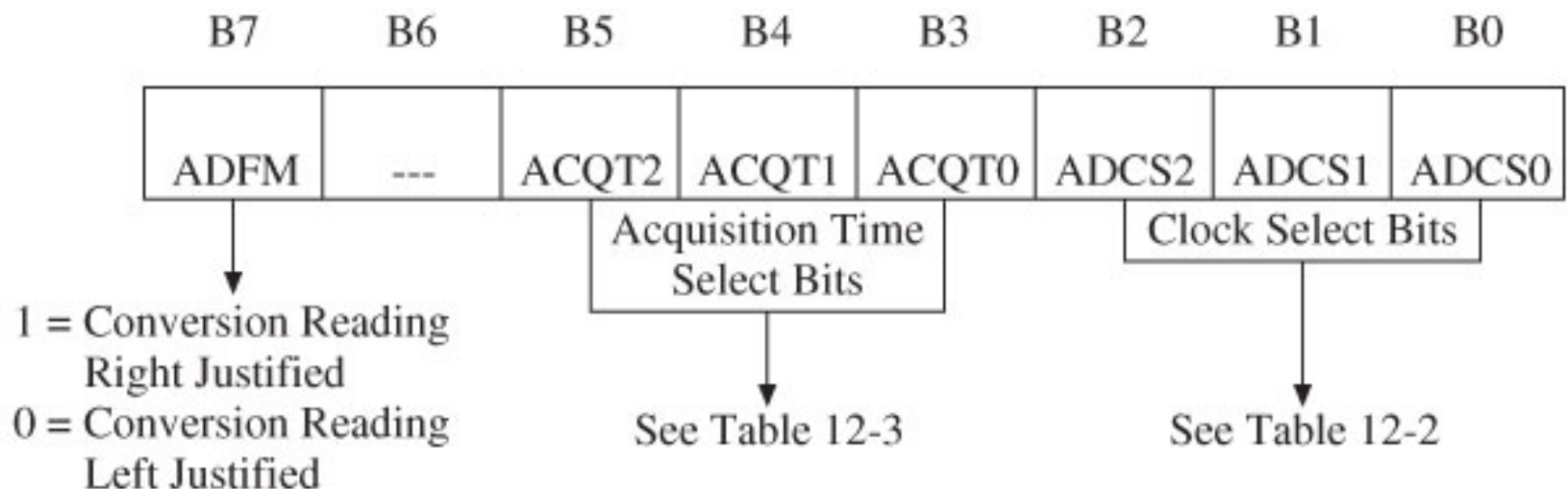- Select acquisition time and clock frequency
- Right or left justify output reading



PICDEM™ 2 PLUS DEMO BOARD ©2006


PICtail™

RE2	RA5	+5V
RE3	RA4	
RA7	RA3	
RA6	RC5	
RC7	RC4	
RC6	RC3	
RB7	RA0	GND
RB6	RA1	
RB5	RA2	
RB4	RC0	
RB3	RC1	
RB2	RC2	+5V
RB1	+5V	
RB0	GND	
RD1	RD0	
RD3	RD2	
RD5	RD4	
RD7	RD6	
RE1	RE0	+5V
GND		GND

Digital to Analog Conversion

- ◆ D/A, DAC, or D-to-A
 - Converting discrete signals into analog values that represent the magnitude of the input signal compared to a standard or reference
 - Output is discrete analog steps
 - Increasing the resolution (number of bits)
 - Step size is reduced
 - Approximates a continuous analog signal


D/A Converter Circuits

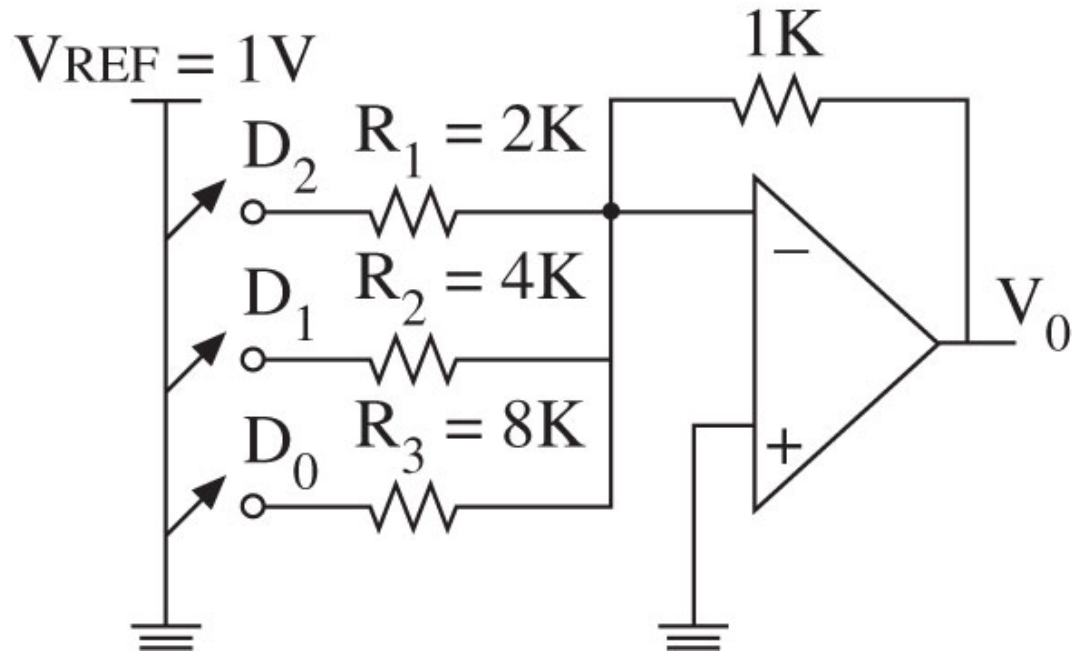

$$I_o = I_T = I_1 + I_2 + I_3 = \frac{V_{REF}}{R_1} + \frac{V_{REF}}{R_2} + \frac{V_{REF}}{R_3} = \frac{V_{REF}}{1\text{ k}} \left(\frac{1}{2} + \frac{1}{4} + \frac{1}{8} \right) = 0.875\text{ mA}$$

$$V_O = -R_f I_T = -(1\text{ k}) \times (0.875\text{ mA}) = -0.875\text{ V} = \left| \frac{7}{8}\text{ V} \right|$$

IC D/A Converters

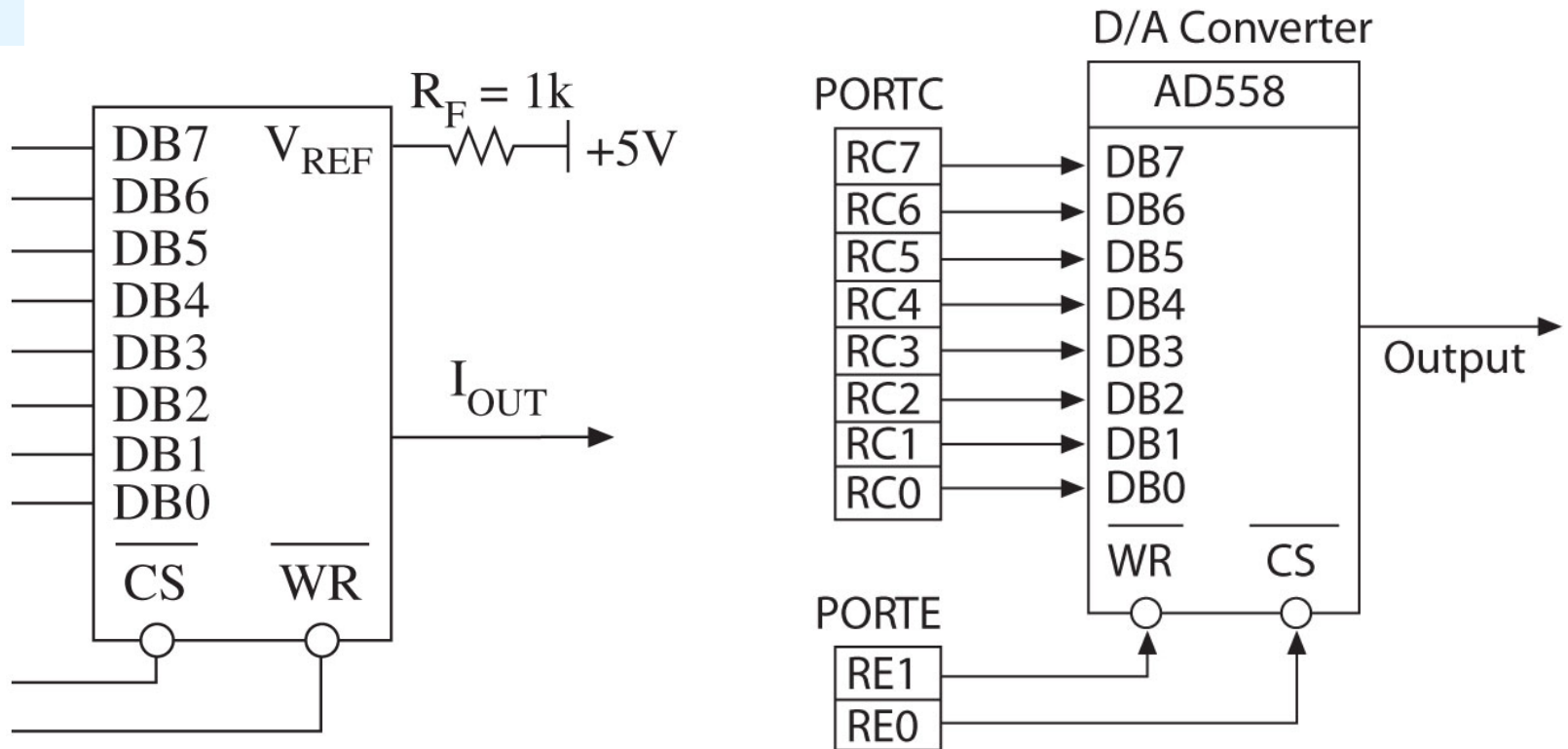

$$I_O = \frac{V_{REF}}{R_{REF}} \left(\frac{DB7}{2} + \frac{DB6}{4} + \frac{DB5}{8} + \dots + \frac{DB0}{2^8} \right)$$

$$I_O = 5 \text{ mA} \left(\frac{1}{2} + \frac{0}{4} + \frac{0}{8} + \frac{1}{16} + \frac{0}{32} + \frac{0}{64} + \frac{0}{128} + \frac{1}{256} \right) = 2.832 \text{ mA}$$