

Floating-Point Arithmetic

ELEC 418

Advanced Digital Systems

Dr. Ron Hayne

Images Courtesy of Thomson Engineering



IEEE 754 Floating-Point

- ◆ **Fraction**

- Sign-Magnitude

- ◆ **Exponent**

- Biased Notation

- ◆ **IEEE Single Precision Format**

S	Exponent	Fraction
1 bit	8 bits	23 bits

- ◆ **IEEE Double Precision Format**

S	Exponent	Fraction
1 bit	11 bits	52 bits

Special Cases

Single Precision		Double Precision		Object Represented
Exponent	Fraction	Exponent	Fraction	
0	0	0	0	0
0	nonzero	0	nonzero	\pm denormalized number
255	0	2047	0	\pm infinity
255	nonzero	2047	nonzero	NaN (not a number)

A Simple Floating-Point Format

◆ $N = F \times 2^E$

■ Fraction

- 4-bit 2's Complement
- s.fff
- Range -1 to +0.875

■ Exponent

- 4-bit 2's Complement
- eeee
- Range -8 to +7

■ Normalization

- Shift left until sign bit and next bit are different


■ Zero

- $F = 0.000$
- $E = 1000$
- $N = 0.000 \times 2^{-8}$

Floating-Point Multiplication


$$(F_1 \times 2^{E_1}) \times (F_2 \times 2^{E_2}) = (F_1 \times F_2) \times 2^{(E_1 + E_2)} \\ = F \times 2^E$$

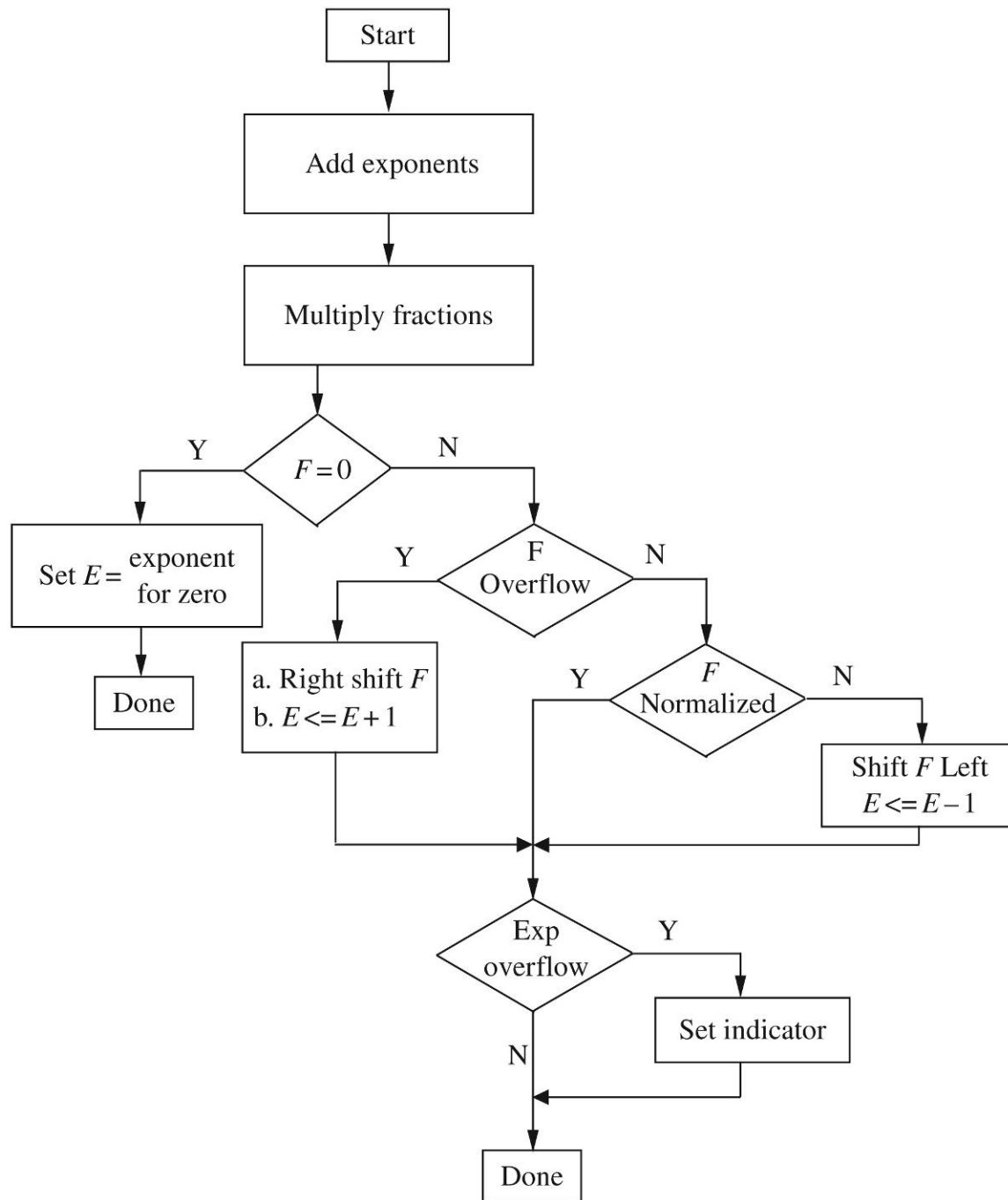1. Add exponents
2. Multiply fractions
3. If product is 0, adjust for proper 0
4. Normalize product fraction
5. Check for exponent overflow or underflow
6. Round product fraction




Floating-Point Hardware

FIGURE 7-7: Major Components of a Floating-Point Multiplier

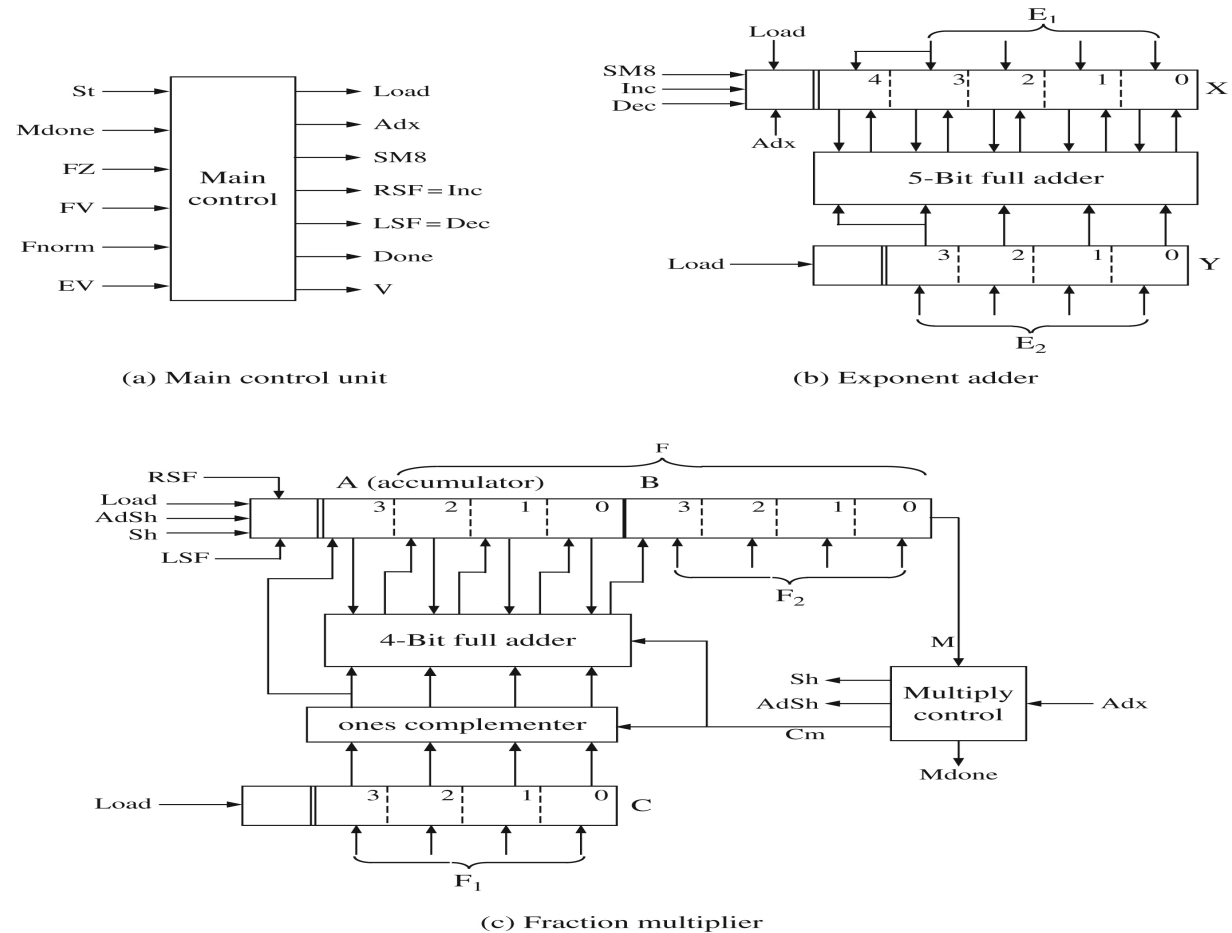


Floating-Point Hardware

FIGURE 7-7: Major Components of a Floating-Point Multiplier

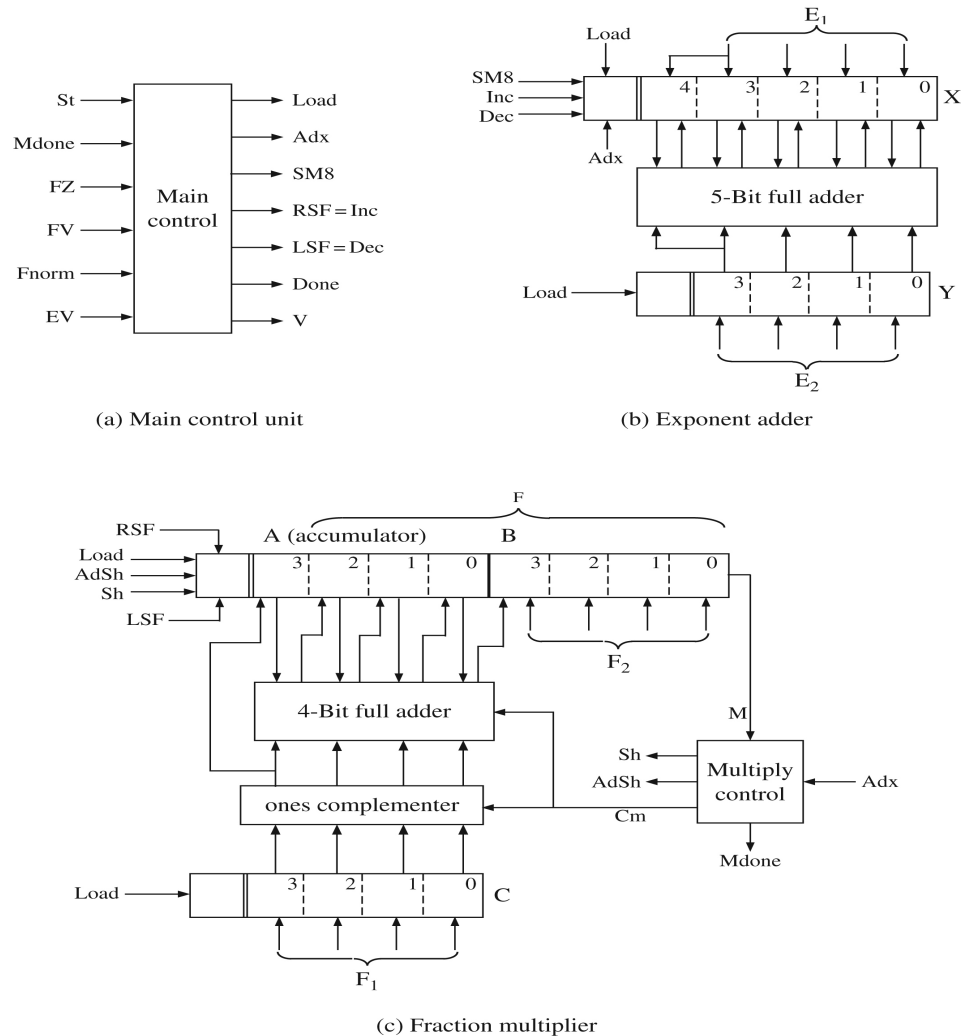

SM Chart

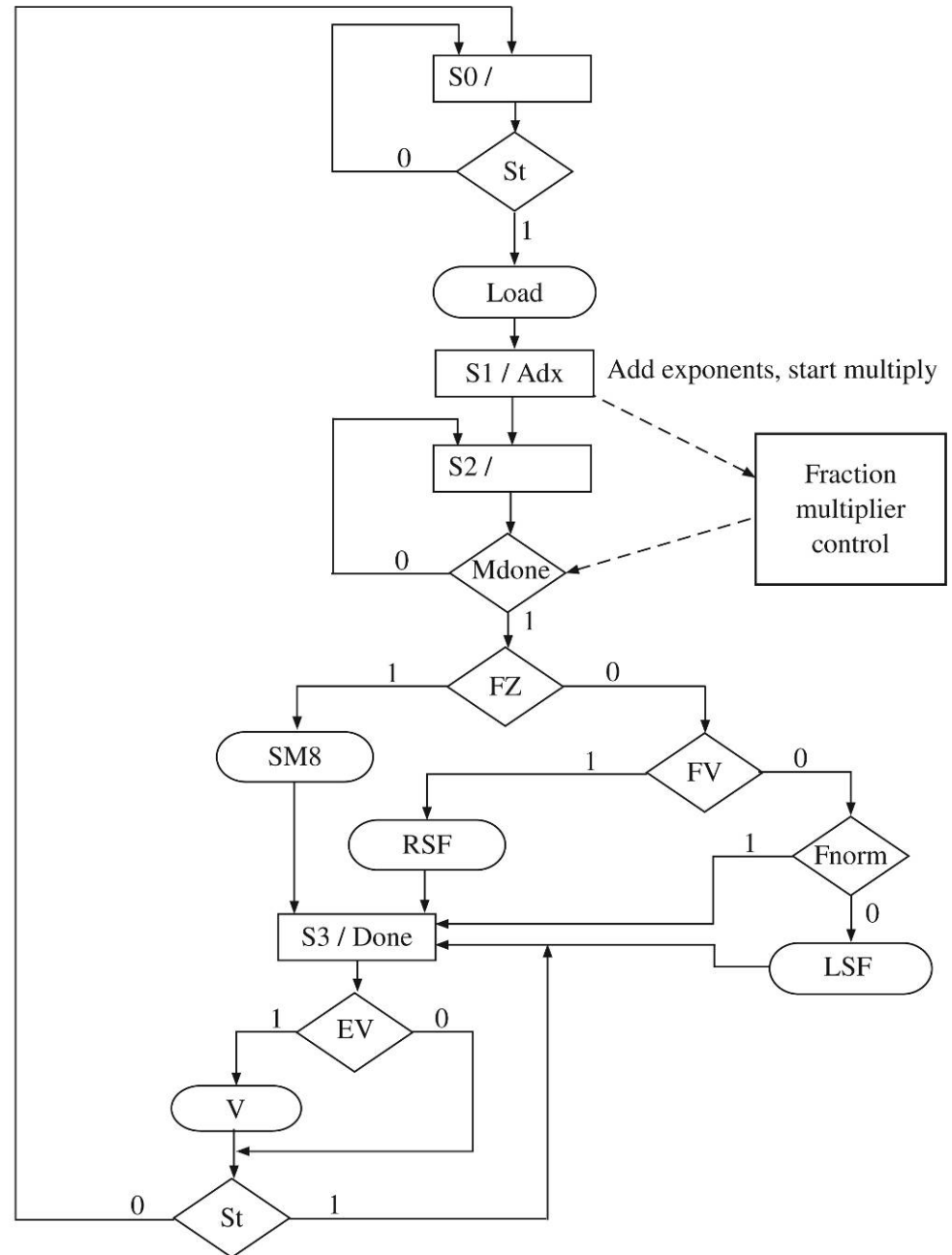

VHDL Model

```
library IEEE;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;

entity FMUL is
  port(CLK, St: in std_logic;
        F1, E1, F2, E2: in std_logic_vector(3 downto 0);
        F: out std_logic_vector(6 downto 0);
        E: out std_logic_vector(4 downto 0);
        V, done: out std_logic);
end FMUL2;
```

VHDL Model

architecture BEHAVE of FMUL is

```
signal A, B, C: std_logic_vector(3 downto 0);--F regs
signal compout, addout: std_logic_vector(3 downto 0);
alias M: std_logic is B(0);
signal X, Y: std_logic_vector(4 downto 0);  -- E regs

signal Load, Adx, SM8, RSF, LSF: std_logic; -- Main
signal AdSh, Sh, Cm, Mdone: std_logic; -- Mult

signal PS1, NS1: integer range 0 to 3;-- Main state
signal State, Nextstate: integer range 0 to 4;-- Mult
```

VHDL Model

```
begin
```

```
  main_control: process(PS1, St , Mdone, X, A, B)
```

```
  begin
```

```
    Load <= '0'; Adx <= '0'; NS1 <= 0; SM8 <= '0';
```

```
    RSF <= '0'; LSF <= '0'; V <= '0'; done <= '0';
```

```
    case PS1 is
```

```
      when 0 =>
```

```
        if St = '1' then
```

```
          Load <= '1';
```

```
          NS1 <= 1;
```

```
        end if;
```

```
      when 1 =>
```

```
        Adx <= '1';
```

```
        NS1 <= 2;
```


VHDL Model

```
when 2 =>
  if Mdone = '1' then
    if A = 0 then -- FZ
      SM8 <= '1';
    elsif A = 4 and B = 0 then -- FV
      RSF <= '1';
    elsif A(2) = A(1) then -- not Fnorm
      LSF <= '1';
    end if;
    NS1 <= 3;
  else
    NS1 <= 2;
  end if;
```

VHDL Model

```
when 3 =>
    done <= '1';
    if X(4) /= X(3) then -- EV
        V <= '1';
    end if;
    if ST = '0' then
        NS1 <= 0;
    end if;
end case;
end process main_control;
```

Multiplier Control

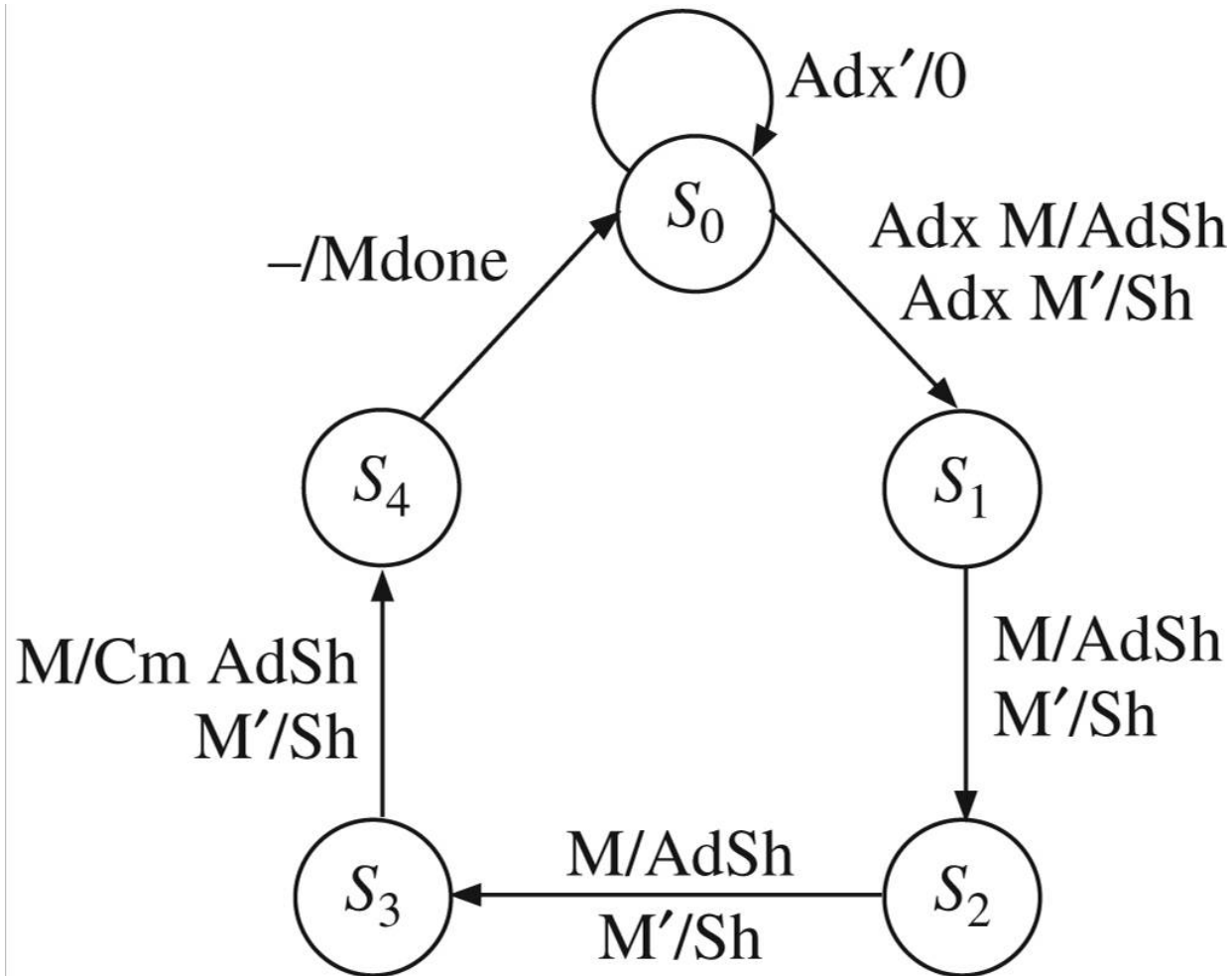

VHDL Model

```
mul2c: process(State, Adx, M)
begin
    AdSh <= '0'; Sh <= '0'; Cm <= '0'; Mdone <= '0';
    Nextstate <= 0;
    case State is
        when 0 =>
            if Adx = '1' then
                if M = '1' then
                    AdSh <= '1';
                else
                    Sh <= '1';
                end if;
                Nextstate <= 1;
            end if;
```


VHDL Model

```
when 1 | 2 =>
  if M = '1' then
    AdSh <= '1';
  else
    Sh <= '1';
  end if;
Nextstate <= State + 1;
```

VHDL Model

```
when 3 =>
    if M = '1' then
        Cm <= '1';
        AdSh <= '1';
    else
        Sh <= '1';
    end if;
    Nextstate <= 4;
when 4 =>
    Mdone <= '1';
    Nextstate <= 0;
end case;
end process mul2c;
```

Data Path

FIGURE 7-7: Major Components of a Floating-Point Multiplier


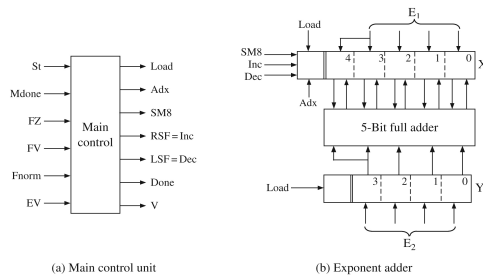
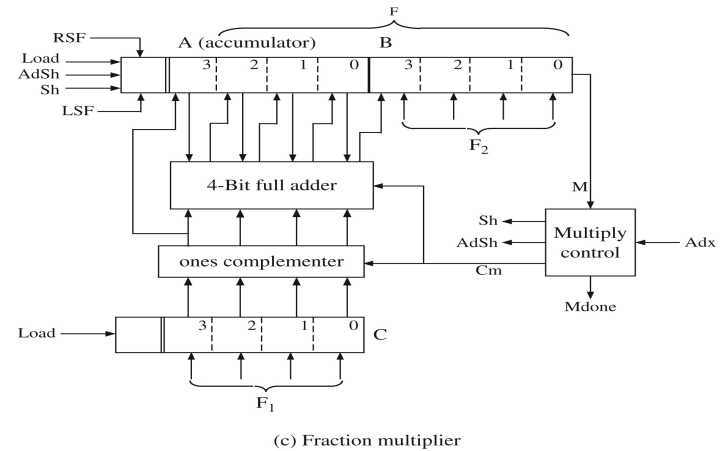
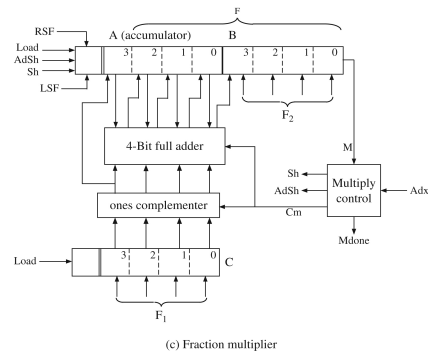


FIGURE 7-7: Major Components of a Floating-Point Multiplier

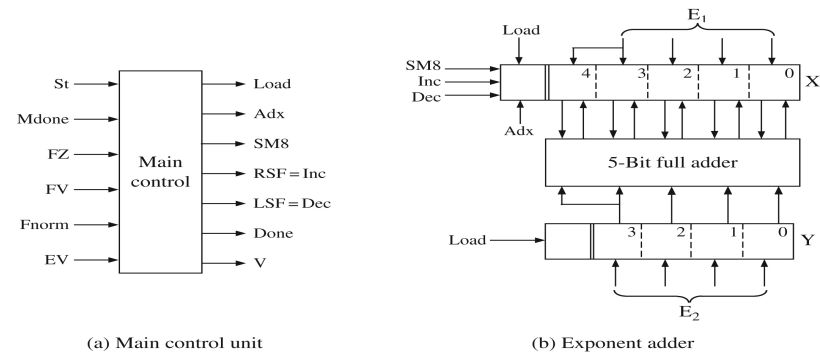

VHDL Model

```
compout <= not C when Cm = '1' else C;
addout <= A + compout + Cm;
datapath: process (CLK)
begin
    if rising_edge (CLK) then
        PS1 <= NS1;
        State <= Nextstate;
        if Load = '1' then
            X <= E1(3) & E1;
            Y <= E2(3) & E2;
            A <= "0000";
            B <= F2;
            C <= F1;
        end if;
```

VHDL Model

```
if ADX = '1' then
    X <= X + Y;
end if;
if SM8 = '1' then
    X <= "11000";
end if;
```

VHDL Model

```
if RSF = '1' then
    A <= '0' & A(3 downto 1);
    B <= A(0) & B(3 downto 1);
    X <= X + 1;
end if;

if LSF = '1' then
    A <= A(2 downto 0) & B(3);
    B <= B(2 downto 0) & '0';
    X <= X - 1;
end if;
```


VHDL Model

```
    if AdSh = '1' then
        A <= compout(3) & addout(3 downto 1);
        B <= addout(0) & B(3 downto 1);
    end if;
    if Sh = '1' then
        A <= A(3) & A(3 downto 1);
        B <= A(0) & B(3 downto 1);
    end if;
end if;

end process datapath;

F <= A(2 downto 0) & B;
E <= X;
end BEHAVE;
```


VHDL Simulation

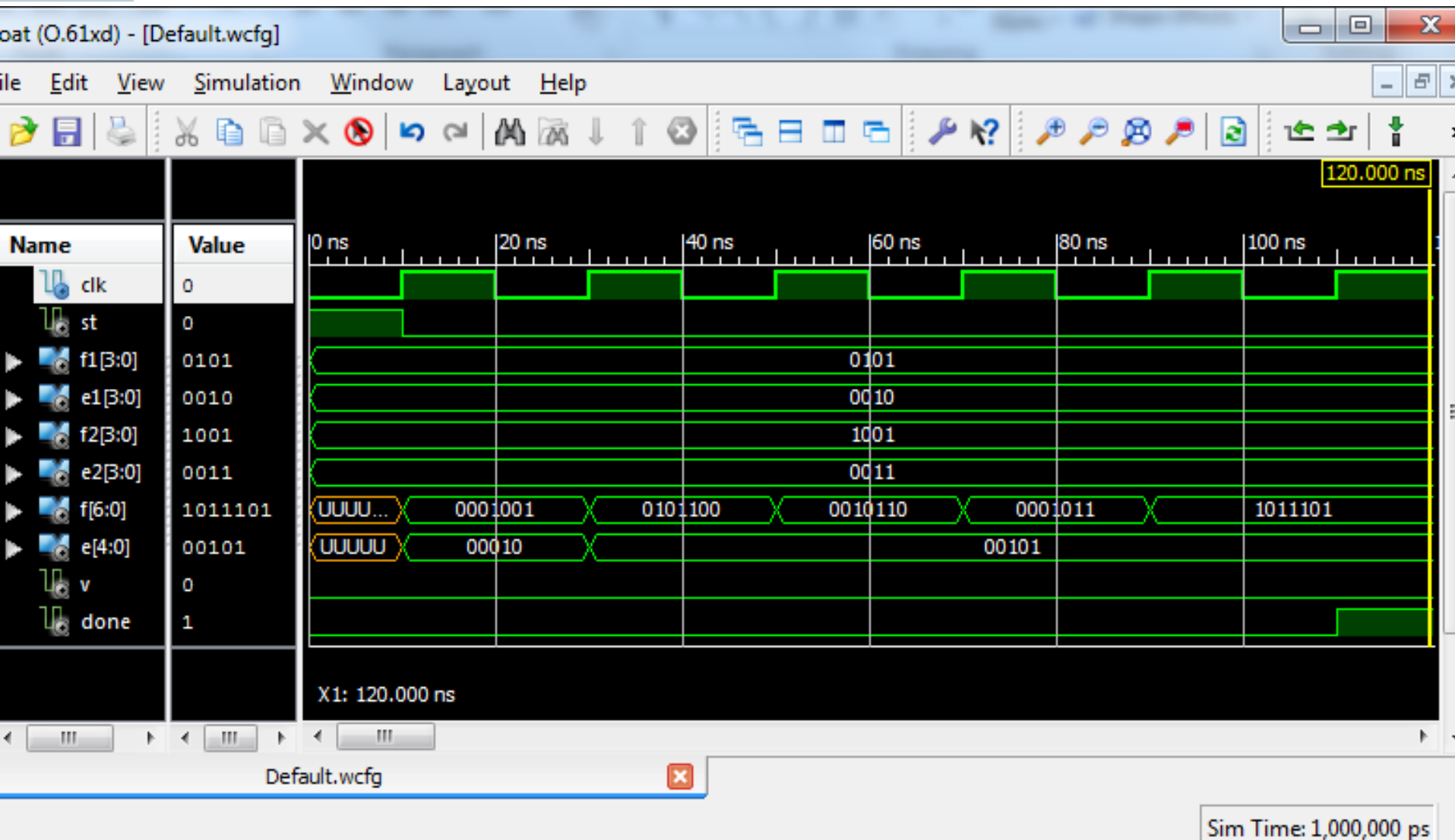

FPGA Implementation

VIO Console - DEV...

Bus/Signal	Value
St	
Done	0
F1i	5
E1i	2
F2i	9
E2i	3
F	5D
E	05
V	0

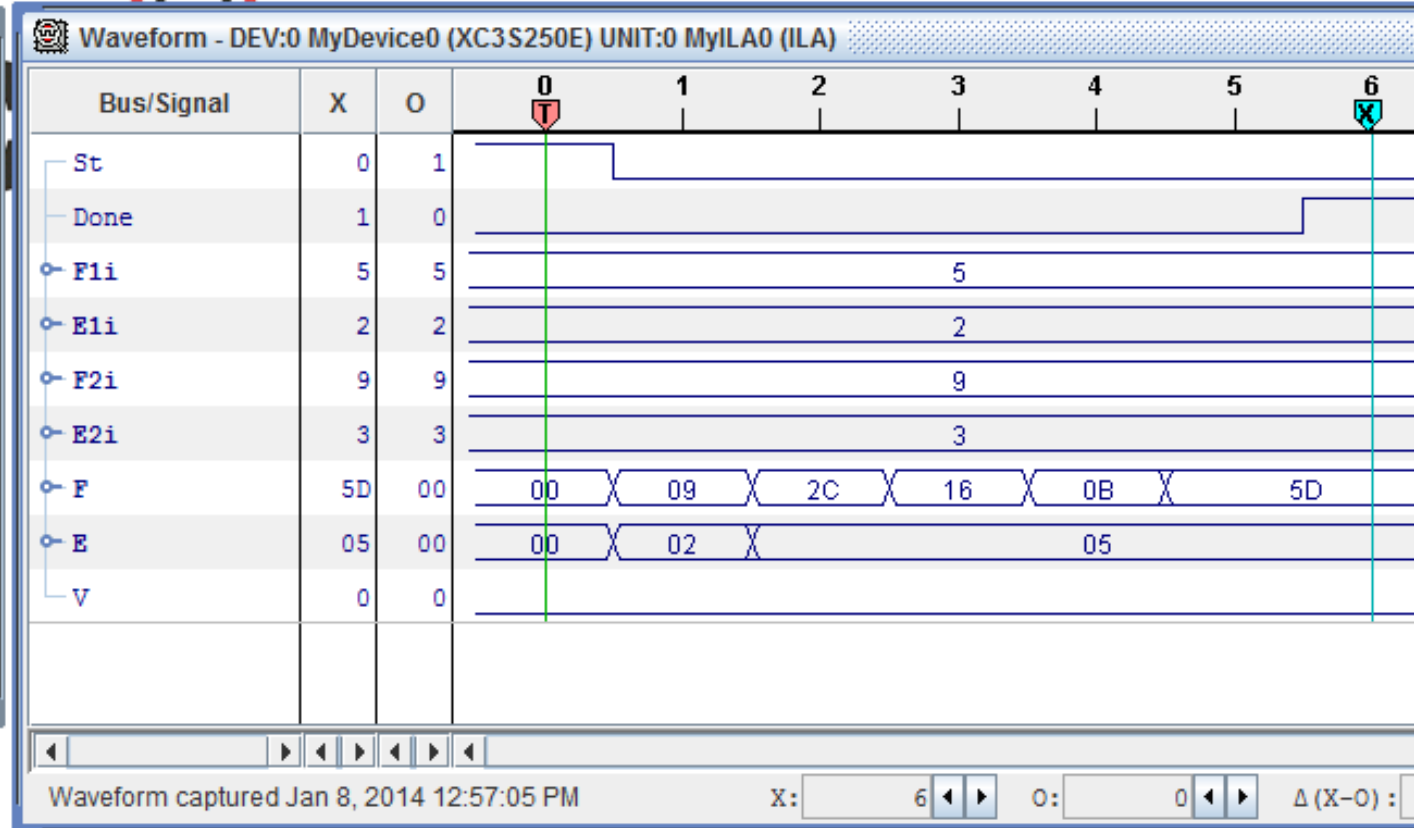

Floating-Point Addition


$$(F_1 \times 2^{E_1}) + (F_2 \times 2^{E_2}) = F \times 2^E$$

1. Compare exponents. If not equal, shift smaller fraction to right and add 1 to exponent (repeat).
2. Add fractions.
3. If result is 0, adjust for proper 0.
4. If fraction overflow, shift right and add 1.
5. If unnormalized, shift left and subtract 1 (repeat).
6. Check for exponent overflow.
7. Round fraction. If not normalized, go to step 4.

Floating-Point Hardware

- ◆ Comparator for exponents (step 1a)
- ◆ Shift register (right), incrementer (step 1b)
- ◆ ALU (adder) to add fractions (step 2)
- ◆ Shifter (right/left), incrementer/decrementer (steps 4,5)
- ◆ Overflow detector (step 6)
- ◆ Rounding hardware (step 7)

Floating-Point Adder

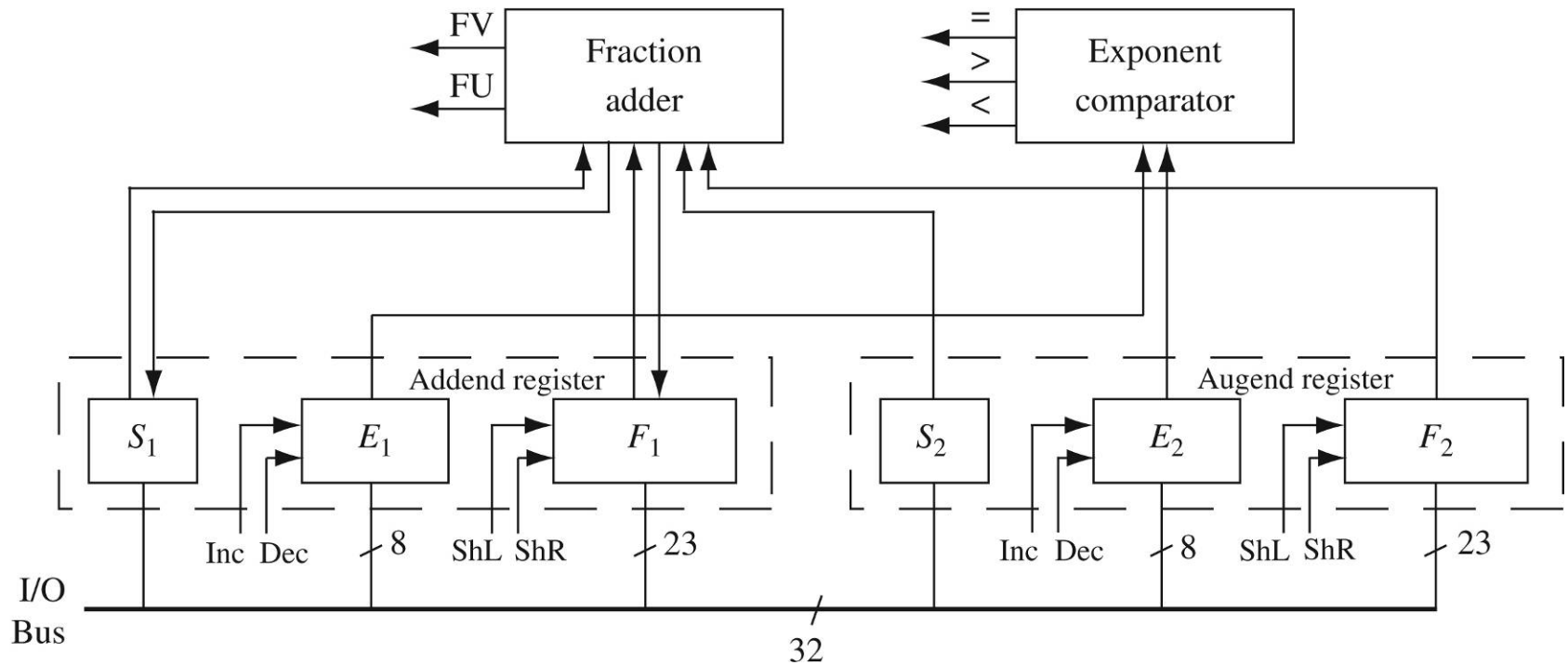

* IEEE Format

VHDL Model

```
entity FPADD is
```

```
    port(CLK, St: in std_logic;
```

```
          done, ovf, unf: out std_logic;
```

```
          FPinput: in std_logic_vector(31 downto 0);
```

```
          FPsum: out std_logic_vector(31 downto 0));
```

```
end FPADD;
```

```
architecture FPADDER of FPADD is
```

```
    signal F1, F2: std_logic_vector(25 downto 0);
```

```
    signal E1, E2: std_logic_vector(7 downto 0);
```

```
    signal S1, S2, FV, FU: std_logic;
```

```
    signal F1comp, F2comp: std_logic_vector(27 downto 0);
```

```
    signal Addout, Fsum: std_logic_vector(27 downto 0);
```

```
    signal State: integer range 0 to 6;
```

VHDL Model

begin

```
F1comp <= not("00" & F1) + 1 when S1 = '1' else  
          "00" & F1;
```

```
F2comp <= not("00" & F2) + 1 when S2 = '1' else  
          "00" & F2;
```

```
Addout <= F1comp + F2comp;
```

```
Fsum <= Addout when Addout(27) = '0' else  
        not Addout + 1;
```

```
FV <= Fsum(27) xor Fsum(26);
```

```
FU <= not F1(25);
```

```
FPsum <= S1 & E1 & F1(24 downto 2);
```

VHDL Model

```
process (CLK)
begin
  if rising_edge (CLK) then
    case State is
      when 0 =>
        if St = '1' then
          E1 <= FPinut(30 downto 23); S1 <= FPinut(31);
          F1(24 downto 0) <= FPinut(22 downto 0) & "00";
          if FPinut = 0 then
            F1(25) <= '0';
          else
            F1(25) <= '1';
          end if;
          done <= '0'; ovf <= '0'; unf <= '0'; State <= 1;
        end if;
      end case;
    end if;
  end if;
```

VHDL Model

```
when 1 =>
```

```
    E2 <= FPinut(30 downto 23); S2 <= FPinut(31);
```

```
    F2(24 downto 0) <= FPinut(22 downto 0) & "00";
```

```
    if FPinut = 0 then
```

```
        F2(25) <= '0';
```

```
    else
```

```
        F2(25) <= '1';
```

```
    end if;
```

```
    State <= 2;
```


VHDL Model

```
when 2 =>
  if F1 = 0 or F2 = 0 then
    State <= 3;
  else
    if E1 = E2 then
      State <= 3;
    elsif E1 < E2 then
      F1 <= '0' & F1(25 downto 1); E1 <= E1 + 1;
    else
      F2 <= '0' & F2(25 downto 1); E2 <= E2 + 1;
    end if;
  end if;
```

VHDL Model

```
when 3 =>
  S1 <= Addout(27);
  if FV = '0' then
    F1 <= Fsum(25 downto 0);
  else
    F1 <= Fsum(26 downto 1); E1 <= E1 + 1;
  end if;
  State <= 4;
when 4 =>
  if F1 = 0 then
    E1 <= "00000000"; State <= 6;
  else
    State <= 5;
  end if;
```

VHDL Model

```
when 5 =>
  if E1 = 0 then
    unf <= '1'; State <= 6;
  elsif FU = '0' then
    State <= 6;
  else
    F1 <= F1(24 downto 0) & '0'; E1 <= E1 - 1;
  end if;
when 6 =>
  if E1 = 255 then
    ovf <= '1';
  end if;
  done <= '1'; State <= 0;
end case; end if; end process; end FPADDER;
```

Summary

- ♦ IEEE Floating-Point Formats
- ♦ Simple Floating-Point Format
- ♦ Floating-Point Multiplication
- ♦ Floating-Point Addition