

Notes – AC Part 2

Slides from Dr. Barsanti

Power in Single Phase AC Circuits

- Real Power
- Reactive Power
- Apparent Power
- Power Factor
- Complex Power
- Examples

Real Power P

Real Power: The same as the average power and is sometimes called the active power. It has units of watts.

- $P = P_{\text{avg}} = V_{\text{rms}} I_{\text{rms}} \cos(\Phi_v - \Phi_i) = V_{\text{rms}} I_{\text{rms}} \text{ pf}$

$$\text{Power factor} = \text{pf} = \cos(\Phi_v - \Phi_i)$$

Power Factor Angle

$$\Phi_{pf} = \Phi_v - \Phi_i$$

Lagging PF: For inductive loads, the current lags the voltage so that $0 < \Phi_{pf} < 180$.

Leading PF: For capacitive, the current leads the voltage so that $-180 < \Phi_{pf} < 0$.

ELI the ICE man

P(t) for general RLC Load

- Recall that:

$$P(t) = v(t)i(t) = V \cos(\omega t + \Phi_v) I \cos(\omega t + \Phi_i)$$

$$P(t) = \frac{1}{2} V I \{ \cos(\Phi_v - \Phi_i) + \cos(2\omega t + \Phi_v + \Phi_i) \}$$

- Can you show that

$$P(t) = V_{\text{rms}} I_{\text{rms}} \cos \Phi_{\text{pf}} \{ 1 + \cos[2(\omega t + \Phi_v)] \} + \\ V_{\text{rms}} I_{\text{rms}} \sin \Phi_{\text{pf}} \sin[2(\omega t + \Phi_v)] ?$$

Real, Reactive, and Apparent Power

- *Real Power (units = watts)*

$$P_{avg} = P = V_{rms} I_{rms} \cos \Phi_{pf}$$

- *Reactive Power (units = VAR)*

$$Q = V_{rms} I_{rms} \sin \Phi_{pf}$$

- *Apparent Power (units = VA)*

$$|S| = V_{rms} I_{rms}$$

Complex Power

- Given the general RLC case let


$$\tilde{V} = V_{rms} \angle \Phi_v \quad \text{and} \quad \tilde{I} = I_{rms} \angle \Phi_i$$

- Then the complex power is defined

$$\begin{aligned} \tilde{S} &= \tilde{V} \tilde{I}^* = (V_{rms} \angle \Phi_v)(I_{rms} \angle -\Phi_i) \\ &= V_{rms} I_{rms} \angle (\Phi_v - \Phi_i). \end{aligned}$$

- In rectangular form


$$S = V_{rms} I_{rms} \cos(\Phi_v - \Phi_i) + j V_{rms} I_{rms} \sin(\Phi_v - \Phi_i).$$

$$S = P + jQ$$


Power Triangle

$$\begin{array}{ccccc} S & = & P & + & jQ \\ \uparrow & & \uparrow & & \uparrow \\ \text{complex} & & \text{real} & & \text{reactive} \\ \text{power} & & \text{power} & & \text{power} \end{array}$$

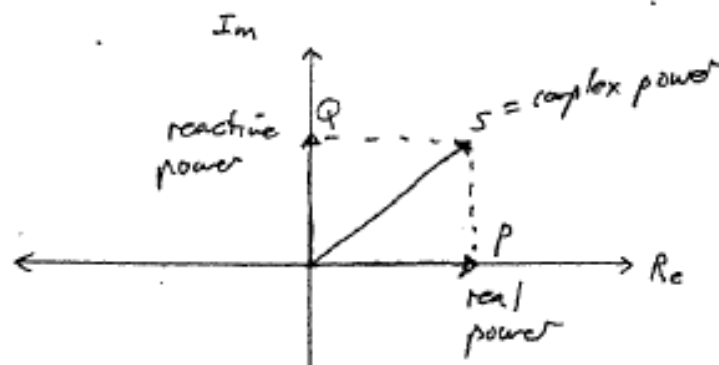which may be conveniently sketched in the complex plane to reveal the power triangle



Passive sign convention

With + conventional current entering the + voltage terminal of a device, then

$P > 0$: real power absorbed by device

$P < 0$: real power delivered by device

$Q > 0$: reactive power absorbed by device


$Q < 0$: reactive power delivered by device

Measuring PF

- In the lab we can find PF without measuring voltage and current phase angles since;

$$PF = \frac{P}{|S|} = \frac{\text{real power}}{\text{apparent power}} = \frac{\text{watt meter reading}}{\text{Volt meter} \times \text{ammeter}}$$

Ex. 1 Derive P , Q and S for the source

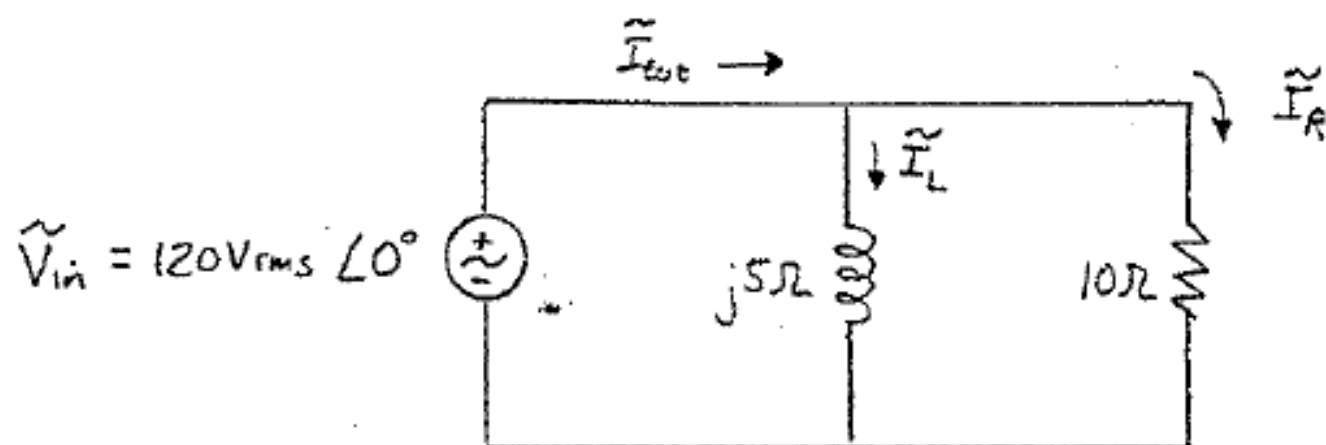

$$\tilde{I}_R = \frac{\tilde{V}_{in}}{R} = \frac{120V_{rms} \angle 0^\circ}{10\Omega} = 12A_{rms} \angle 0^\circ$$

$$\tilde{I}_L = \frac{\tilde{V}_{in}}{jX_L} = \frac{120V_{rms} \angle 0^\circ}{5\Omega \angle 90^\circ} = 24A_{rms} \angle -90^\circ$$

$$\tilde{I}_{tot} = \tilde{I}_R + \tilde{I}_L = 26.83A_{rms} \angle -63.43^\circ$$

- EX 1 cont..

and the current into the $+$ side of V_{in}

$$\tilde{I}_{in} = -\tilde{I}_{tot} = 26.83 \text{ Arms } \angle +116.57^\circ$$

$$S = \tilde{V}_{in} \tilde{I}_{in}^* = (120 \text{ Vrms } \angle 0^\circ) (26.83 \text{ Arms } \angle -116.57^\circ)$$

$$S = 3219.94 \text{ VA } \angle -116.57^\circ$$

$$S = -1440 \text{ w} - j 2880 \text{ var}$$

- $P = 1440 \text{ w}$ delivered
- $Q = 2880 \text{ var}$ delivered

Power Factor Correction

- What is the big deal about the power factor?


Since $|S| = \sqrt{P^2 + Q^2} = V_{rms} I_{rms}$ then for a fixed supply voltage and a given real power P , the larger the Q the larger the required I_{rms} . This means all the distribution equipment (lines, cables, transformers, circuit breakers, etc.) must be sized for the larger I_{rms} . Additionally, larger $I^2 R$ losses will occur in transmission lines.

Thus we want to keep Q small so that

$$PF = \frac{P}{\sqrt{P^2 + Q^2}} \sim 1$$


Example 2

Ex. 2. Calculate the power to be delivered by a capacitor connected in parallel with the previous load in order to increase the source power factor to 0.95 lagging

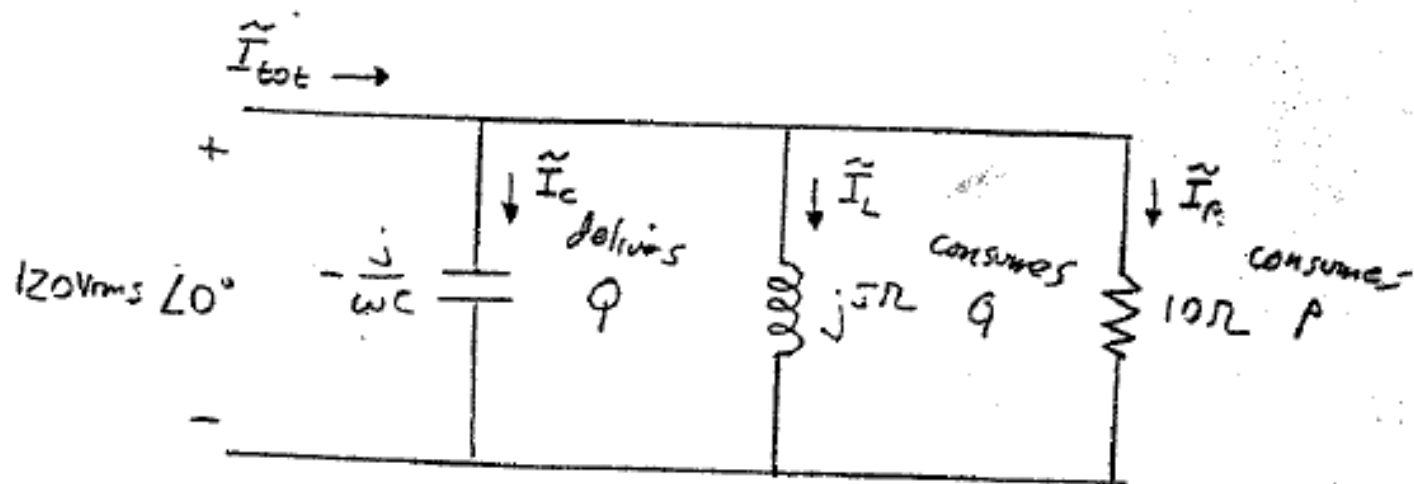

Ex 2...

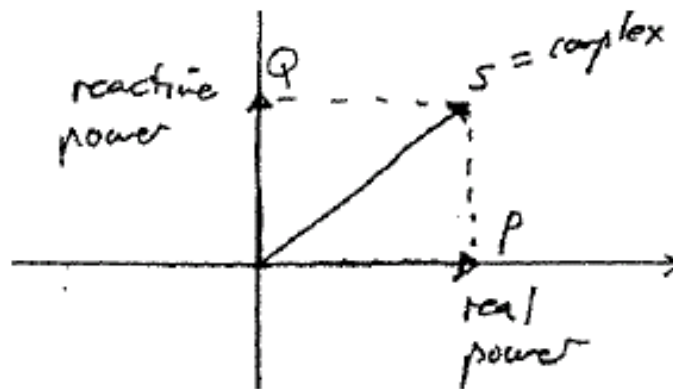- Recall: $P_{old} = 1440 \text{ W}$, $Q_{old} = 2880 \text{ VAR}$,
and $S_{old} = 3220 \text{ VA}$.
- We require $\text{pf} = \cos \Phi_{new} = 0.95 \Rightarrow \Phi_{new} = 18.2$
- Using the power triangle



$$\tan \Phi_{new} = \frac{Q_{new}}{P_{old}}$$

$$\begin{aligned} Q_{new} &= P_{old} \tan \Phi_{new} \\ &= 1440 \tan (18.2) \\ &= \mathbf{473 \text{ VAR}} \end{aligned}$$

$$\begin{aligned} Q_{cap} &= Q_{old} - Q_{new} \\ &= \mathbf{2407 \text{ VAR}} \end{aligned}$$

Example 3

Compare currents circuits of Ex 1 and Ex 2

- Circuit 1 has

$$PF_1 = \frac{P}{S} = \frac{1440}{3220} = 0.44 \quad I_1 = 26.8 \text{ A}$$


- Circuit 2 has

$$PF_2 = 0.95 \quad I_2 = \frac{S}{V} = \frac{\sqrt{1440^2 + 473^2}}{120} = \frac{1516}{120} = 12.6 \text{ A}$$

- Clearly the higher PF leads to smaller required current.


Adding Complex Powers

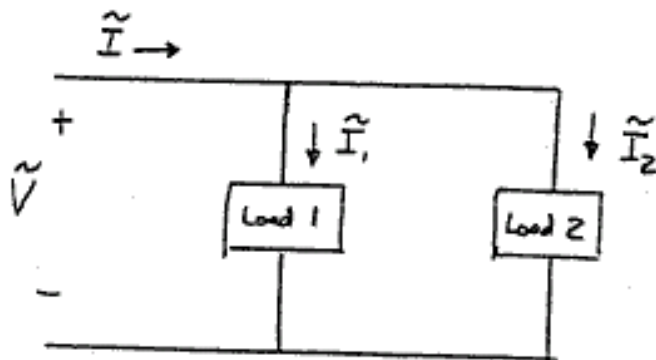- The total power is the sum of the component powers regardless of their interconnection.



$$\begin{aligned}\tilde{S} &= \tilde{V} \tilde{I}^* = \tilde{V} \{ \tilde{I}_1^* + \tilde{I}_2^* \} \\ &= (P_1 + jQ_1) + (P_2 + jQ_2) \\ &= (P_1 + P_2) + j(Q_1 + Q_2) \\ &= P_{\text{TOT}} + j Q_{\text{TOT}}\end{aligned}$$

EX 4 Find S_1 and S_2

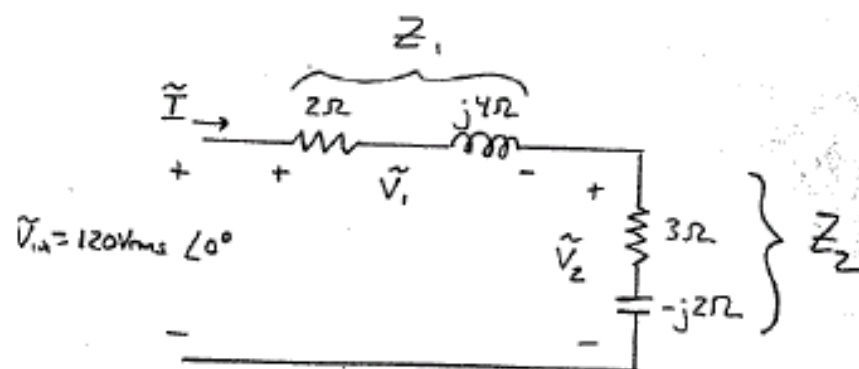

$$\tilde{I} = \frac{\tilde{V}}{Z_1 + Z_2} = \frac{120V \angle 0}{(2 + j4) + (3 - j2)} = 22.3A \angle -21.8$$

$$\tilde{V}_1 = Z_1 \tilde{I} = (4.47 \angle 63.4)(22.3 \angle -21.8) = 99.6V \angle 41.6$$

$$\tilde{V}_2 = Z_2 \tilde{I} = (3.61 \angle -33.7)(22.3 \angle -21.8) = 80.3V \angle -55.5$$

EX 4 cont.

$$S_1 = \widetilde{V}_1 \widetilde{I}_1^* = 2220 \text{ VA} \angle 63.4 = 993 \text{ W} + j 1986 \text{ VAR}$$

$$S_2 = \widetilde{V}_2 \widetilde{I}_2^* = 1790 \text{ VA} \angle -33.7 = 1489 \text{ W} - j 993 \text{ VAR}$$

$$S_{TOT} = \widetilde{V} \widetilde{I}^* = (120\text{V} \angle 0)(22.3\text{A} \angle 21.8) = 2673\text{VA} \angle 21.8$$

$$S_{TOT} = 2482.3\text{W} + j 993 \text{ VAR}$$

And therefore

$$S_{TOT} = P_{TOT} + j Q_{TOT} = S_1 + S_2 = P_1 + P_2 + j(Q_1 + Q_2)$$