

Sequential Analysis

ELEC 311

Digital Logic and Circuits

Dr. Ron Hayne


Images Courtesy of Cengage Learning




State Tables and Graphs

Present State	Next State		Output Z
	X = 0	X = 1	
S0	S1	S0	0
S1	S3	S2	0
S2	S3	S0	0
S3	S3	S0	1


Analysis Example

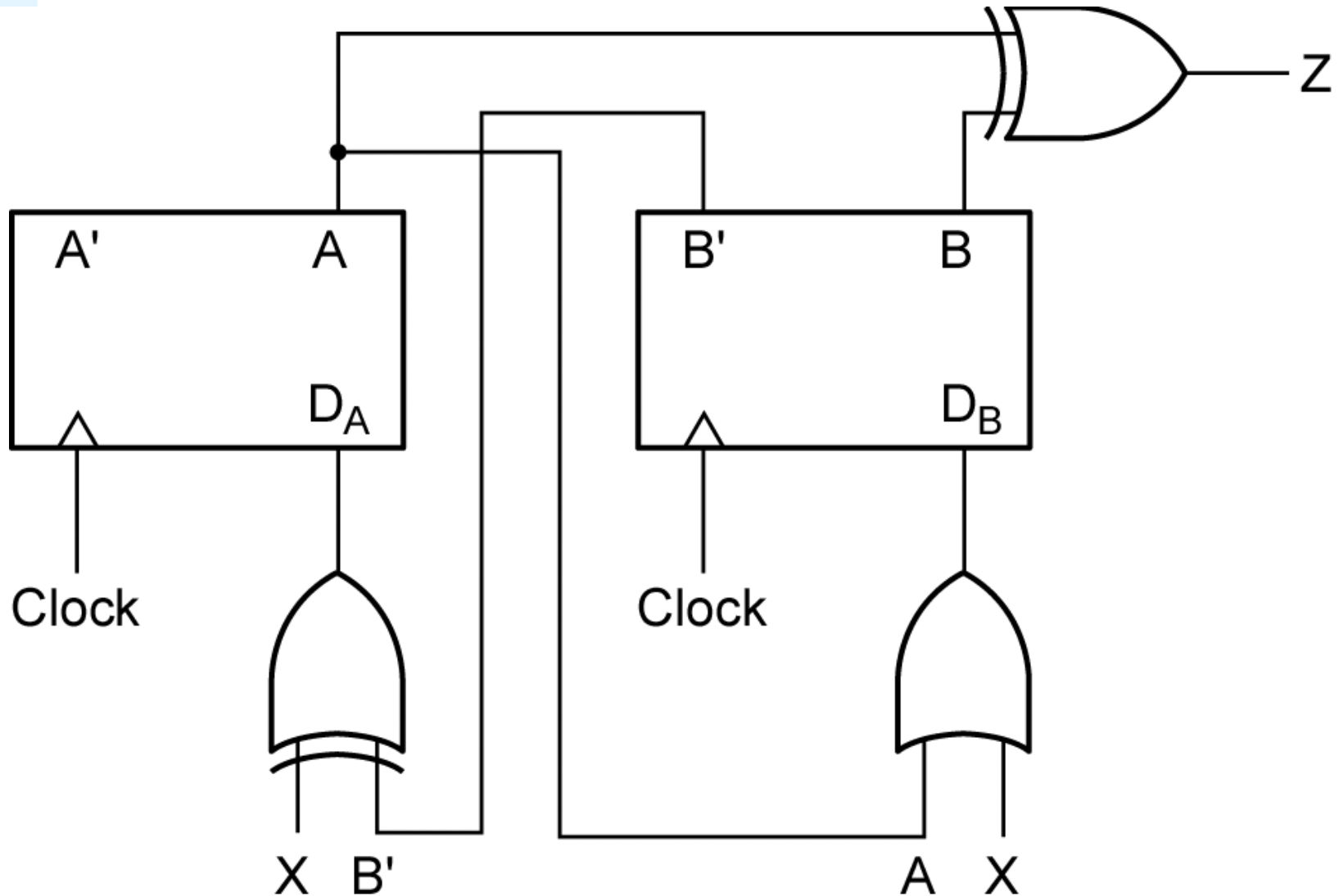


Timing Diagram

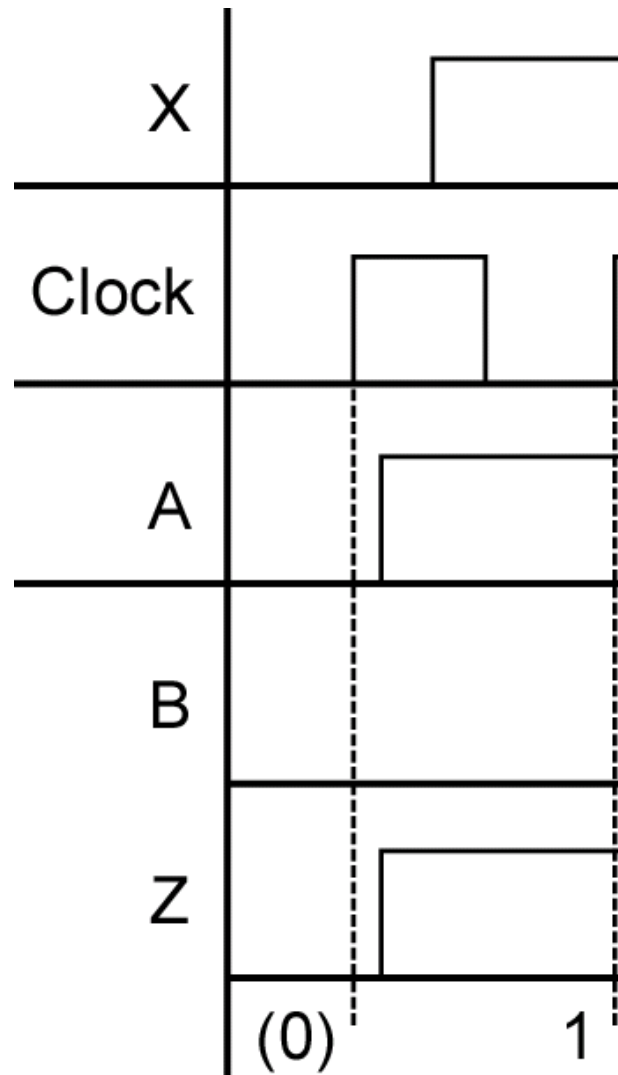


Timing Diagram

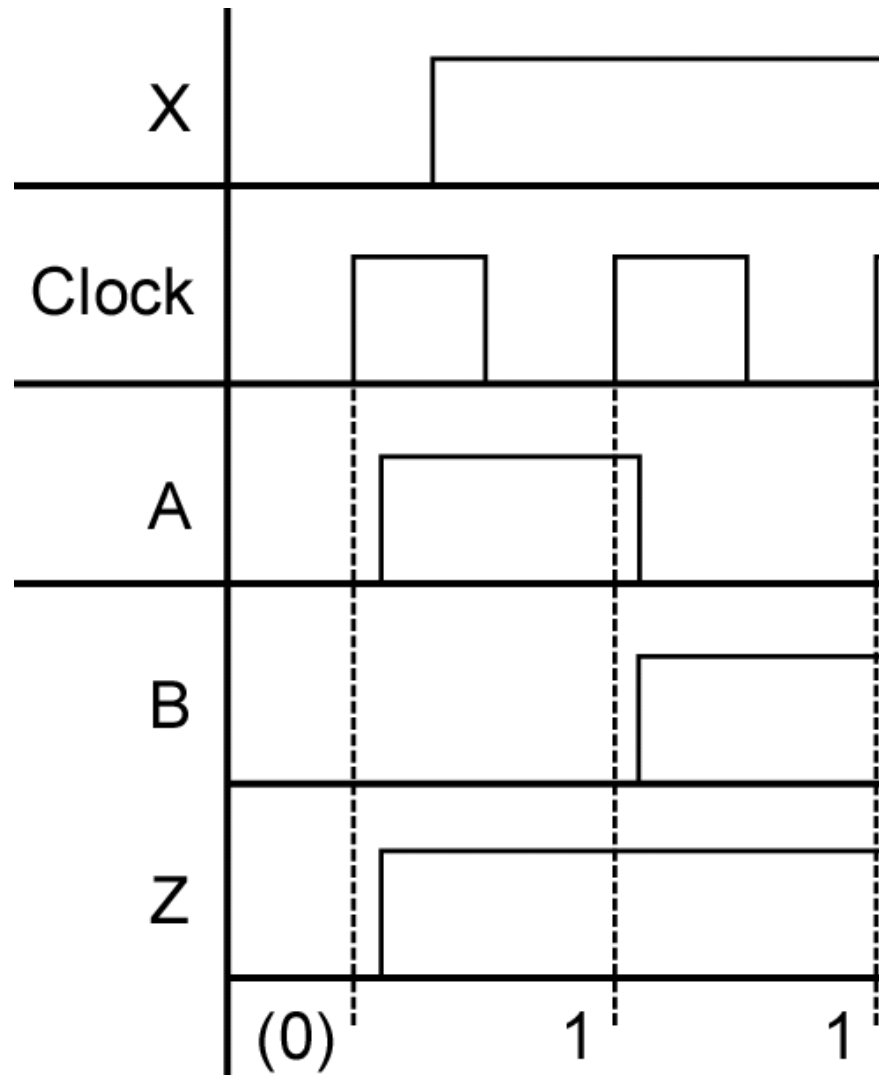


Timing Diagram

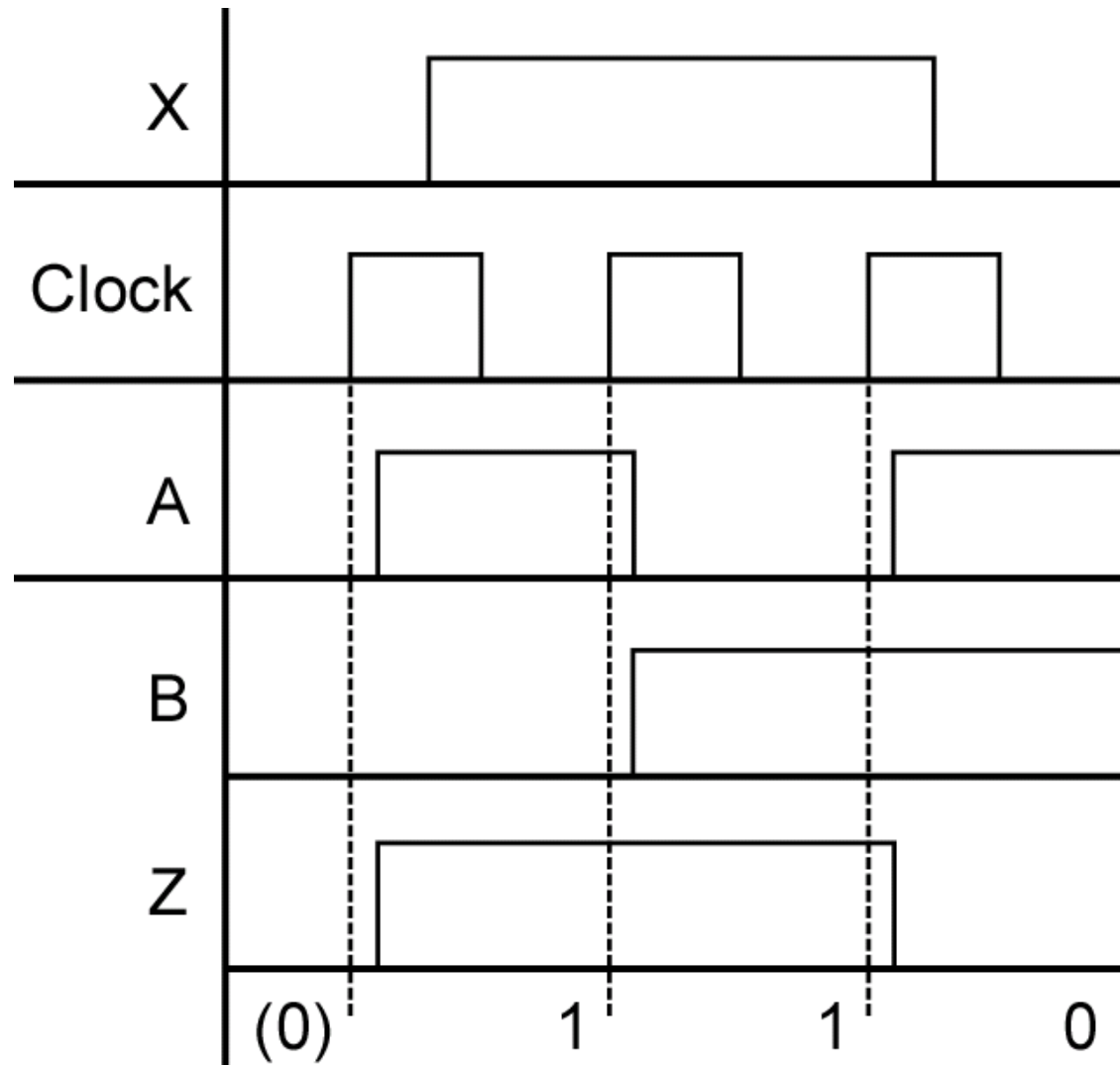


Timing Diagram

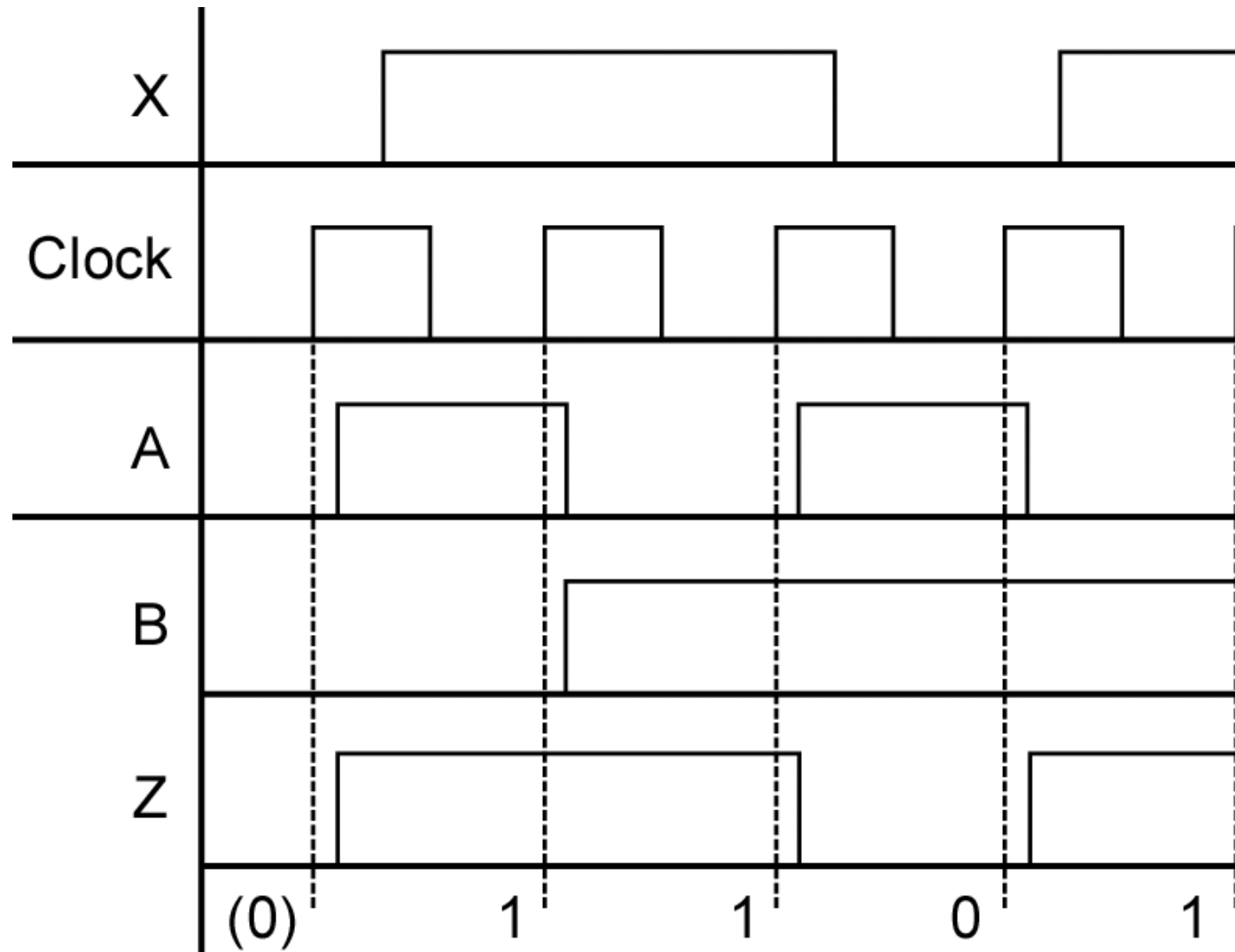


Timing Diagram

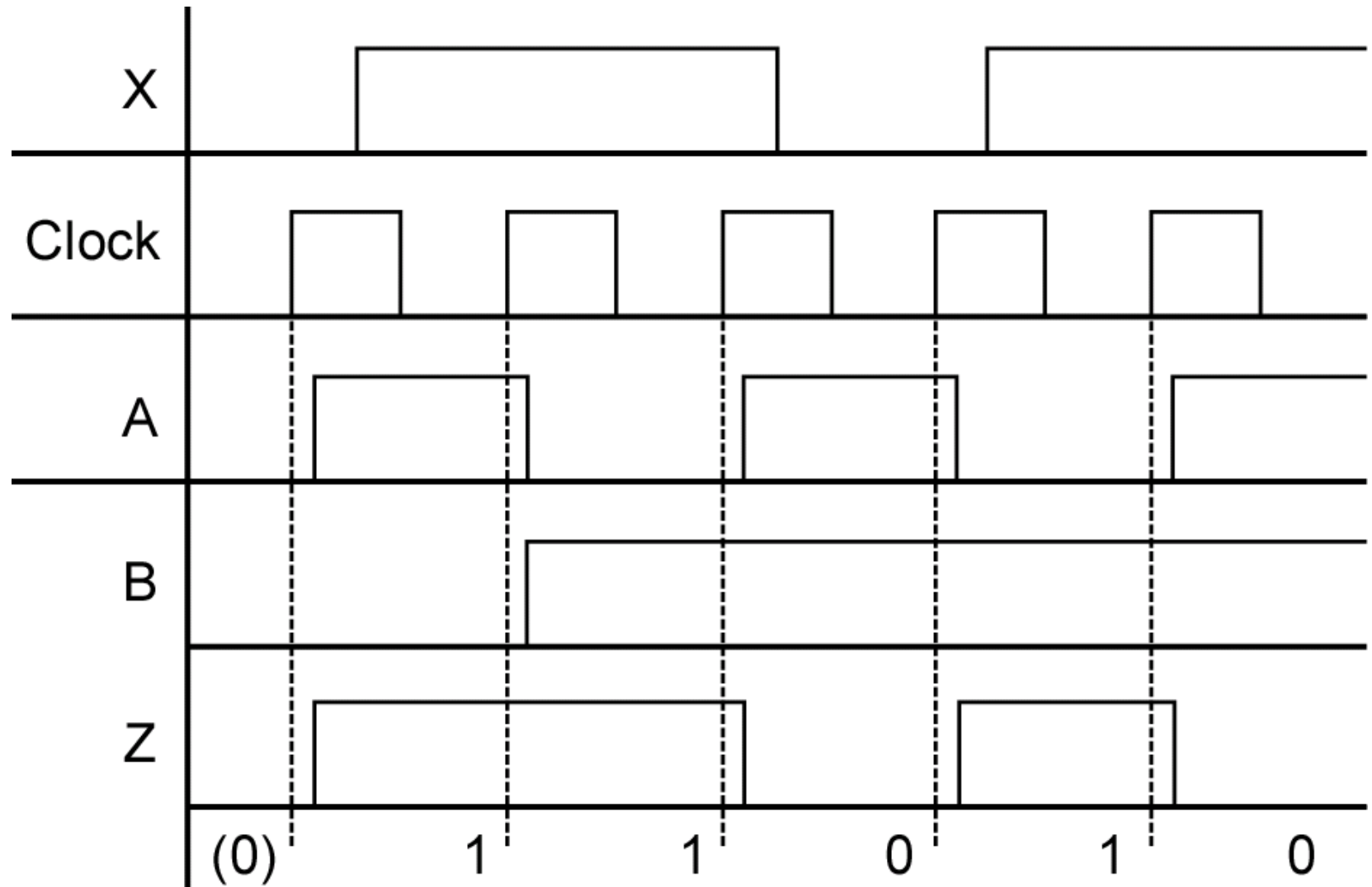


Analysis Example (cont)

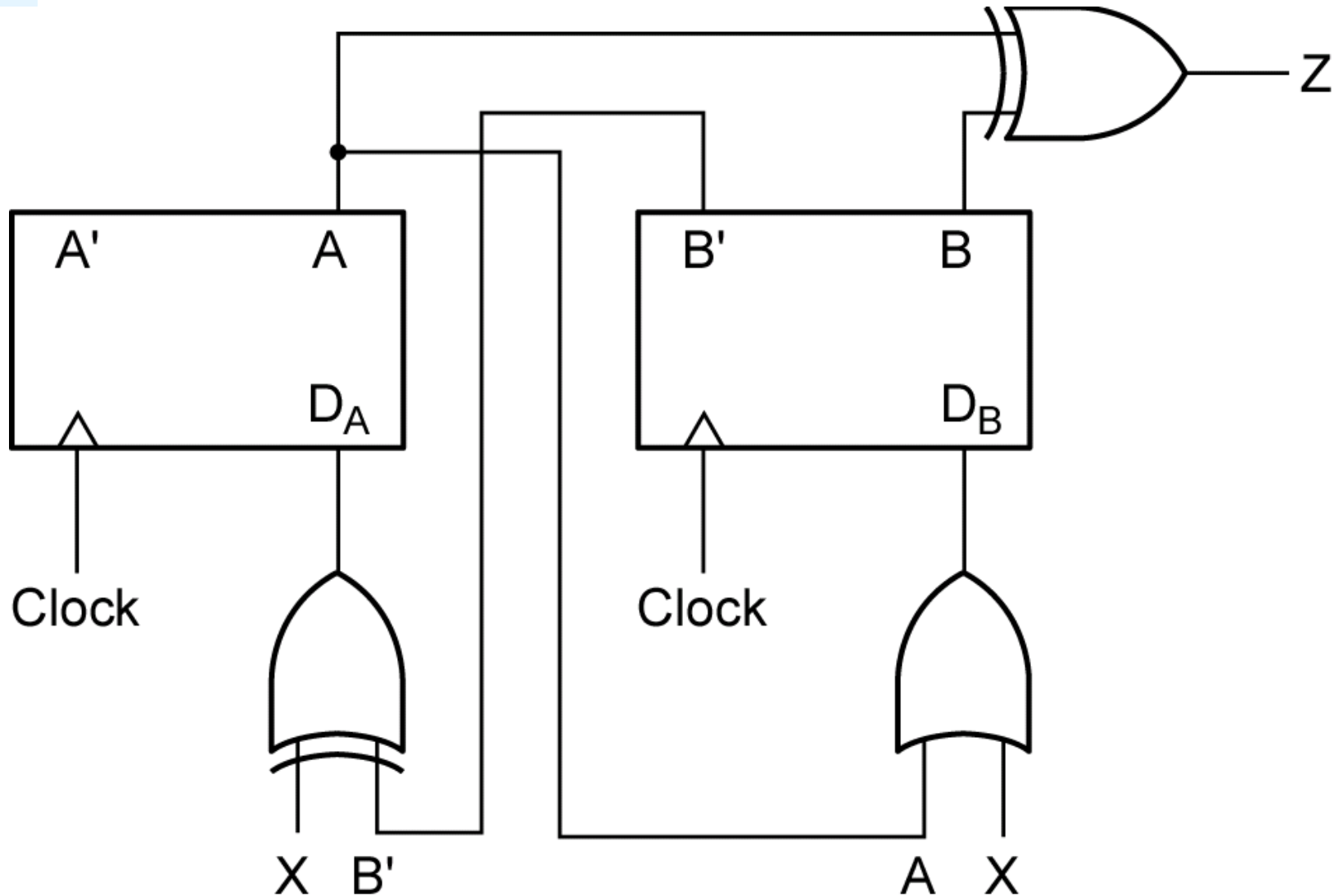

Timing Diagram

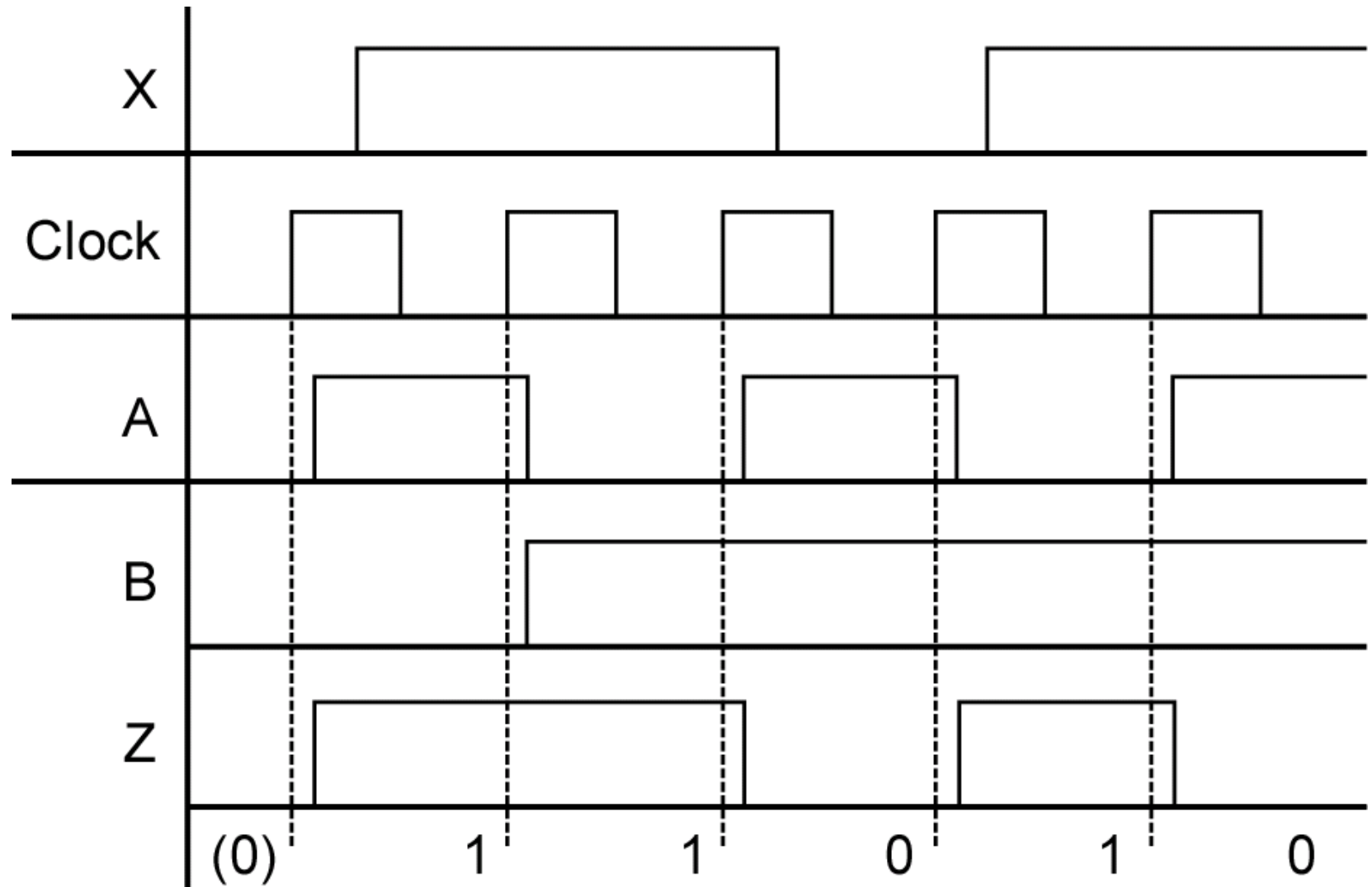

Sequential Circuits

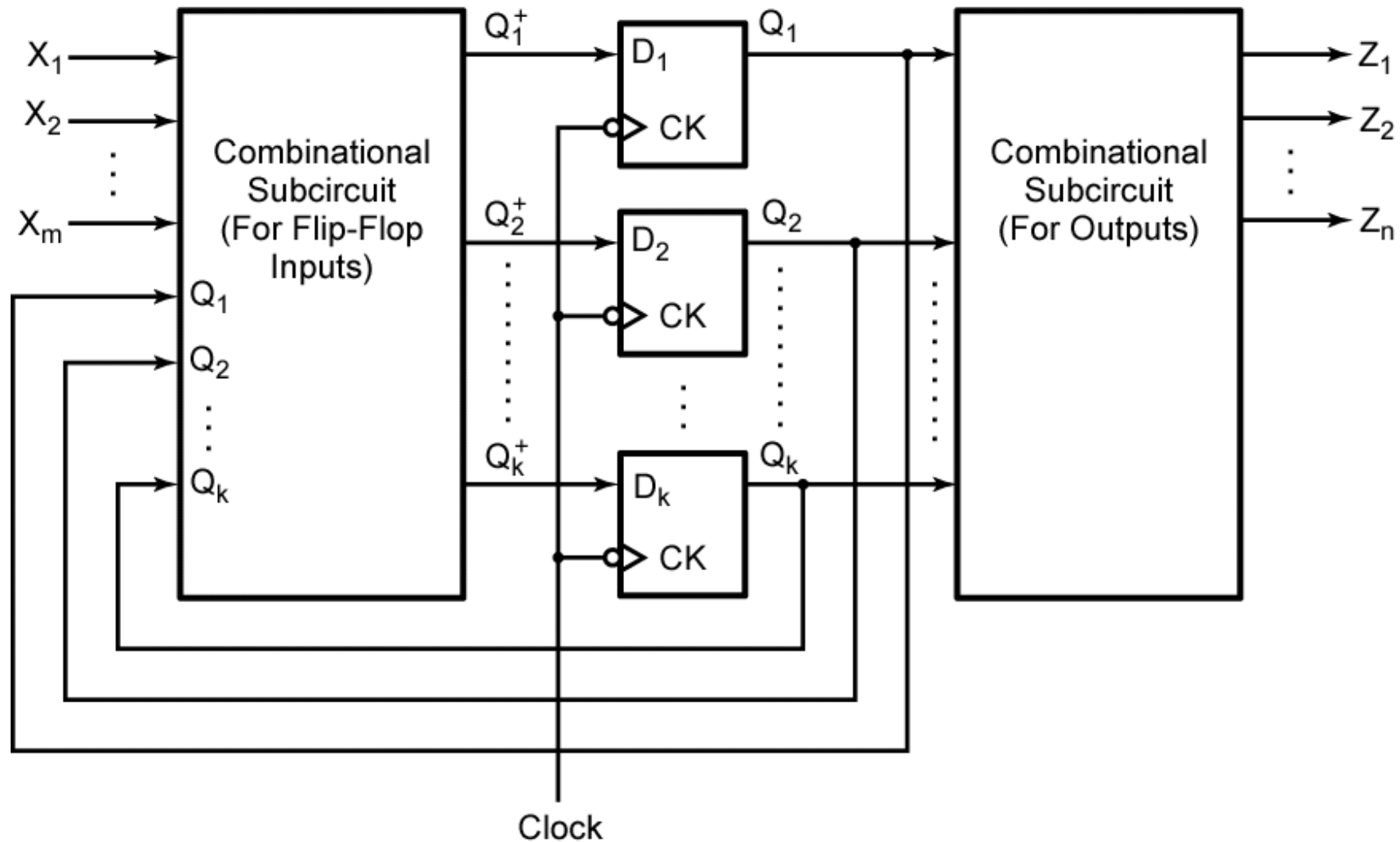

Summary

- ◆ Sequential Analysis
 - State Tables
 - State Graphs
 - Timing Diagrams