

ELEC-313
Lab 4: DC Motor Driver

October 10, 2013

Date Performed: October 09, 2013
Partners: Charles Pittman
Stephen Wilson

1 Objective

The objective is to construct, measure, and observe the operation of a DC motor driver.

2 Equipment

Compact L298 Motor Driver Kit	Function generator: HP 33120A
6 V DC Motor	Multimeter:
Power supply: HP E3631A	Oscilloscope: Agilent 54622D

3 Schematics

4 Procedure

4.1 Part One

4.2 Part Two

5 Results

Enable	L ₁	L ₂	V _{out}	LED	Motor
L	L	L	−0.01 V	off	off
L	L	H	−0.01 V	off	off
L	H	L	−0.01 V	off	off
L	H	H	−0.01 V	off	off
H	L	L	−0.18 V	off	off
H	L	H	5.7 V	red	CW
H	H	L	5.5 V	green	CCW
H	H	H	0.01 V	both	off

Table 1: Logic Table

Duty Cycle	V _{out}
20%	−3.01 V
30%	−3.39 V
40%	−3.76 V
50%	−4.13 V
60%	−4.49 V
70%	−4.84 V
80%	−5.19 V

Table 2: Pulse-width modulation

6 Comparison of Results

7 Conclusion