

Introduction

ELEC 418

Advanced Digital Systems

Dr. Ron Hayne

Images Courtesy of Thomson Engineering



Admin


- ◆ Course materials available online
- ◆ <http://ece.citadel.edu/hayne/>
 - Students are encouraged to print lecture slides in advance and use them to take notes in class

Homework

◆ Xilinx ISE


- Xilinx ISE WebPACK VHDL Tutorial
 - Review from ELEC 311
 - ◆ Up to UCF File Creation
- Xilinx ISE Simulator (ISim) Tutorial
 - VHDL Simulator for ELEC 418
 - Will Need for Project 1

VHDL Counter Example

 


Control Signals			Next State				
$ClrN$	LdN	PT	Q_3^+	Q_2^+	Q_1^+	Q_0^+	
0	X	X	0	0	0	0	(clear)
1	0	X	D_3	D_2	D_1	D_0	(parallel load)
1	1	0	Q_3	Q_2	Q_1	Q_0	(no change)
1	1	1	present state + 1				(increment count)

VHDL Simulation (ISim)

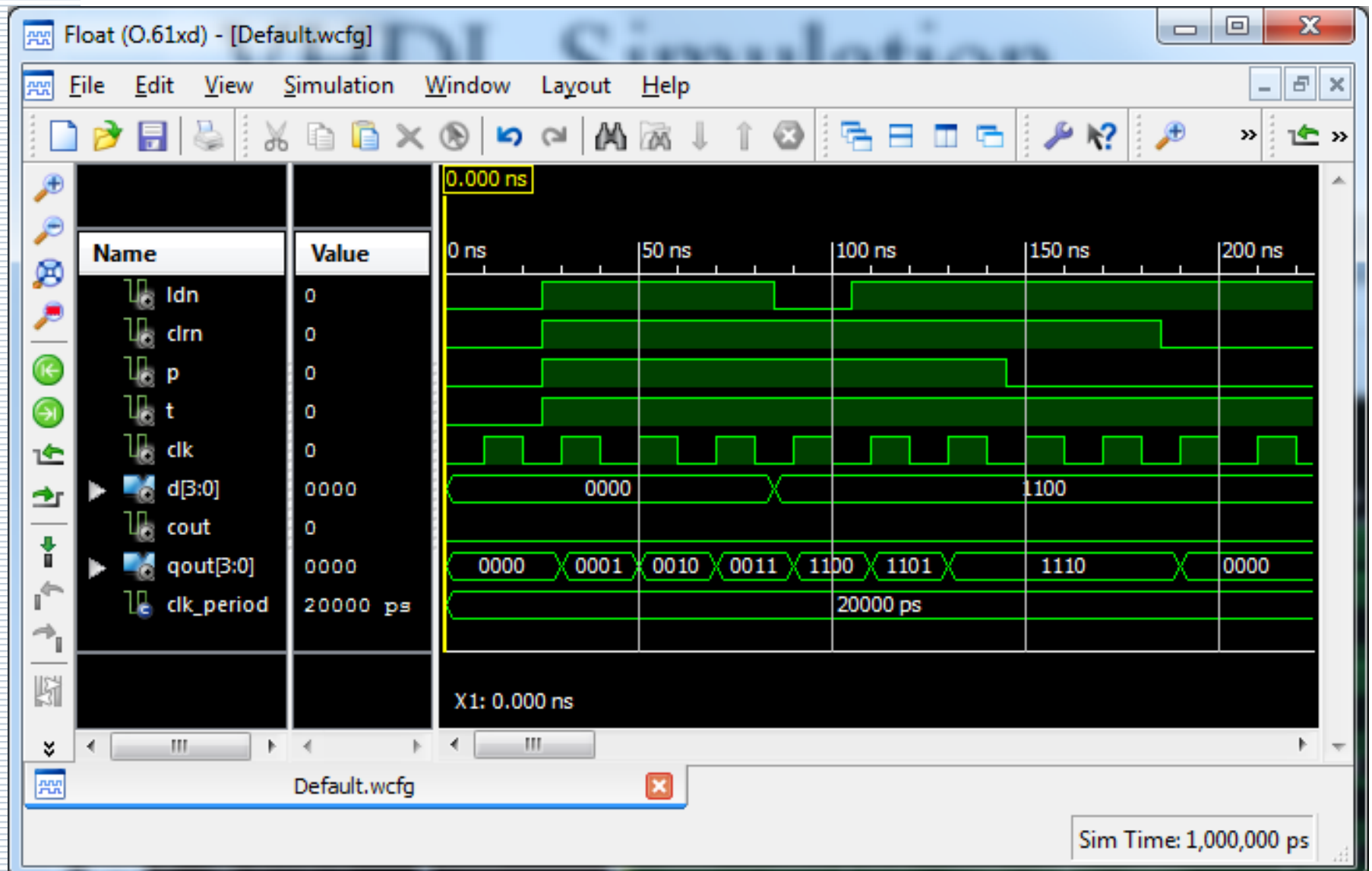

Hardware Demonstration

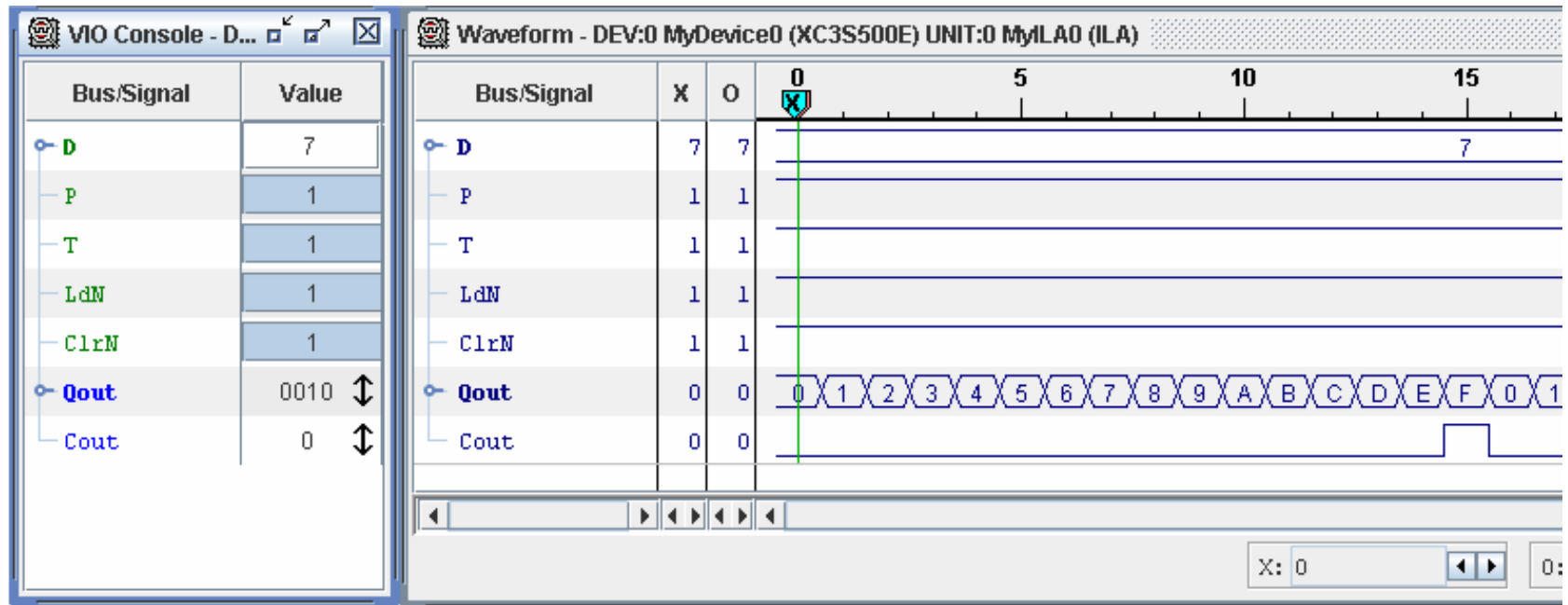

Questions?



Review of Logic Design

- ◆ Chapter 1
 - Combinational Logic
 - Boolean Algebra
 - Flip-Flops and Latches
 - Sequential Circuit Design
 - Tristate Logic and Busses


Sequential Circuit Design

- ◆ Moore

- $Z = f(Q)$

- ◆ Mealy


- $Z = f(X, Q)$

 

Design Example

◆ Sequence Detector

 
- The circuit will examine a string of 0's and 1's applied to the X input and generate an output $Z = 1$ only when the input sequence ends in 1 0 1



■ Typical Sequence


X = 0 0 1 1 0 1 1 0 0 1 0 1 0 1 0 0
Z = 0 0 0 0 0 1 0 0 0 0 0 1 0 1 0 0

Moore State Graph & Table

 

Present State	Next State		Present Output (Z)
	X = 0	X = 1	
S_0	S_0	S_1	0
S_1	S_2	S_1	0
S_2	S_0	S_3	0
S_3	S_2	S_1	1

Mealy State Graph & Table

 

Present State	Next State		Present Output	
	$X = 0$	$X = 1$	$X = 0$	$X = 1$
S_0	S_0	S_1	0	0
S_1	S_2	S_1	0	0
S_2	S_0	S_1	0	1

Summary

- ◆ Admin
 - Course Outline
 - Grading
 - Homework
- ◆ Review of Logic Design
 - Sequential Circuit Design