

ELEC-311
Project 2
Combinational Circuit Design

Charles Pittman

October 1, 2013

1 Objective

First Objective

Given a function, design a combinational logic circuit.

Second Objective

Minimize the circuit using a Karnaugh map.

Third Objective

Create the circuit using only NAND gates.

2 Discussion

The circuit to be constructed was a 2-bit comparator. A 2-bit comparator takes two 2-bit numbers, $P = P_1P_0$ and $Q = Q_1Q_0$, and produces an output, $GT = 1 \iff P > Q$. The truth table describing this function is shown in Table 1. This can be displayed more concisely as a summation of min-terms: $\sum_m(P_1, P_0, Q_1, Q_0) = (4, 8, 9, 12, 13, 14)$.

Using a Karnaugh map (Fig 1), a minimal form of the function was found: $GT = P_0\bar{Q}_1\bar{Q}_0 + P_1P_0\bar{Q}_0 + P_1\bar{Q}_1$. This function was then translated into the circuit shown in Fig 2. Finally, this circuit was again translated into one using only NAND gates (Fig 3).

3 Results

mt	P	Q	P_1	P_0	Q_1	Q_0	$GT (P > Q)$
0	0	0	0	0	0	0	0
1	0	1	0	0	0	1	0
2	0	2	0	0	1	0	0
3	0	3	0	0	1	1	0
4	1	0	0	1	0	0	1
5	1	1	0	1	0	1	0
6	1	2	0	1	1	0	0
7	1	3	0	1	1	1	0
8	2	0	1	0	0	0	1
9	2	1	1	0	0	1	1
10	2	2	1	0	1	0	0
11	2	3	1	0	1	1	0
12	3	0	1	1	0	0	1
13	3	1	1	1	0	1	1
14	3	2	1	1	1	0	1
15	3	3	1	1	1	1	0

Table 1: Truth table for 2-bit comparator.

		P_0, P_1			
		00	01	11	10
Q_0, Q_1	00	0 1	4 1	12 1	8 1
	01	1	5	13 1	9 1
	11	3	7	15	11
	10	2	6	14 1	10

Figure 1: Karnaugh map used to minimize function.

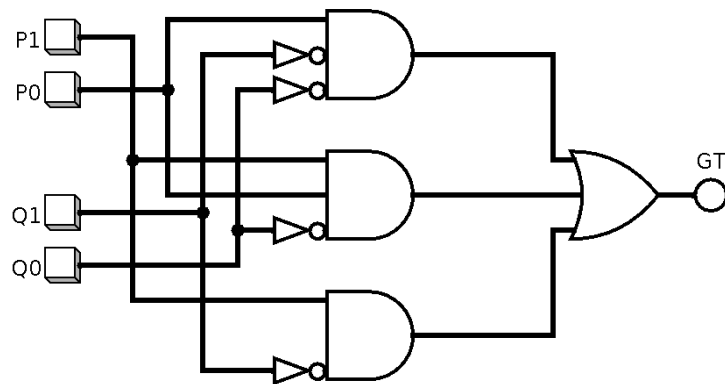


Figure 2: Circuit implemented from function.

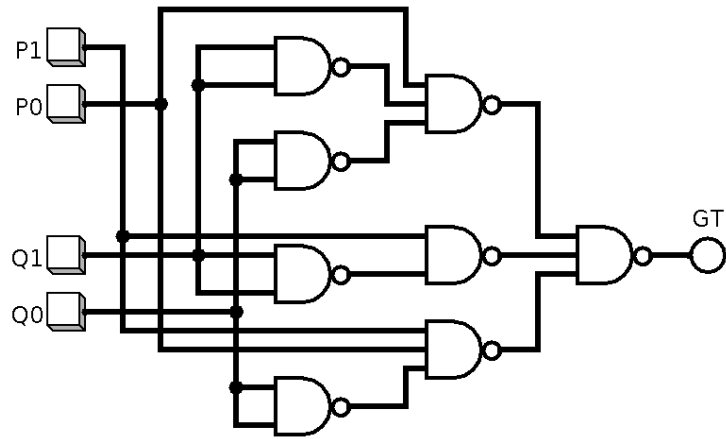


Figure 3: Identical circuit using only NAND gates.