

ELEC-313
Lab 7: MOSFET Amplifier Circuits

November 11, 2013

Date Performed: November 06, 2013
Partners: Charles Pittman
Stephen Wilson

1 Objective

2 Equipment

Transistor: 2N7000

Function Generator: HP 33120

Oscilloscope: Agilent 54622D

Resistors: $100\ \Omega$, $300\ \Omega$, $470\ \Omega$, $1\ \text{k}\Omega$ (x2)

$33\ \text{k}\Omega$, $100\ \text{k}\Omega$ (x2)

Power supply: HP E3631A

Multimeter: HP 34401A

Capacitors: $0.1\ \mu\text{F}$

3 Schematics

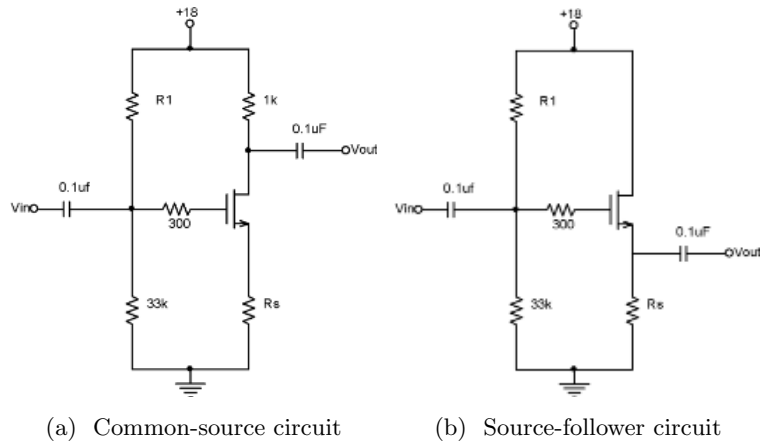


Figure 1: Circuits used in this lab.

4 Procedure

4.1 Common-Source Amplifier

4.2 Source-Follower Amplifier

5 Results

6 Conclusion

7 Equations

$$V_{o,L} = V_{o,NL} \frac{R_L}{R_o + R_L} \quad (1)$$

V_{in} (mV)	V_{out} (V)
200	0.382
300	0.566
400	0.760
500	0.939
600	1.140
700	1.340
800	1.530
900	1.721
1000	1.90

Table 1: Common-source amplifier

V_{in} (mV)	V_{out} (mV)
200	182
300	268
400	360
500	451
600	541
700	634
800	725
900	813
1000	906

Table 2: Source-follower amplifier