

Three Phase Power

Three Phase Systems

- Generation of Three Phase Voltages
- Three Phase Power
- Three Phase Circuit Analysis

Three Phase Systems

- Nearly all electric power generated and distributed is in the form of 3 phase AC.
- These systems consists of 3 phase generators, transmission lines and loads.
- Advantages over single phase systems
 - More efficient (more power per kg of metal)
 - Instantaneous power is a constant, not pulsing or oscillating

A 3 phase generator consists of 3 single phase generators w/ equal magnitude but different phase angle (0,-120,-240 degrees).

Or $0, \frac{-2\pi}{3}, \frac{-4\pi}{3}$ radians

It is as if each generator was started at different time delays $t = \phi/\omega = (0, \frac{2\pi}{3\omega}, \frac{4\pi}{3\omega})$




Each of these generators could be connect to Identical loads as in figure (c). Each producing Identical phase delayed currents.

$$I_A = \frac{V \angle 0}{Z \angle \theta} = I \angle -\theta$$


$$I_B = \frac{V \angle -120}{Z \angle \theta} = I \angle -120 - \theta$$

$$I_C = \frac{V \angle -240}{Z \angle \theta} = I \angle -240 - \theta$$

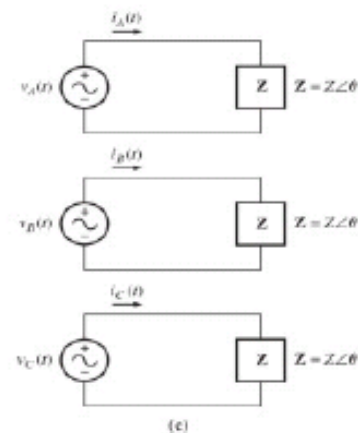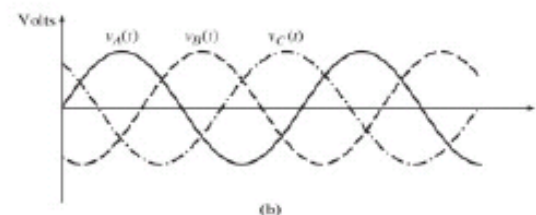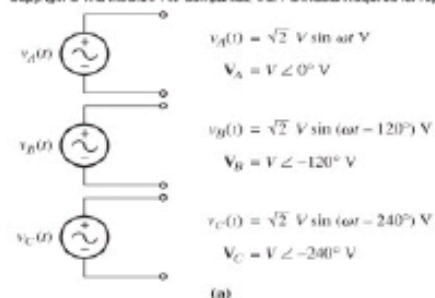Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




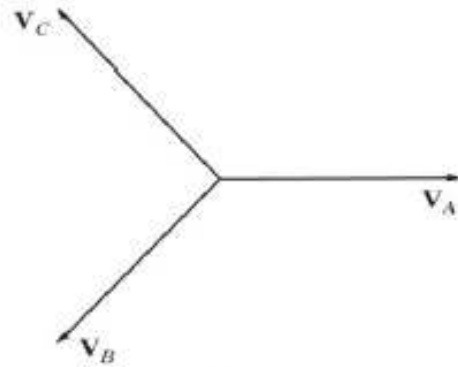Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



(a)

a) *abc* sequence

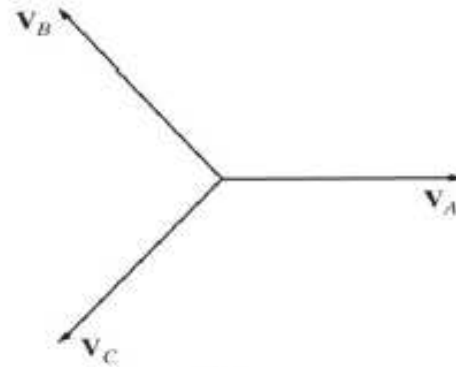


(b)

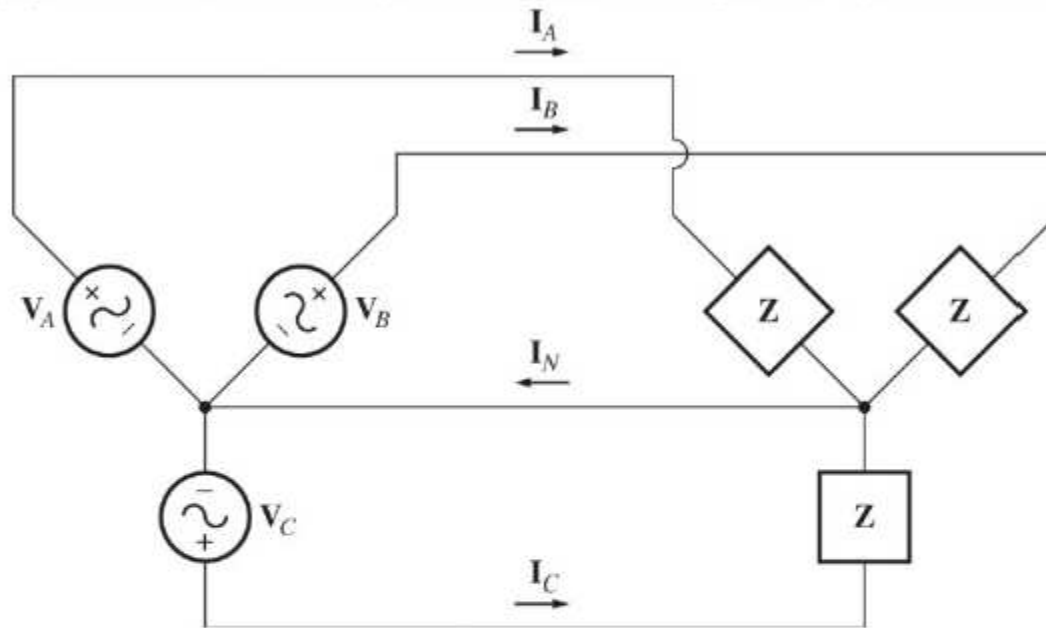b) *acb* sequence


Can you show that $V_A + V_B + V_C = 0$?

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




We can also connect negative terminals of the three generator and loads together to form a three phase circuit. With the neutral wire only four wires are required. Note: $I_N = I_A + I_B + I_C = 0$ for a balanced 3 phase generator and balanced load.

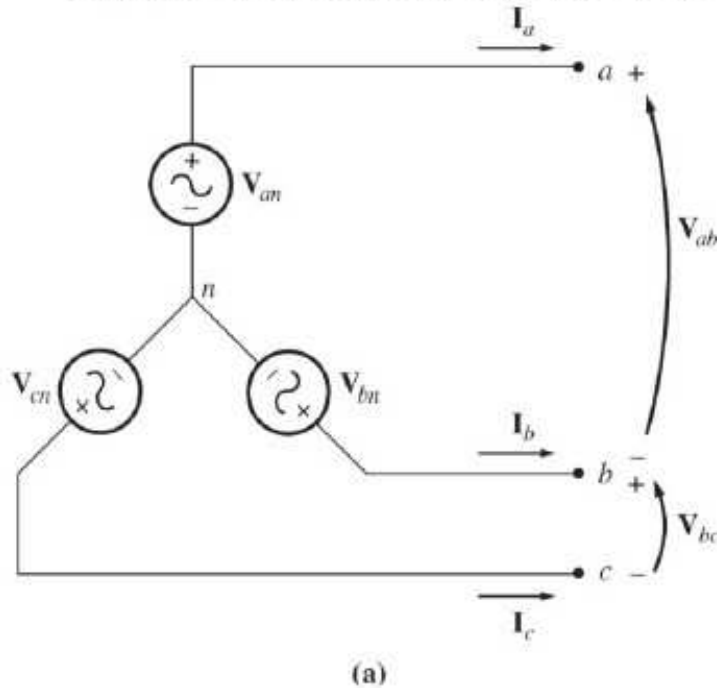Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




a) Y-connected generators

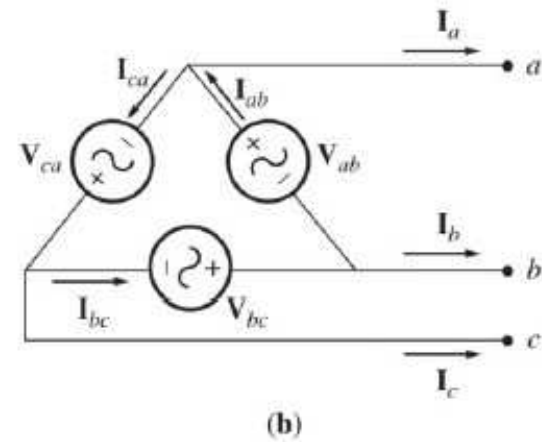

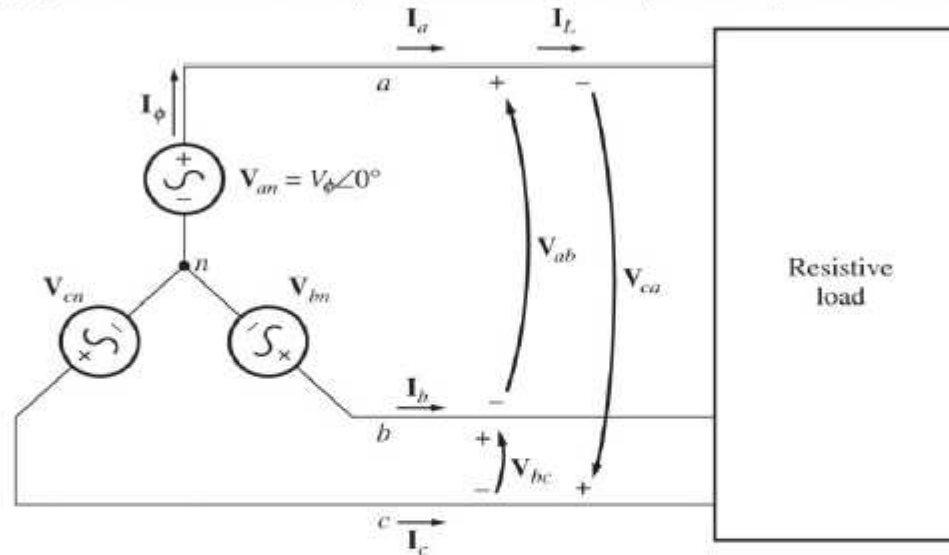b) Δ connected generators

Y connected generator

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



Each generator is also called a phase. The voltage and current in a single generator are called the phase voltage (V_{ϕ}) and phase currents (I_{ϕ})

Y connection

- *Phase Voltages*

$$V_{an} = V_{\phi} < 0^{\circ}$$

$$V_{bn} = V_{\phi} < -120^{\circ}$$

$$V_{cn} = V_{\phi} < -240^{\circ}$$

- *Phase Currents (assuming resistive loads)*

$$I_a = I_{\phi} < 0^{\circ}$$

$$I_b = I_{\phi} < -120^{\circ}$$

$$I_c = I_{\phi} < -240^{\circ}$$

Y connection

- *Line (to Line) Voltages*


$$\begin{aligned} V_{ab} &= V_{an} - V_{bn} = V_{\phi} \angle 0^{\circ} - V_{\phi} \angle -120^{\circ} \\ &= \sqrt{3}V_{\phi} \angle 30^{\circ} \end{aligned}$$

$$V_{LL} = \sqrt{3}V_{\phi} \quad Y \text{ connection}$$

- *Phase Currents = Line currents*

$$I_a = I_{\phi} = I_L \quad Y \text{ connection}$$

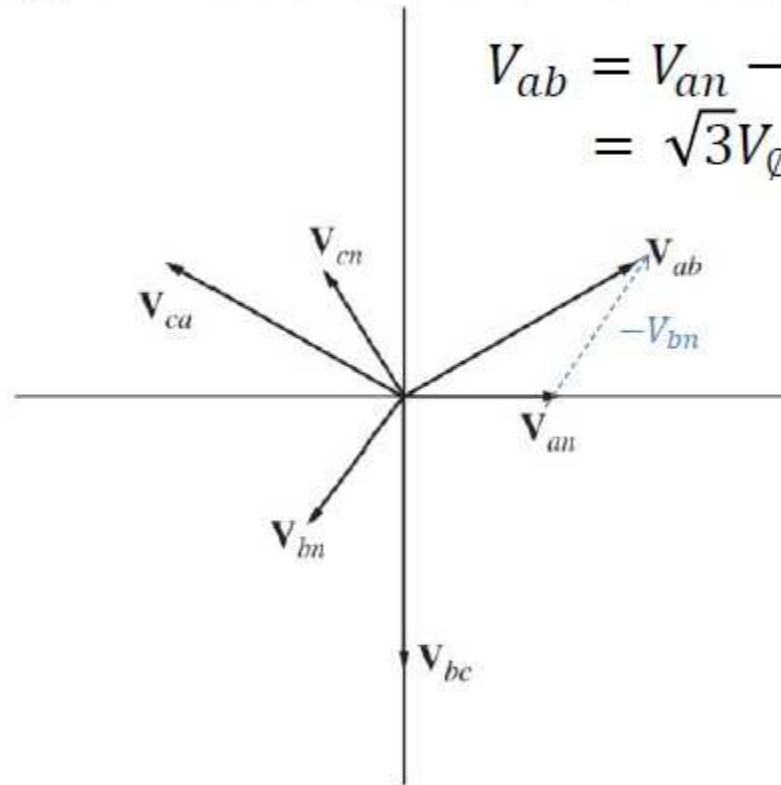
Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



$$\begin{aligned} V_{ab} &= V_{an} - V_{bn} \\ &= \sqrt{3}V_{\phi} \angle 30^{\circ} \end{aligned}$$

DELTA CONNECTED GENERATOR

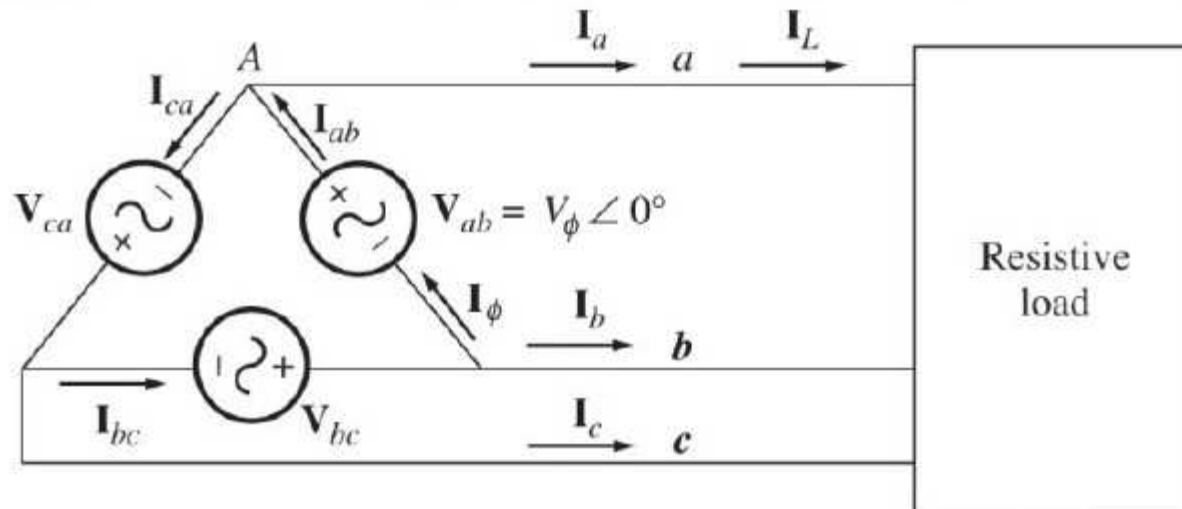Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



Δ connection

- *Line Voltages = Phase voltages*

$$V_{ab} = V_{\phi} < 0^{\circ}$$

$$V_{bc} = V_{\phi} < -120^{\circ}$$

$$V_{ca} = V_{\phi} < -240^{\circ}$$

- *Line Currents (assuming resistive loads)*

$$I_a = I_{ab} - I_{ca} = I_{\phi} < 0^{\circ} - I_{\phi} < 120^{\circ}$$

$$I_a = \sqrt{3}I_{\phi} < -30^{\circ}$$

Δ connection


- *Line (to Line) Voltages*

$$V_{ab} = V_{LL} \quad \Delta \text{ connection}$$

- *Phase Currents = Line currents*


$$I_a = I_L = \sqrt{3} I_\phi \quad \Delta \text{ connection}$$

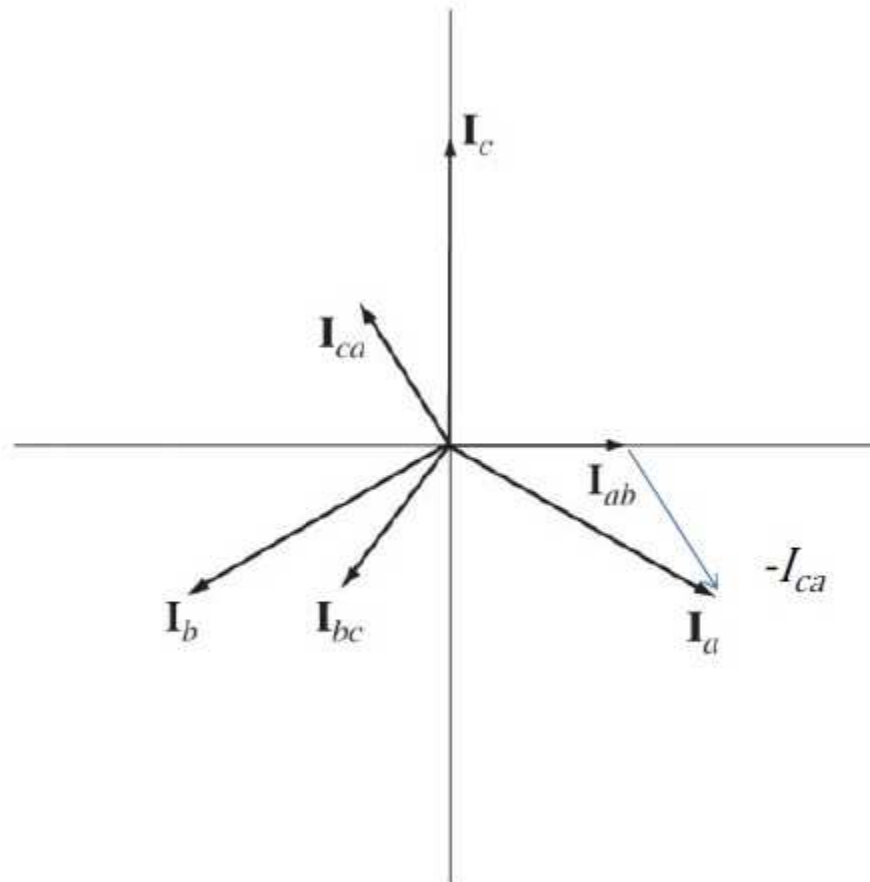Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



Three Phase Power

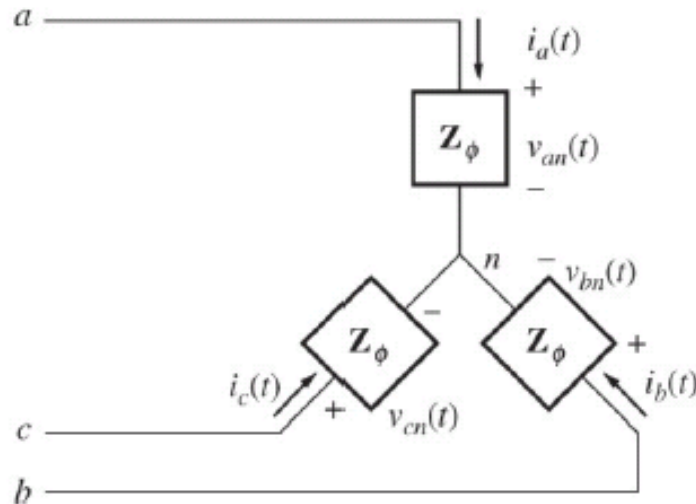Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



$$v_{an}(t) = \sqrt{2}V_{\phi} \cos(\omega t)$$

$$v_{bn}(t) = \sqrt{2}V_{\phi} \cos(\omega t - 120)$$

$$v_{cn}(t) = \sqrt{2}V_{\phi} \cos(\omega t - 240)$$

$$i_a(t) = \sqrt{2}I_{\phi} \cos(\omega t - \theta)$$

$$i_b(t) = \sqrt{2}I_{\phi} \cos(\omega t - \theta - 120)$$

$$i_c(t) = \sqrt{2}I_{\phi} \cos(\omega t - \theta - 240)$$


$$p_a(t) = 2V_{\phi}I_{\phi} \cos(\omega t) \cos(\omega t - \theta) = V_{\phi}I_{\phi} [\cos(\theta) - \cos(2\omega t - \theta)]$$


$$p_b(t) = 2V_{\phi}I_{\phi} \cos(\omega t - 120) \cos(\omega t - \theta - 120) = V_{\phi}I_{\phi} [\cos(\theta) - \cos(2\omega t - \theta - 240)]$$



$$p_c(t) = 2V_{\phi}I_{\phi} \cos(\omega t - 240) \cos(\omega t - \theta - 240) = V_{\phi}I_{\phi} [\cos(\theta) - \cos(2\omega t - \theta - 480)]$$

$$\begin{aligned} p_{tot}(t) &= p_a(t) + p_b(t) + p_c(t) \\ &= 3V_{\phi}I_{\phi} \cos(\theta) \\ &= \text{constant} \end{aligned}$$

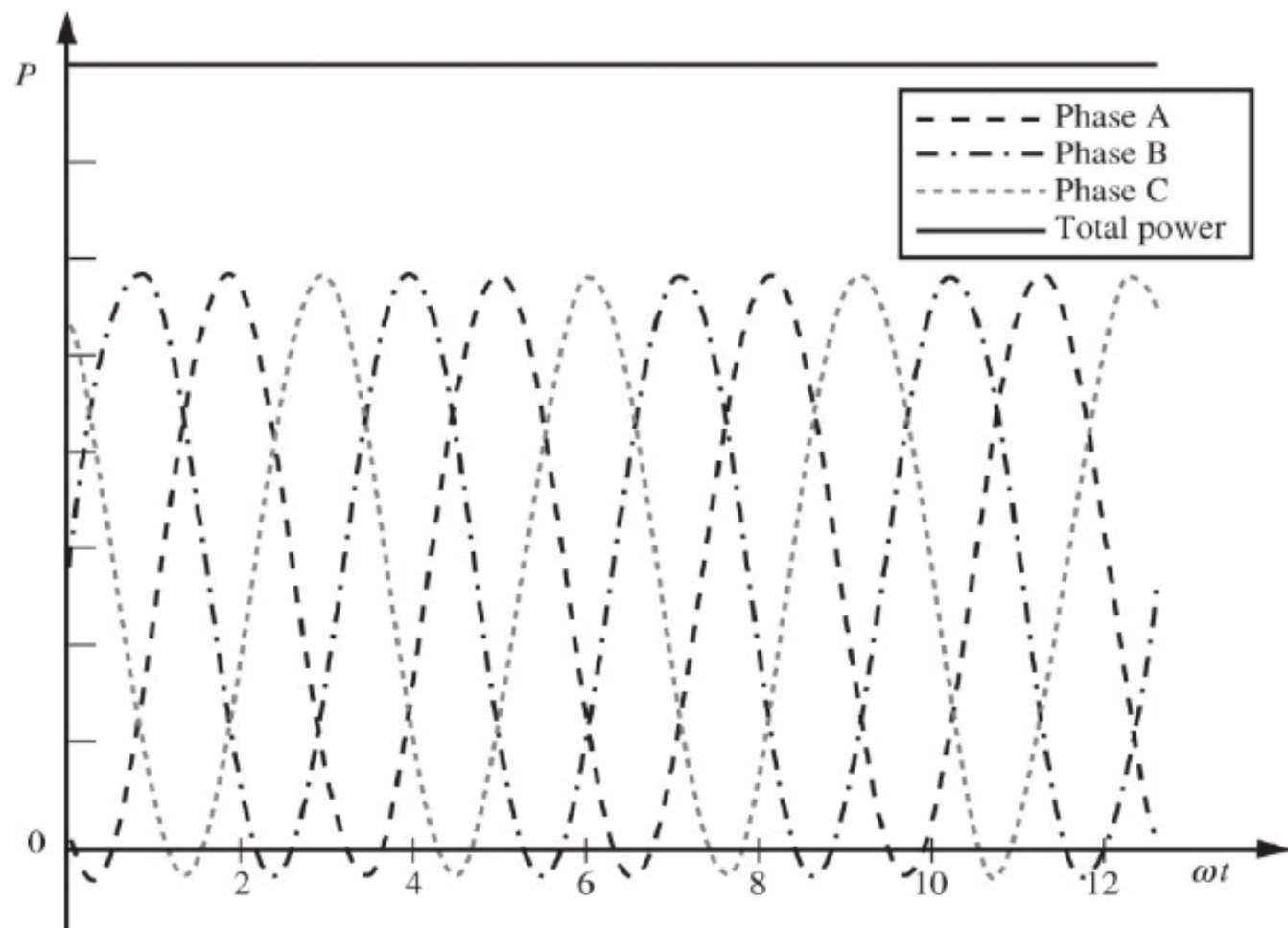Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



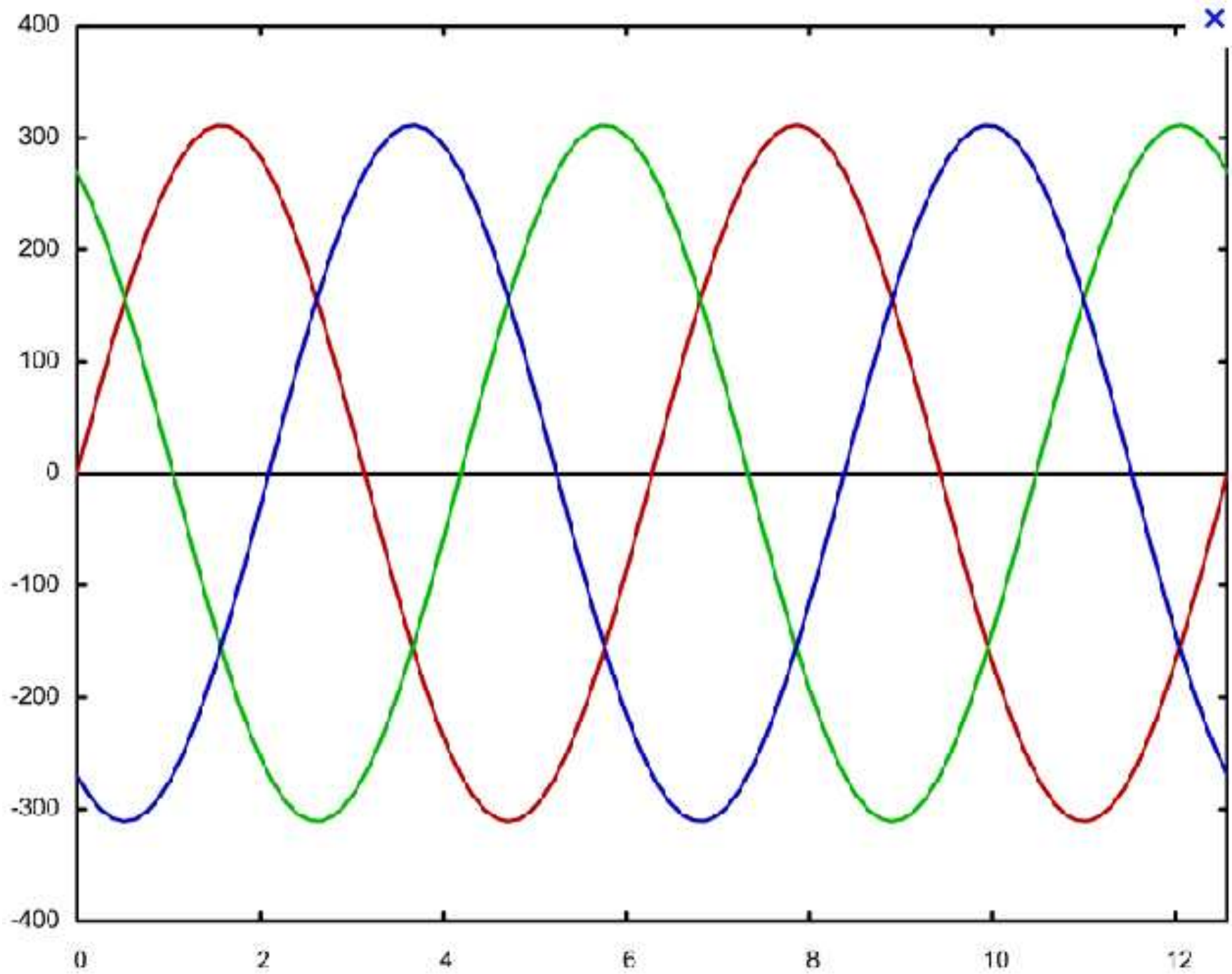

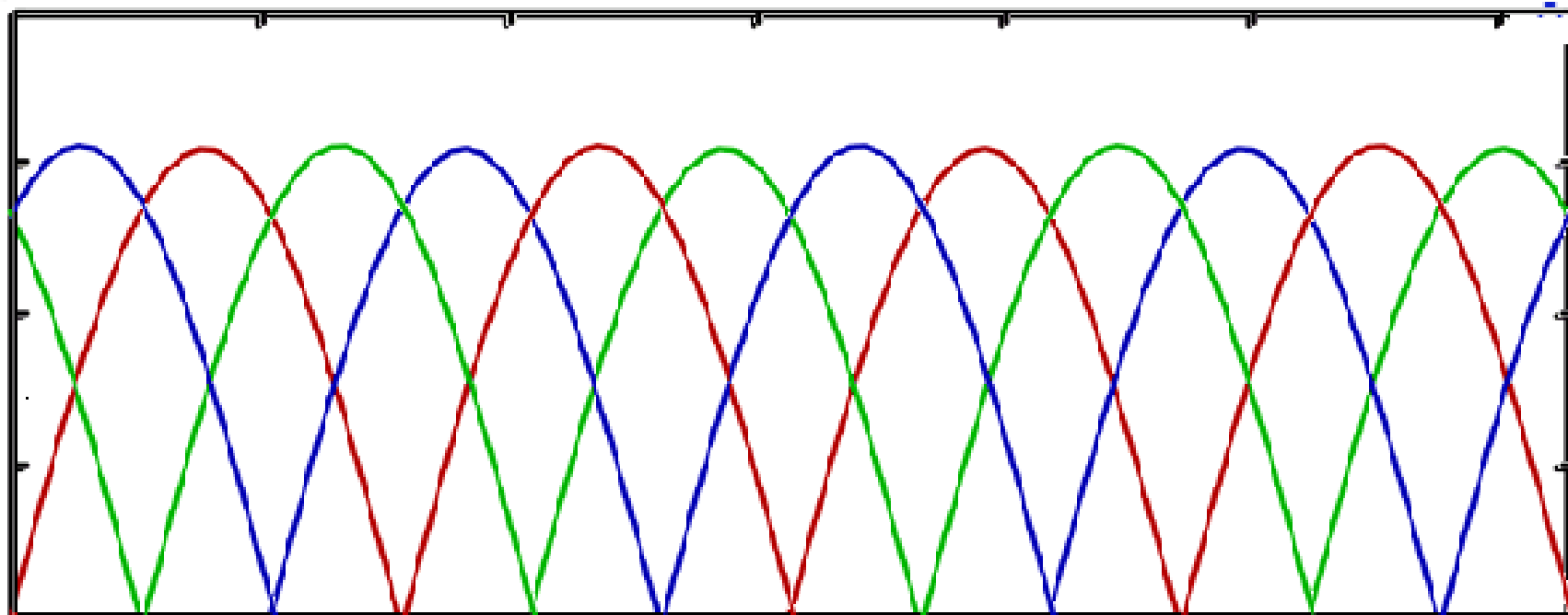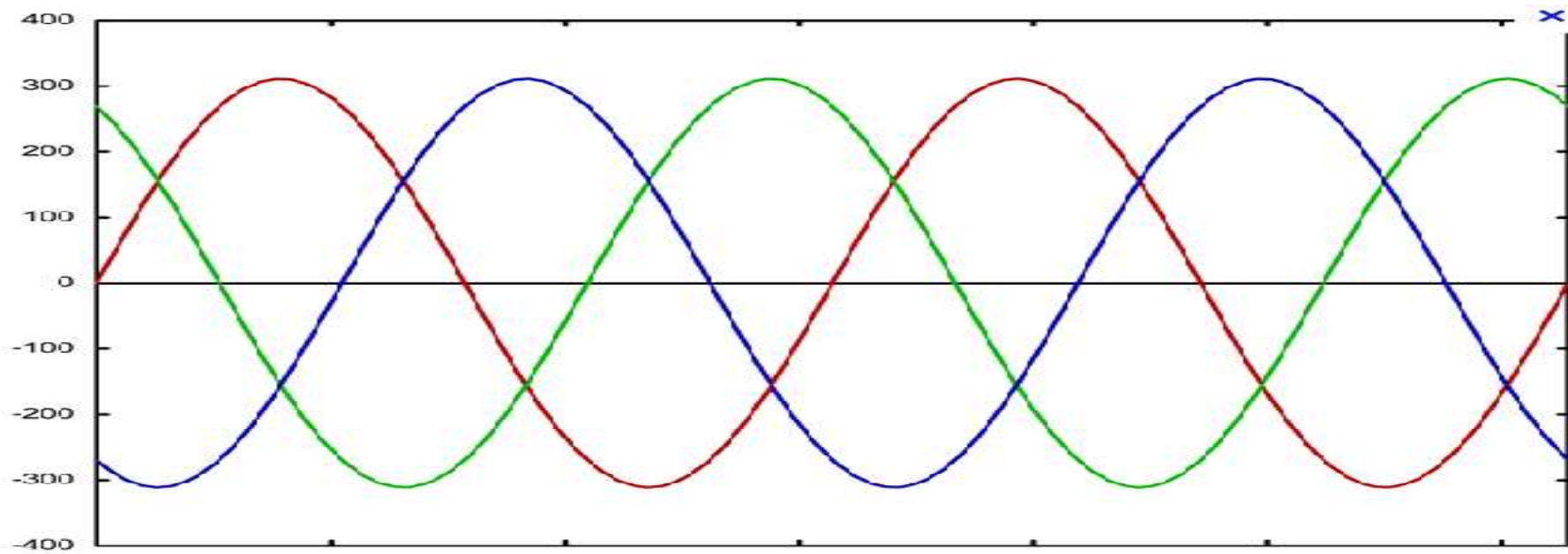

Power Equations for phase and line quantities

- The power supplied to a balanced three phase load in terms of the phase quantities is:

$$P = 3V_{\phi}I_{\phi}\cos(\theta), \quad Q = 3V_{\phi}I_{\phi}\sin(\theta), \quad S = 3V_{\phi}I_{\phi}$$

- Or equivalently in terms of the line quantities


$$P = \sqrt{3}V_{LL}I_L\cos(\theta), \quad Q = \sqrt{3}V_{LL}I_L\sin(\theta), \quad S = \sqrt{3}V_LI_L$$

Power Equations for phase and line quantities

- All voltages and currents on previous page are RMS values.
- Using the line quantities is generally preferred since easier to measure and equations are same for Y or Δ config.
- Note: θ is angle between phase voltage and phase currents and not between line voltage and line currents.

Analysis of Balanced 3 phase Circuits

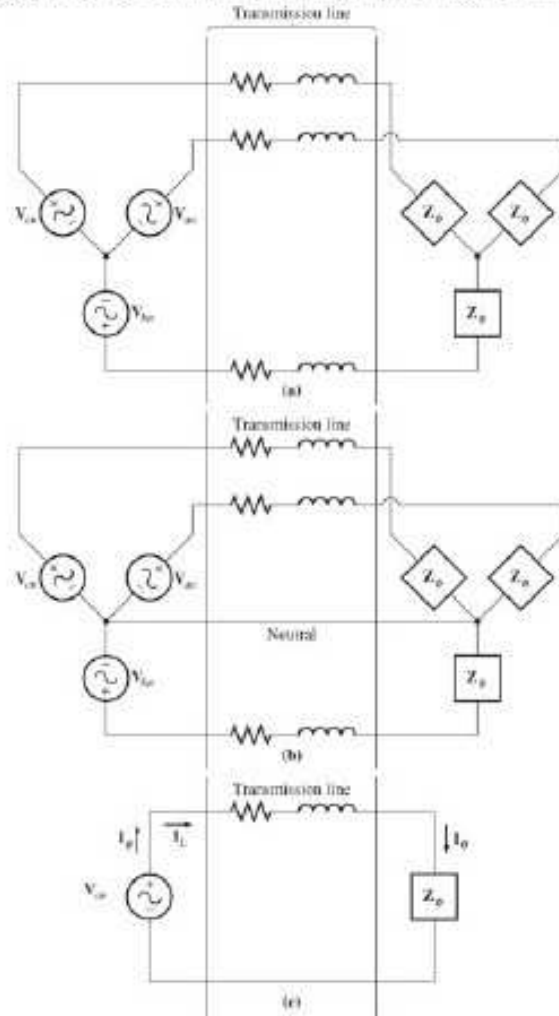
Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



- Use a single phase equivalent circuit approach.
- Requires the use of a neutral return path.
- If Δ configuration is encountered it must be converted to a Y


$$Z_Y = \frac{Z_\Delta}{3}$$

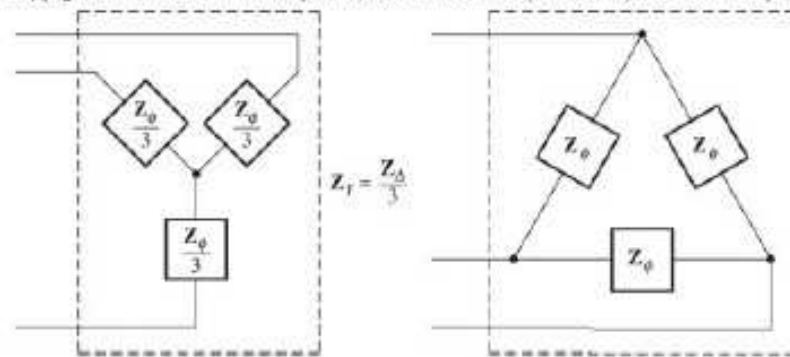Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




Three Phase Loads

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

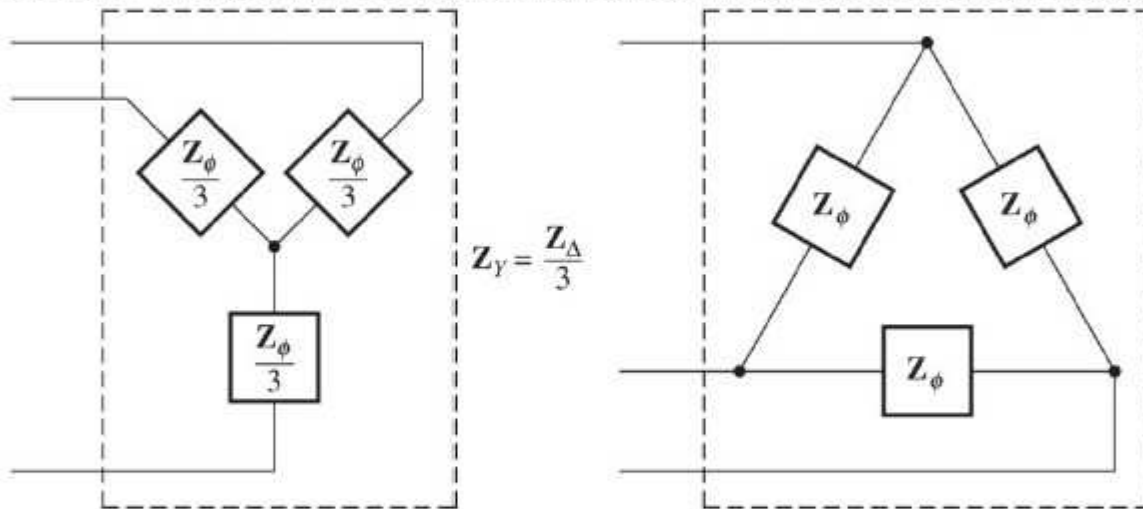

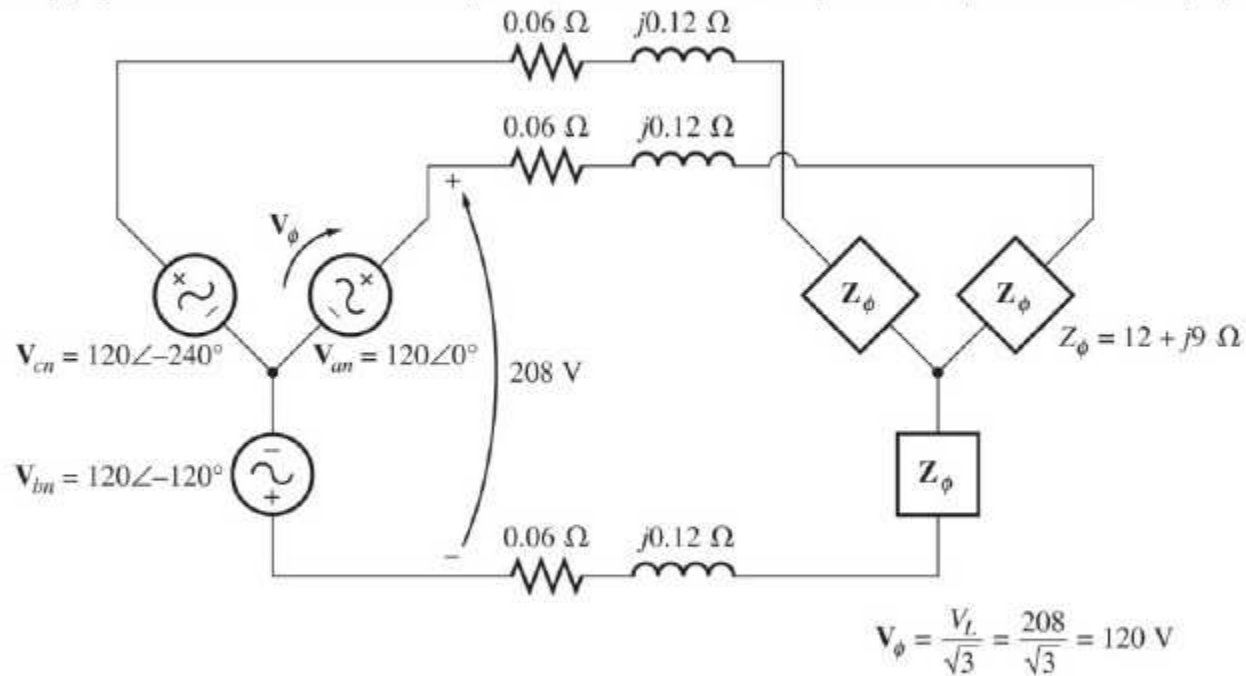
Example 1...

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



Solution...

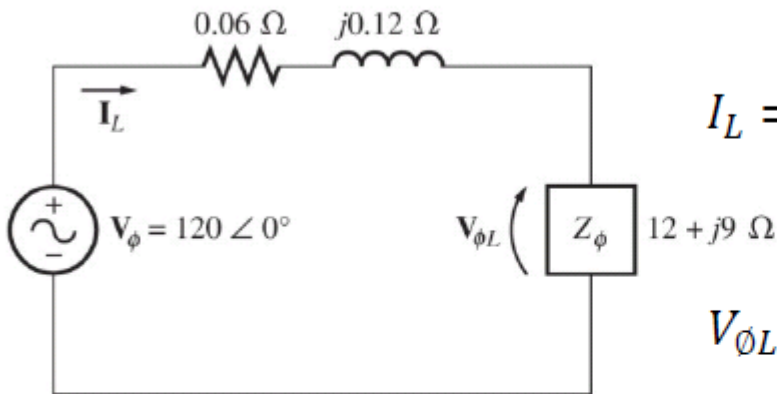Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



$$I_L = \frac{120 \angle 0}{(0.06 + j0.12) + (12 + j9)} = 7.94 \angle -37.1^\circ$$

$$V_{\phi L} = (7.94 \angle -37.1)(12 + j9) = 119.1 \angle -0.2^\circ$$


$$P_{Load} = 3V_\phi I_\phi \cos(\theta) = 3(119.1)(7.94) \cos(36.9) = 2270 \text{ w}$$

$$Q_{Load} = 3V_\phi I_\phi \sin(\theta) = 3(119.1)(7.94) \sin(36.9) = 1702 \text{ var}$$

$$S_{Load} = 3V_\phi I_\phi = 3(119.1)(7.94) = 2839 \text{ var}$$

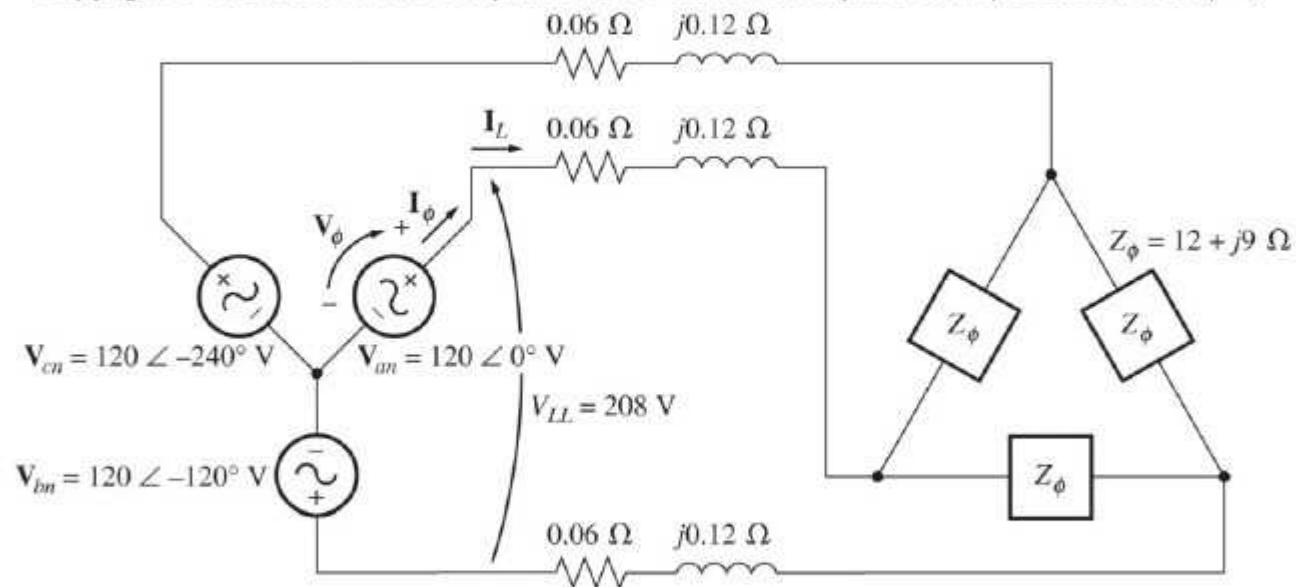
Example 2... Δ connected load

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



Solution...

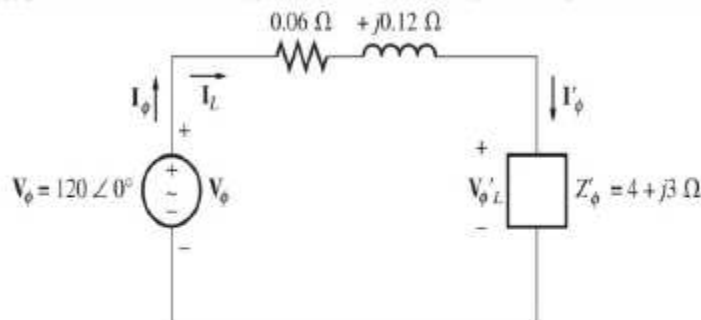Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



$$I_L = \frac{120 \angle 0}{(0.06 + j0.12) + (4 + j3)} = 23.4 \angle -37.5^\circ$$

$$V_{\phi L} = (23.4 \angle -37.5)(4 + j3) = 117 \angle -0.6^\circ$$


$$P_{Load} = 3V_\phi I_\phi \cos(\theta) = 3(117)(23.4)\cos(36.9) = 6571 \text{ w}$$

$$Q_{Load} = 3V_\phi I_\phi \sin(\theta) = 3(117)(23.4)\sin(36.9) = 4928 \text{ var}$$

$$S_{Load} = 3V_\phi I_\phi = 3(117)(23.4) = 8213 \text{ var}$$


One Line Diagram

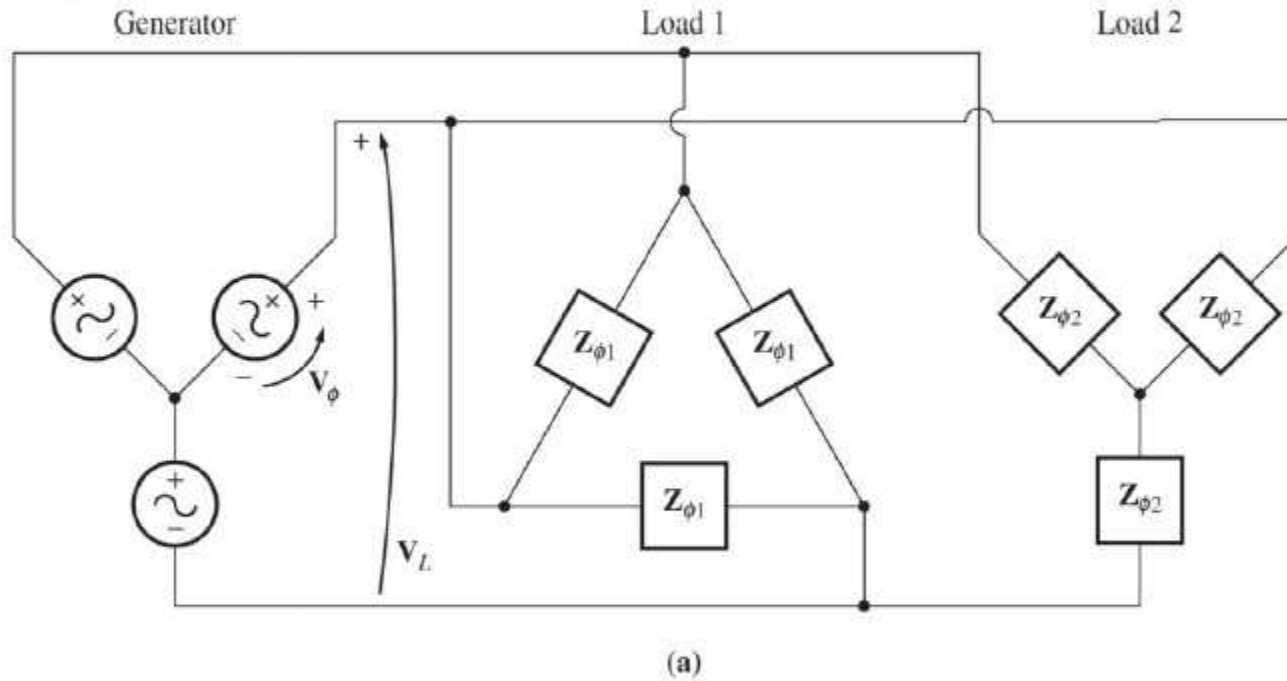Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



One Line Diagram

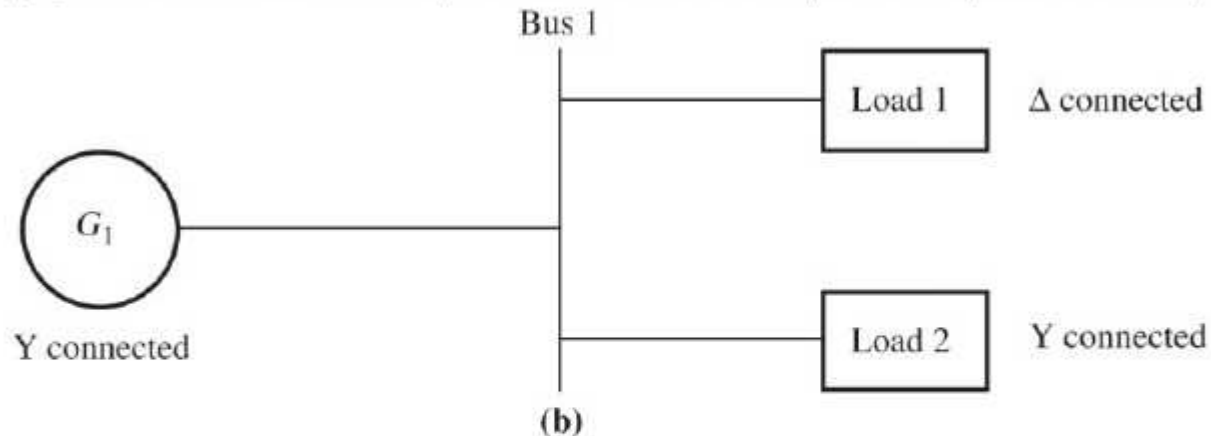
Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



If the line transmission lines can be assumed to have negligible impedances, then a one line diagram simplification can be made.

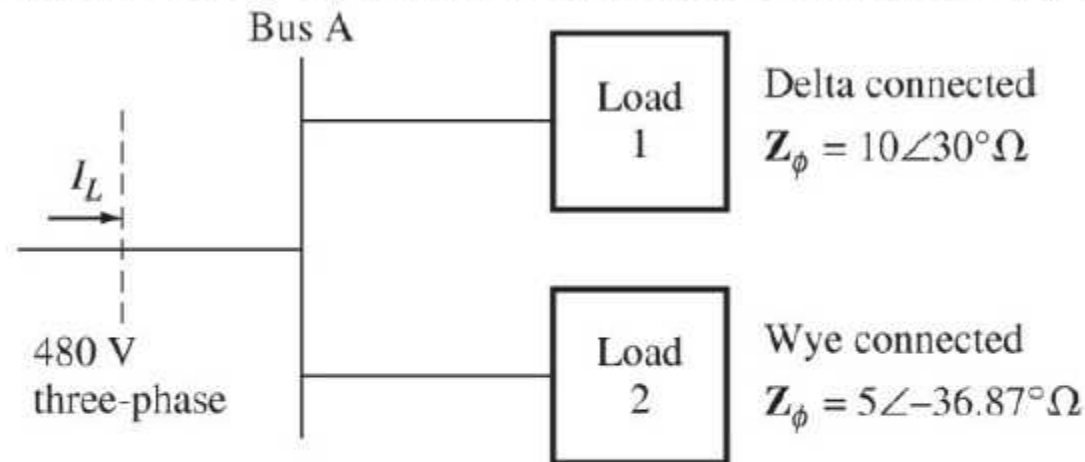Example... Find the total Power.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



$$I_{\phi 1} = \frac{480}{10} = 48A$$

$$P_1 = 3V_{\phi 1}I_{\phi 1} \cos(30) = 3(480)(48) \cos(30) = 59.9 \text{ kw}$$

$$Q_1 = 3V_{\phi 1}I_{\phi 1} \sin(30) = 3(480)(48) \sin(30) = 34.6 \text{ kvar}$$

Example continued ... Find the total Power and PF

$$I_{\phi 2} = \frac{480/\sqrt{3}}{5} = 55.4A$$

$$P_2 = 3V_{\phi 2}I_{\phi 2} \cos(-36.87) = 3 \frac{480}{\sqrt{3}} (55.4) \cos(-36.87) = 36.8 \text{ kw}$$

$$Q_2 = 3V_{\phi 2}I_{\phi 2} \sin(-36.87) = 3 \frac{480}{\sqrt{3}} (55.4) \sin(-36.87) = -27.6 \text{ kvar}$$


$$P_{tot} = 59.9 + 36.8 = 96.7 \text{ kw}$$

$$Q_{tot} = 34.6 + 3 - 27.6 = 7.0 \text{ kvar}$$


$$\theta = \tan^{-1} \frac{Q}{P} = \tan^{-1} \frac{7}{96.7} = 4.14^\circ$$

$$PF = \cos(\theta) = 0.997 \text{ lagging}$$

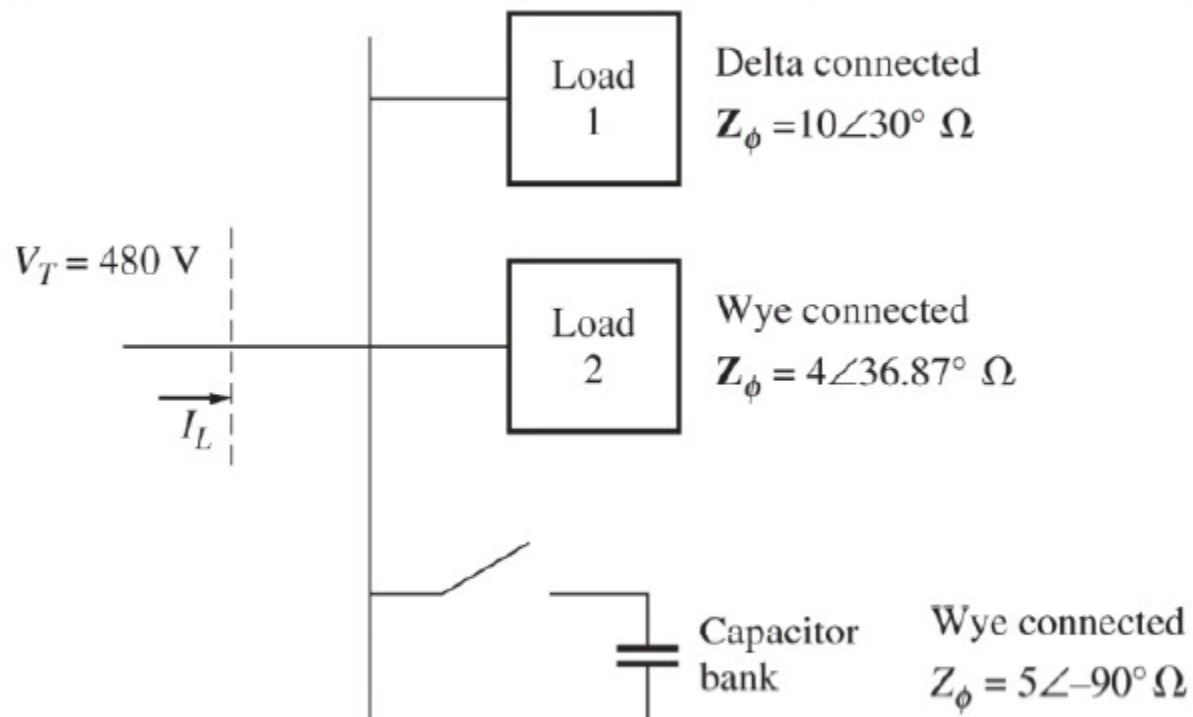Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



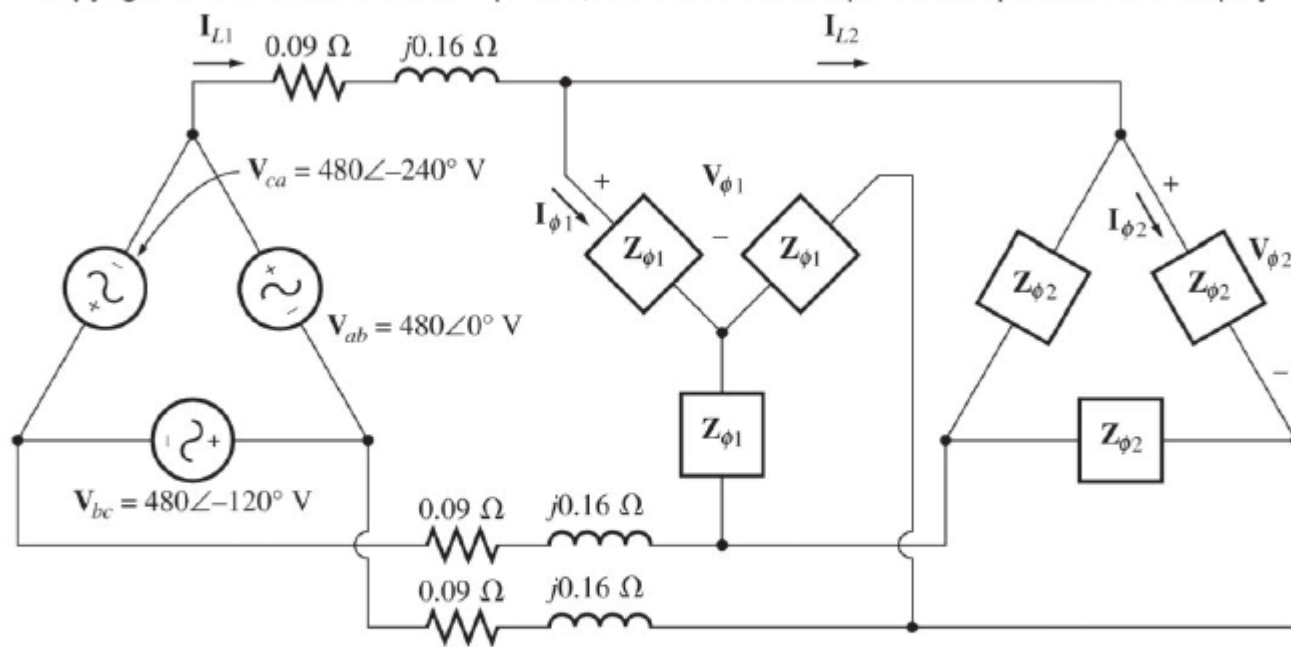Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



Generator

Load 1

Load 2

$$Z_{\phi 1} = 2.5\angle 36.87^\circ \Omega$$

$$Z_{\phi 2} = 5\angle -20^\circ \Omega$$