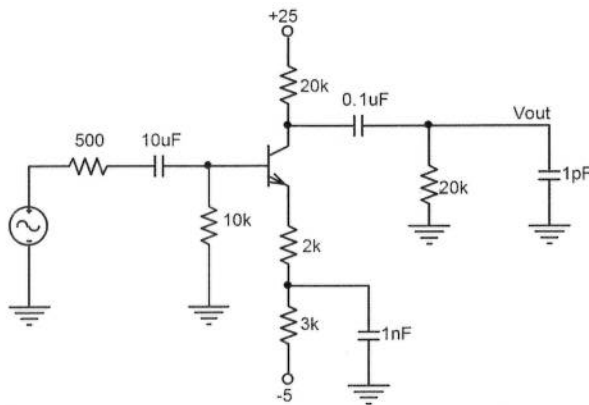


1. Recalling that the gain of a common emitter amplifier can be approximated by R_C/R_E , sketch an approximate magnitude frequency response for the circuit below. Label the following:

- Midband gain(s) in dB
- Frequency rolloff rates in dB/decade

It is not necessary to label the frequency breakpoints




w/ 1nF Cap open (Low Freq)

$$\text{gain} \approx \frac{10k}{5k} \Rightarrow 6 \text{ dB}$$


w/ 1nF cap short (higher freq)

$$\text{gain} \approx \frac{10k}{2k} = 5 \Rightarrow 14 \text{ dB}$$

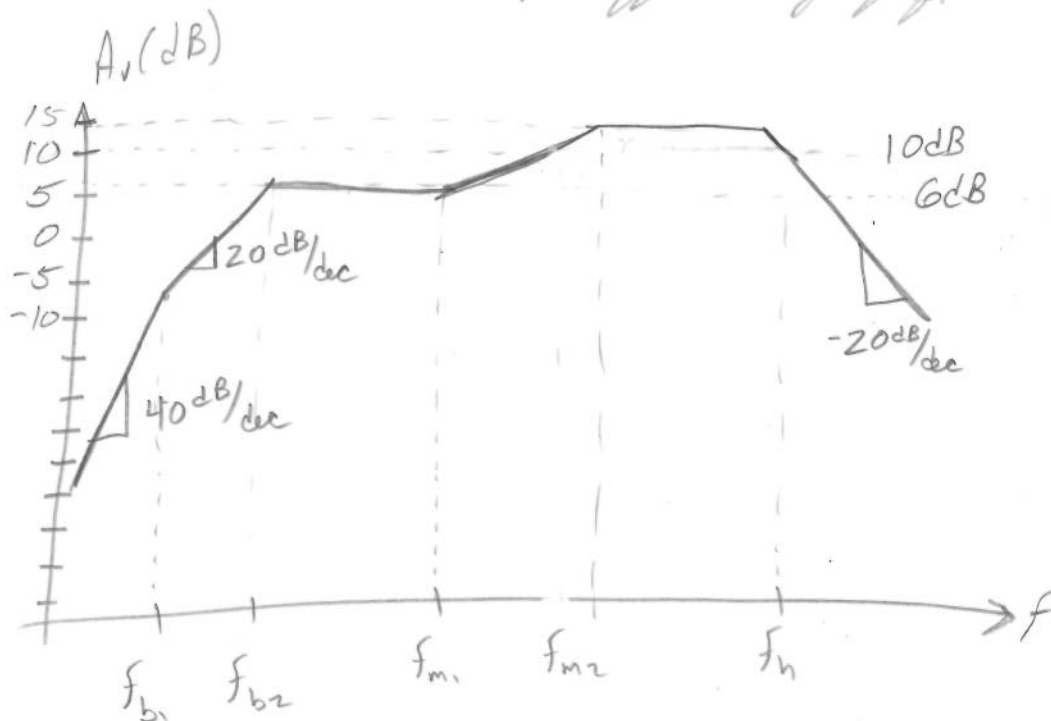- 10uF & 0.1uF affect low freq
- 1nF affects mid-band gain
- 1pF affects high freq.



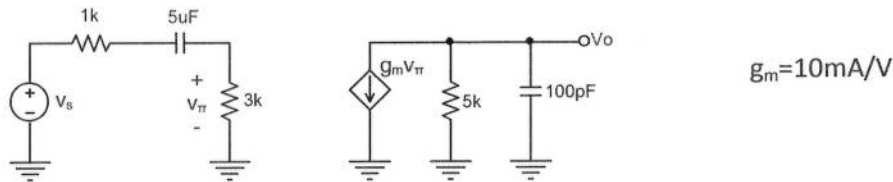2. Determine the midband gain and the high and low frequency breakpoints for the small signal model of an amplifier shown below.




Midband gain
$$\left. \begin{aligned} V_{\pi} &= V_s \cdot \frac{3}{4} \\ V_o &= -g_m V_{\pi} \cdot 5k \end{aligned} \right\} V_o = -(10) \left(\frac{3}{4} \right) (5) V_s \Rightarrow \frac{V_o}{V_s} = \underline{\underline{-37.5 \text{ V/V}}}$$

$$f_L = \frac{1}{2\pi R_{\pi} C} = \frac{1}{2\pi (4k) (5\mu F)} = \underline{\underline{7.96 \text{ Hz}}}$$


*note if a 1V source is placed @ the 100pF, V_{π} still = 0V
 $\therefore R_{\pi} = 5k$

$$f_h = \frac{1}{2\pi \cdot 5k \cdot 100pF} = \underline{\underline{318 \text{ kHz}}}$$

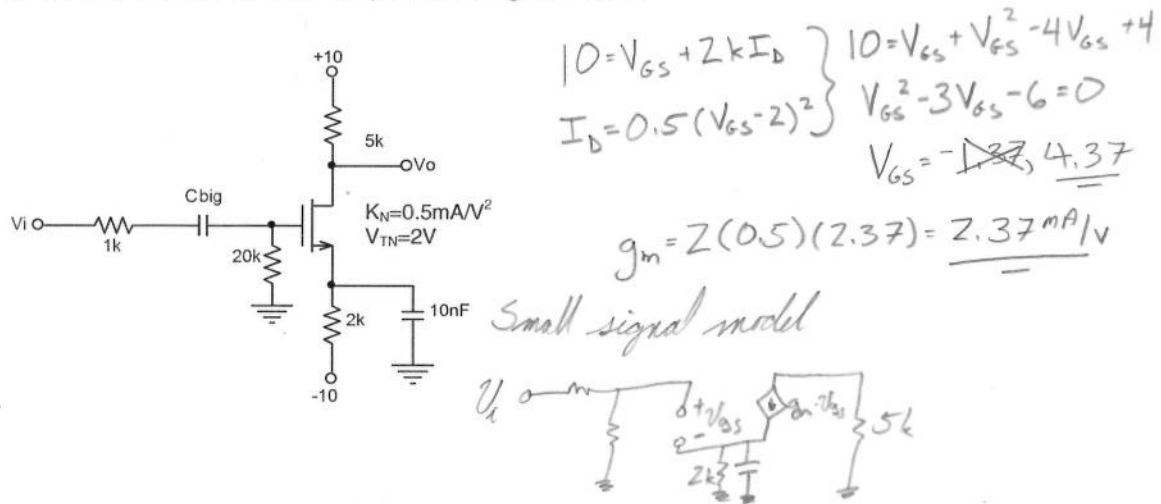3. Determine the two midband break frequencies for the amplifier shown below. You do not need to determine any other break frequencies or gain values.



From 10nF:

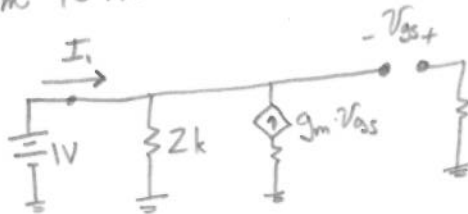


$$I_1 = \frac{1V}{2k} + g_m$$

$$R_m = 2k \parallel \frac{1}{g_m} = 348 \Omega$$


$$f_{m1} = \frac{1}{2\pi(2k)(10nF)} = 7.96 \text{ kHz}$$

$$f_{m2} = \frac{1}{2\pi(348)(10nF)} = 45.7 \text{ kHz}$$

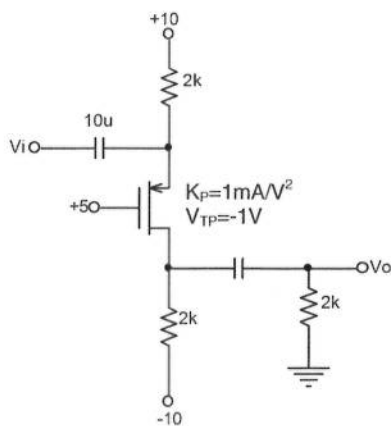4. For the common gate circuit below, determine the midband gain and the low frequency breakpoint. Assume the coupling capacitor on the output is very large.



DC


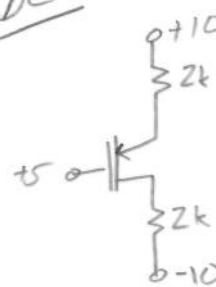


$$\begin{aligned}
 5 &= V_{SG} + 2k I_D \\
 I_D &= 1(V_{SG} - 1)^2 \\
 5 &= V_{SG} + 2(V_{SG}^2 - 2V_{SG} + 1) \\
 2V_{SG}^2 - 3V_{SG} - 3 &= 0 \\
 V_{SG} &= \underline{\underline{2.186}}, I_D = \underline{\underline{1.41mA}}
 \end{aligned}$$

Small-Signal Model


$$g_m = 2(1)(2.186 - 1) = \underline{\underline{2.37mA/V}}$$

AC circuit

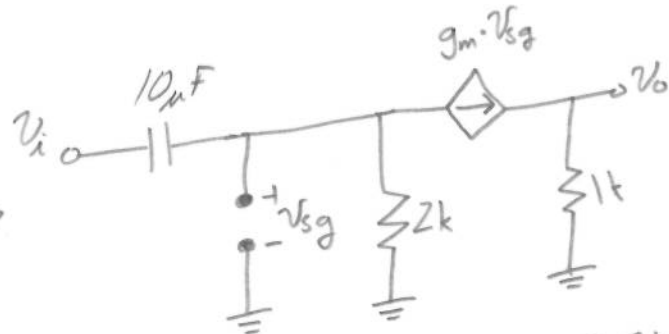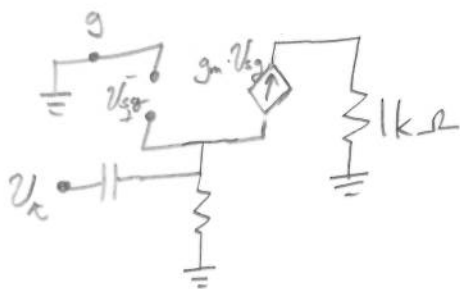

$$V_o = 2.37(V_i)(1) = 2.37 \cdot V_i \Rightarrow \underline{\underline{A_v = 2.37}}$$

R_{Th} from 10uF

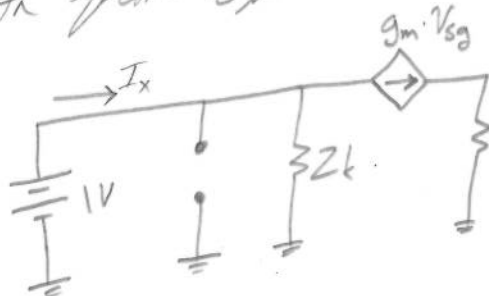

$$I_x = \frac{1V}{2k} + g_m$$

$$R_{Th} = 2k \parallel \frac{1}{g_m} = 348\Omega$$

$$\therefore f_L = \frac{1}{2\pi(348)(10\mu F)} = \underline{\underline{45.7Hz}}$$