

1. Design a falling-edge triggered J-K flip-flop with an active-high asynchronous clear.

- a) Draw the logic symbol and a truth table.
- b) Write a complete VHDL model (entity and behavioral architecture).


2. Draw the circuit generated by the following VHDL model. Completely label all components and signals.

```
entity SR2 is
  port(S, CLK: in bit;
        D : in bit_vector(1 downto 0);
        Q: out bit_vector(1 downto 0));
end SR2;

architecture DATAFLOW of SR2 is
  signal M, R: bit_vector(1 downto 0);
begin
  M <= D when S = '1' else (R(0)&R(1));
  process(CLK)
  begin
    if rising_edge(CLK) then
      R <= M;
    end if;
  end process;
  Q <= R;
end DATAFLOW;
```

## ① J-K Flip-Flop

a)

 

CLR	J	K	CLK	$Q^+$
1	x	x	x	0
0	0	0	↓	Q
0	1	0	↓	1
0	0	1	↓	0
0	1	1	↓	$Q'$

b) entity JKFF is  
 port (CLR, J, K, CLK : in bit;  
 Q : out bit);

end JKFF;

architecture Behave of JKFF is  
 signal QI : bit;

begin  
 process (CLR, CLK)

begin

if CLR = '1' then

QI <= '0';

elsif falling-edge(CLK) then

if J = '1' and K = '0' then

QI <= '1';

elsif J = '0' and K = '1' then

QI <= '0';

```

    elsif J = '1' and K = '1' then
        QI <= not QI;
    end if;
end if;
end process
Q <= QI;
end Behavior;

```

SRZ

(2)

