

ELEC-313  
Lab 4: DC Motor Driver

October 9, 2013

Date Performed: October 09, 2013  
Partners: Charles Pittman  
Stephen Wilson

## 1 Objective

The objective is to construct, measure, and observe the behavior of two common diode circuits: a voltage rectifier, and a voltage regulator.

## 2 Equipment

Compact L290 Motor Driver Kit	Function generator: HP 33120A
6 V DC Motor	Multimeter:
Power supply: HP E3631A	Oscilloscope: Agilent 54622D

## 3 Schematics

## 4 Procedure

### 4.1 Part One

### 4.2 Part Two

## 5 Results

Enable	L <sub>1</sub>	L <sub>2</sub>	V <sub>out</sub>	LED	Motor
L	L	L	−0.01 V	off	off
L	L	H	−0.01 V	off	off
L	H	L	−0.01 V	off	off
L	H	H	−0.01 V	off	off
H	L	L	−0.18 V	off	off
H	L	H	5.7 V	red	CW
H	H	L	5.5 V	green	CCW
H	H	H	0.01 V	both	off

Table 1: Logic Table

Duty Cycle	V <sub>out</sub>
20%	−3.01 V
30%	−3.39 V
40%	−3.76 V
50%	−4.13 V
60%	−4.49 V
70%	−4.84 V
80%	−5.19 V

Table 2: Pulse-width modulation

## 6 Comparison of Results

## 7 Conclusion

## 8 Equations

$$\%_{diff} = \frac{|nominal - measured|}{nominal} \times 100\% \quad (1)$$

$$V_r = V_{max} - V_{min} \quad (2)$$

$$\%_{reg} = \frac{V_{load} - V_{noload}}{V_{noload}} \times 100\% \quad (3)$$