

Design Examples

ELEC 418

Advanced Digital Systems

Dr. Ron Hayne

Images Courtesy of Thomson Engineering



BCD to 7-Segment Display

FIGURE 4-2:
Seven-Segment
Display


 
 


FIGURE 4-2:
Seven-Segment
Display

 

BCD to 7-Segment Display

```
entity BCD_Seven is
    port (BCD: in std_logic_vector(3 downto 0);
          Seven: out std_logic_vector(7 downto 1));
end BCD_Seven;
```


```
architecture Behave of BCD_Seven is
begin
    process (BCD)
    begin
```

BCD to 7-Segment Display


```
case BCD is
  when "0000" => Seven <= "0111111";
  when "0001" => Seven <= "0000110";
  when "0010" => Seven <= "1011011";
  when "0011" => Seven <= "1001111";
  when "0100" => Seven <= "1100110";
  when "0101" => Seven <= "1101101";
  when "0110" => Seven <= "1111101";
  when "0111" => Seven <= "0000111";
  when "1000" => Seven <= "1111111";
  when "1001" => Seven <= "1101111";
  when others => null;
end case;
end process;
end Behave;
```

Synchronization & Debouncing

**FIGURE 4-22:
Debouncing
Mechanical
Switches**

 


(a) Switch bouncing

 


(b) Debouncing and synchronizing circuit

**FIGURE 4-22:
Debouncing
Mechanical
Switches**


 


(a) Switch bouncing

 

(b) Debouncing and synchronizing circuit

Single Pulser

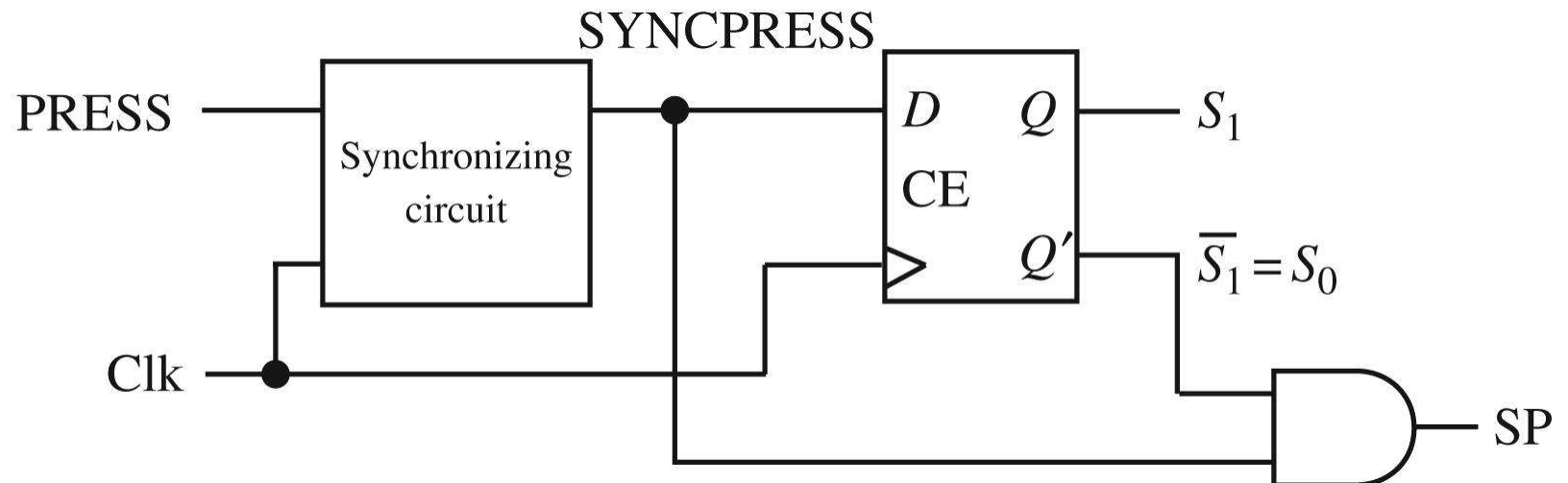 

Behavioral Model

```
entity PULSE is
    port(SW, CLK: in std_logic;
          SP: out std_logic);
end PULSE;

architecture Behave of PULSE is
    signal Sync: std_logic_vector(2 downto 0) := "000";
begin
    process(CLK)
    begin
        if rising_edge(CLK) then
            Sync <= SW & Sync(2) & Sync(1);
        end if;
    end process;
    SP <= Sync(1) and not Sync(0);
end Behave;
```

VHDL Test Bench

```
entity Pulse_Test is  
end Pulse_Test;
```

```
architecture Behave of Pulse_Test is
```

```
    component PULSE
```

```
        port(SW, CLK: in std_logic;  
             SP: out std_logic);
```

```
    end component;
```

```
    signal SW, CLK: std_logic := '0';
```

```
    signal SP: std_logic;
```

```
    constant CLK_period: time := 100 ns;
```


```
begin
```

```
    uut: PULSE port map(SW, CLK, SP);
```



VHDL Test Bench

```
tb : process
begin
    wait for 48 ns;
    SW <= '1'; wait for 1 ns;
    SW <= '0'; wait for 1 ns;
    SW <= '1'; wait for 1 ns;
    SW <= '0'; wait for 1 ns;
    SW <= '1'; wait for 1 ns;
    SW <= '0'; wait for 1 ns;
    SW <= '1'; wait for 1 ns;
    SW <= '0'; wait for 1 ns;
    SW <= '1'; wait for 1 ns;
    SW <= '0'; wait for 1 ns;
    SW <= '1'; wait for 1 ns;
    SW <= '0'; wait for 1 ns;
    SW <= '1'; wait for 1 ns;
    SW <= '0'; wait for 1 ns;
    SW <= '1'; wait for 485 ns;
    SW <= '0'; wait for 1 ns;
    SW <= '1'; wait for 1 ns;
    SW <= '0'; wait for 1 ns;
    SW <= '1'; wait for 1 ns;
    SW <= '0'; wait for 1 ns;
    SW <= '1'; wait for 1 ns;
    SW <= '0'; wait for 1 ns;
    SW <= '1'; wait for 1 ns;
    SW <= '0'; wait for 1 ns;
    SW <= '1'; wait for 1 ns;
    SW <= '0';
    wait;
end process;
end;
```

VHDL Simulation

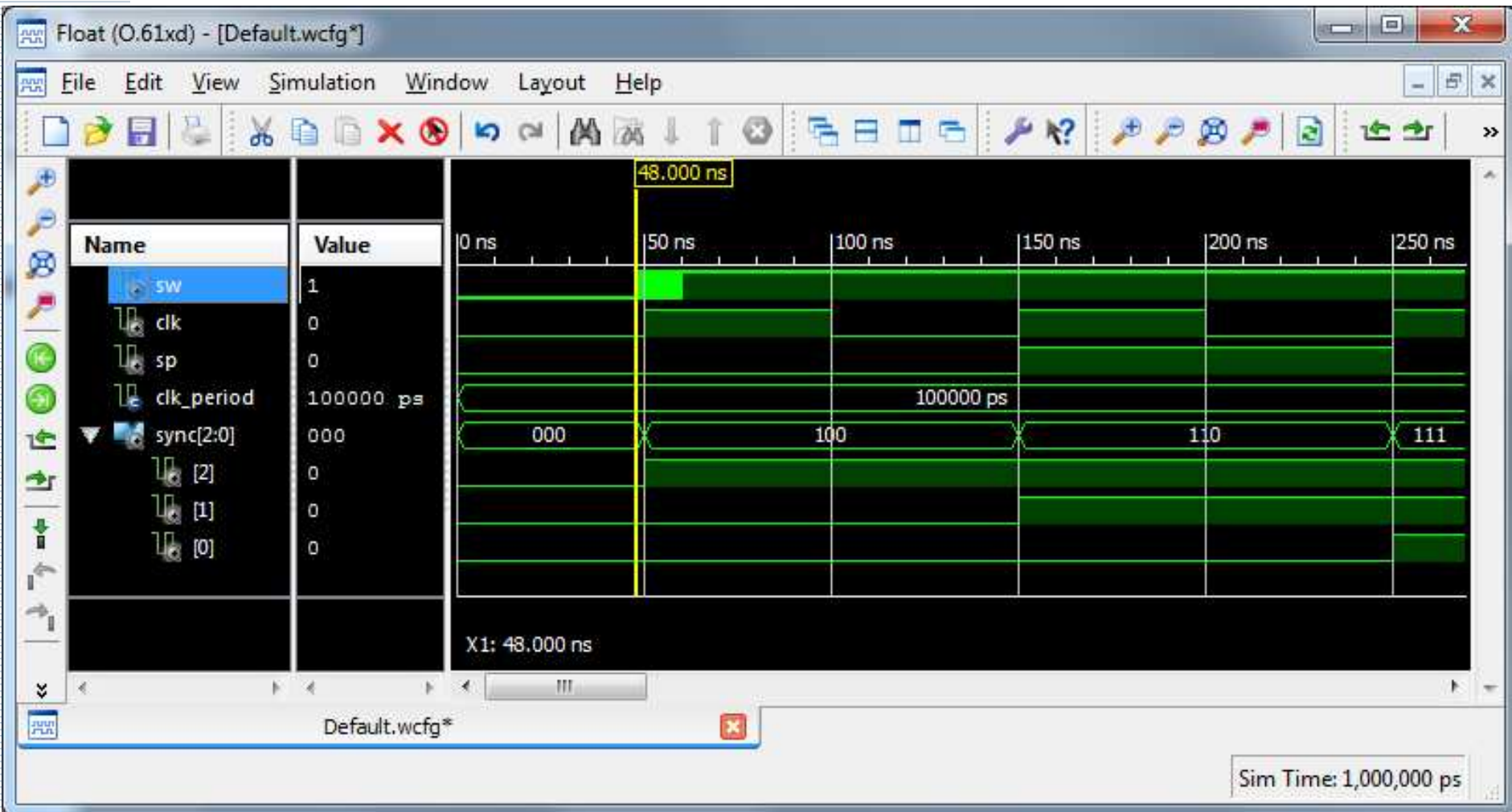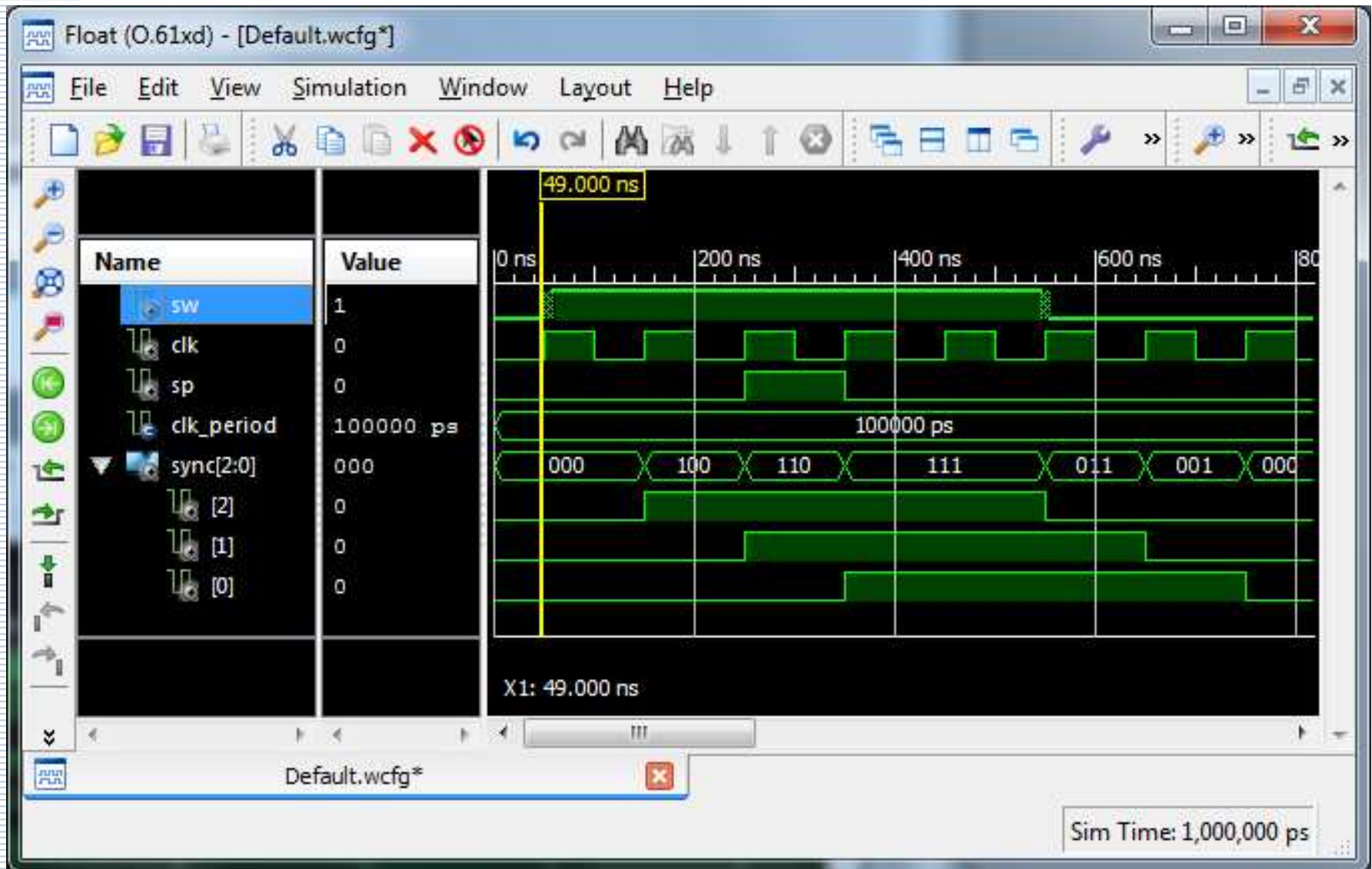


VHDL Simulation




Adders

- ♦ **Ripple-Carry Adder**
 - Concatenation of Full Adders
- ♦ **Carry Look-Ahead Adder**
 - Fast Adder
 - Carry signals calculated in advance
- ♦ **Serial Adder**
 - Single Full Adder
 - Shift and add one bit at a time

Ripple-Carry Adder

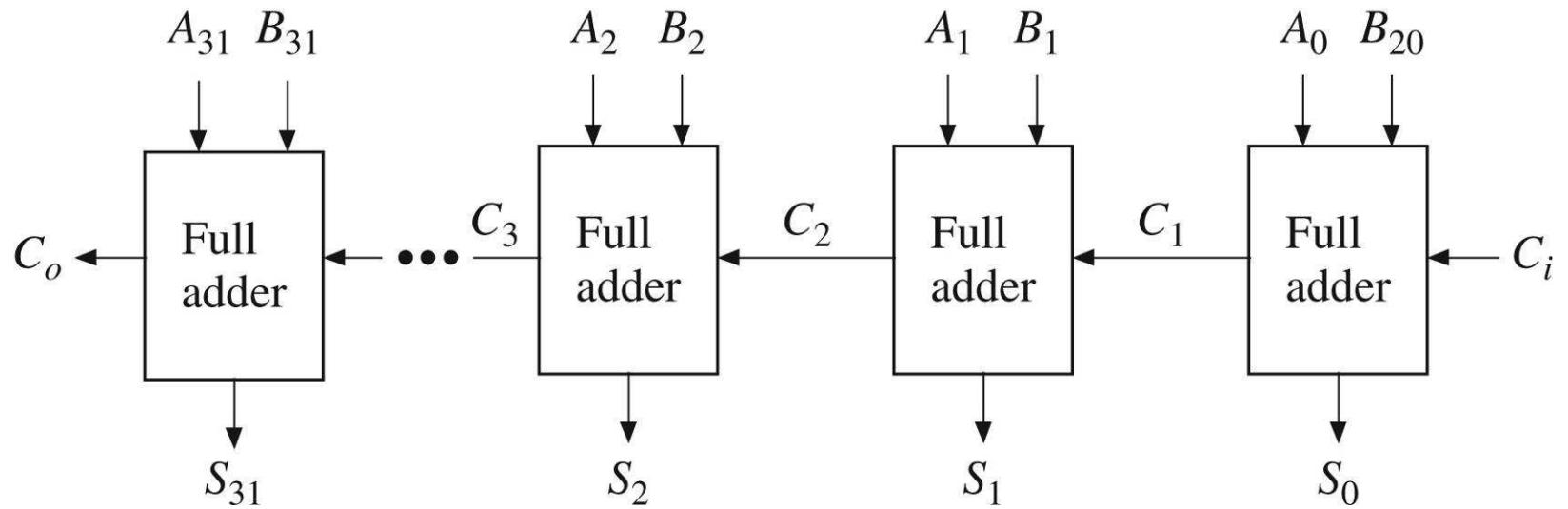

Carry Look-Ahead Adder

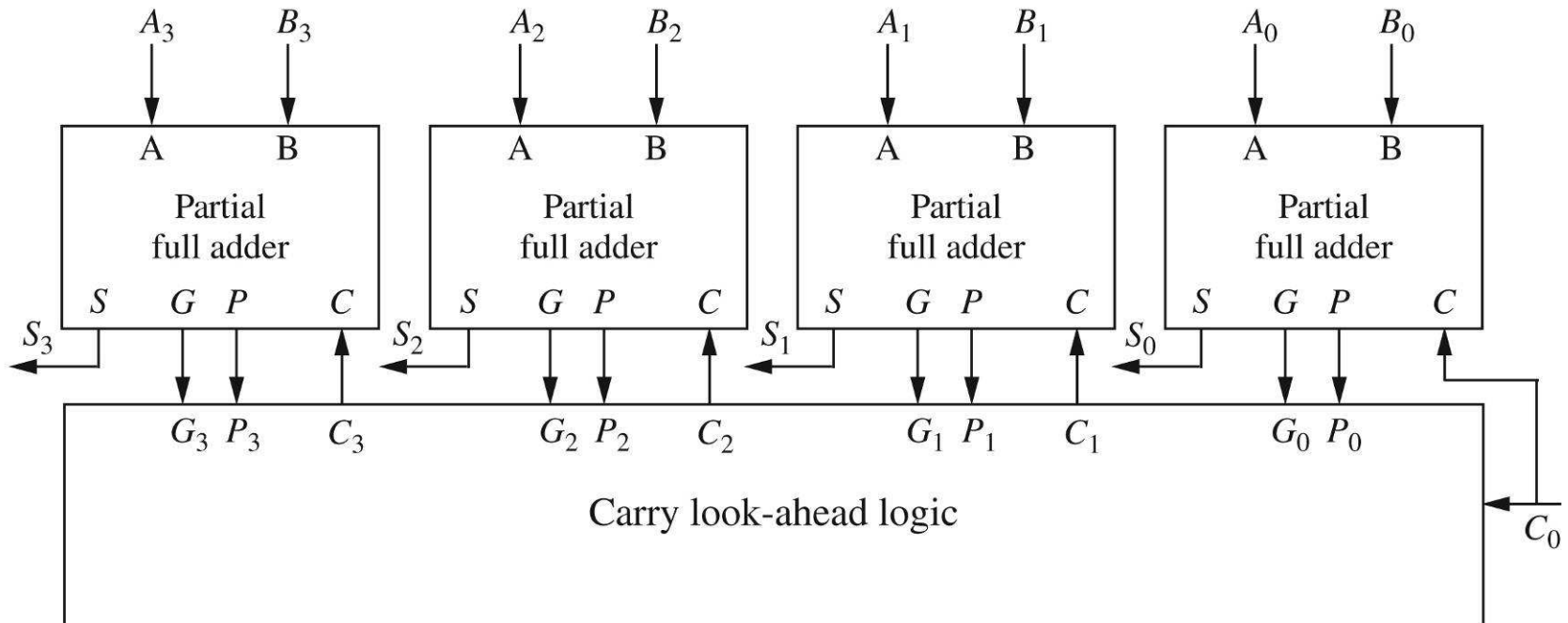

Carry Look-Ahead (CLA)

$$S_i = A_i \oplus B_i \oplus C_i$$

$$C_{i+1} = A_i B_i + (A_i \oplus B_i) C_i$$

$$G_i = A_i B_i \quad \text{Generate (both 1)}$$

$$P_i = A_i \oplus B_i \quad \text{Propagate (either 1)}$$

$$S_i = P_i \oplus C_i$$

$$C_{i+1} = G_i + P_i C_i$$

4-bit CLA Adder

$$C_1 = G_0 + P_0C_0$$


$$C_2 = G_1 + P_1C_1 = G_1 + P_1G_0 + P_1P_0C_0$$

$$C_3 = G_2 + P_2C_2 = G_2 + P_2G_1 + P_2P_1G_0 + P_2P_1P_0C_0$$

$$C_4 = G_3 + P_3C_3 = G_3 + P_3G_2 + P_3P_2G_1 + P_3P_2P_1G_0 + P_3P_2P_1P_0C_0$$

- Limited by fan-in

16-bit CLA Adder

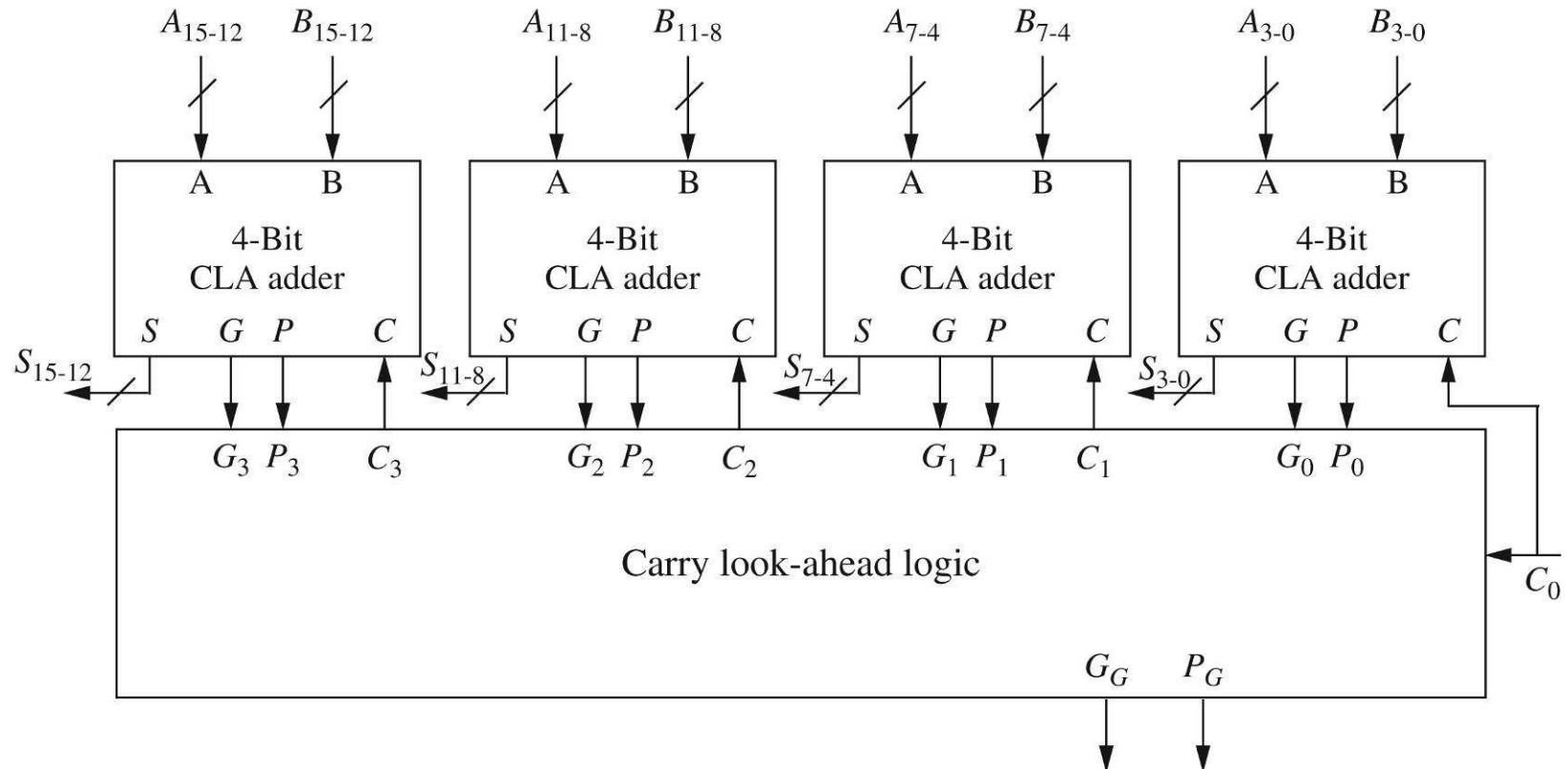

16-bit CLA Adder

```
entity CLA16 is
    port(A, B: in std_logic_vector(15 downto 0);
         Ci: in std_logic;
         S: out std_logic_vector(15 downto 0);
         Co, PG, GG: out std_logic);
end CLA16;
```

16-bit CLA Adder

architecture Structure of CLA16 is
component CLA4

```
    port(A, B: in std_logic_vector(3 downto 0);  
          Ci: in std_logic;  
          S: out std_logic_vector(3 downto 0);  
          Co, PG, GG: out std_logic);
```

end component;

component CLALogic is

```
    port(G, P: in std_logic_vector(3 downto 0);  
          Ci: in std_logic;  
          C: out std_logic_vector(3 downto 1);  
          Co, PG, GG: out std_logic);
```

end component;

16-bit CLA Adder

```
signal G, P: std_logic_vector(3 downto 0);
signal C: std_logic_vector(3 downto 1);
begin
    CarryLogic: CLALogic port map(G, P, Ci, C, Co, PG,
                                   GG);
    ADD0: CLA4 port map(A(3 downto 0), B(3 downto 0), Ci,
                        S(3 downto 0), open, P(0), G(0));
    ADD1: CLA4 port map(A(7 downto 4), B(7 downto 4),
                        C(1), S(7 downto 4), open, P(1), G(1));
    ADD2: CLA4 port map(A(11 downto 8), B(11 downto 8),
                        C(2), S(11 downto 8), open, P(2), G(2));
    ADD3: CLA4 port map(A(15 downto 12), B(15 downto 12),
                        C(3), S(15 downto 12), open, P(3), G(3));
end Structure;
```

Behavioral Model

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;

entity Adder_Behave16 is
    Port ( A : in  std_logic_vector (15 downto 0);
          B : in  std_logic_vector (15 downto 0);
          Ci : in  std_logic;
          S : out std_logic_vector (15 downto 0);
          Co : out std_logic);
end Adder_Behave16;
```


Behavioral Model

```
architecture Behave of Adder_Behave16 is
    signal sum17: std_logic_vector(16 downto 0);
begin
    sum17 <= ('0' & A) + ('0' & B) + (X"0000" & Ci);
    S <= sum17(15 downto 0);
    Co <= sum17(16);
end Behave;
```

FPGA Synthesis Results

Adder Type	Ripple-Carry	CLA	Behavioral
Number of LUTs	32	65	16
Combinational Path Delay (ns)	22.7	12.5	7.6
Levels of Logic	18	9	19


Serial Adder

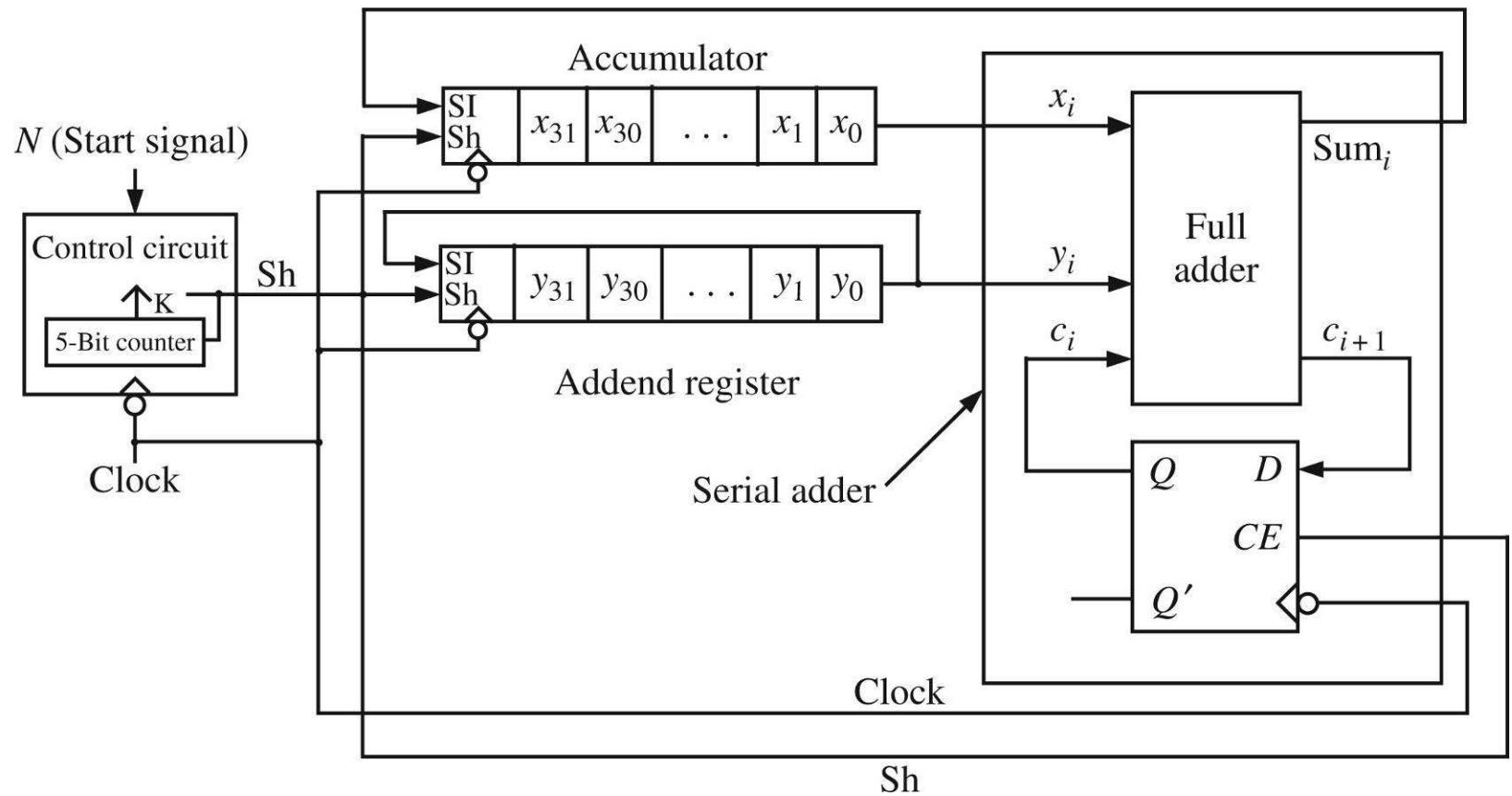

Adder Comparison

Adder size	Ripple-Carry Adder Delay	CLA Delay	Serial Adder Delay
4 bit	$8t_g$	$5-6t_g$	$16t_g$
16 bit	$32t_g$	$7-8t_g$	$64t_g$
32 bit	$64t_g$	$9-10t_g$	$128t_g$
64 bit	$128t_g$	$9-10t_g$	$256t_g$


Data Path and Controller

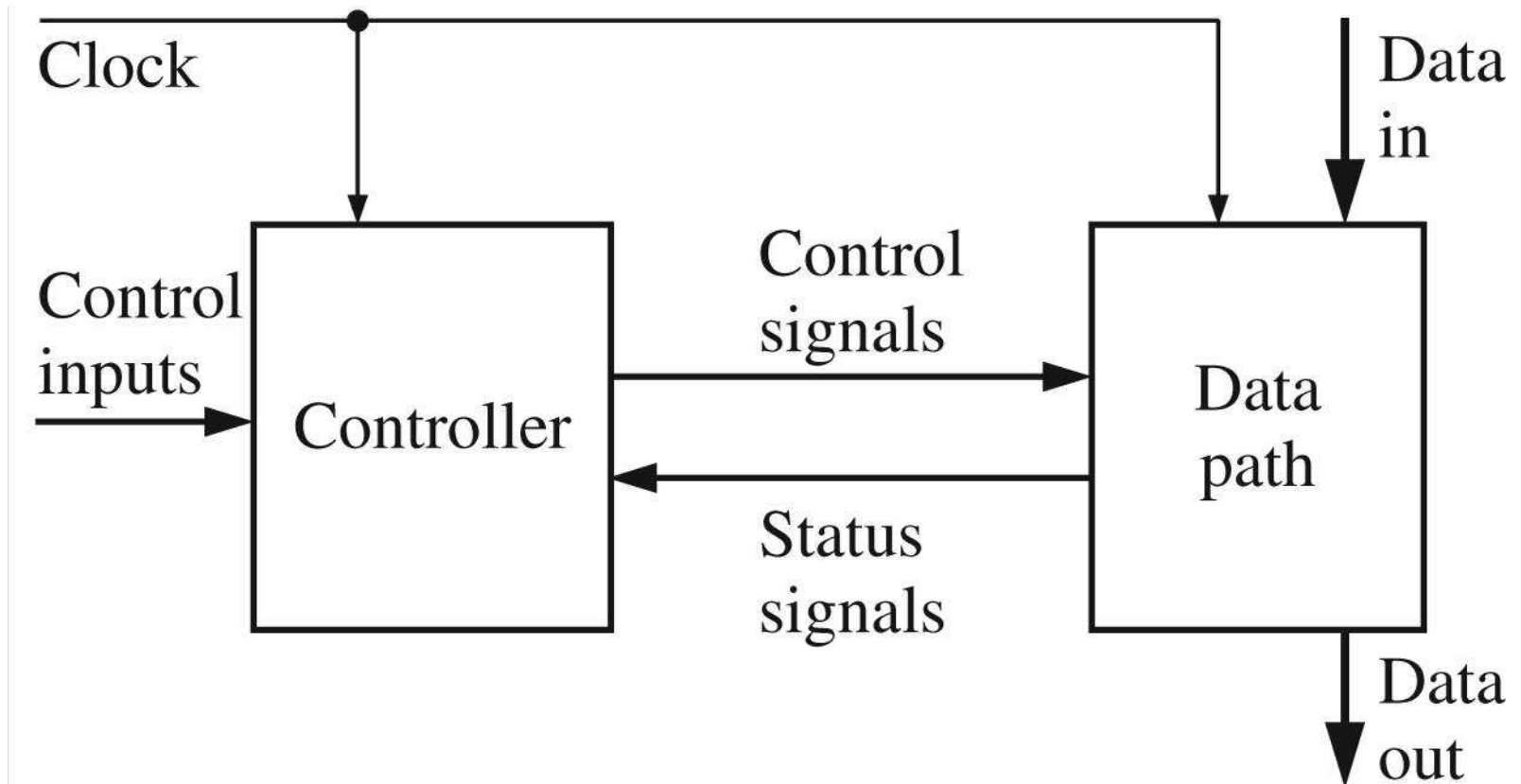


Add-and-Shift Multiplier

- ♦ 4-bit Multiplicand
- ♦ 4-bit Multiplier
- ♦ 8-bit Product
- ♦ 4-bit Adder
- ♦ Controller

Add-and-Shift Multiplier

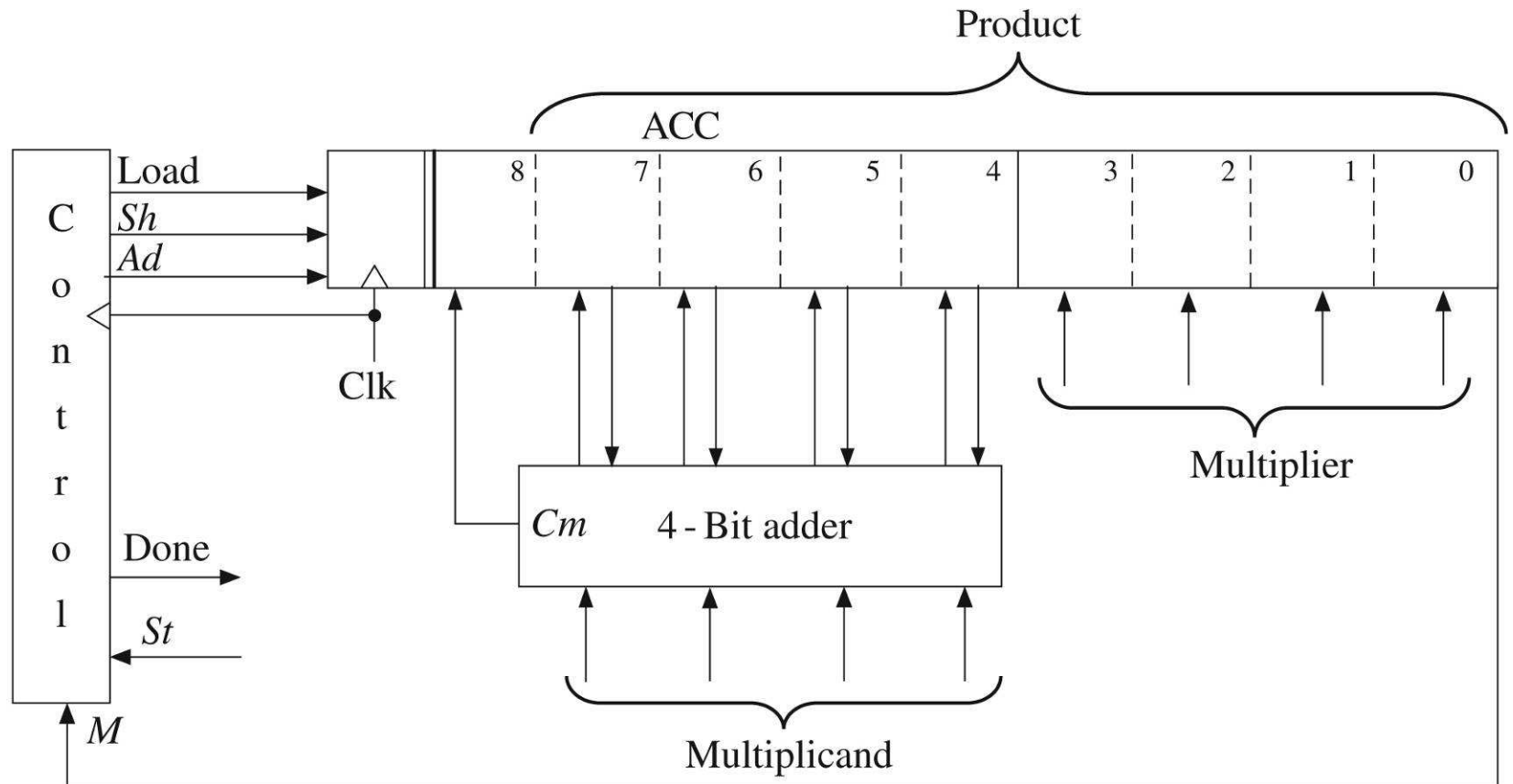

Multiplier Control

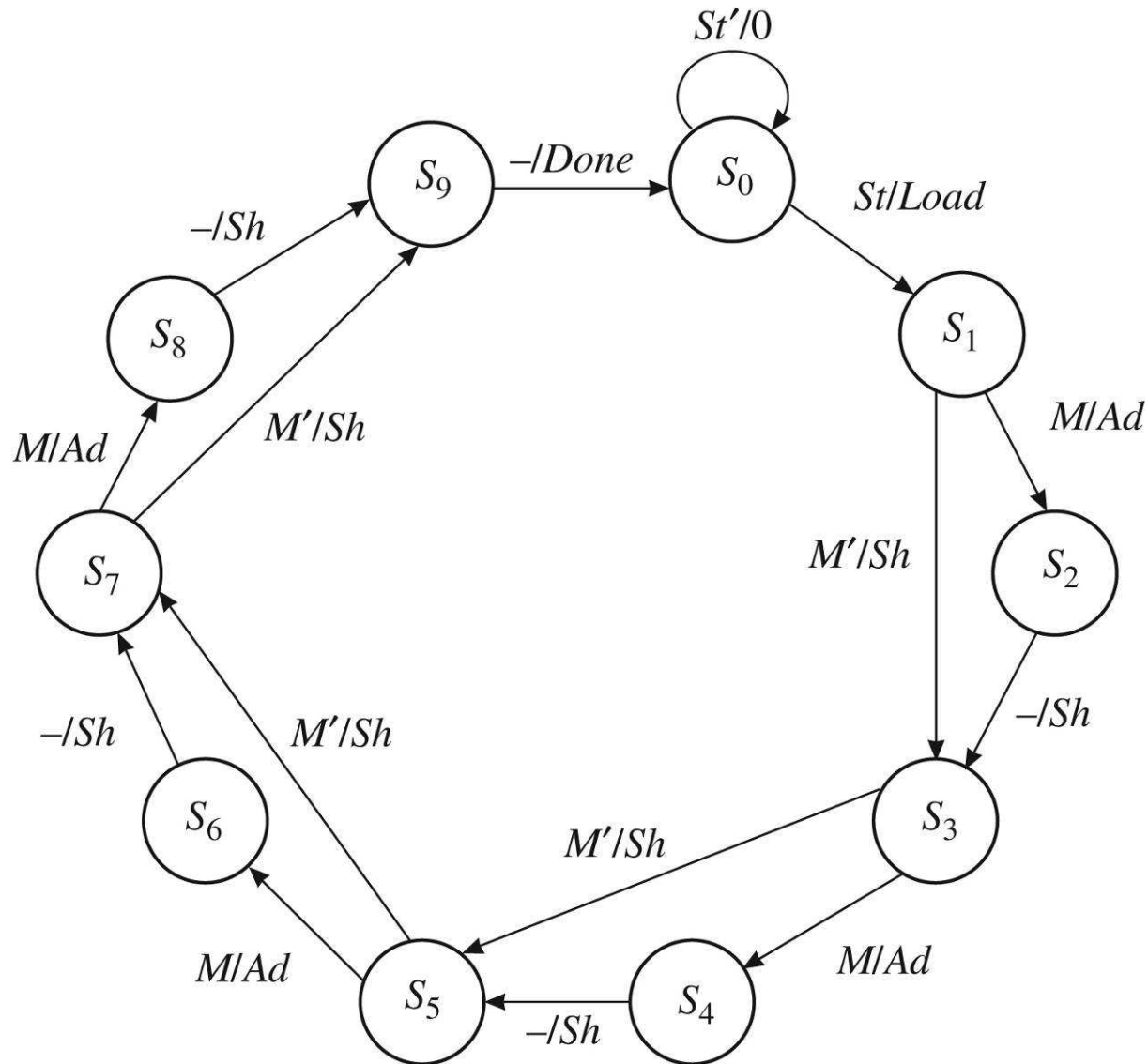

Behavioral Model

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;

entity Mult4X4 is
  port(Clk, St: in std_logic;
        Mplier, Mcand: in std_logic_vector(3 downto 0);
        Product: out std_logic_vector(7 downto 0);
        Done: out std_logic);
end Mult4X4;
```

Behavioral Model

```
architecture Behave of Mult4X4 is
    signal State: integer range 0 to 9;
    signal ACC: std_logic_vector(8 downto 0);
    alias M: std_logic is ACC(0); -- bit 0 of ACC
begin
    process(Clk)
    begin
        if rising_edge(CLK) then
            case State is
                when 0=>
                    if St='1' then -- Load
                        ACC(8 downto 4) <= "00000";
                        ACC(3 downto 0) <= Mplier;
                        State <= 1;
                    end if;
            end case;
        end if;
    end process;
end architecture;
```


Behavioral Model

```
when 1 | 3 | 5 | 7 =>
  if M = '1' then -- Add
    ACC(8 downto 4) <= '0' & ACC(7 downto 4)
                        + Mcand;
    State <= State + 1;
  else -- Shift
    ACC <= '0' & ACC(8 downto 1);
    State <= State + 2;
  end if;
```


Behavioral Model

```
when 2 | 4 | 6 | 8 => -- Shift
    ACC <= '0' & ACC(8 downto 1);
    State <= State + 1;
when 9 => -- end of cycle
    State <= 0;
end case;
end if;
end process;
Done <= '1' when State = 9 else '0';
Product <= ACC(7 downto 0);
end Behave;
```

VHDL Simulation

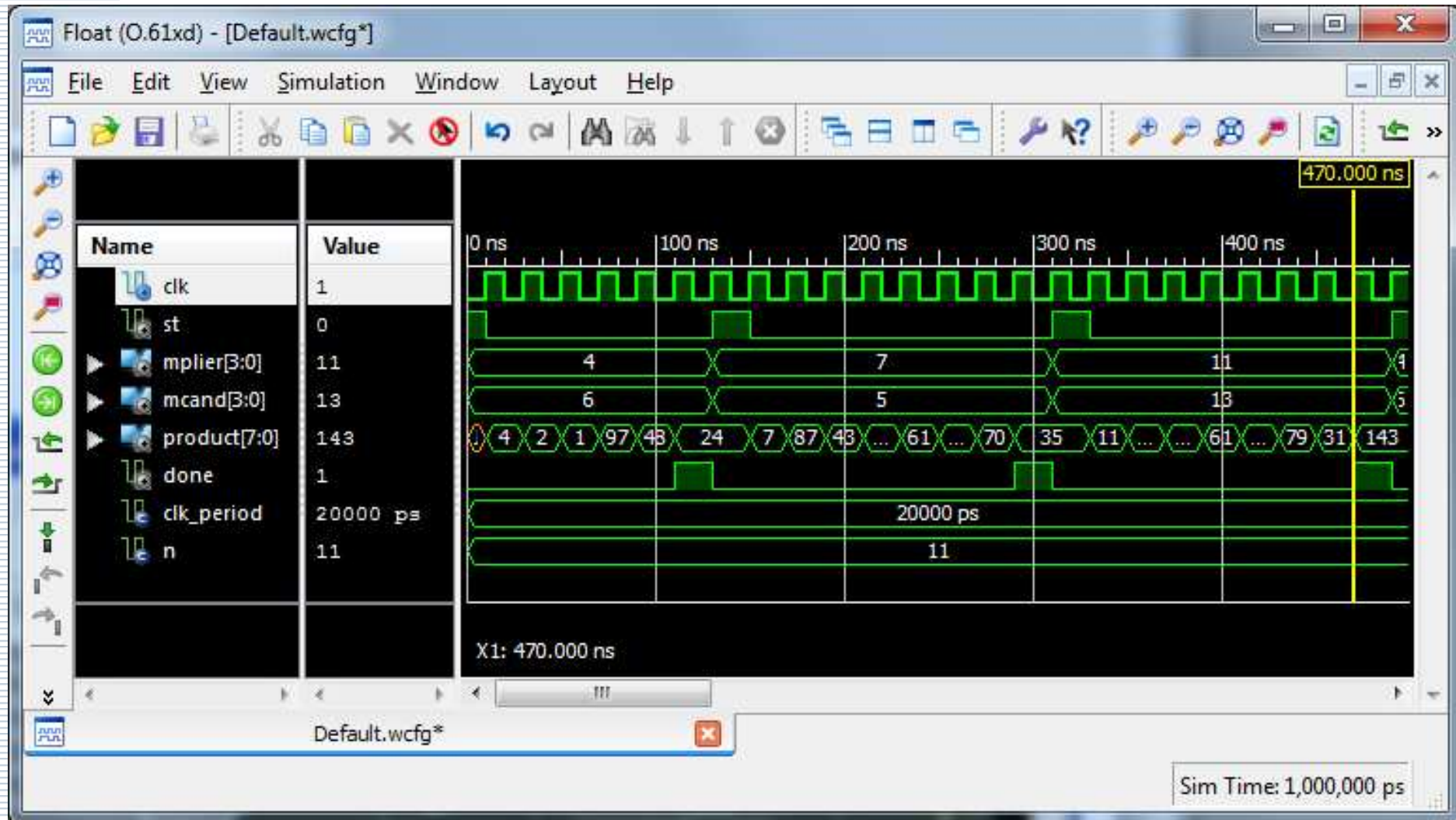

FPGA Implementation

- ♦ **Xilinx Spartan3e**
 - 250K System Gates
 - 50 MHz Clock
- ♦ **ChipScope Pro**
 - Virtual Input/Output Core (VIO)
 - Integrated Logic Analyzer (ILA)
- ♦ **Real-Time Verification**
 - Captures On-chip Signals
 - Off-chip Analysis via JTAG Programming Cable

VHDL Test Bench

```
entity testmult4x4 is
    port(CLK: in std_logic);
end testmult4x4;
```

```
architecture test1 of testmult4x4 is
    component mult4x4
        port(Clk, St: in std_logic;
            Mplier, Mcand: in std_logic_vector(3 downto 0);
            Product: out std_logic_vector(7 downto 0);
            Done: out std_logic);
    end component;
```

VHDL Test Bench

```
component ila
```

```
    port(control: in  std_logic_vector(35 downto 0);
```

```
          clk: in std_logic;
```

```
          trig0: in std_logic_vector(17 downto 0));
```

```
end component;
```

```
component vio
```

```
    port(control: in std_logic_vector(35 downto 0);
```

```
          clk: in std_logic;
```

```
          sync_in: in std_logic_vector(8 downto 0);
```

```
          sync_out: out std_logic_vector(8 downto 0));
```

```
end component;
```

VHDL Test Bench

```
signal ...
```

```
signal ...
```

```
begin
```

```
    mult1: mult4x4 port map(CLK, St, Mplier, Mcand,  
                             Product, Done);
```

```
    i_ila: ila port map(control0, clk, trig0);
```


```
    i_vio: vio port map(control1, clk, sync_in,  
                          sync_out);
```

VHDL Test Bench

```
trig0(17) <= st;  
trig0(16 downto 13) <= Mplier;  
trig0(12 downto 9) <= Mcand;  
trig0(8 downto 1) <= Product;  
trig0(0) <= Done;  
sync_in(8 downto 1) <= Product;  
sync_in(0) <= Done;  
St <= sync_out(8);  
Mplier <= sync_out(7 downto 4);  
Mcand <= sync_out(3 downto 0);
```

```
end test1;
```

ChipScope Pro Analyzer

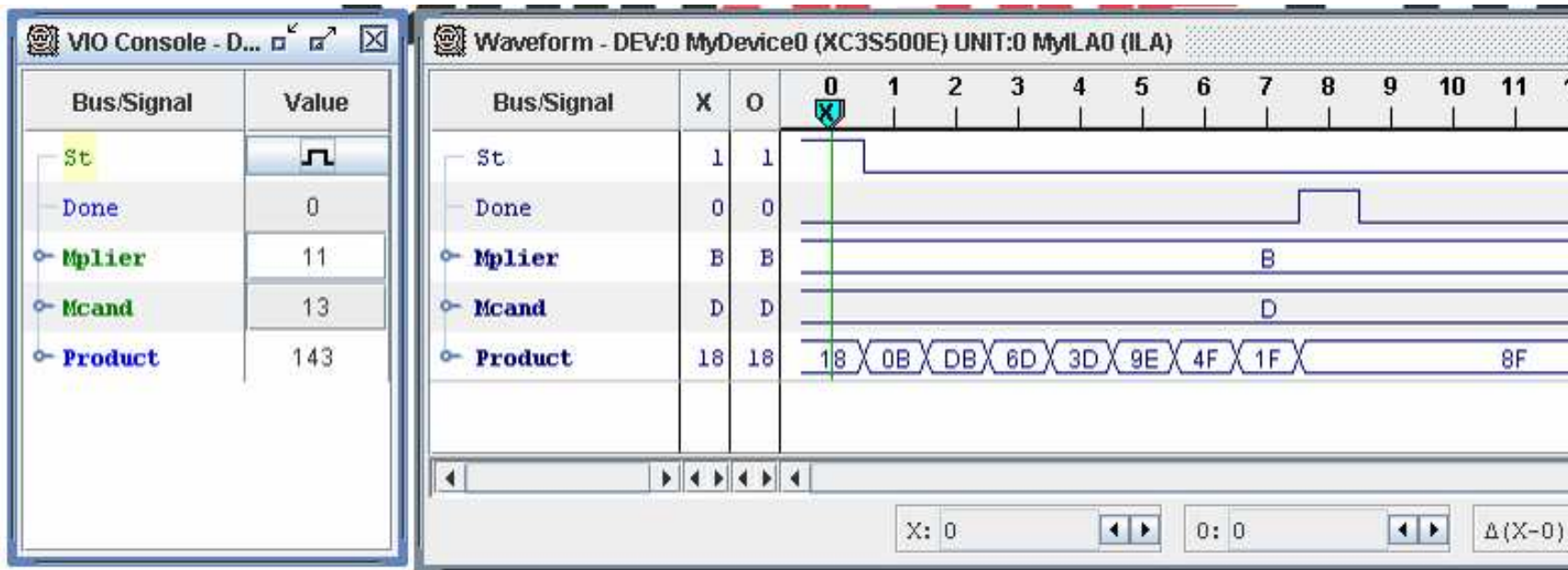


Array Multiplier


				X_3	X_2	X_1	X_0
				Y_3	Y_2	Y_1	Y_0
				X_3Y_0	X_2Y_0	X_1Y_0	X_0Y_0
		X_3Y_1		X_2Y_1	X_1Y_1	X_0Y_1	
		C_{12}		C_{11}	C_{10}		
	C_{13}	S_{13}	S_{12}	S_{11}	S_{10}		
	X_3Y_2	X_2Y_2	X_1Y_2	X_0Y_2			
	C_{22}	C_{21}	C_{20}				
C_{23}	S_{23}	S_{22}	S_{21}	S_{20}			
X_3Y_3	X_2Y_3	X_1Y_3	X_0Y_3				
C_{32}	C_{31}	C_{30}					
C_{33}	S_{33}	S_{32}	S_{31}	S_{30}			
P_7	P_6	P_5	P_4	P_3	P_2	P_1	P_0

Multiplicand
 Multiplier
 Partial product 0
 Partial product 1
 First row carries
 First row sums
 Partial product 2
 Second row carries
 Second row sums
 Partial product 3
 Third row carries
 Third row sums
 Final product

Array Multiplier

 

VHDL Simulation

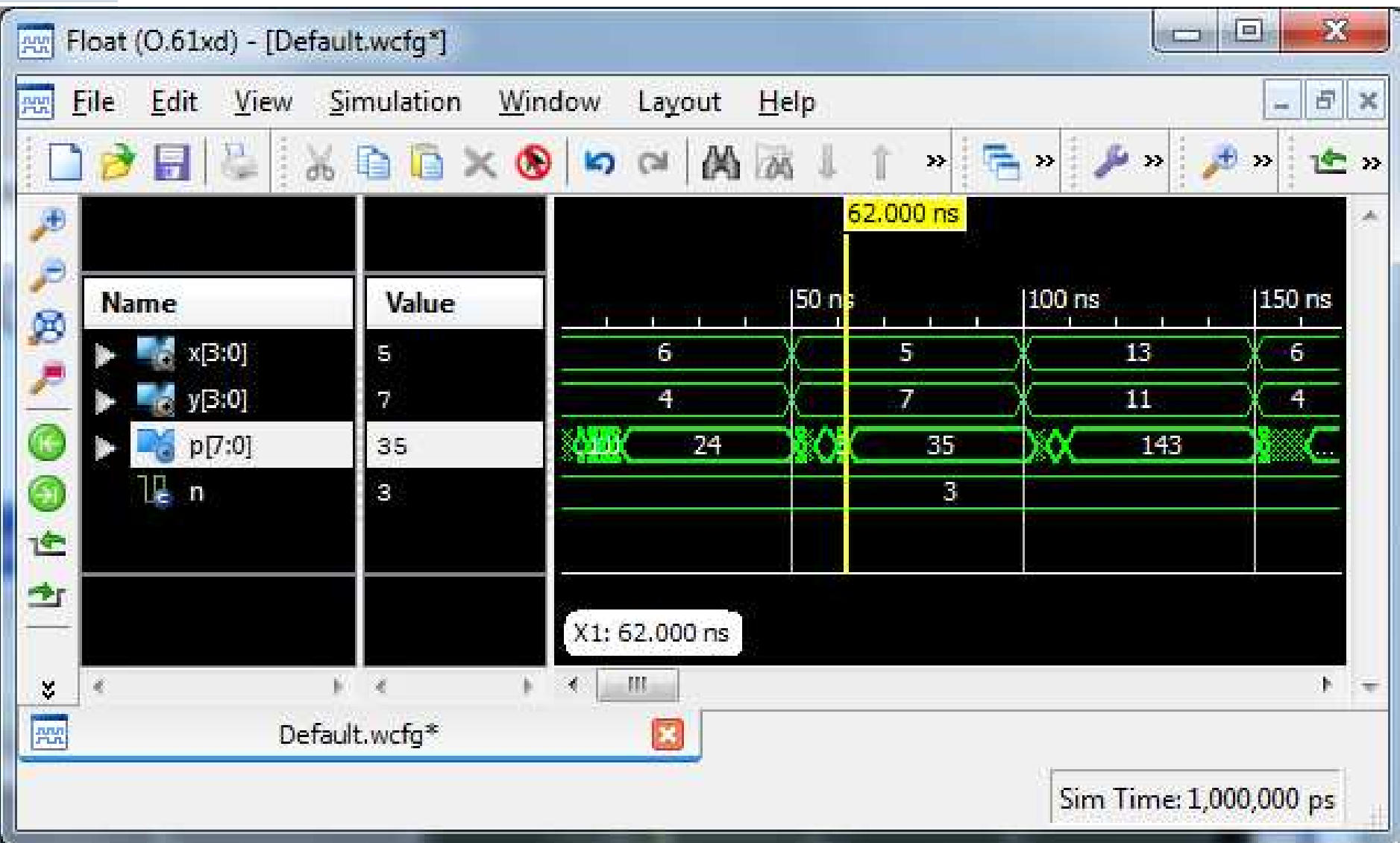

Hardware Requirements

- ♦ **n-bit Multiplication (2n-bit Product)**
 - n^2 And Gates
 - $(n-1)$ x n-bit Adders
- ♦ **16-bit Multiplication**
 - 256 And Gates
 - 15 x 16-bit Adders
- ♦ **32-bit Multiplication**
 - 1024 And Gates
 - 31 x 32-bit Adders

Signed Multiplication

- ♦ Signed Binary Fractions

- 2's Complement

- S.XXX

- $\pm . 1/2 \ 1/4 \ 1/8$

- ♦ Four Cases


- + +

- - +


- + -

- - -


2's Complement Multiplier

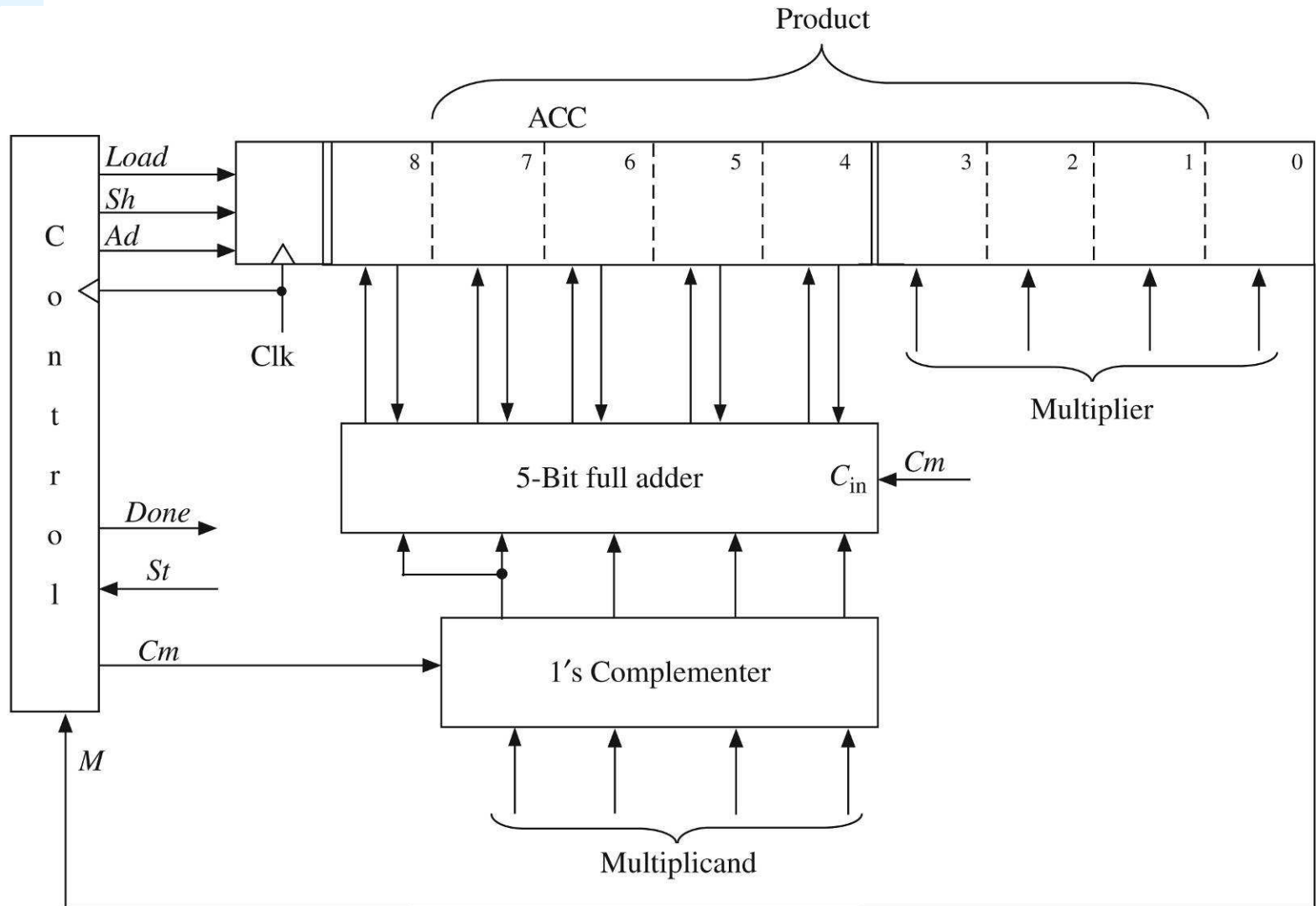


Multiplier Control

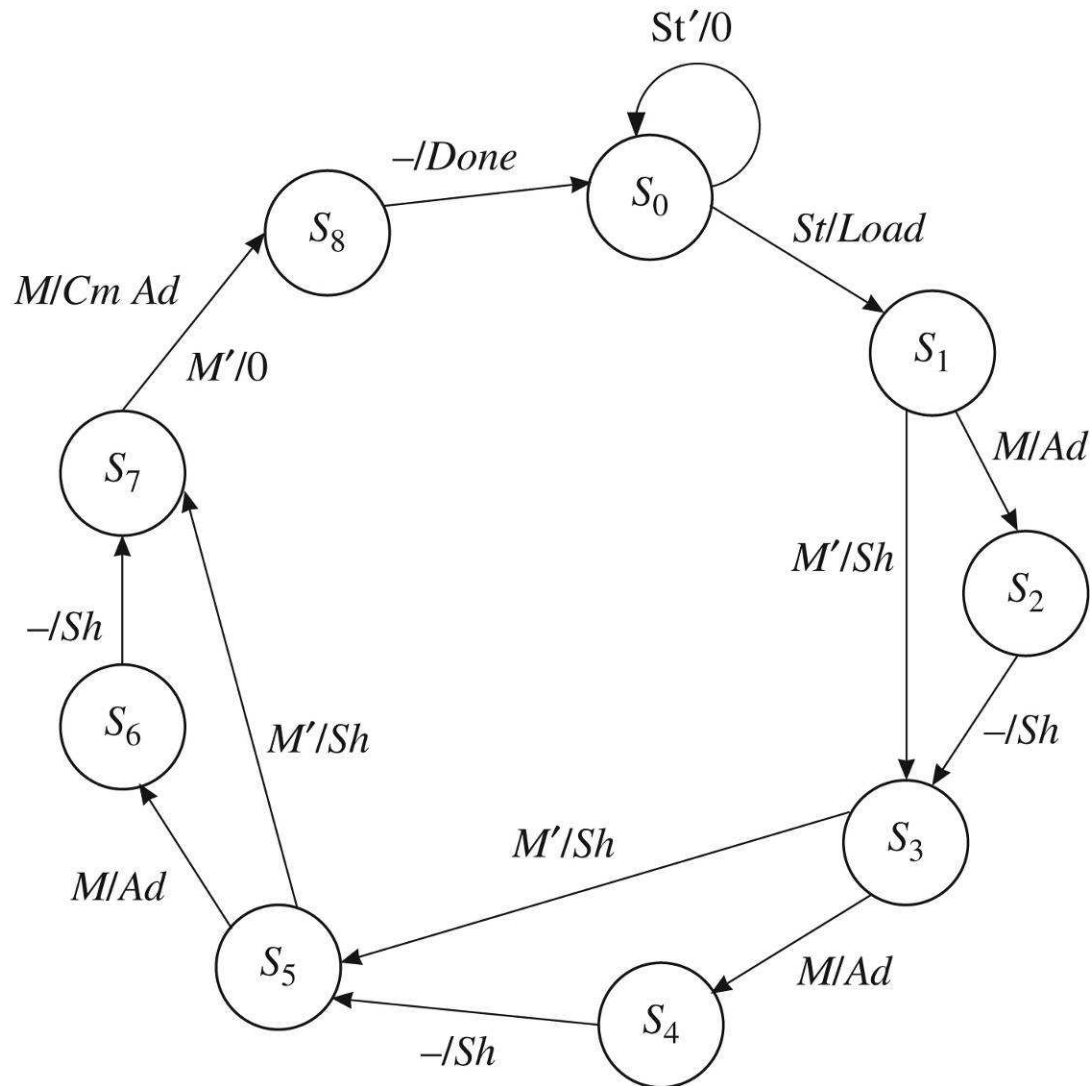

Faster Multiplier

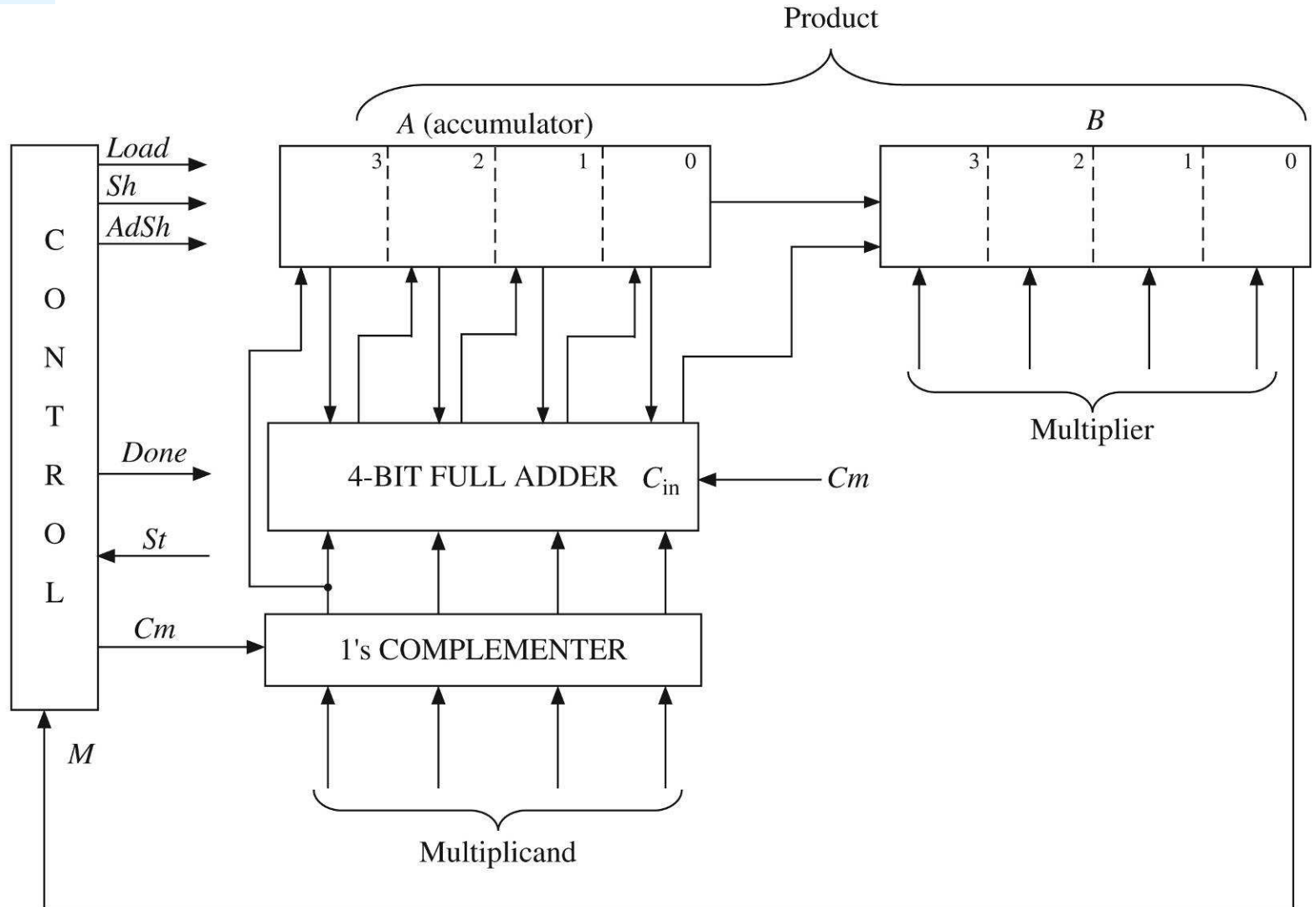

Multiplier Control

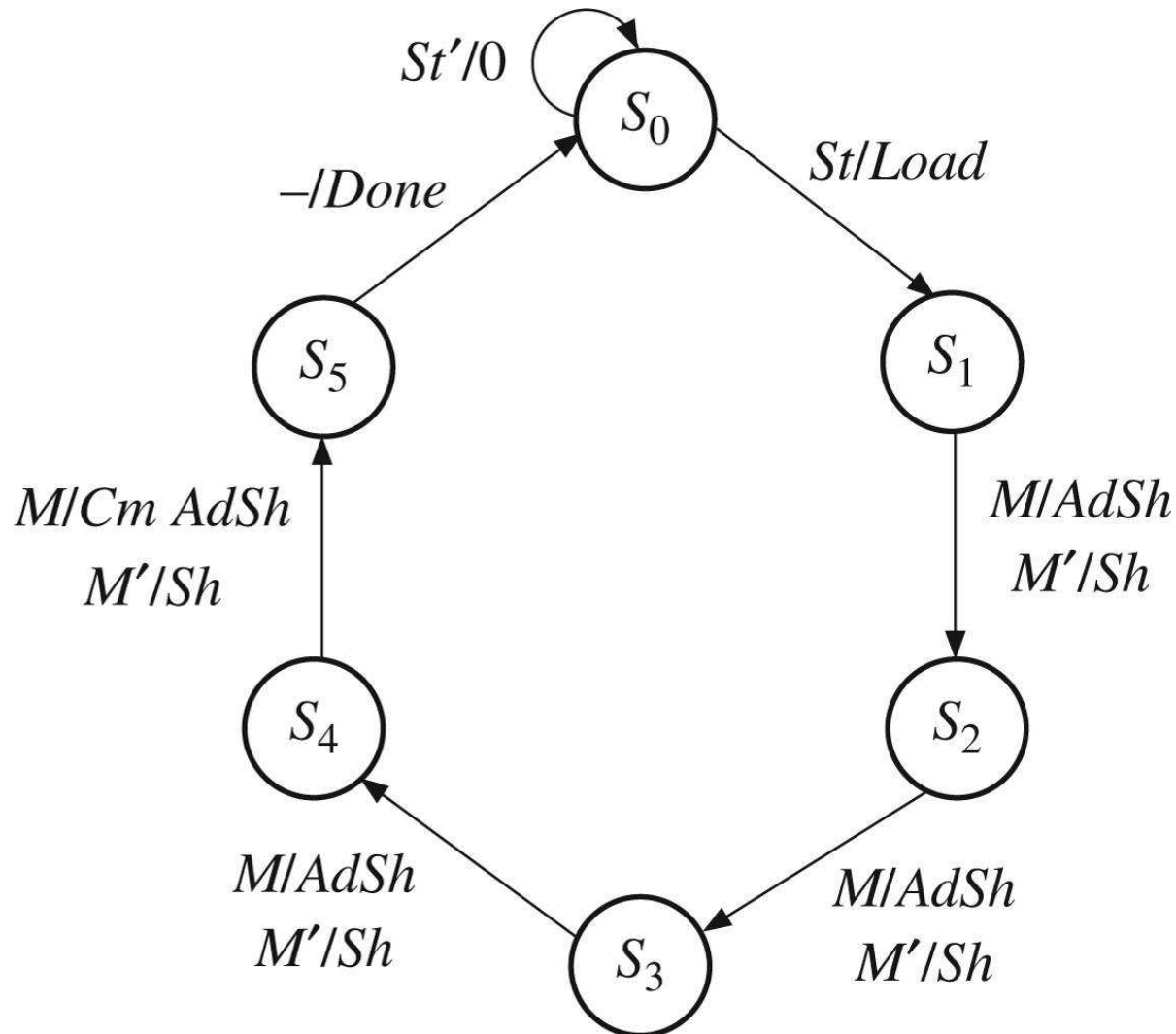

Behavioral Model

```
-- This VHDL model explicitly defines control signals
```

```
library IEEE;
```

```
use IEEE.std_logic_1164.all;
```

```
use IEEE.std_logic_unsigned.all;
```

```
entity Mult2C is
```

```
    port(CLK, St: in std_logic;
```

```
          Mplier, Mcand: in std_logic_vector(3 downto 0);
```

```
          Product: out std_logic_vector (6 downto 0);
```

```
          Done: out std_logic);
```

```
end Mult2C;
```

Behavioral Model

```
architecture Behave2 of Mult2C is
    signal State, Nextstate: integer range 0 to 5;
    signal A, B, compout, addout:
        std_logic_vector(3 downto 0);
    signal AdSh, Sh, Load, Cm: std_logic;
    alias M: std_logic is B(0);
begin
    process(State, St, M)
    begin
        Load <= '0';
        AdSh <= '0';
        Sh <= '0';
        Cm <= '0';
        Done <= '0';
```

Behavioral Model

```
case State is
  when 0 =>
    if St = '1' then
      Load <= '1';
      Nextstate <= 1;
    else
      Nextstate <= 0;
    end if;
  when 1 | 2 | 3 => -- "add/shift" State
    if M = '1' then
      AdSh <= '1';
    else
      Sh <= '1';
    end if;
  Nextstate <= State + 1;
```

Behavioral Model

```
when 4 =>                                -- add complement if sign
    if M = '1' then
        Cm <= '1';
        AdSh <= '1';
    else
        Sh <= '1';
    end if;
    Nextstate <= 5;
when 5 =>
    Done <= '1';
    Nextstate <= 0;
end case;
end process;
```

Behavioral Model


```
compout <= not Mcand when Cm = '1' else Mcand;  
addout <= A + compout + Cm;
```

```
process (CLK)  
begin  
    if rising_edge (CLK) then  
        if Load = '1' then  
            A <= "0000";  
            B <= Mplier;  
        end if;  
        if AdSh = '1' then  
            A <= compout(3) & addout(3 downto 1);  
            B <= addout(0) & B(3 downto 1);  
        end if;  
    end if;  
end process;
```

Behavioral Model

```
    if Sh = '1' then
        A <= A(3) & A(3 downto 1);
        B <= A(0) & B(3 downto 1);
    end if;
    State <= Nextstate;
end if;
end process;
Product <= A(2 downto 0) & B;
end ehav2;
```

Test Bench

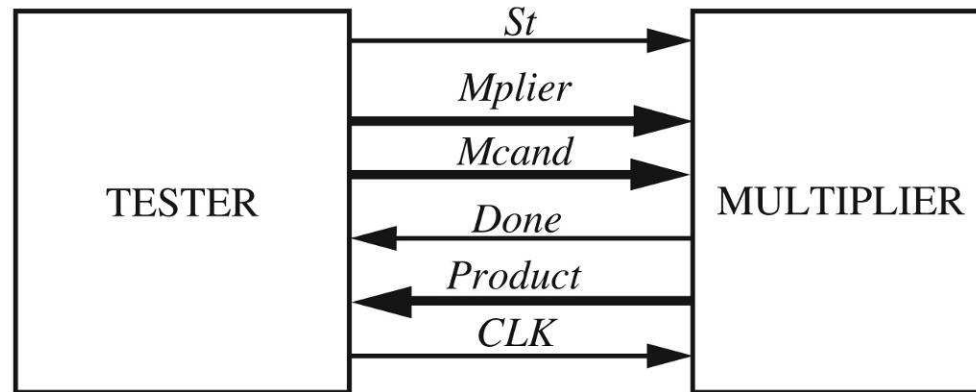


```
constant Mcandarr: arr :=  
  ( "0100", "1100", "1100", "0010", "0010");  
constant Mplierarr: arr :=  
  ( "0110", "0110", "1010", "0101", "1011");  
constant Productarr: arr2 :=  
  ("0011000", 1101000, "0011000", "0001010", "1110110");
```


Test Bench

```
stim_proc: process
begin
  for i in 1 to N loop
    Mcand <= Mcandarr(i);
    Mplier <= Mplierarr(i);
    St <= '1';
    wait until rising_edge(CLK);
    St <= '0';
    wait until falling_edge(Done);
    assert Product = Productarr(i)
      report "Incorrect Product"
      severity error;
  end loop;
  report "TEST COMPLETED";
end process;
```

VHDL Simulation

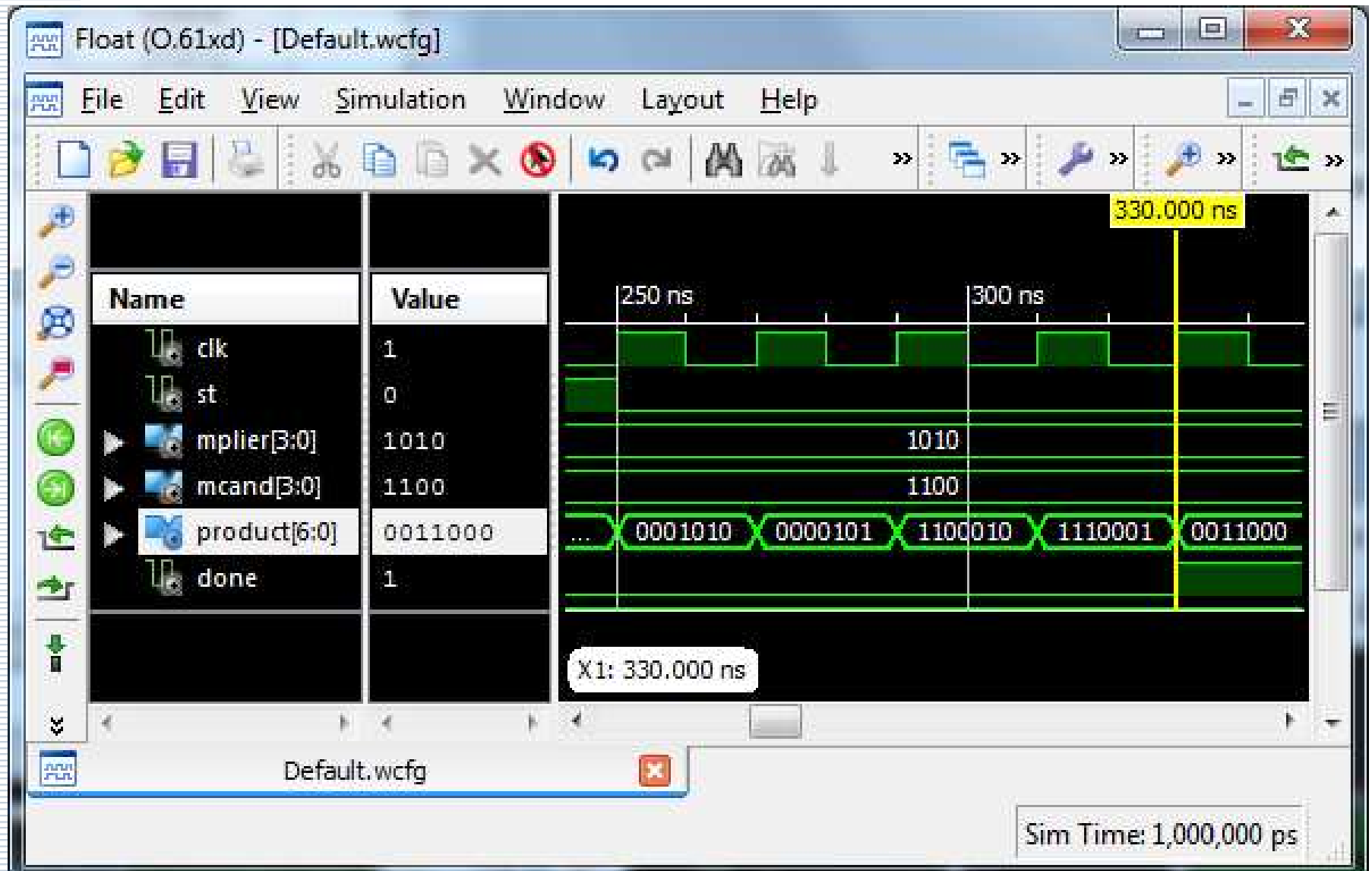

FPGA Implementation

- ♦ **Xilinx Spartan3e**
 - 250K System Gates
 - 50 MHz Clock
- ♦ **ChipScope Pro**
 - Virtual Input/Output Core (VIO)
 - Integrated Logic Analyzer (ILA)
- ♦ **Real-Time Verification**
 - Captures On-chip Signals
 - Off-chip Analysis via JTAG Programming Cable

Summary

- ♦ **Design Examples**
 - BCD to 7-Segment Display
 - Adders
 - Multipliers
- ♦ **VHDL Models**
- ♦ **VHDL Test Benches**
- ♦ **FPGA Implementations**
 - ChipScope Pro