

# Microelectronics Circuit Analysis and Design

Donald A. Neamen

## Chapter 1

### *Semiconductor Materials and Devices*

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 1-1

In this chapter, we will:

- Gain a basic understanding of semiconductor material properties
  - Two types of charged carriers that exist in a semiconductor
  - Two mechanisms that generate currents in a semiconductor
- Determine the properties of a pn junction
  - Ideal current-voltage characteristics of a pn junction diode
- Examine dc analysis techniques for diode circuits using various models to describe the nonlinear diode characteristics
- Develop an equivalent circuit for a diode that is used when a small, time-varying signal is applied to a diode circuit

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 1-2

## Intrinsic Semiconductors


- Ideally 100% pure material
  - Elemental semiconductors
    - Silicon (Si)
      - Most common semiconductor used today
    - Germanium (Ge)
      - First semiconductor used in p-n diodes
  - Compound semiconductors
    - Gallium Arsenide (GaAs)

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 1-3

## Silicon (Si)

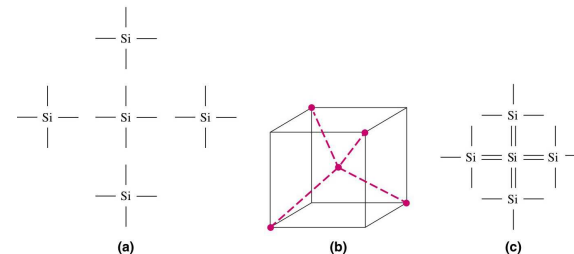

Covalent bonding of one Si atom with **four** other Si atoms to form tetrahedral unit cell.


Valence electrons available at edge of crystal to bond to additional Si atoms.

Neamen


Microelectronics, 4e  
McGraw-Hill

Chapter 1-4

## Effect of Temperature

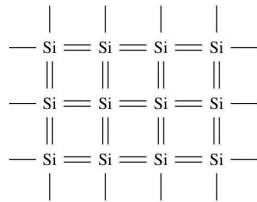

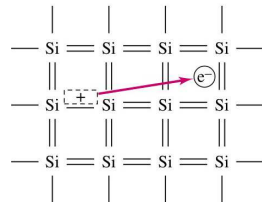At 0°K, no bonds are broken.  
Si is an **insulator**.



As temperature increases, a bond can break, releasing a valence electron and leaving a broken bond (hole).


Current can flow.

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 1-5

## Movement of Holes

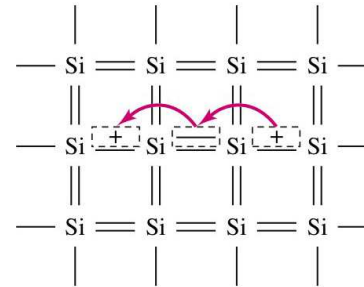

A valence electron in a nearby bond can move to fill the broken bond, making it appear as if the 'hole' shifted locations.

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 1-6

## Intrinsic Carrier Concentration

$$n_i = BT^{3/2} e^{\frac{-E_g}{2kT}}$$

B – coefficient related to specific semiconductor  
T – temperature in Kelvin  
 $E_g$  – semiconductor bandgap energy  
k – Boltzmann's constant

$$n_i(\text{Si}, 300\text{K}) = 1.5 \times 10^{10} \text{ cm}^{-3}$$

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 1-7

## Extrinsic Semiconductors


- Impurity atoms replace some of the atoms in crystal
  - Column V atoms in Si are called donor impurities.
  - Column III in Si atoms are called acceptor impurities.

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 1-8

## Phosphorous – Donor Impurity in Si

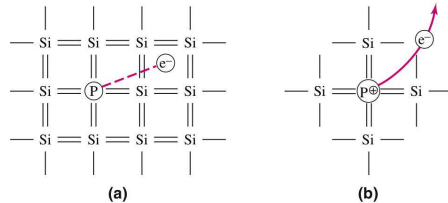

Phosphorous (P) replaces a Si atom and forms four covalent bonds with other Si atoms.


The **fifth** outer shell electron of P is easily **freed** to become a conduction band electron, adding to the number of electrons available to conduct current.

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 1-9

## Boron – Acceptor Impurity in Si

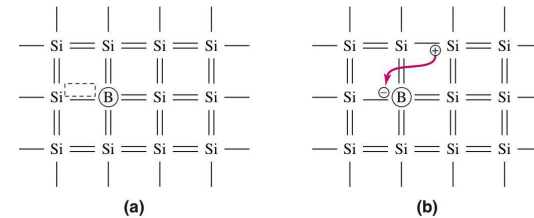

Boron (B) replaces a Si atom and forms only **three** covalent bonds with other Si atoms.

The missing covalent bond is a hole, which can begin to move through the crystal when a valence electron from another Si atom is taken to form the fourth B-Si bond.

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 1-10

## Electron and Hole Concentrations

$n_i$  = intrinsic carrier concentration (geo. Mean)

$n$  = electron concentration

$p$  = hole concentration

$$n_i^2 = n \cdot p$$

n-type:

$n = N_D$ , the donor concentration

$$p = n_i^2 / N_D$$

p-type:

$p = N_A$ , the acceptor concentration


$$n = n_i^2 / N_A$$

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 1-11

## Drift Currents

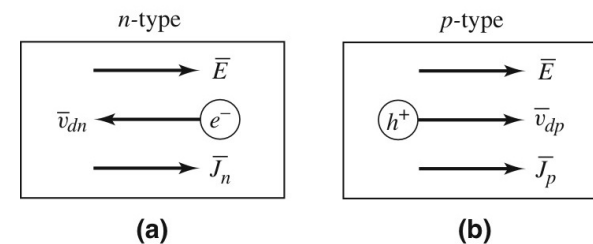

Electrons and hole flow in opposite directions when under the influence of an electric field at different velocities.


The drift currents associated with the electrons and holes are in the same direction.

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 1-12

## Diffusion Currents

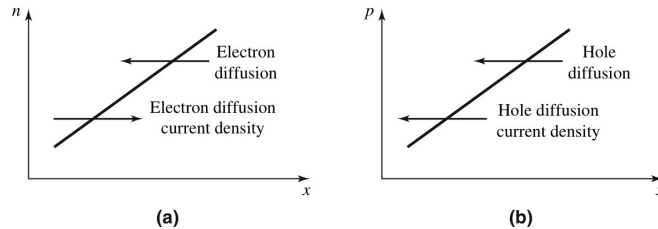

Both electrons and holes flow from high concentration to low.


The diffusion current associated with the electrons flows in the opposite direction when compared to that of the holes.

Neamen

Microelectronics, 4e  
McGraw-Hill


Chapter 1-13

## p-n Junctions

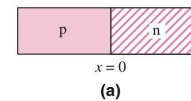

A simplified 1-D sketch of a p-n junction (a) has a doping profile (b).

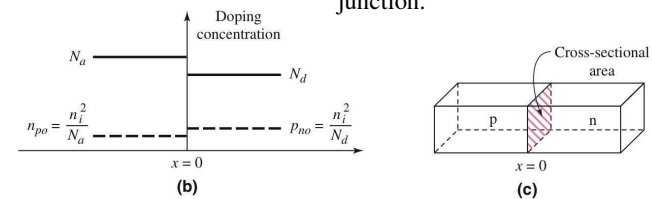The 3-D representation (c) shows the cross sectional area of the junction.




Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 1-14

## Built-in Potential

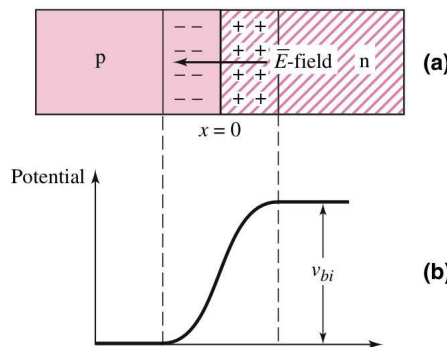

This movement of carriers creates a space charge or depletion region with an induced electric field near  $x = 0$ .

A potential voltage,  $V_{bi}$ , is developed across the junction.

Copyright © The McGraw-Hill Companies, Inc.  
Permission is granted for reproduction or display.

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 1-15

## Built-in Potential

$$V_{bi} = \frac{kT}{e} \ln \left[ \frac{N_a N_d}{n_i^2} \right] = V_T \ln \left[ \frac{N_a N_d}{n_i^2} \right]$$


- $V_T = \frac{kT}{e} = \text{thermal voltage} = 0.026 \text{ V}$
- $k$  = Boltzman's constant
- $T$  = absolute temperature
- $e$  = electric charge magnitude
- $N_a$  = acceptor concentration
- $N_d$  = donor concentration
- $n_i$  = intrinsic carrier concentration

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 1-16

### Reverse Bias

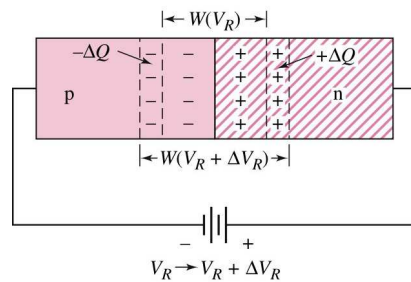

Increase in space-charge width,  $W$ , as  $V_R$  increases to  $V_R + \Delta V_R$ .


Creation of more fixed charges ( $-\Delta Q$  and  $+\Delta Q$ ) leads to junction capacitance.

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 1-17

### Forward Biased p-n Junction

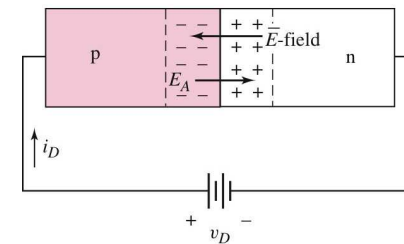


Applied voltage,  $v_D$ , induces an electric field,  $E_A$ , in the opposite direction as the original space-charge electric field, resulting in a smaller net electric field and smaller barrier between n and p regions.

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 1-18

### Circuit Symbol

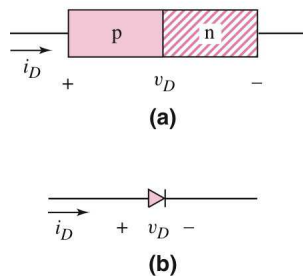


Conventional current direction and polarity of voltage drop is shown

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 1-19
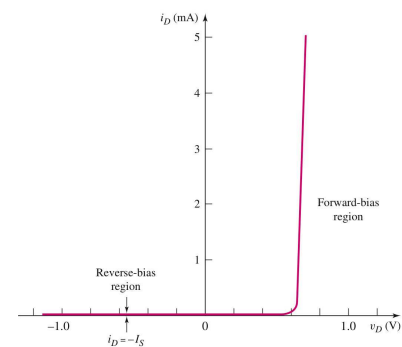
### Ideal Current-Voltage (I-V) Characteristics



The p-n junction only conducts significant current in the forward-bias region.

$i_D$  is an exponential function in this region.

Essentially no current flows in reverse bias.

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 1-20

## Ideal Diode Equation

A fit to the I-V characteristics of a diode yields the following equation, known as the ideal diode equation:

$$I_D = I_s (e^{\frac{qv_D}{kT}} - 1)$$

$kT/q$  is also known as the thermal voltage,  $V_T$ .

$V_T = 25.9$  mV when  $T = 300$ K, room temperature.


$$I_D = I_s (e^{\frac{v_D}{V_T}} - 1)$$

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 1-21

## Breakdown Voltage

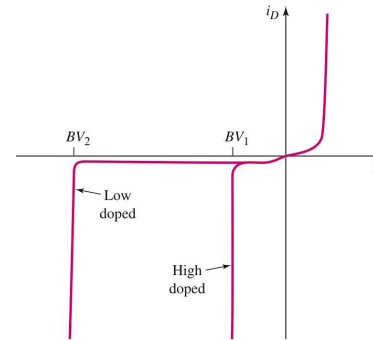

The magnitude of the breakdown voltage (BV) is smaller for heavily doped diodes as compared to more lightly doped diodes.


Current through a diode increases rapidly once breakdown has occurred.

Neamen


Microelectronics, 4e  
McGraw-Hill

Chapter 1-22

## dc Model of Ideal Diode

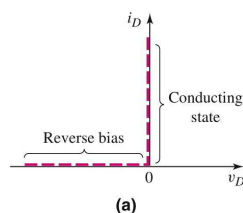

### Equivalent Circuits

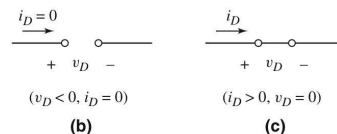

Assumes  $v_{bi} = 0$ .

No current flows when reverse biased (b).


No internal resistance to limit current when forward biased (c).

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 1-23

## Half-Wave Diode Rectifier

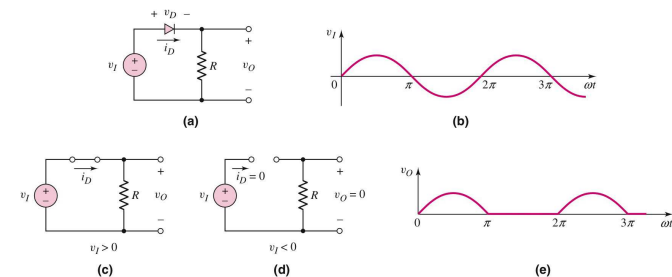


Diode only allows current to flow through the resistor when  $v_i \geq 0$ V. Forward-bias equivalent circuit is used to determine  $v_o$  under this condition.

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 1-24

## Graphical Analysis Technique

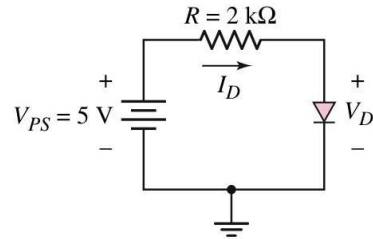


Simple diode circuit where  $I_D$  and  $V_D$  are not known.

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 1-25

## Load Line Analysis

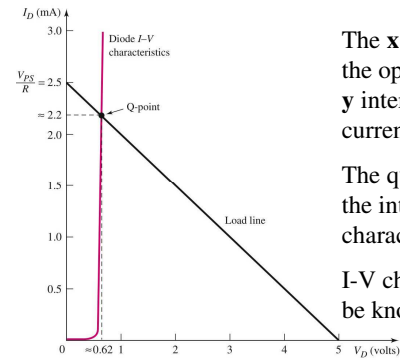

The x intercept of the load line is the open circuit voltage and the y intercept is the short circuit current.

The quiescent point or Q-point is the intersection of diode I-V characteristic with the load line.


I-V characteristics of diode must be known.

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 1-26

## Piecewise Linear Model

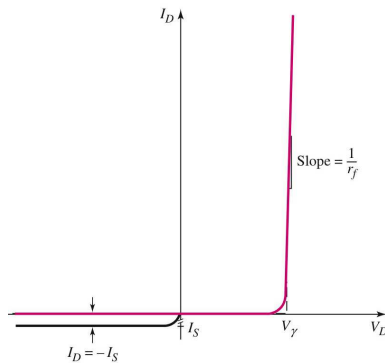


Two linear approximations are used to form piecewise linear model of diode.

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 1-27

## Diode Piecewise Equivalent Circuit

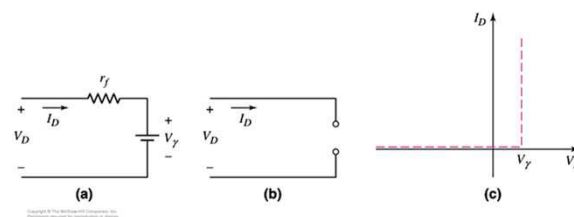

The diode is replaced by a battery with voltage,  $V_\gamma$ , with a resistor,  $r_f$ , in series when in the 'on' condition (a) and is replaced by an open when in the 'off' condition,  $V_D < V_\gamma$ .


If  $r_f = 0$ ,  $V_D = V_\gamma$  when the diode is conducting.

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 1-28

## Q-point

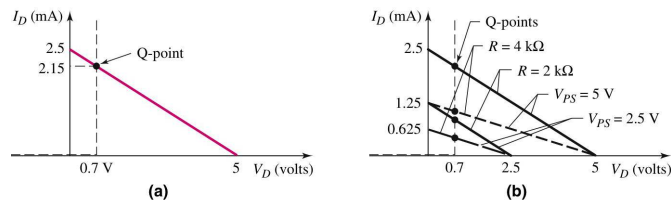

The x intercept of the load line is the open circuit voltage and the y intercept is the short circuit current.


The Q-point is dependent on the power supply voltage and the resistance of the rest of the circuit as well as on the diode I-V characteristics.

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 1-29

## ac Circuit Analysis

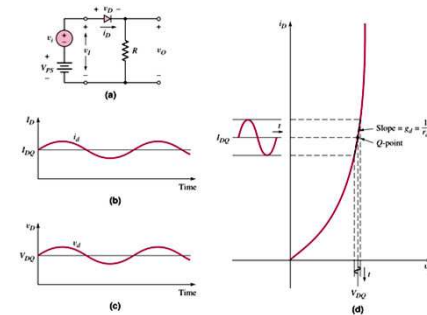

Combination of dc and sinusoidal input voltages modulate the operation of the diode about the Q-point.

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 1-30

## ac Circuit Analysis

$$v_D = V_D + v_d$$

$$i_D = I_S \left( e^{\frac{v_D}{V_T}} - 1 \right) \cong I_S \left( e^{\frac{v_D}{V_T}} \right) = I_S \left( e^{\frac{V_D}{V_T}} \right) \left( e^{\frac{v_d}{V_T}} \right)$$

For small signals when  $v_d \ll V_T$

$$e^{v_d/V_T} \cong 1 + v_d/V_T$$

$$\text{Then } I_S \left( e^{\frac{V_D}{V_T}} \right) \left( 1 + v_d/V_T \right) = I_D \left( 1 + v_d/V_T \right) = I_{DQ} + i_d$$


$$I_{DQ} \cong I_S \left( e^{\frac{V_D}{V_T}} \right) \quad \text{and} \quad i_d \cong \left( \frac{I_{DQ}}{V_T} \right) v_d$$

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 1-31

## ac Circuit Analysis

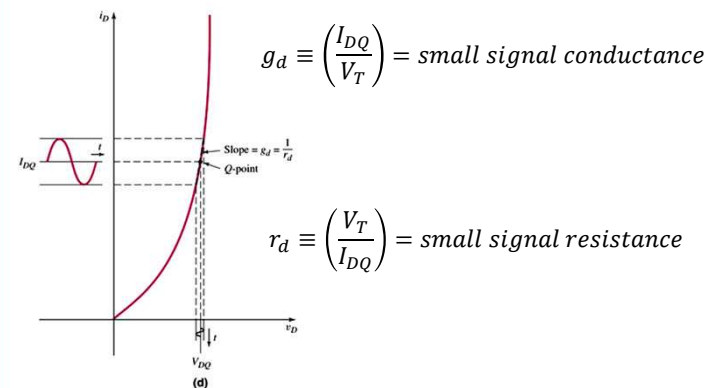



Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 1-32



## Zener Diode I-V Characteristics

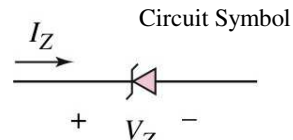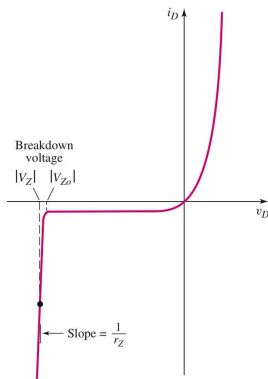

Usually operated in reverse bias region near the breakdown or Zener voltage,  $V_Z$ .


Note the convention for current and polarity of voltage drop.

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 1-33

## Example Zener Diode

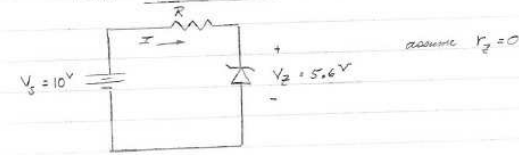

Find  $R$  to limit  $I < 3\text{mA}$

$$I = \frac{V_S - V_Z}{R} \Rightarrow R = \frac{10 - 5.6}{3\text{mA}} = 1.47\text{k}\Omega$$


The output voltage will remain at  $5.6\text{V}$  even if the current or power supply voltage change over time.

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 1-34

## Photogenerated Current

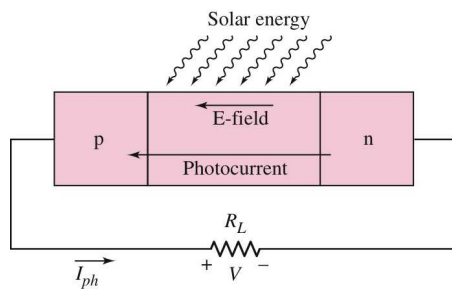


When the energy of the photons is greater than  $E_g$ , the photon's energy can be used to break covalent bonds and generate an equal number of electrons and holes to the number of photons absorbed.

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 1-35

## Optical Transmission System

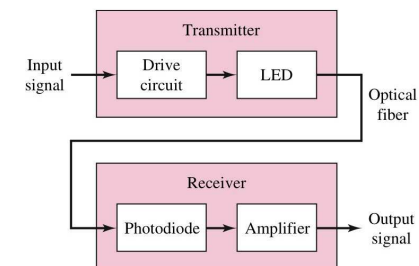


LED (**L**ight **E**mitting **D**iode) and photodiode are p-n junctions.

Neamen


Microelectronics, 4e  
McGraw-Hill

Chapter 1-36

## Schottky Barrier Diode

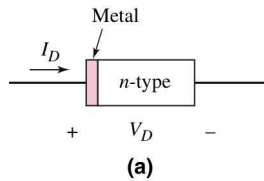

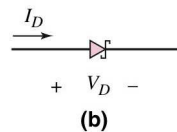A metal layer replaces the p region of the diode.



Circuit symbol showing conventional current direction of current and polarity of voltage drop.

Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display


Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 1-37

## Comparison of I-V Characteristics:

Forward Bias

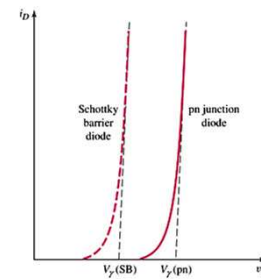


The built-in voltage of the Schottky barrier diode,  $V_g(\text{SB})$ , is about  $\frac{1}{2}$  as large as the built-in voltage of the p-n junction diode,  $V_g(\text{pn})$ .

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 1-38

Ex. Schottky Diode

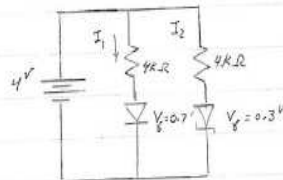

\* let  $r_f = 0$ .

$$I_1 = \frac{4 - 0.7}{4} = 0.825 \text{ mA}$$

$$I_2 = \frac{4 - 0.3}{4} = 0.925 \text{ mA}$$

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 1-39