

ELEC-313  
Lab 3: Diode Circuits

September 29, 2013

Date Performed: September 25, 2013  
Partners: Charles Pittman  
Stephen Wilson

## Contents

<b>1</b>	<b>Objective</b>	<b>3</b>
<b>2</b>	<b>Equipment</b>	<b>3</b>
<b>3</b>	<b>Schematics</b>	<b>3</b>
<b>4</b>	<b>Procedure</b>	<b>3</b>
4.1	Rectifier . . . . .	3
4.2	Voltage Regulator . . . . .	5
<b>5</b>	<b>Results</b>	<b>5</b>
<b>6</b>	<b>Conclusion</b>	<b>5</b>
<b>7</b>	<b>Equations</b>	<b>5</b>

## List of Figures

1	Circuits used in this lab. . . . .	3
2	AC input vs. DC output of circuit, where $R_L = 10\text{ k}\Omega$ . . . . .	4

## List of Tables

1	AC input vs. DC output of rectifier circuit, where $R_L = 10\text{ k}\Omega$ . . . . .	3
2	Effect of $R_L$ on DC output . . . . .	4
3	. . . . .	4

## 1 Objective

The objective is to observe the basic operation of a diode. In addition, the Shockley equation (Eq 2) is used to find the diode's reverse saturation current ( $I_S$ ) and thermal voltage ( $V_T$ ) using values measured in the lab.

## 2 Equipment

Diode: 1N4007

Zener diode: 1N5231

Resistors:  $47\Omega$

Capacitor:  $1\mu\text{F}$

Resistive decade box: HeathKit IN-3117

Power supply: HP E3631A

Function generator: HP 33120A

Multimeter: Fluke 8010A

Oscilloscope: Agilent 54622D

## 3 Schematics

(a) Circuit used for Parts A and Part B.

(b) Circuit used for Part C.

Figure 1: Circuits used in this lab.

## 4 Procedure

### 4.1 Rectifier

$V_S$ (V)	$V_{max}$ (V)	$V_{min}$ (V)	$V_r$ (V)	$V_{DC}$ (V)	% Ripple
1	0.488	0.369	0.119	0.429	24.4
2	1.41	1.10	0.310	1.26	22.0
3	2.39	1.88	0.510	2.14	21.3
4	3.31	2.38	0.930	2.85	28.1
5	4.25	3.19	1.06	3.72	24.9

Table 1: AC input vs. DC output of rectifier circuit, where  $R_L = 10\text{ k}\Omega$

$R_L$ k $\Omega$	$V_{max}$ V	$V_{min}$ V	$V_r$ V	$V_{DC}$	% Ripple
1	4.13	0.440	3.69	2.29	89.3%
10	4.25	3.19	1.06	3.72	24.9%
100	4.321	4.193	0.128	4.257	2.962%

Table 2: Effect of  $R_L$  on DC output

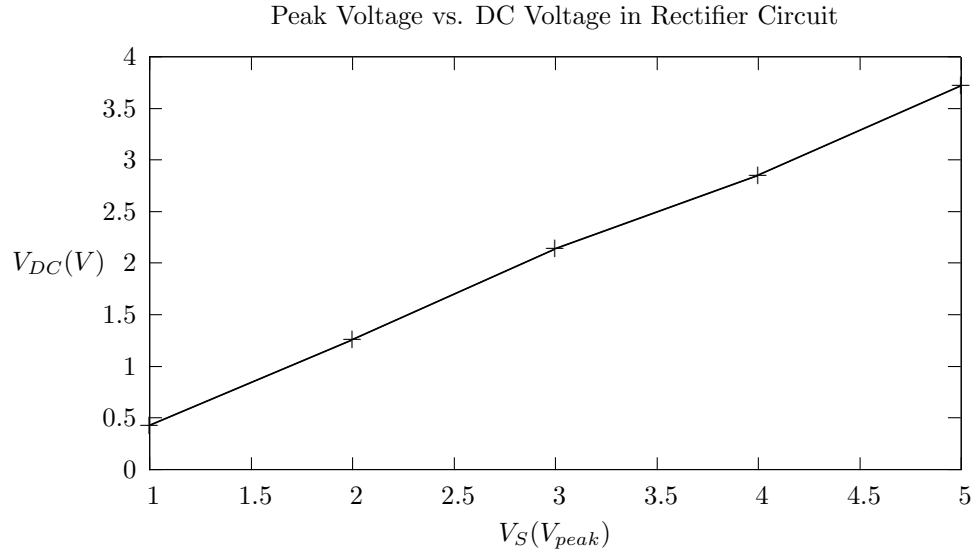


Figure 2: AC input vs. DC output of circuit, where  $R_L = 10\text{ k}\Omega$

			Measured			Calculated			
$R_L$	$V_L$	$I_L$	$V_{OC}$	$V_S(\text{Drop})$	Meas(V)	%reg(VL)	$V_{OC}(V)$	%diffVOC	VS(Drop)PSpice(V)
$\Omega$	V	mA	V	V			V		V
100	5.163	50.9	6.10		7.5	4.20%	6.12	0.359%	7.5
330	5.318	15.62	7.87		5.9	1.17%	7.88	0.102%	5.8
1000	5.11	5.27	8.60		5.3	5.28%	8.90	3.327%	5.3
No Load	(inf)	5.38							

Table 3

## 4.2 Voltage Regulator

## 5 Results

## 6 Conclusion

## 7 Equations

$$\%_{diff} = \frac{|nominal - measured|}{nominal} 100\% \quad (1)$$

$$I_D = I_S \left( e^{\frac{V_D}{V_T}} - 1 \right) \quad (2)$$

$$m = \frac{\ln(I_2) - \ln(I_1)}{V_2 - V_1} = \frac{1}{V_T} \quad (3)$$