

Boolean Algebra (Continued)

ELEC 311


Digital Logic and Circuits

Dr. Ron Hayne

Images Courtesy of Cengage Learning



Exclusive-OR (XOR)

 

X	Y	$X \oplus Y$
0	0	0
0	1	1
1	0	1
1	1	0

$$X \oplus Y = X'Y + XY'$$

XOR Theorems


$$X \oplus 0 = X$$

$$X \oplus 1 = X'$$

$$X \oplus X = 0$$

$$X \oplus X' = 1$$


Equivalence

 

X	Y	$X \equiv Y$
0	0	1
0	1	0
1	0	0
1	1	1

$$(X \equiv Y) = XY + X'Y'$$

Equivalence (XNOR)

 

X	Y	$X \oplus Y$
0	0	0
0	1	1
1	0	1
1	1	0

X	Y	$X \equiv Y$
0	0	1
0	1	0
1	0	0
1	1	1


Project 1

- ◆ Combinational Circuit Analysis
 - Determine input/output relationship of function
 - Boolean Equation
 - Truth Table
 - Implement logic circuit with FPGA
 - Schematic capture design tools
 - Test circuit to verify operation
 - Project Report
- ◆ Teams of 2 persons

Xilinx ISE Design Suite

- ◆ Enter description of logic circuit
 - Schematic editor
 - VHDL
- ◆ Use a logic synthesizer to generate a netlist
- ◆ Use implementation tools to map logic gates and interconnections into the FPGA
- ◆ Generate a bitstream programming file
- ◆ Configure device
 - Download the bitstream to the FPGA chip

Schematic

 

or


VHDL Source Code

```
entity leddcd is
  port(
    d: in std_logic_vector(3 downto 0);
    s: out std_logic_vector(6 downto 0);
  );
end;


architecture leddcd_arch of leddcd is
begin
  s <= "1110111" when d="0000" else
       "0010010" when d="0001" else
       "1101101";
end leddcd_arch;
```

Synthesize

Netlist

 

Map, Place & Route

 


Generate Bitstream

Bitstream

```
101010010101100101
010110101010110101
010110100101101011
01010100010101010
101010101001101010
110110110101001010
110100101011001011
001011001010101001
010101101001101001
011001100010101010
101010100110010101
```

Download and Test



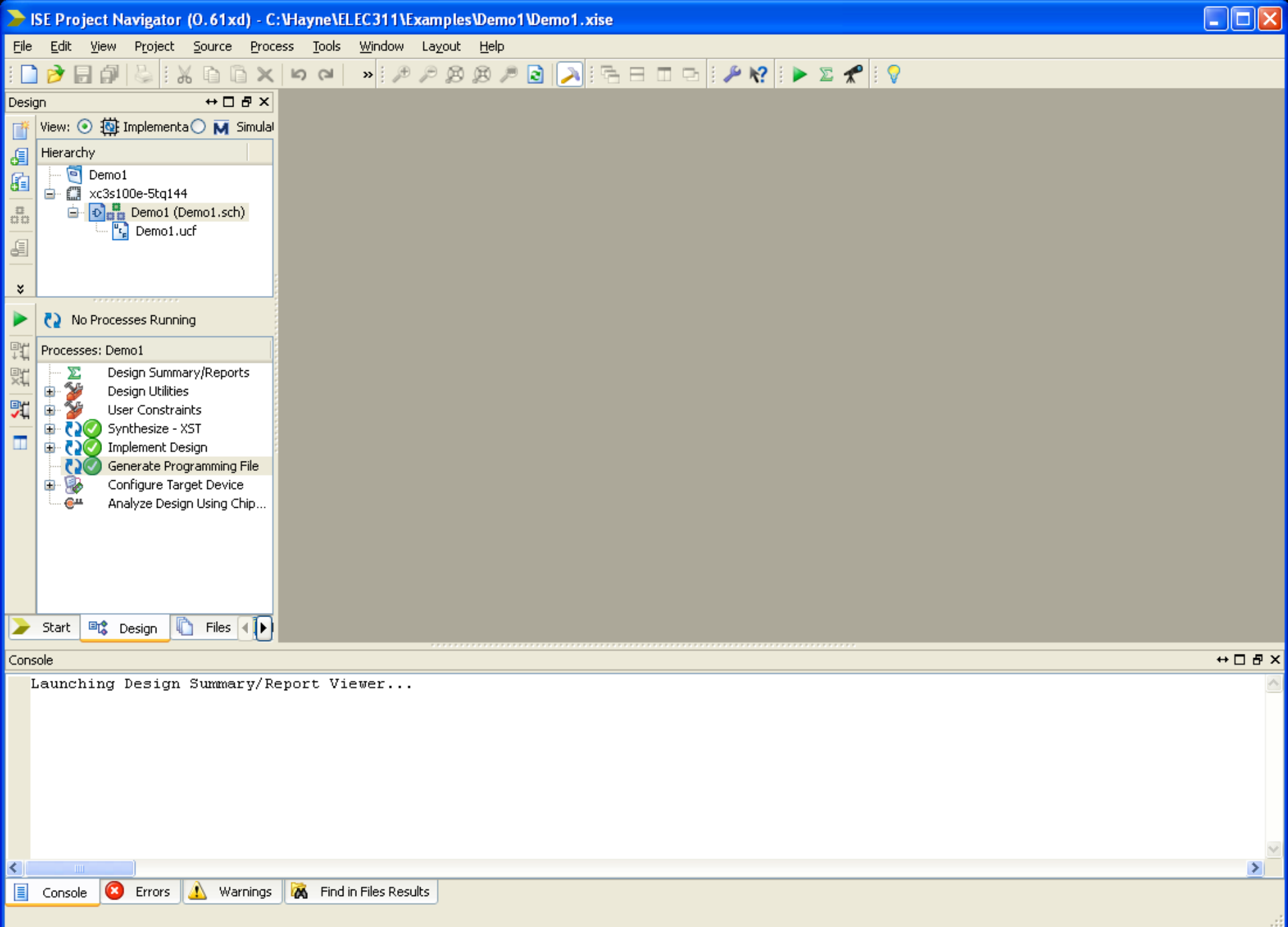

New Project

- ◆ File → New Project
 - Project Name
 - Demo1
 - Project Location
 - C:\xxx\xxx
 - Top-Level Module Type
 - Schematic
- Device Family
 - Spartan3E
- Device
 - XC3S100E
- Package
 - TQ144 (BASYS)
 - CP132 (BASYS 2)
- Speed Grade
 - -5

New Source

◆ Project → New Source

- Schematic
 - Demo1

◆ Schematic Editor

- Symbols
 - Category list
 - Symbol list
- Drawing area
- Tools
 - Add wire
 - Add I/O marker

ISE Project Navigator (0.61xd) - C:\Hayne\ELEC311\Examples\Demo1\Demo1.xise - [Demo1.sch*]

File Edit View Project Source Process Add Tools Window Layout Help

Symbols

Categories

- IO_Latch
- LUT
- Latch
- Logic
- Memory
- Mux
- Shift_Register
- Shifter

Symbols

- and12
- and16
- and2
- and2b1
- and2b2
- and3
- and3b1
- and3b2

Symbol Name Filter

Orientation

Rotate 0

Symbol Info

Files Libraries Symbols

Demo1.sch* Design Summary

Console

```
Running createsch...
Command Line: createsch -intstyle ise -family spartan3e C:/Hayne/ELEC311/Examples/Demo1/Demo1.sch

Process "Creating Schematic" completed successfully

Started : "Launching Schematic Editor to edit Demo1.sch".
Launching Design Summary/Report Viewer...
```

add wire

add I/O marker

X

Y

Z

AND2

AND3

INV

INV

OR2


XY

F

Demo1 Schematic

- ◆ Categories
 - Logic
- ◆ Symbols
 - and2
 - and3
 - inv
 - or2
- ◆ Add wires
 - Point to point
 - Stubs
- ◆ I/O Markers
 - Input marker
 - Output marker
 - Rename Port


FPGA

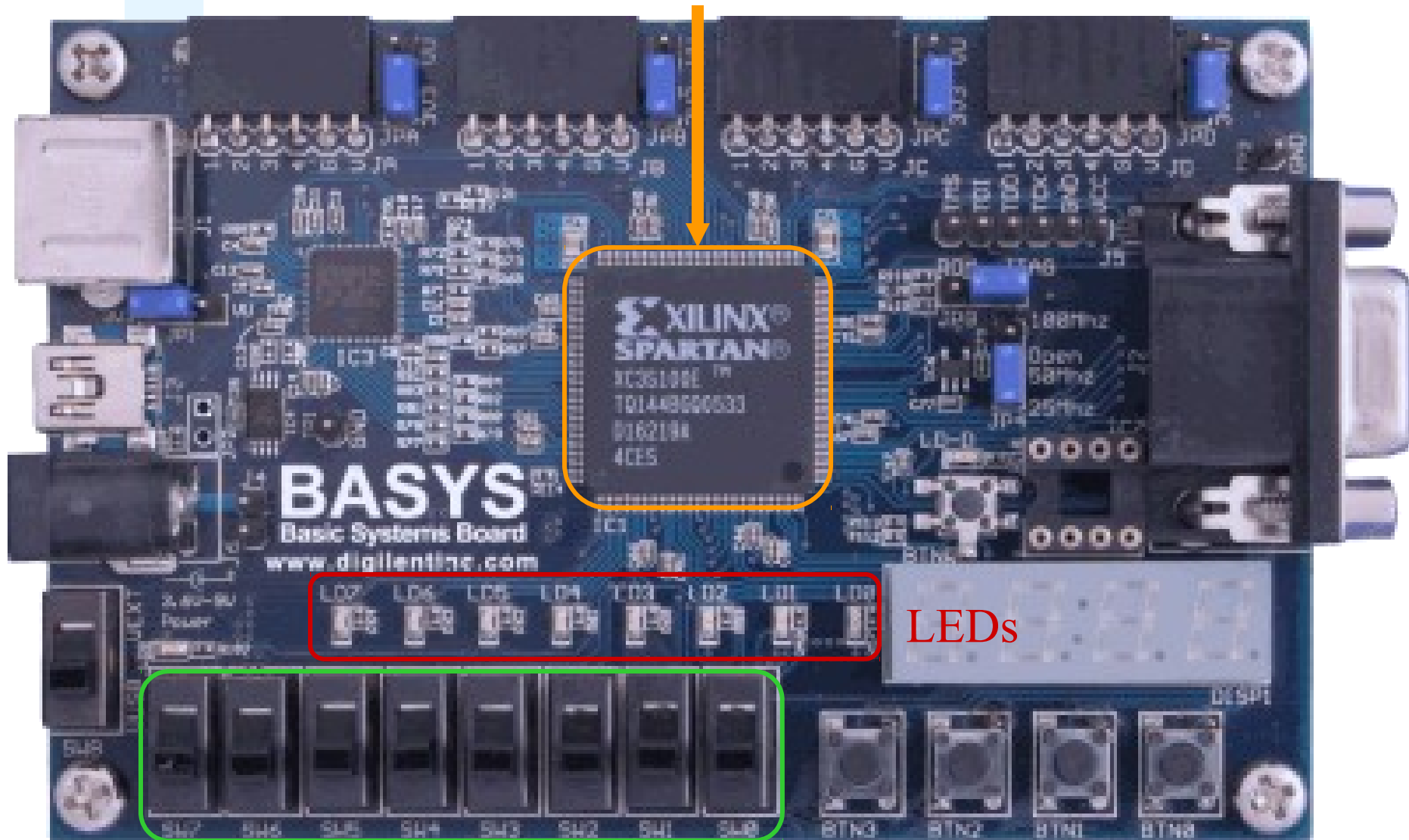

LEDs

Switches

FPGA Pins

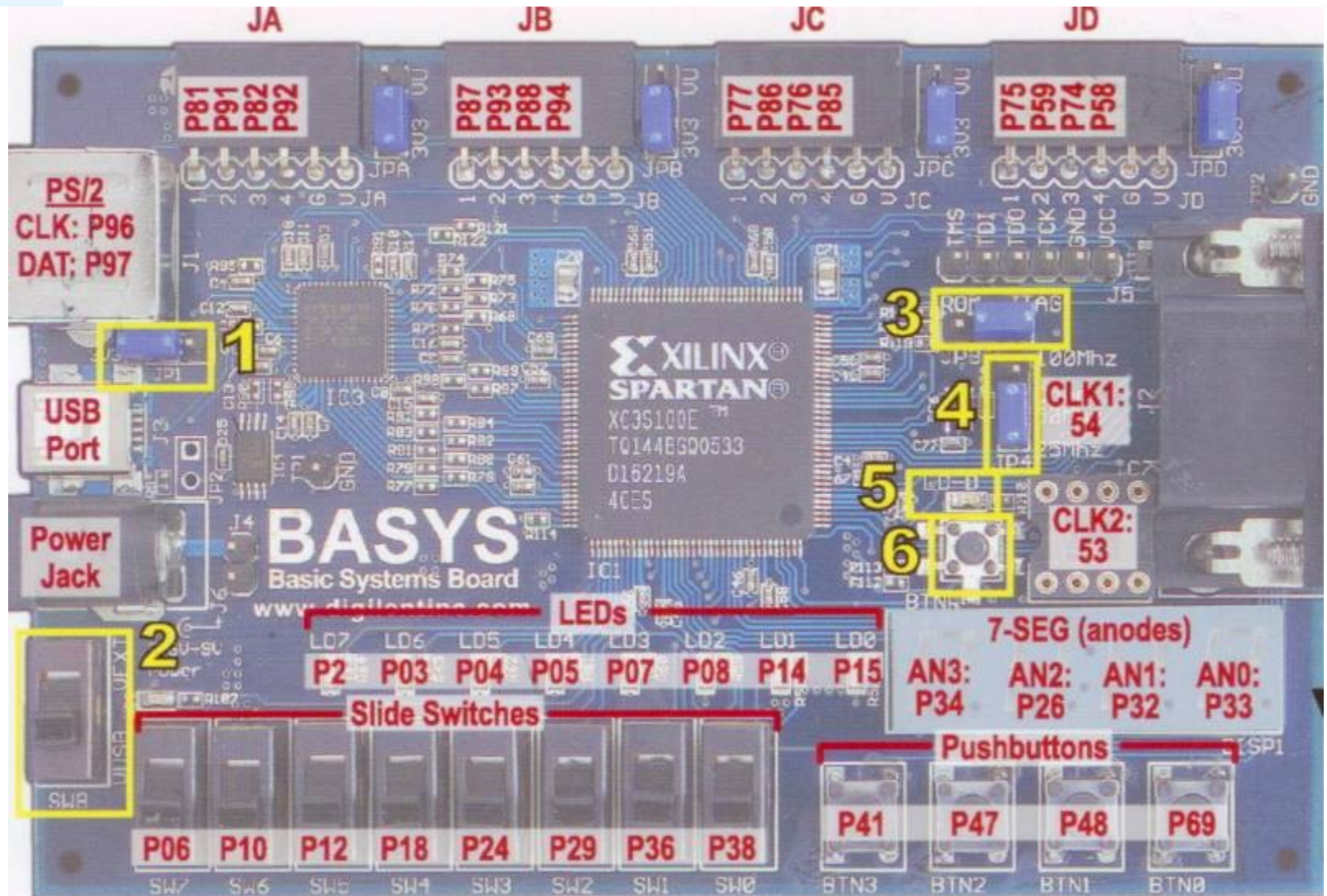

Constrain the Design

- ◆ User Constraints → I/O Pin Planning – Pre-Synthesis
 - Implementation Constraints File
 - Demol.ucf
 - PlanAhead
 - I/O Ports
 - Site

I/O Name	Location	BASYS	BASYS 2
X	SW2	P29	K3
Y	SW1	P36	L3
Z	SW0	P38	P11
XY	LD1	P14	M11
F	LD0	P15	M5

RTL Design - Demo1.ucf (target) * | xc3s100etq144-5

Sources



Search:

vh Demo1.vhf [work]
 Constraints (1)
 constrs_1
 Demo1.ucf

Sources RTL Netlist Timing Con..

I/O Port Properties




Z

Name: Z


General Configure

Properties Clock Regions

Package

 

Device

 


I/O Ports


Name	Dir	Neg Diff Pair	Site	Bank	I/O Std	Vcco	Vref	Drive Strength	Slew Type	Pull Type
All ports (5)										
Scalar ports (5)										
F	Output		P15	3	LVC MOS25	2.5		12 SLOW		
X	Input		P29	3	LVC MOS25	2.5		12 SLOW		
XY	Output		P14	3	LVC MOS25	2.5		12 SLOW		
Y	Input		P36	3	LVC MOS25	2.5		12 SLOW		
Z	Input		P38	2	LVC MOS25	2.5		12 SLOW		

Synthesize & Implement

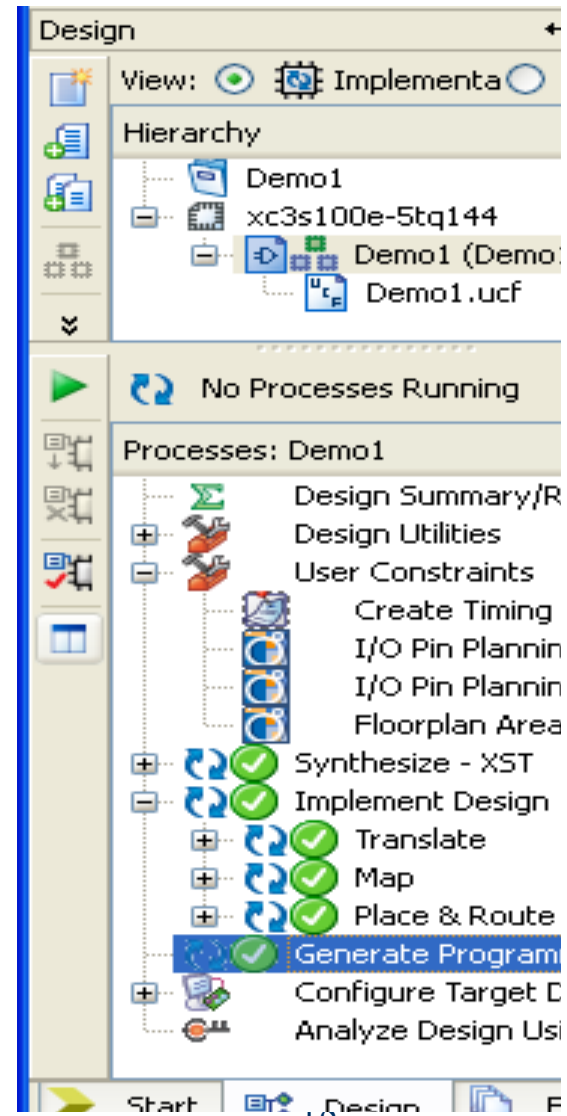- ◆ Synthesize Design
- ◆ Implement Design
- ◆ Generate Programming File



BASYS Configuration

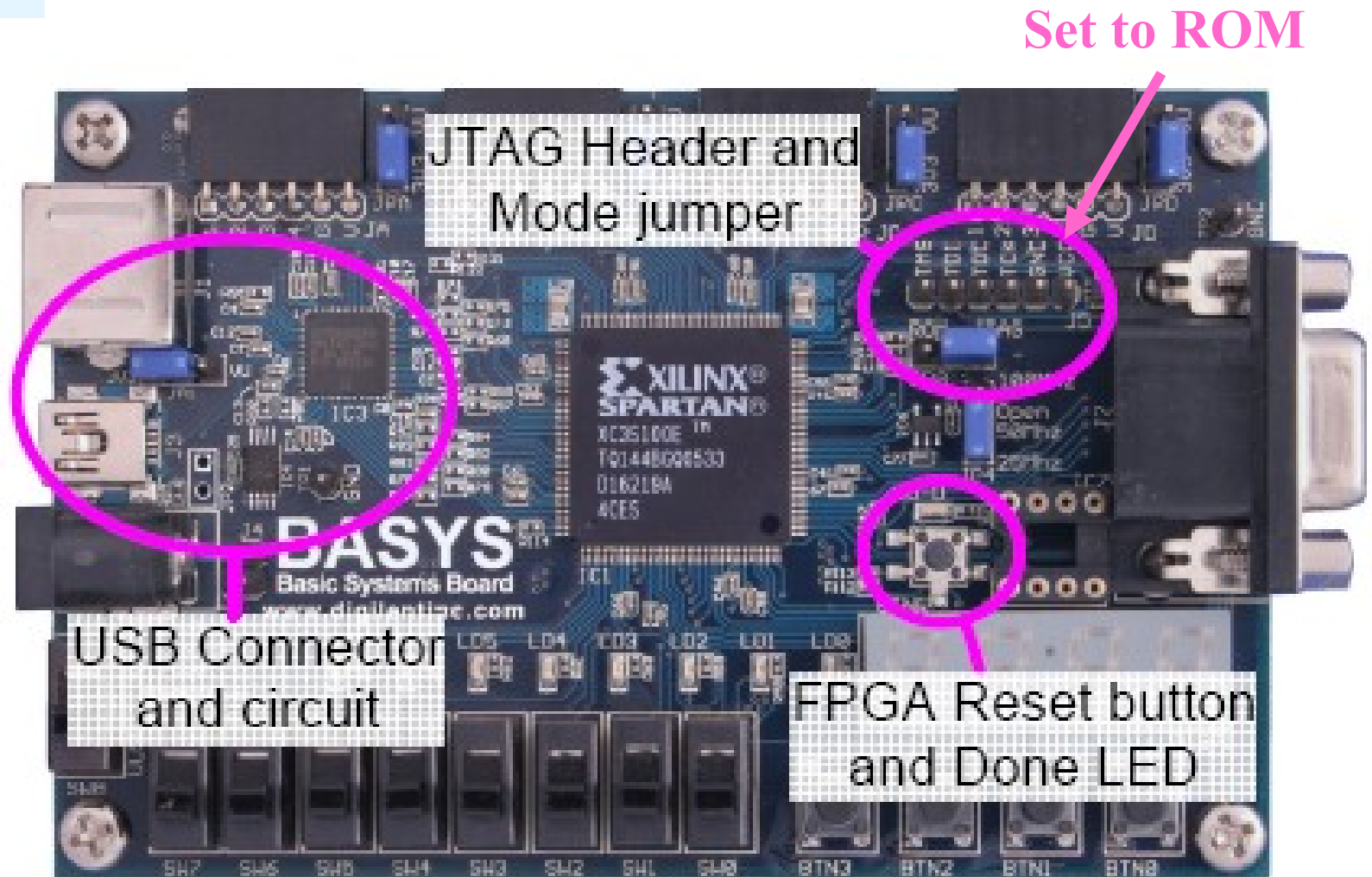

Configure Device

- ◆ Configure Device (Adept)
 - Initialize Chain
 - XCF02S (PROM)
 - demo1.bit
 - Program
 - Cycle Power (Reset)

BASYS

Connect: Onboard USB

Product: Basys - 100

Config

Test

Register I/O

File I/O

I/O Ex

Settings**FPGA**

XC3S100E

Browse...

Program

PROM

XCF02S

demo1.bit

Browse...

Program

Initialize Chain

Device 2: XCF02S

Set Config file for XCF02S: "C:\Hayne\ELEC311\Examples\Demo1\demo1.bit"

Preparing to program XCF02S...

Erasing device...

Programming...

Programming Successful.

Test the Design



Project Report

- ◆ Cover Sheet
 - Project Name/Number
 - Authors
 - Professor's Initials
- ◆ Objectives
- ◆ Discussion
 - Boolean Equation
 - Truth Table
 - Circuit Schematic
- ◆ Conclusion
 - Test Results