

ELEC-313
Lab 8: Bipolar Junction Transistor
Characterization

November 20, 2013

Date Performed: November 13, 2013
Partners: Charles Pittman
Stephen Wilson

Contents

| | | |
|---|------------|---|
| 1 | Objective | 3 |
| 2 | Equipment | 3 |
| 3 | Schematics | 3 |
| 4 | Procedure | 3 |
| 5 | Results | 4 |
| 6 | Conclusion | 8 |
| 7 | Equations | 8 |

List of Figures

| | | |
|---|---|---|
| 1 | Common-emitter transistor circuit | 3 |
| 2 | V_{CE} vs. I_C | 7 |
| 3 | V_{CE} vs. I_C , $V_{CE} > 0$ | 8 |

List of Tables

| | | |
|----|--|---|
| 1 | $I_B = 20 \mu\text{A}$ | 4 |
| 2 | $I_B = 50 \mu\text{A}$ | 5 |
| 3 | $I_B = 80 \mu\text{A}$ | 5 |
| 4 | $I_B = 100 \mu\text{A}$ | 6 |
| 5 | Average values of β per I_B | 6 |
| 6 | $V_{CE} = 5 \text{ V}$ | 6 |
| 7 | $V_{CE} = 10 \text{ V}$ | 6 |
| 8 | $V_{CE} = 15 \text{ V}$ | 7 |
| 9 | Average values of β per V_{CE} | 7 |
| 10 | h_{oe} vs. r_o | 7 |

1 Objective

The objective is to plot the output characteristic of a common-emitter transistor circuit, and use it to determine the current gain and output conductance.

2 Equipment

Transistor: 2N7000 Power supply: HP E3631A
Function generator: HP 33120 Multimeter: HP 34401A
Oscilloscope: Agilent 54622D Capacitors: 0.1 μF
Resistors: 100 Ω , 300 Ω , 470 Ω , 1 k Ω (x2) 33 k Ω , 100 k Ω (x2)

3 Schematics

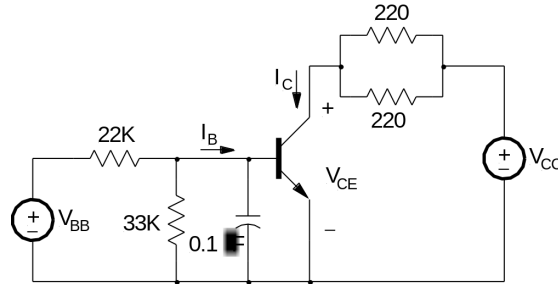


Figure 1: Common-emitter transistor circuit

4 Procedure

The following steps were observed to plot the output characteristic of a common emitter transistor circuit:

1. Construct the circuit of Figure 1. Use the +6 V power supply for V_{BB} and the +25 V supply for V_{CC} . Be sure to keep the connection distance between the capacitor and the transistor short. Use the HP multimeter to measure the base current (I_B) on the source side of the capacitor and Fluke multimeters to measure the collector voltage and current (V_{CE} and I_C).
2. Adjust V_{BB} so that base current (I_B) is 20 μA .
3. Adjust V_{CC} from 0.5 – 1.5 V in 0.25 V steps, then from 2 – 20 V in 2 V steps.

4. At each step measure the collector current, I_C , and the collector-to-emitter voltage, V_{CE} . If I_B has drifted, readjust V_{BB} before recording the values of I_C and V_{CE} .
5. Adjust V_{BB} for a base current of 50 μA , 80 μA , and 100 μA . Repeat steps 3 and 4 at each I_B value.

5 Results

| V_{CC} (V) | I_C (mA) | V_{CE} (V) | β |
|-----------------|---------------|-----------------|---------|
| 0.50 | 0.232 | 0.454 | 11.60 |
| 0.75 | 0.233 | 0.705 | 11.65 |
| 1.00 | 0.234 | 0.954 | 11.70 |
| 1.25 | 0.237 | 1.204 | 11.85 |
| 1.50 | 0.237 | 1.454 | 11.85 |
| 2 | 0.242 | 1.954 | 12.10 |
| 4 | 0.25 | 3.95 | 12.30 |
| 6 | 0.25 | 5.95 | 12.60 |
| 8 | 0.26 | 7.95 | 12.75 |
| 10 | 0.26 | 9.96 | 12.85 |
| 12 | 0.26 | 11.95 | 13.10 |
| 14 | 0.27 | 13.94 | 13.30 |
| 16 | 0.27 | 15.95 | 13.40 |
| 18 | 0.27 | 17.95 | 13.50 |
| 20 | 0.27 | 19.95 | 13.70 |

Table 1: $I_B = 20 \mu\text{A}$

| V_{CC} (V) | I_C (mA) | V_{CE} (V) | β |
|-----------------|---------------|-----------------|---------|
| 0.50 | 2.73 | 0.178 | 54.60 |
| 0.75 | 4.34 | 0.236 | 86.80 |
| 1.00 | 4.96 | 0.41 | 99.20 |
| 1.25 | 4.95 | 0.662 | 99.00 |
| 1.50 | 4.97 | 0.91 | 99.40 |
| 2 | 4.98 | 1.41 | 99.60 |
| 4 | 5.15 | 3.39 | 103.00 |
| 6 | 5.25 | 5.38 | 105.00 |
| 8 | 5.39 | 7.36 | 107.80 |
| 10 | 5.58 | 9.34 | 111.60 |
| 12 | 5.77 | 11.31 | 115.40 |
| 14 | 5.97 | 13.28 | 119.40 |
| 16 | 6.21 | 15.26 | 124.20 |
| 18 | 6.45 | 17.23 | 129.00 |
| 20 | 6.69 | 19.20 | 133.80 |

Table 2: $I_B = 50 \mu\text{A}$

| V_{CC} (V) | I_C (mA) | V_{CE} (V) | β |
|-----------------|---------------|-----------------|---------|
| 0.50 | 3.08 | 0.135 | 38.50 |
| 0.75 | 4.95 | 0.163 | 61.88 |
| 1.00 | 6.8 | 0.191 | 85.00 |
| 1.25 | 8.58 | 0.229 | 107.25 |
| 1.50 | 9.1 | 0.421 | 113.75 |
| 2 | 9.4 | 0.881 | 117.50 |
| 4 | 10.79 | 2.71 | 134.88 |
| 6 | 11.03 | 4.68 | 137.88 |
| 8 | 11.45 | 6.63 | 143.13 |
| 10 | 11.99 | 8.56 | 149.88 |
| 12 | 12.72 | 10.47 | 159.00 |
| 14 | 13.41 | 12.39 | 167.63 |
| 16 | 14.20 | 14.29 | 177.50 |
| 18 | 15.05 | 16.20 | 188.13 |
| 20 | 15.85 | 18.10 | 198.13 |

Table 3: $I_B = 80 \mu\text{A}$

| V_{CC} (V) | I_C (mA) | V_{CE} (V) | β |
|-----------------|---------------|-----------------|---------|
| 0.50 | 3.21 | 0.12 | 32.10 |
| 0.75 | 5.11 | 0.143 | 51.10 |
| 1.00 | 7.02 | 0.164 | 70.20 |
| 1.25 | 8.93 | 0.186 | 89.30 |
| 1.5 | 10.79 | 0.214 | 107.90 |
| 2 | 10.33 | 0.77 | 103.30 |
| 4 | 11.33 | 2.67 | 113.30 |
| 6 | 13.95 | 4.34 | 139.50 |
| 8 | 15.63 | 6.14 | 156.30 |
| 10 | 16.60 | 8.02 | 166.00 |
| 12 | 17.98 | 9.95 | 179.80 |
| 14 | 19.20 | 11.70 | 192.00 |
| 16 | 20.70 | 13.69 | 207.00 |
| 18 | 22.40 | 15.53 | 224.00 |
| 20 | 23.80 | 17.37 | 238.00 |

Table 4: $I_B = 100 \mu\text{A}$

| I_B (μA) | β_{avg} |
|-------------------------|---------------|
| 20 | 12.55 |
| 50 | 105.85 |
| 80 | 132.00 |
| 100 | 137.99 |

Table 5: Average values of β per I_B

| I_B (μA) | I_C (mA) | β |
|----------------------------|---------------|---------|
| 20 | 0.25 | 12.26 |
| 50 | 5.20 | 104.00 |
| 80 | 11.10 | 138.75 |
| 100 | 14.67 | 146.68 |

Table 6: $V_{CE} = 5 \text{ V}$

| I_B (μA) | I_C (mA) | β |
|----------------------------|---------------|---------|
| 20 | 0.26 | 12.97 |
| 50 | 5.64 | 112.84 |
| 80 | 12.47 | 155.88 |
| 100 | 18.00 | 180.00 |

Table 7: $V_{CE} = 10 \text{ V}$

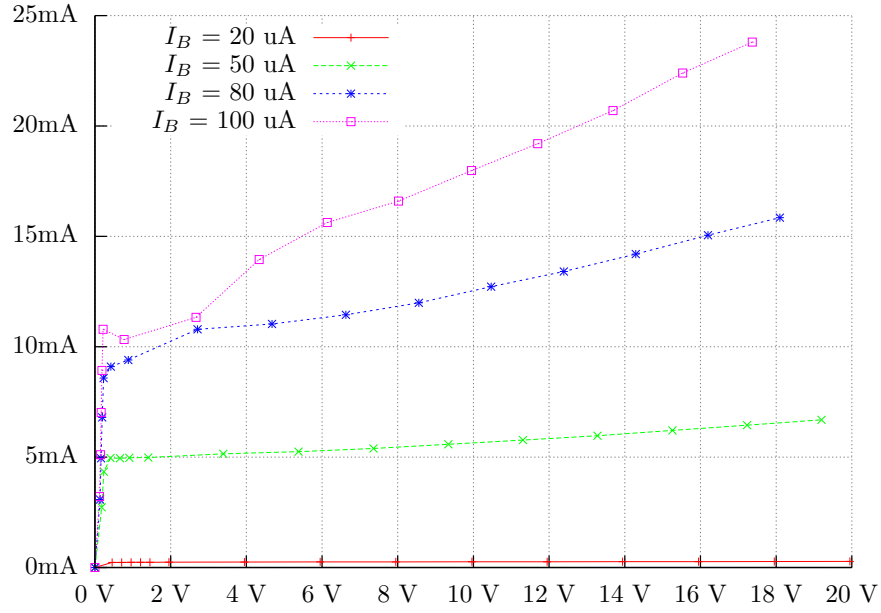


Figure 2: V_{CE} vs. I_C

| I_B (μA) | I_C (mA) | β |
|----------------------------|---------------|---------|
| 20 | 0.27 | 13.32 |
| 50 | 6.18 | 123.61 |
| 80 | 14.50 | 181.25 |
| 100 | 22.93 | 229.30 |

Table 8: $V_{CE} = 15 \text{ V}$

| V_{CE} (V) | β_{avg} |
|--------------|---------------|
| 5 | 100.42 |
| 10 | 115.42 |
| 15 | 136.87 |

Table 9: Average values of β per V_{CE}

| I_B (μA) | h_{oe} | r_o ($\text{k}\Omega$) |
|----------------------------|----------|-------------------------------|
| 20 | 1.700E-6 | 58.82 |
| 50 | 9.950E-5 | 10.10 |
| 80 | 3.669E-4 | 2.726 |
| 100 | 7.412E-4 | 1.349 |

Table 10: h_{oe} vs. r_o

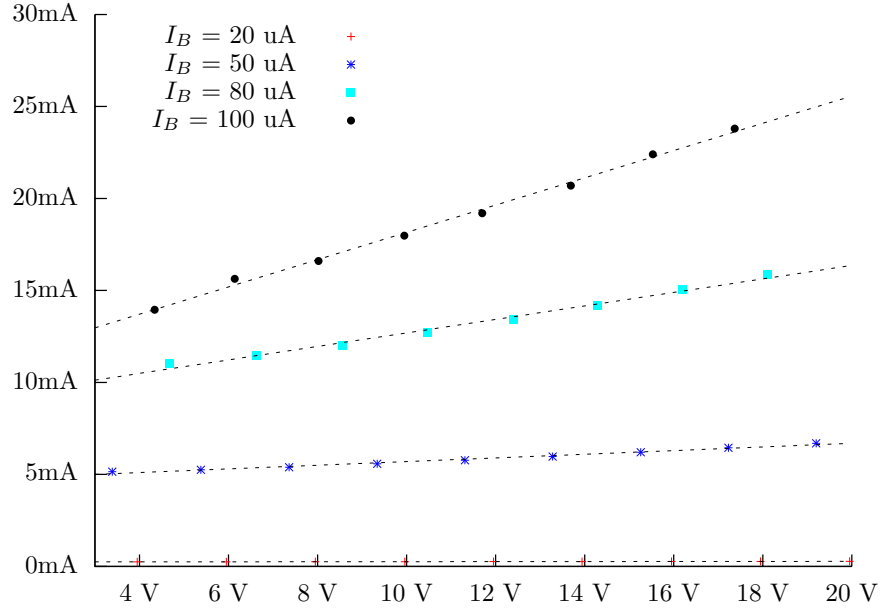


Figure 3: V_{CE} vs. I_C , $V_{CE} > 0$

6 Conclusion

As shown in Figure 2, the family of curves associated with the four I_B currents loosely follow the typical plots of Bipolar Junction Transistors (BJTs). The mode of operation of the transistor transitions to the forward-active mode when V_{CE} is greater than approximately 0.2 V. Also, as I_B increases, the slope of the I_C to V_{CE} increases.

Tables 1, 2, 3, and 4 show that as I_B increases, the ratio of I_C to I_B (current gain, β) also increases. This change in β seems to “taper off” as I_B increases such that if one were to plot mean β vs. I_B , it would resemble logarithmic growth.

Figure 3 shows the slope of each of the family of curves for V_{CE} values greater than 3 V. The output conductance (h_{oe}) was conducted with the slope of each of the four the trend line equations and Equation 2. As I_B increased, h_{oe} increased.

7 Equations

$$\beta = \frac{I_C}{I_B} \quad (1)$$

$$h_{oe} \approx \frac{1}{r_o} = \frac{\Delta I_C}{\Delta V_{CE}} \quad (2)$$