

ELEC 302-81
Lab 4
Transformers in Three Phase Circuits

February 25, 2013

Date Performed:	February 11, 2013
Partners:	Rawley Dent Charles Pittman
Instructor:	Dr. Weatherford

1 Purpose of Experiment

The purpose of this experiment was to observe the basic principals of balanced three-phase transformer circuits. Y-Y and Y- Δ connected transformer banks were constructed separately to observe any differences, particularly in their respective loads. Primary and secondary voltages, currents, and powers were first calculated, and then actual measurements were gathered to compare.

2 Procedure

2.1 EMS Workstation Set-up

At the Lab-Volt EMS workstation, the DAI 24-V supply was turned on, and the DAI USB connector was connected between the EMS workstation and the PC. On the LVDAM EMS application software, the metering windows for E_1 , E_2 , I_1 , I_2 , P_1 , 3ϕ power, E_3 , I_3 , and $E_1 + E_2 + E_3$ were opened. Under *Options* \rightarrow *Acquisition Settings*, the *Sample Window* dialog box was set to extended, and under *View*, the continuous refresh option was checked.

2.2 The Three Phase Source

The circuit represented by Figure 1 was constructed. The main power switch was set to ON and the voltage control knob adjusted to 120-V line-to-line. Both the installed analog EMS voltmeter and the metering window were monitored for proper indications. The line voltages were then measured and recorded in Table 1. The main power switch was set to OFF and the voltage control knob turned fully CCW. The circuit represented by Figure 2 was constructed. The main power switch was set to ON and the voltage supply was adjusted to read 120-V line-to-line. The installed analog EMS voltmeter was used for this since the 120-V were to be measured across voltage sources 4-5 only. The phase voltages were then measured and recorded in Table 1. The main power switch was set to OFF and the voltage control knob turned fully CCW.

2.3 Y-Y Connected Transformer

The circuit represented by Figure 3 was constructed. The Y-connected load was $(600 + j300)\Omega$. The main power switch was set to ON, and the voltage control knob adjusted to 120-V line-to-line. Both the installed analog EMS voltmeter and the metering window were monitored for correct voltage. The values for primary and secondary line voltages, primary and secondary line currents, and primary input power were measured and recorded in Table 6. A Fluke multimeter was used to measure the RMS voltage across the load, E_4 , and recorded in Table 6. The main power switch was set to OFF and the voltage control knob turned fully CCW.

2.4 Y- Δ Connected Transformer

The circuit represented by Figure 4 was constructed. The Y-connected load was $(600 + j300)\Omega$. The main power switch was set to ON, and the voltage control knob adjusted to 120-V line-to-line. Both the analog EMS voltmeter and the metering window were monitored for correct voltage. The values for primary and secondary line voltage, primary and secondary line current, and primary input power were measured and recorded in Table 6. A Fluke multimeter was used to measure the RMS voltage across the load, E_4 , and recorded in Table 6. The main power switch was set to OFF and the voltage control knob turned fully CCW.

3 Results

	E_1 V	E_2 V	E_3 V	$E_1+E_2+E_3$ V
V_{LL}	120.4	117.1	116.3	0.998
V_ϕ	69.77	64.56	69.01	5.15

Table 1: Measured line and phase voltages for Part 1

Case	Primary		Secondary		Load
	Line V	Phase V	Line V	Phase V	Phase V
Y-Y	120	69.3	120	11	69.3
Y- Δ	120	69.3	69.3	11	40

Table 2: Computed Voltages

Case	Primary		Secondary		Load
	Line A	Phase A	Line A	Phase A	Phase A
Y-Y	0.1033	0.1033	0.1033	0.1033	0.1033
Y- Δ	0.0596	0.0596	0.0344	0.0344	0.0344

Table 3: Computed Currents

Case	Primary Power W	Secondary Power W	Load Power W
Y-Y	19.20	19.20	19.2
Y- Δ	6.40	6.4	6.4

Table 4: Computed Powers

Case	Primary		Secondary		3ϕ	Load
	Voltage E_1 V	Current I_1 A	Voltage E_3 V	Current I_3 A	Input Power B W	Voltage E_4 V
Y-Y	121.2	0.112	119.5	0.097	19.8	58.4
Y- Δ	120.1	0.151	68.4	0.055	4.7	32.4

Table 5: Measured Values

Case	Primary		Secondary		3ϕ	Load
	Voltage E_1 V	Current I_1 A	Voltage E_3 V	Current I_3 A	Input Power B W	Voltage E_4 V
Y-Y	0.99	7.77	3.03	0.42	6.49	18.7
Y- Δ	0.17	77.2	37.3	1.21	8.36	23.46

Table 6: Percent Deviations

Case	Efficiency η
Y-Y	54.29%
Y- Δ	72.53%

Table 7: Transformer Efficiency

Equations Used:

$$\text{Transformer Efficiency} = \eta = \left(\frac{P_{out}}{P_{in}} \right) \cdot 100\%$$

$$\text{Percent Deviation} = \left(\frac{\text{calculated} - \text{measured}}{\text{measured}} \right) \cdot 100\%$$

4 Conclusions

The line and phase voltages of the source were measured in part 1. In Figure 1, the three source voltages are in a Δ -connection, and hence the voltage values for each phase are the same as the supply line-voltage. When the voltages are added, they approximate 0-V due to Kirchoff's voltage law. In Figure 2, the three source voltages are in a Y-connection, and hence the voltage values for each phase are $\frac{1}{\sqrt{3}}$ times the line voltage of 120-V. When the voltages are added, they approximate 0-V, since the connection is assumed to be balanced. When the Phasor Analyzer was analyzed on the PC, it was confirmed that the phasors were equal with 120 degrees phase shift for both the line and phase voltage measurements. The fact that the addition of the phasors was not exactly zero is most likely due to the fact that the voltage values measured were not exactly equal to each other.

When the transformer efficiencies for both connections were calculated, it was found that the Y- Δ connection was more efficient than the Y-Y connection. In the Y- Δ connection, the secondary Δ configuration helped make the transformer bank more stable and thus more efficient. This was most likely due to the fact that a Y- Δ has no problem with third-harmonic components in its voltages.

Circuits Tested

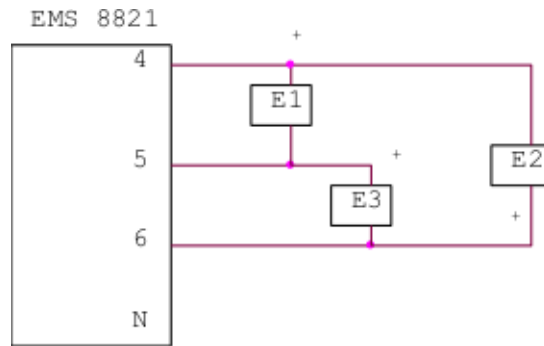


Figure 1: Circuit used to measure line voltages for Part 1

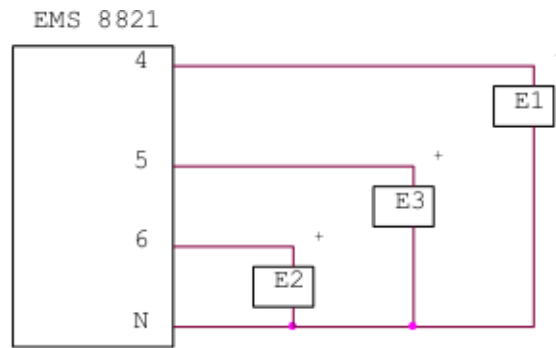


Figure 2: Circuit used to measure phase voltages for Part 1

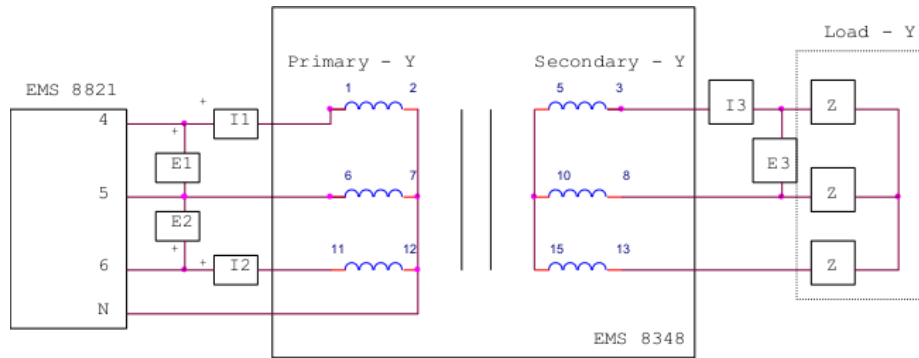


Figure 3: Y-Y connected three-phase transformer for Part 2

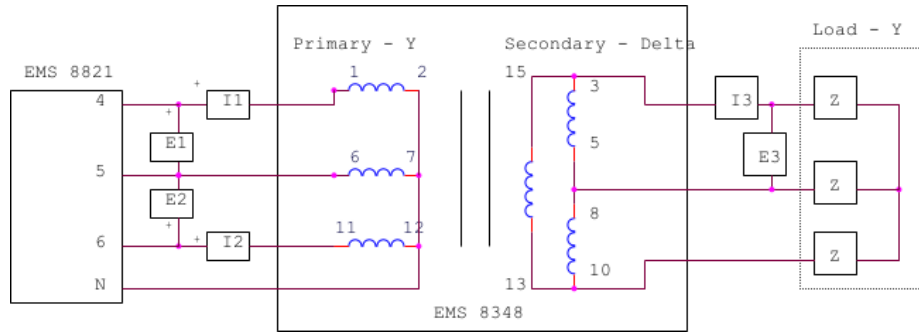


Figure 4: Y-Δ connected three-phase transformer for Part 3