

VHDL

ELEC 311

Digital Logic and Circuits

Dr. Ron Hayne

Images Courtesy of Cengage Learning




VHDL Tools


- ◆ Hardware Description Language Tools
 - Text Editor
 - Design Entry
 - Compiler
 - Syntax
 - Simulator
 - Test Bench
 - Functional Verification
 - Synthesis tool
 - Libraries
 - Target Technology

VHDL Model

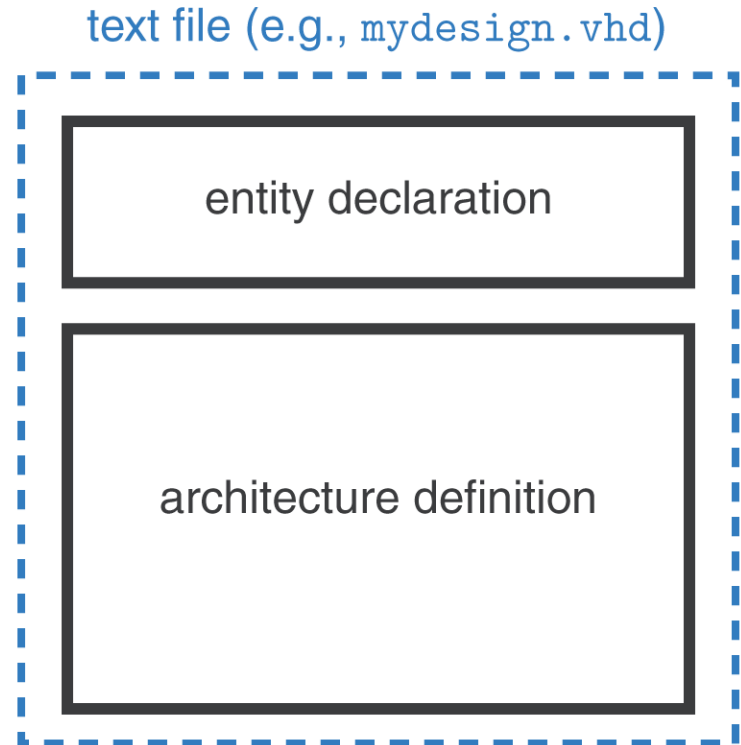- ◆ Entity
 - Component interface
 - Inputs
 - Outputs
- ◆ Architecture
 - Structural
 - Dataflow
 - Behavioral



Propagation Delays

 

-- when A changes, these concurrent
-- statements all execute at the same time

D <= A and B after 2 ns;
E <= not A after 1 ns;
F <= A or C after 3 ns;

Bit_Vectors



-- the hard way


```
C(3) <= A(3) and B(3);
```

```
C(2) <= A(2) and B(2);
```

```
C(1) <= A(1) and B(1);
```


```
C(0) <= A(0) and B(0);
```

Multiplexers

 


-- conditional signal assignment statement
`F <= I0 when A = '0' else I1;`

Design Hierarchy

 

4-bit Adder Example

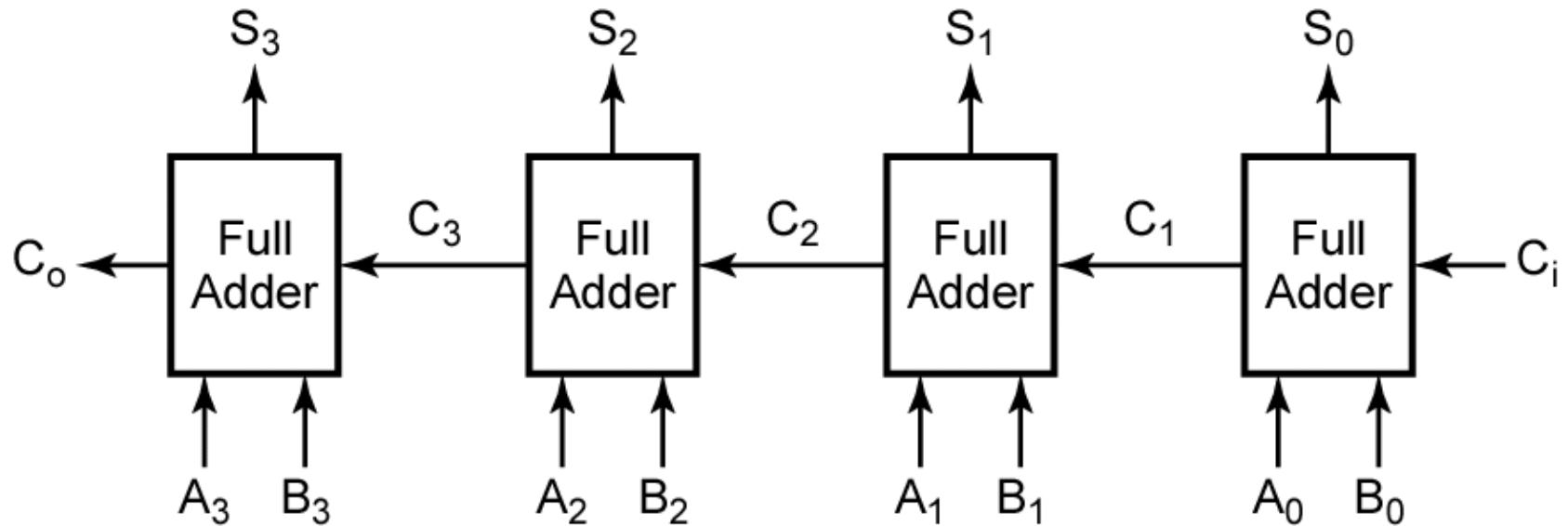

VHDL Types

◆ Predefined Types

bit	character	severity_level
bit_vector	integer	string
boolean	real	time

◆ IEEE Standard Logic

```
type STD_ULOGIC is ( 'U', -- Uninitialized
                    'X', -- Forcing Unknown
                    '0', -- Forcing 0
                    '1', -- Forcing 1
                    'Z', -- High Impedance
                    'W', -- Weak Unknown
                    'L', -- Weak 0
                    'H', -- Weak 1
                    '-' -- Don't care
                    );
subtype STD_LOGIC is resolved STD_ULOGIC;
```

VHDL Operators

<i>integer Operators</i>		<i>boolean Operators</i>	
+	addition	and	AND
-	subtraction	or	OR
*	multiplication	nand	NAND
/	division	nor	NOR
mod	modulo division	xor	Exclusive OR
rem	modulo remainder	xnor	Exclusive NOR
abs	absolute value	not	complementation
**	exponentiation	&	concatenation

VHDL Libraries and Packages

- ◆ library IEEE;
- ◆ use IEEE.numeric_bit.all;
- ◆ library IEEE;
- ◆ use IEEE.std_logic_1164.all;
- ◆ use IEEE.numeric_std.all;
- ◆ use work.project3_gates.all;


Project 3 VHDL

- ◆ Structural Description
 - Entity
 - Structural Architecture
- ◆ Package
 - Component declarations
 - Dataflow descriptions

Project 3 Xilinx

- ◆ New Project
 - Top-Level Source Type → HDL
- ◆ Project → New Source
 - VHDL Module
- ◆ Project → Add Copy of Source
 - `project3_gates.vhd`

New Source

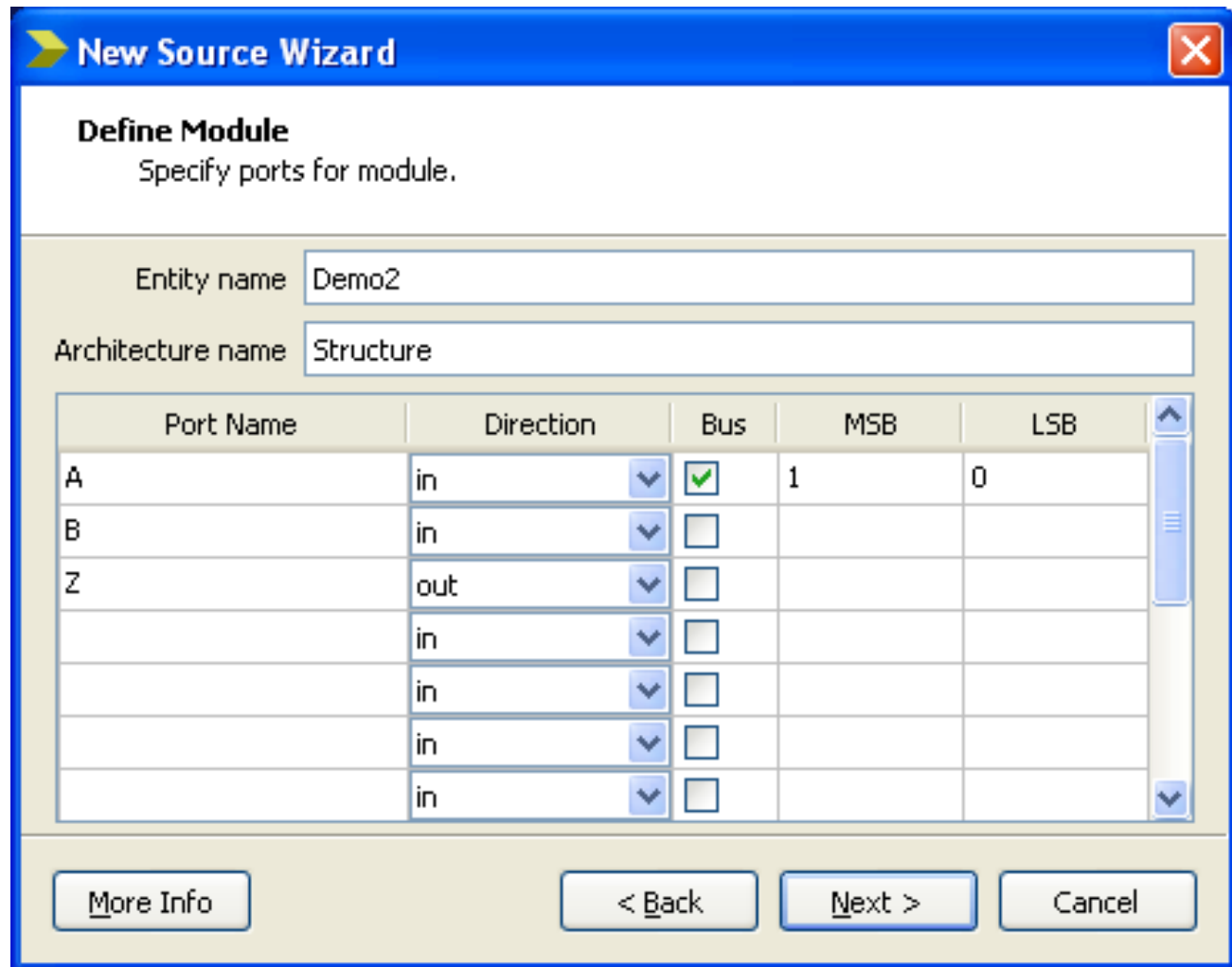

New Source Wizard

Define Module
Specify ports for module.

Entity name: Demo2

Architecture name: Structure

Port Name	Direction	Bus	MSB	LSB
A	in	<input checked="" type="checkbox"/>	1	0
B	in	<input type="checkbox"/>		
Z	out	<input type="checkbox"/>		
	in	<input type="checkbox"/>		
	in	<input type="checkbox"/>		
	in	<input type="checkbox"/>		
	in	<input type="checkbox"/>		

[More Info](#) [< Back](#) [Next >](#) [Cancel](#)

ISE Project Navigator (0.61xd) - C:\Hayne\ELEC311\Examples\Demo2\Demo2.xise - [Demo2.vhd]

File Edit View Project Source Process Tools Window Layout Help

Design

View: Implementa Simul

Hierarchy

- Demo2
 - xc3s100e-5tq144
 - Demo2 - Structure (Demo2)
 - G1 - ExclusiveOR - DATA
 - G2 - ExclusiveOR - DATA
 - FullAdder - DATAFLOW (proj)

No Processes Running

Processes: Demo2 - Structure

- Design Summary/Reports
- Design Utilities
- User Constraints
- Synthesize - XST
 - View RTL Schematic
 - View Technology Sche...
 - Check Syntax**
 - Generate Post-Synthe...
- Implement Design
- Generate Programming File
- Configure Target Device
- Analyze Design Using Chip...

```
19 -----
20 library IEEE;
21 use IEEE.STD_LOGIC_1164.ALL;
22 use IEEE.STD_LOGIC_ARITH.ALL;
23 use IEEE.STD_LOGIC_UNSIGNED.ALL;
24 use work.project3_gates.all;
25
26 ---- Uncomment the following library declaration if instantiating
27 ---- any Xilinx primitives in this code.
28 --library UNISIM;
29 --use UNISIM.VComponents.all;
30
31 entity Demo2 is
32     Port ( A : in  STD_LOGIC_VECTOR (1 downto 0);
33           B : in  STD_LOGIC;
34           Z : out STD_LOGIC);
35 end Demo2;
36
37 architecture Structure of Demo2 is
38     signal C: std_logic;
39 begin
40     G1: ExclusiveOR port map (A(1), A(0), C);
41     G2: ExclusiveOR port map (C, B, Z);
42 end Structure;
43
44
```

Start Design Files

Demo2.vhd Design Summary

Console

Compiling vhd1 file "C:/Hayne/ELEC311/Examples/Demo2/Demo2.vhd" in Library work.
Entity <Demo2> compiled.
Entity <Demo2> (Architecture <Structure>) compiled.

Process "Check Syntax" completed successfully

Console Errors Warnings Find in Files Results

311_10 15 Ln 24 Col 29 VHDL

Summary

- ◆ Entity
- ◆ Architecture
 - Structural
 - Dataflow
 - Behavioral
- ◆ Types
- ◆ Operators
- ◆ Libraries and Packages