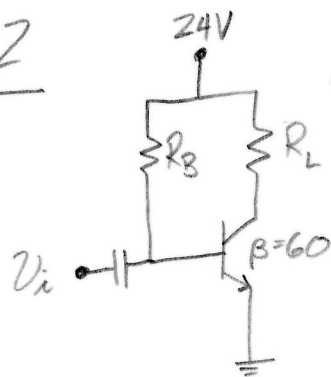


8.2




a) $P_{Q, \max} = 25W$

Max power @ $V_{CE} = 12V \Rightarrow I_C = \frac{25W}{12V} = 2.08A$

$\therefore R_L = \frac{12V}{2.08A} = \underline{5.76\Omega}$

$I_B = \frac{I_C}{\beta} = \frac{2.08}{60} = 34.7mA \Rightarrow R_B = \frac{23.3V}{34.7mA} = \underline{672\Omega}$

b) AC circuit

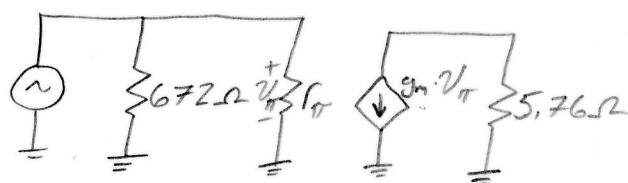

$r_\pi = \frac{60 \cdot 0.026}{2.08} = \underline{0.750\Omega}$

$g_m = \frac{2.08}{0.026} = \underline{80A/V}$

$V_\pi = V_i = 0.012 \sin \omega_0 t$ $V_o = -g_m \cdot V_i \cdot 5.76 = 461 V_i$


$V_o = -5.53 \sin \omega_0 t = 3.91 V_{rms}$

$\therefore P_{AC} = \frac{3.91 V_{rms}^2}{5.76\Omega} = \underline{2.66W}$ ← Power dissipated by R_L

$\therefore P_{TRANSISTOR} = 25W - 2.66W = \underline{22.3W}$

- 35W
- @ 50V, $I = 0.7A$
- @ 4A, $V = 8.75$
- @ 25V, $I = 1.4A$
- @ 10V, $I = 3.5A$
- @ 40V, $I = 0.875$

8.5

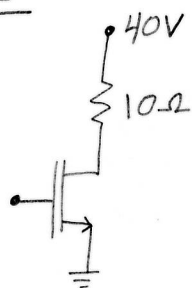


$I_{D, \max} = 4A$

$V_{DS, \max} = 50V$

$P_{D, \max} = 35W$

$K_n = 0.25 A/V^2$

$V_{TN} = 4V$

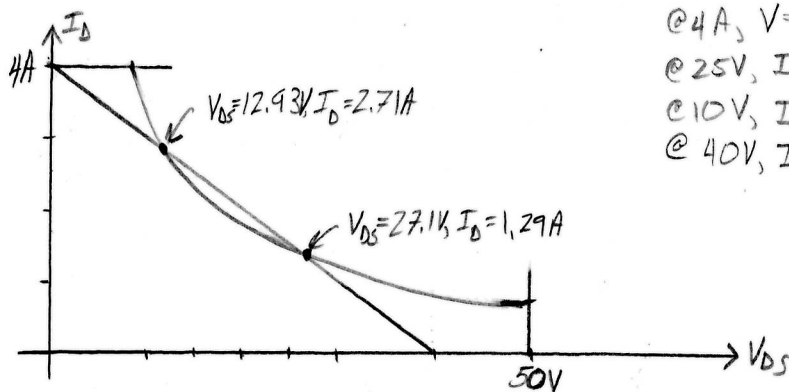

Load line: $V_{DS} = 40 - 10I_D$

$I_D = \frac{40 - V_{DS}}{10} = -\frac{1}{10} V_{DS} + 4$

@ max power, $V_{DS} = 20V, I_D = 2A$

$P = \underline{40W}$

Max Power Curve: $I_D = \frac{35}{V_{DS}}$

$-\frac{1}{10} V_{DS} + 4 = \frac{35}{V_{DS}} \Rightarrow -V_{DS}^2 + 40V_{DS} = 350$

$V_{DS} = 12.93, 27.07$

$I_D = 2.71, 1.29A$

* Anything between $12.93 < V_{DS} < 27.07$ will exceed 35W!

8.5 b) $I_D = 0.25(V_{GG} - 4)^2$

$V_{DS} = 40 - 10I_D$

$P_D = I_D \cdot V_{DS}$

c) @ $V_{GG} = 7V$

$P_D = 39.4W$ which exceeds $P_{D,MAX} = \underline{35W}$

$V_{GG} = 5V: I_D = 250mA, V_{DS} = 37.5V, P_D = 9.375W$

$V_{GG} = 6V: I_D = 1A, V_{DS} = 30V, P_D = 30W$

$V_{GG} = 7V: I_D = 2.25A, V_{DS} = 17.5V, P_D = 39.375W$

$V_{GG} = 8V: I_D = 4A, V_{DS} = 0 \leftarrow \text{Not in saturation!}$

$I_D = 0.25(2(V_{GG} - 4)V_{DS} - V_{DS}^2) = \frac{40 - V_{DS}}{10}$

$40 - V_{DS} = 2.5(8V_{DS} - V_{DS}^2)$

$2.5V_{DS}^2 - 21V_{DS} + 40 = 0$

$V_{DS} = 2.92V, I_D = 3.71A, P_D = 10.83W$

$V_{GG} = 9V \leftarrow \text{also in triode}$


$I_D = 0.25(2(9-4)V_{DS} - V_{DS}^2) = \frac{40 - V_{DS}}{10}$

$40 - V_{DS} = 2.5(10V_{DS} - V_{DS}^2)$

$2.5V_{DS}^2 - 26V_{DS} + 40 = 0$

$V_{DS} = 1.88V, I_D = 3.81A, P_D = 7.17W$

8.26

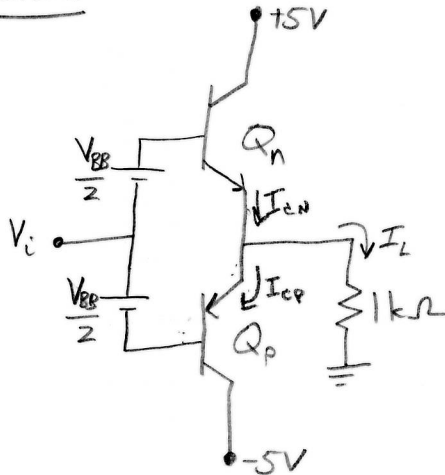

$I_S = 2 \times 10^{-15}A$

a) $I_{CnQ} = I_{CpQ} = 1mA \Rightarrow 1mA = 2 \times 10^{-15} e^{V_{BE}/0.026}$

$V_{BE} = 0.7V \Rightarrow V_{BB} = \underline{1.4V}$

$P_Q = 1mA \cdot 5V = \underline{5mW}$

b) Assuming $I_C = I_E$, we have four equations:

① $I_{Cn} = I_L + I_{Cp}$

② $V_{EBP} = V_T \ln(I_{Cp}/I_S)$

③ $V_{BEN} = V_T \ln(I_{Cn}/I_S)$

④ $V_{EBP} + V_{BEN} = V_{BB}$

We have 4 equations & 4 unknowns ($I_{Cn}, I_{Cp}, V_{EBP}, V_{BEN}$), with a mix of linear and exponential relationships - we must iterate through 4 equations!

We can start with assuming Q_n is off & Q_p is on, and $I_L = -3.5mA$

① $I_{Cn} = 0 \Rightarrow I_{Cp} = I_L = 3.5mA$

② $V_{EBP} = 0.026 \ln(3.5mA/2fA) = 733mV$

$$\textcircled{4} V_{BEN} = 1.4 - V_{EBP} = 1.4 - 0.733 = 667 \text{ mV}$$

$$\textcircled{3} I_{CN} = 2 \text{ fA} e^{(0.667/0.026)} = 277 \mu\text{A}$$

2nd iteration

$$\textcircled{1} I_{CP} = 277 \mu\text{A} - (-3.5 \text{ mA}) = 3.78 \text{ mA}$$

$$\textcircled{2} V_{EBP} = 0.026 \ln(3.78 \text{ mA} / 2 \text{ fA}) = 735 \text{ mV}$$

$$\textcircled{4} V_{BEN} = 1.4 - 0.735 = 665 \text{ mV}$$

$$\textcircled{3} I_{CN} = 2 \text{ fA} e^{(0.665/0.026)} = 257 \mu\text{A}$$

3rd iteration

$$\textcircled{1} I_{CP} = 3.76 \text{ mA}$$

$$\textcircled{2} V_{EBP} = 735 \text{ mV}$$

$$\textcircled{4} V_{BEN} = 665 \text{ mV}$$

$$\textcircled{3} I_{CN} = 258 \mu\text{A}$$

4th iteration

$$\textcircled{1} I_{CP} = 3.76 \text{ mA}$$

$$\textcircled{2} V_{EBP} = 735 \text{ mV}$$

$$\textcircled{4} V_{BEN} = 665 \text{ mV}$$

$$\textcircled{3} I_{CN} = 258 \mu\text{A}$$

$$V_i = -3.5 \text{ V} + V_{BEN} - V_{BB}/2 = -3.5 + 0.665 - 0.7 = -3.535 \text{ V, or}$$


$$V_i = -3.5 \text{ V} - V_{EBP} + V_{BB}/2 = -3.5 - 0.735 + 0.7 = -3.535 \text{ V}$$

$$\text{c) } P_{QN} = (5 + 3.5)(258 \mu\text{A}) = 2.19 \text{ mW}$$

$$P_{QP} = (-3.5 + 5)(3.76 \text{ mA}) = 5.64 \text{ mW}$$

$$P_L = (3.5)(3.5 \text{ mA}) = 12.25 \text{ mW}$$

8.28

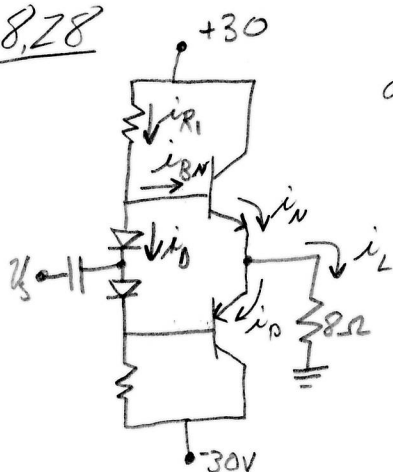

$$\text{a) } i_L = \frac{24 \text{ V}}{8 \Omega} = 3 \text{ A}$$

$$i_N \approx i_L = 3 \text{ A} \Rightarrow i_{BN} = \frac{3 \text{ A}}{41} = 73.2 \text{ mA}$$

$$\text{for } i_D = 25 \text{ mA}, i_{R1} = 25 \text{ mA} + 73.2 \text{ mA} = 98.2 \text{ mA}$$

$$\text{Need } V_{R1}: V_{R1} = 30 - (24 + V_{BEN})$$

$$V_{BEN} = 0.026 \ln\left(\frac{3 \text{ A}}{6 \text{ pA}}\right) = 700 \text{ mV} \Rightarrow V_{R1} = 5.3 \text{ V}$$

$$\therefore R_1 = \frac{5.3 \text{ V}}{98.2 \text{ mA}} = 54 \Omega$$

$$\text{With } i_D = 25 \text{ mA } V_D = 0.026 \ln\left(\frac{25 \text{ mA}}{6 \text{ pA}}\right) = 576 \text{ mV}$$

$$\therefore V_{EBP} = 2(576 \text{ mV}) - 700 \text{ mV} = 451.8 \text{ mV}$$

$$i_P = 6 \text{ pA} e^{(452/26)} = 211 \mu\text{A}$$

*Technically we could correct i_N , but this is so small it won't matter.

8.28 b) With $V_D = 0$, $i_n = i_p$ & $V_{EBP} = V_{BEN} = V_D$

$$I_D = I_{R1} - I_{BN} \quad \& \quad I_{R1} = \frac{30 - V_{BEN}}{R1}, \quad I_{BN} = \frac{I_S}{\beta+1} e^{V_{BEN}/V_T}$$

$$\therefore I_D = \frac{30 - V_{BEN}}{54} - \frac{6pA}{41} e^{V_{BEN}/0.026}$$

We need another equation relating I_D & V_{BEN}

$$\left. \begin{array}{l} V_{BEN} + V_{EBP} = 2V_D \\ V_D = V_T \ln(I_D/I_S) \end{array} \right\} \begin{array}{l} 2V_{BEN} = 2V_T \ln(I_D/6pA) \\ V_{BEN} = V_T \ln(I_D/6pA) \end{array}$$

We now iterate to find I_D & V_{BEN}

Guess $V_{BEN} = 0.6V$

$$I_D = \frac{30 - 0.6}{54} - \frac{6pA}{41} e^{0.6/0.026} = 542.9 \mu A$$

$$V_{BEN} = 0.026 \ln\left(\frac{542.9 \times 10^{-3}}{6 \times 10^{-12}}\right) = 656 mV$$

2nd iteration

$$I_D = 530.2 \mu A$$


$$V_{BEN} = 655 mV$$

3rd iteration

$$I_D = \underline{530.5 \mu A} = I_n = I_p$$

$$V_{BEN} = \underline{655 mV} = V_{EBP} = V_D$$

9.15

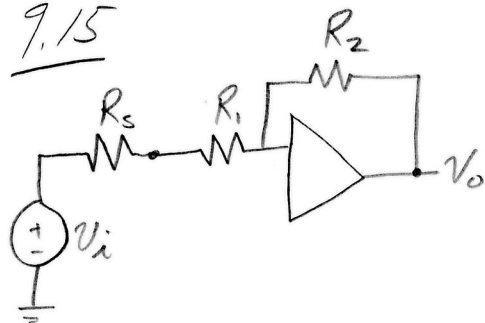

$$a) V_o = \frac{-R_2}{R_1 + R_2} = 30 \pm 2.5\%$$

$$2.5\% \text{ of } 30 = 0.75 \Rightarrow 29.25 < A_v < 30.75$$

Max gain with $R_s = 1k\Omega$, min w/ $R_s = 2k$


$$30.75 = \frac{R_2}{1k + R_1} \quad ; \quad 29.25 = \frac{R_2}{2k + R_1}$$

$$b) \text{ for } V_i = 25mV$$

$$\underline{731.25 < V_o < 768.75mV} \quad \frac{30.75}{29.25} = \frac{2k + R_1}{1k + R_1} \Rightarrow R_1 = \underline{18.5k\Omega}$$

$$R_2 = 30.75(1 + 18.5) = \underline{599.6k\Omega}$$

9.16

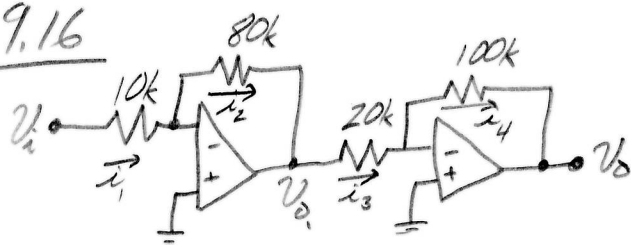

$$A_{v1} = -\frac{80}{10} = -8 \Rightarrow V_{o1} = (-0.15)(8) = \underline{-1.2V}$$

$$A_{v2} = -\frac{100}{20} = -5 \Rightarrow V_o = (-1.2)(-5) = \underline{6V}$$


$$i_1 = \frac{-0.15}{10k} = \underline{-15\mu A} = i_2$$

$$i_3 = \frac{1.2}{20k} = \underline{60\mu A} = i_4$$

$$i_{o1} = i_3 - i_2 = 60\mu A - (-15\mu A) = \underline{75\mu A}$$

$$i_{o2} = i_4 = \underline{60\mu A}$$

9.25

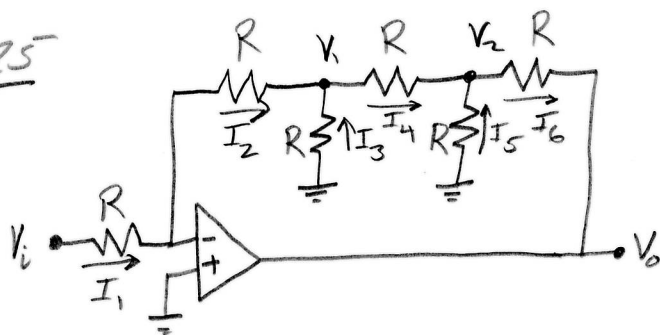

$$\underline{A_v = -8}$$

For figure 9.12, $A_v = -3$

$$I_1 = \frac{V_i}{R} \quad I_2 = I_1$$

$$V_1 = -I_2 \cdot R = -I_1 \cdot R = -V_i$$


$$I_3 = \frac{V_i}{R} = I_1 \Rightarrow I_4 = I_2 + I_3 = 2I_1$$

$$V_2 = V_1 - I_4 \cdot R = -V_i - 2I_1 R = -3V_i$$

$$I_5 = \frac{3V_i}{R} = 3I_1 \Rightarrow I_6 = I_4 + I_5 = 5I_1$$

$$V_o = V_2 - I_6 R = -3V_i - 5I_1 R = -8V_i$$

9.37

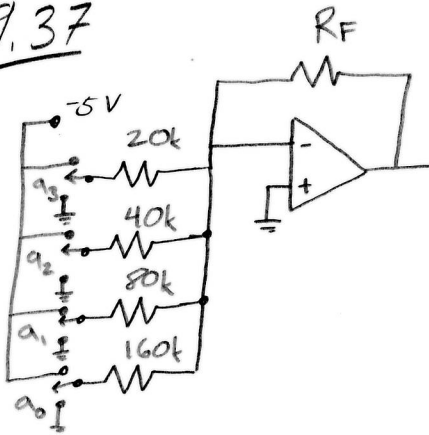

a) For a summing amplifier, the gain of an input x is given by $-R_F/R_x$

$$\text{for } a_3: V_o' = (+5) \cdot \frac{+R_F}{20k} \quad a_1: V_o''' = (+5) \cdot \frac{+R_F}{80k}$$

$$a_2: V_o'' = (+5) \cdot \frac{+R_F}{40k} \quad a_0: V_o'''' = (+5) \cdot \frac{+R_F}{160k}$$

$$b) 2.5 = \frac{5}{10} \cdot R_F \left(\frac{1}{2} \right)$$

$$R_F = \underline{10k\Omega}$$


$$V_o = 5 \left(\frac{a_3 \cdot R_F}{20} + \frac{a_2 \cdot R_F}{40} + \frac{a_1 \cdot R_F}{80} + \frac{a_0 \cdot R_F}{160} \right)$$

$$V_o = \frac{5}{10} \cdot R_F \left(\frac{a_3}{2} + \frac{a_2}{4} + \frac{a_1}{8} + \frac{a_0}{16} \right)$$

$$c) i) V_o = 5 \left(\frac{1}{16} \right) = \underline{0.3125V}$$

$$ii) V_o = 5 \left(\frac{1}{2} + \frac{1}{4} + \frac{1}{8} + \frac{1}{16} \right) = \underline{4.688V}$$

9.52

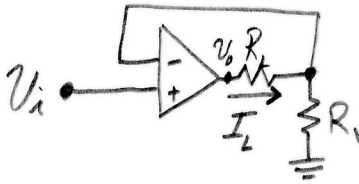

$$a) I_{R_1} = \frac{V_i}{R_1}$$

$$I_L = I_{R_1} = \frac{V_i}{R_1}$$

$$b) V_{R_2} = I_L \cdot R_2 = \frac{V_i}{R_1} \cdot R_2 = \frac{R_2}{R_1} \cdot V_i$$

$$V_o = V_i + V_{R_2} = V_i + \frac{R_2}{R_1} \cdot V_i = \left(1 + \frac{R_2}{R_1} \right) V_i$$

$$\text{for } R_2 = 1k \text{ and } R_1 = 9k$$

$$V_{o,max} = 10V \Rightarrow 10 = \left(1 + \frac{1}{9} \right) V_i \Rightarrow V_{i,max} = \underline{9V}$$

$$I_{L,max} = \frac{9V}{9k\Omega} = \underline{1mA}$$