

ELEC-313  
Lab 5: CMOS Circuits

October 30, 2013

Date Performed: October 16, 2013  
Partners: Charles Pittman  
Stephen Wilson

## Contents

<b>1</b>	<b>Objective</b>	<b>3</b>
<b>2</b>	<b>Equipment</b>	<b>3</b>
<b>3</b>	<b>Schematics</b>	<b>3</b>
<b>4</b>	<b>Procedure</b>	<b>3</b>
4.1	CMOS Inverter . . . . .	3
4.2	CMOS NAND . . . . .	4
<b>5</b>	<b>Results</b>	<b>5</b>
<b>6</b>	<b>Conclusion</b>	<b>7</b>

## List of Figures

1	Circuits used in this lab. . . . .	3
2	Output of CMOS inverter . . . . .	5
3	Transition point in CMOS inverter . . . . .	6
4	Output of CMOS NAND gate . . . . .	6

## List of Tables

1	NAND logic table . . . . .	5
---	----------------------------	---

## 1 Objective

The objective is to construct and observe the operation of a CMOS inverter and NAND gate.

## 2 Equipment

- ALD1105 Dual N-channel and P-channel matched pair MOSFET
- Power supply: HP E3631A
- Oscilloscope: Agilent 54622D
- Function generator: HP 33120A

## 3 Schematics

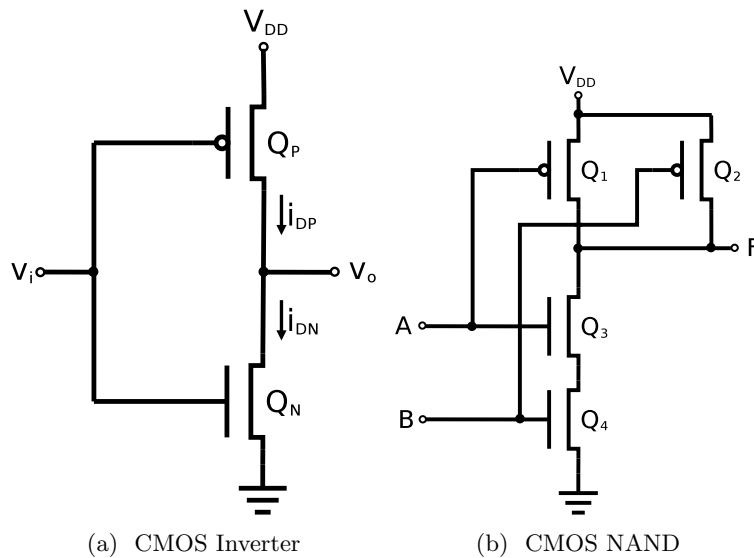


Figure 1: Circuits used in this lab.

## 4 Procedure

### 4.1 CMOS Inverter

1. Construct the circuit of figure 1a.
2. Connect the V+ terminal (Pin 11) to the + supply voltage

3. Connect the  $V^-$  terminal (Pin 4) to the circuit ground.
4. Set VDD to 5 V using the HP source.
5. Use the function generator to input  $V_i$ . Set the function generator to a frequency of 20 kHz and select a triangle wave. Set the wave for 0 to 5 volts using the offset.
6. Connect CHANNEL 1 of the oscilloscope to the input and CHANNEL 2 to the output.
7. Use the x-y plot function of the scope to produce the transfer characteristic  $V_o$  vs.  $V_i$ . (Press the main key, then select the xy softkey, then adjust the voltage scales as needed.)
8. Capture the  $V_o$  vs.  $V_i$  data, so you can recreate the plot for the lab report.
9. Adjust the amplitude and offset of the function generator for an input square wave of 0 to 5 V as measured on the oscilloscope.
10. Adjust the scope and capture both input and output on one screen for the report.
11. Measure the propagation delay times of the output waveform.

## 4.2 CMOS NAND

1. Construct the circuit of figure 1b.
2. Connect the  $v^+$  terminal (Pin 11) to the  $+$  supply voltage.
3. Connect the  $V^-$  terminal (Pin 4) to the circuit ground.
4. Set the  $+$  supply voltage to 5 volts DC using the HP source.
5. Set input A to 0 volts.
6. Use the function generator for input B. Set the function generator to a frequency of 20 kHz and select a square wave. Set the square wave for 0 to 5 V using the offset.
7. Connect CHANNEL 1 of the oscilloscope to the input and CHANNEL 2 to the output.
8. Adjust the scope and capture both input and output on one screen for the report.
9. Repeat step 8 with the input A set to +5 V.

## 5 Results

 


Figure 2: Output of CMOS inverter

A	B	F
0	0	1
0	1	1
1	0	1
1	1	0

Table 1: NAND logic table

 


Figure 3: Transition point in CMOS inverter

 


Figure 4: Output of CMOS NAND gate

## 6 Conclusion

As seen in Figure 2, as the input voltage ( $V_i$ ) is low (0 V),  $V_o$  is high (5 V). Conversely, when  $V_i$  is high,  $V_o$  is low. This relationship of  $V_i$  to  $V_o$  is why the configuration is called an inverter. Also, the transition from high to low on the output happens when the input is approximately between 1 and 3V at  $V_i$ ; that is, when the input voltage is less than one, the output voltage is almost exactly 5 V and when the input voltage is greater than 3V, the output voltage is almost exactly 0 V. (Refer to Figure 2 for a close up of the  $V_i$  to  $V_o$ ). Additionally, the output voltage closely represents a square wave or an on/off relationship as the input voltage is swept back and forth between low and high. It should also be noted that it takes 58.8 nanoseconds for the output voltage response to change from high to low.

The circuit in Figure 1b operates as a NAND gate because when input A is low (0 V), as is the case in the first portion of CMOS NAND experiment, the inverting gate ( $Q_1$ ) is shorted and the non-inverting gate  $Q_3$  is open. Therefore no matter what input B is shown, the output voltage is high (5 V). In the second half of the experiment, when input A is high (5 V),  $Q_1$  is inverted and therefore open and  $Q_3$  is shorted. During this state, when input B is low,  $Q_2$  is inverted and shorted allowing current to flow through it, but  $Q_4$  is open blocking the current and the output voltage is again high. The only time the output voltage is low, is when A is high and B is high, which means both the inverting gates  $Q_1$  and  $Q_2$  are open and don't allow any current to flow through them.

Figure 4 illustrates the NAND gate logic table (Table 1) exactly. When input A is low,  $V_o$  is high whether input B is high or low. When input A is high,  $V_o$  is high while input B is low; when input B goes high,  $V_o$  drops to low.