

ELEC-313  
Lab 9: Common-Emitter Transistor Amplifier

November 29, 2013

Date Performed: November 20, 2013  
Partners: Charles Pittman  
Stephen Wilson

## 1 Objective

The objective is to construct and observe the operation of a common-emitter transistor amplifier.

## 2 Equipment

Transistor: 2N2222A      Capacitor: 0.1  $\mu$ F  
Resistors: 100 k $\Omega$ , 20 k $\Omega$ , 1 k $\Omega$ , 470  $\Omega$       Power supply: HP E3631A  
Function generator: HP 33120      Oscilloscope: Agilent 54622D  
Multimeters: HP 34401A, Fluke 8010A (x2)

## 3 Schematics

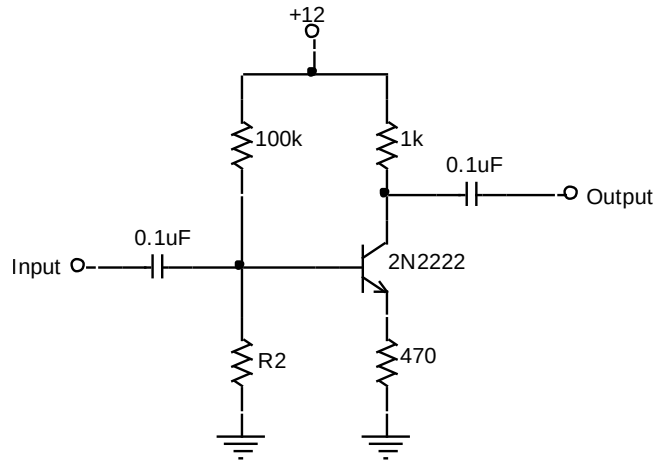


Figure 1: Common-emitter transistor amplifier (without the emitter bypass capacitor).  $R_2 = 20 \text{ k}\Omega$

## 4 Procedure

## 5 Results

$V_B$ (V)	$V_C$ (V)	$V_E$ (V)	$V_i$ (mV)	$V_o$ (mV)	$A_V$
1.788	9.58	1.153	500	970	1.94

Table 1: Transistor amplifier characteristics

$R$ ( $\Omega$ )	$V_{OC}$ (mV)
958	477

Table 2: Port impedances

$R$ (k $\Omega$ )	$V_i$ (V)
13.9	2.57

Table 3: Large-signal performance

## 6 Conclusion

## 7 Equations

$V_B$ (V)	$V_C$ (V)	$V_E$ (V)	$V_i$ (V)	$V_o$ (V)	$A_V$
1.783	9.547	1.164	0.122	6.19	52.0

Table 4: Transistor amplifier characteristics (with emitter bypass capacitor)