

# Latches and Flip-Flops

ELEC 311


Digital Logic and Circuits

Dr. Ron Hayne


*Images Courtesy of Cengage Learning*




# Set-Reset Latch

 


# Set-Reset Latch

 



# Set-Reset Latch

 


# Set-Reset Latch

 


# Switch Debouncing

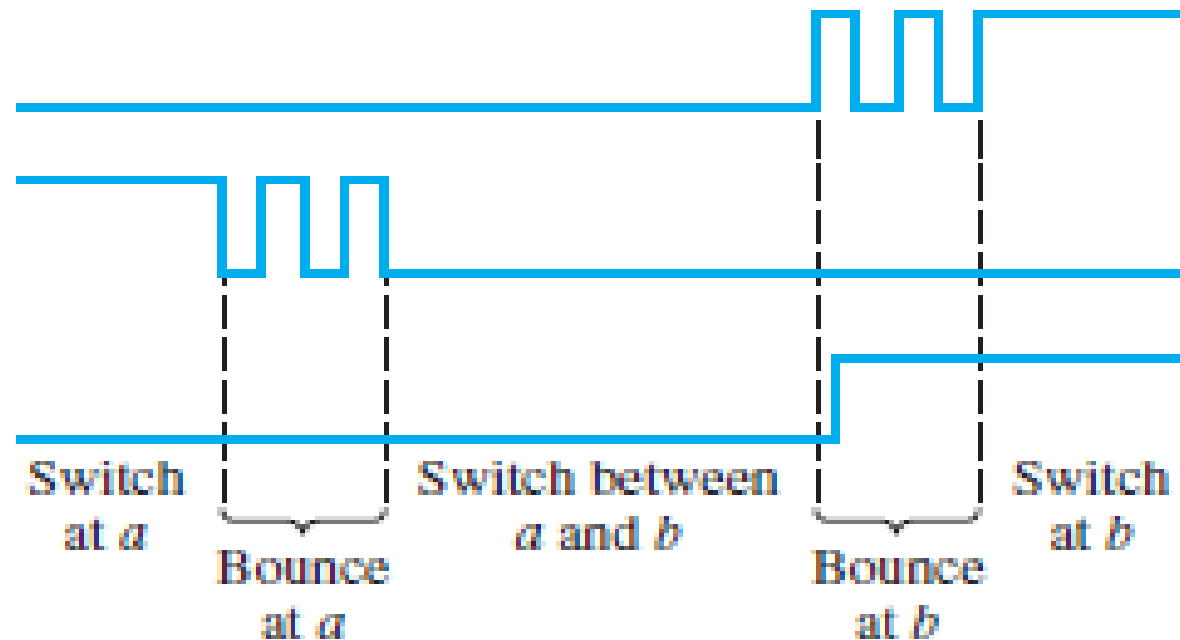 

# D Latch

 

# Edge-Triggered D Flip-Flop

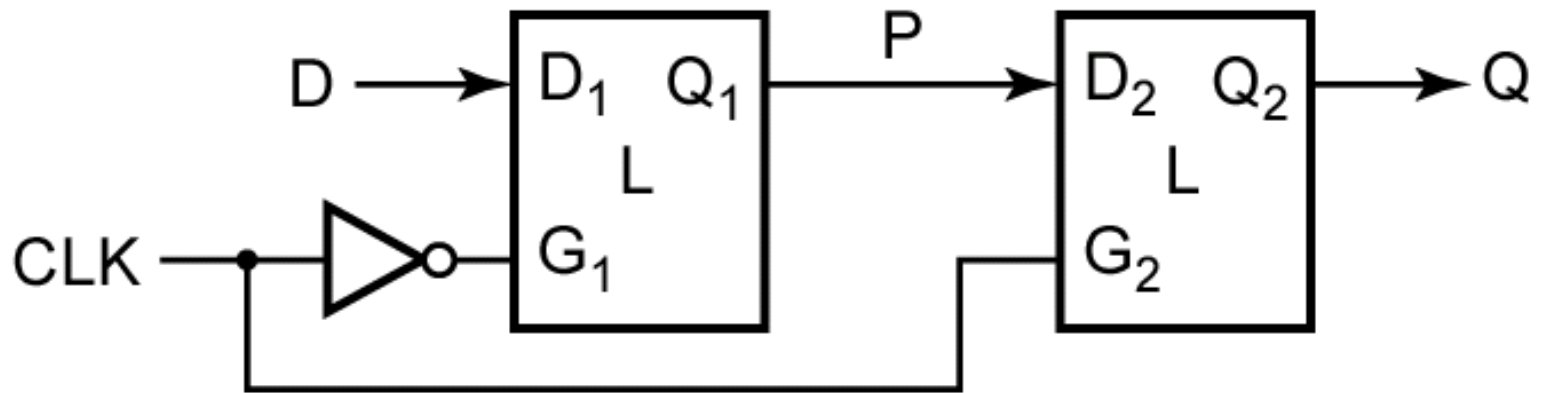






# Timing Parameters

**FIGURE 11-20**  
Setup and Hold  
Times for an  
Edge-Triggered D  
Flip-Flop

© Cengage Learning 2014

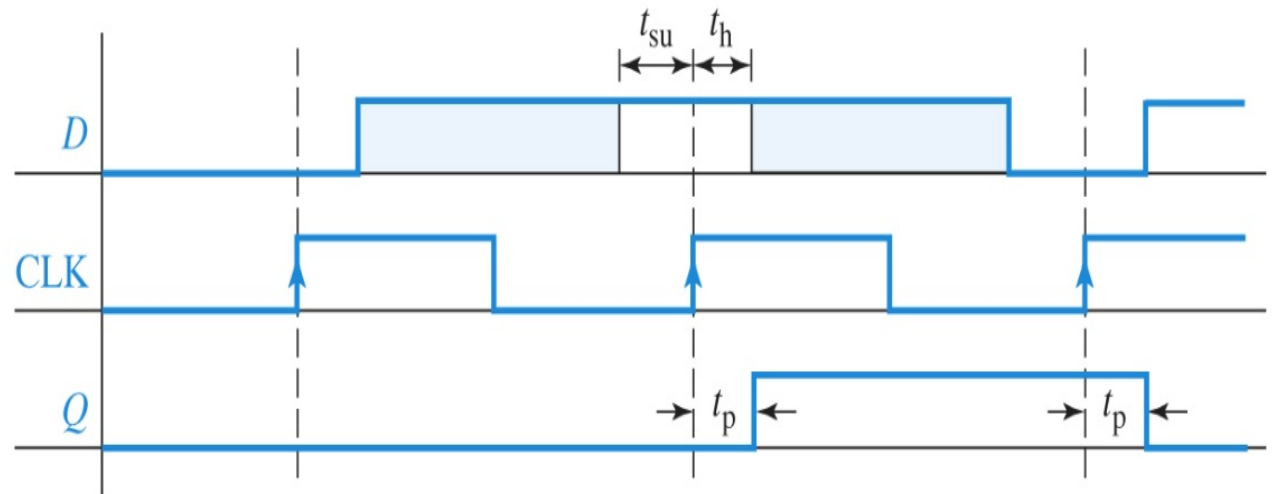


# J-K and T Flip-Flops

  

# J-K FF Timing Diagram

**FIGURE 11-24**  
J-K Flip-Flop  
(Q Changes on  
the Rising  
Edge)

© Cengage Learning 2014

 


(a) J-K flip-flop

J	K	Q	Q <sup>+</sup>
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

$$Q^+ = JQ' + K'Q$$

 (b) Truth table and characteristic equation




(c) J-K flip-flop timing

# T FF Timing Diagram



**FIGURE 11-27**  
Timing Diagram for  
T Flip-Flop (Falling-  
Edge Trigger)

© Cengage Learning 2014

 


(Falling-Edge Triggered)

# Additional Inputs

  

# Sequential Circuits

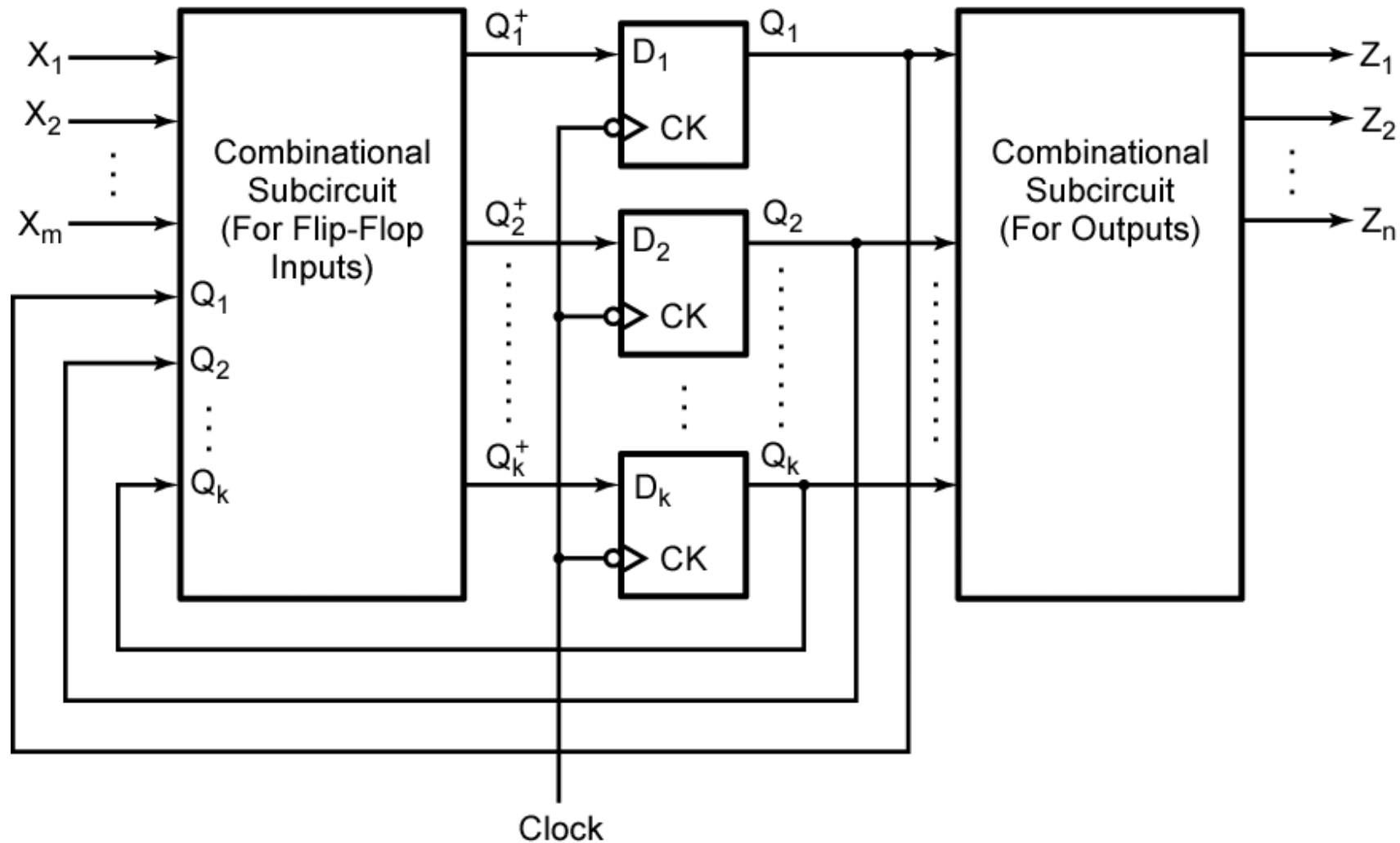

# Summary

- ◆ Latches
  - S-R (Set-Reset)
  - D (Data)
- ◆ Flip-Flops (Edge-Triggered)
  - D (Data)
  - J-K (Set-Reset-Toggle)
  - T (Toggle)