

Microelectronics Circuit Analysis and Design

Donald A. Neamen

Chapter 5

The Bipolar Junction Transistor

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 5-1

In this chapter, we will:


- Discuss the physical structure and operation of the bipolar junction transistor.
- Understand the dc analysis and design techniques of bipolar transistor circuits.
- Examine three basic applications of bipolar transistor circuits.
- Investigate various dc biasing schemes of bipolar transistor circuits, including integrated circuit biasing.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 5-2

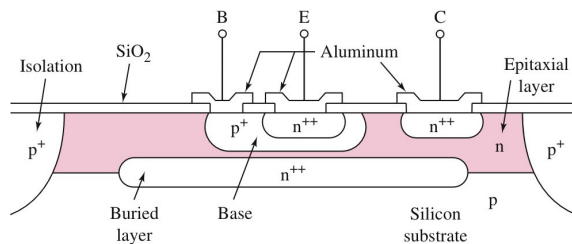Cross Section of Integrated Circuit npn Transistor



Copyright © The McGraw-Hill Companies, Inc.
Permission is required for reproduction or display.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 5-3

Modes of Operation


- Forward-Active
 - B-E junction is forward biased
 - B-C junction is reverse biased
- Saturation
 - B-E and B-C junctions are forward biased
- Cut-Off
 - B-E and B-C junctions are reverse biased
- Inverse-Active (or Reverse-Active)
 - B-E junction is reverse biased
 - B-C junction is forward biased

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 5-4

nnp BJT in Forward-Active

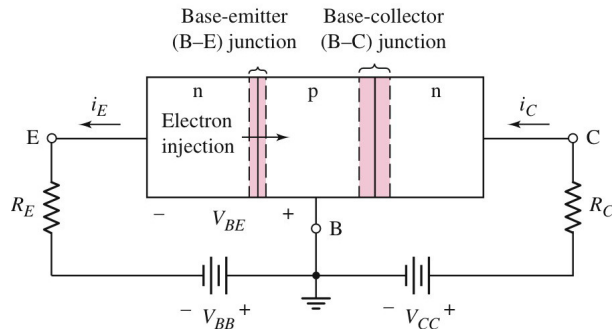


Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 5-5

Electrons and Holes in npn BJT

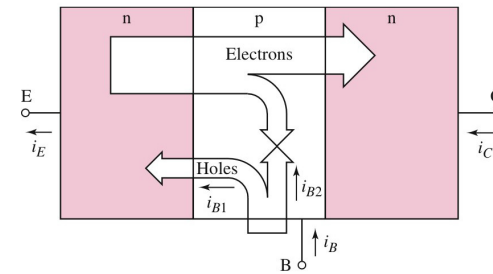

Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 5-6

Electrons and Holes in npn BJT

With a + potential across the C-E terminals.
If a positive voltage is applied to the base (>0.6V), the B-E pn junction is forward biased.


The E side electrons cross the pn junction and many electrons are swept to the positive C side voltage (since the p base material is thin). This results in electron flow from E to C.
(Conventional current flow from C to E).

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 5-7

Circuit Symbols and Current Conventions

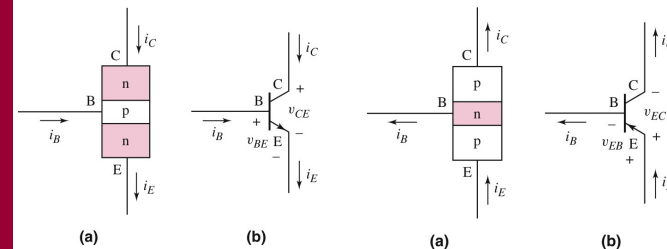

Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 5-8

Current Relationships

$$i_E = i_C + i_B$$

$$i_C = \beta i_B$$

$$i_E = (1 + \beta) i_B$$

$$i_C = \alpha i_E$$


$$\beta = \frac{\alpha}{1 - \alpha}$$

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 5-9

Common-Emitter Configurations

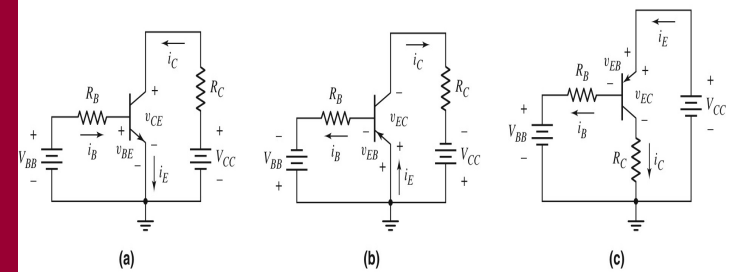


Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 5-10

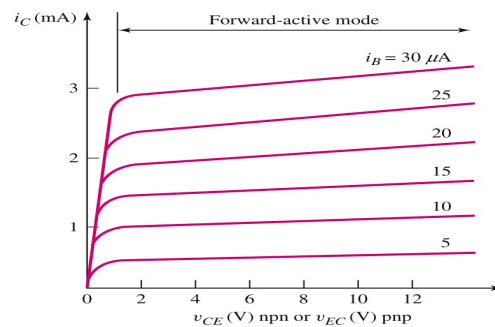Current-Voltage Characteristics of a Common-Emitter Circuit




Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 5-11

Early Voltage/Finite Output Resistance

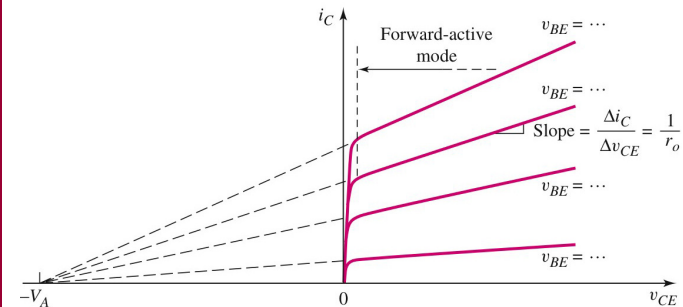


Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 5-12

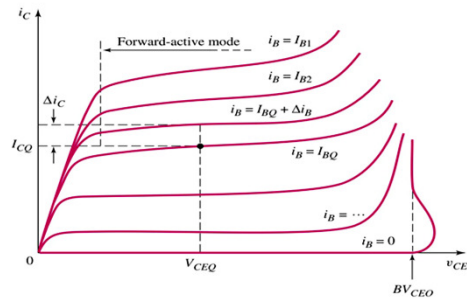Effect of Collector-Base **Breakdown** on Common Emitter I-V Characteristics




Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 5-13

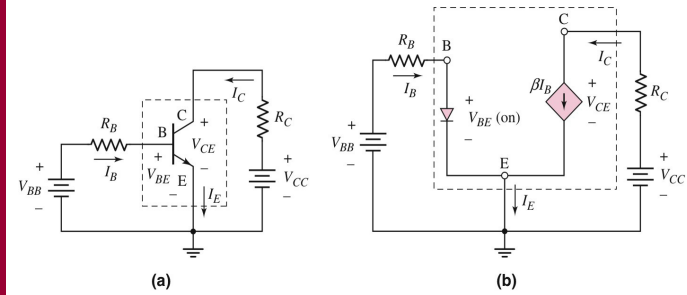DC Equivalent Circuit for npn Common Emitter




Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 5-14

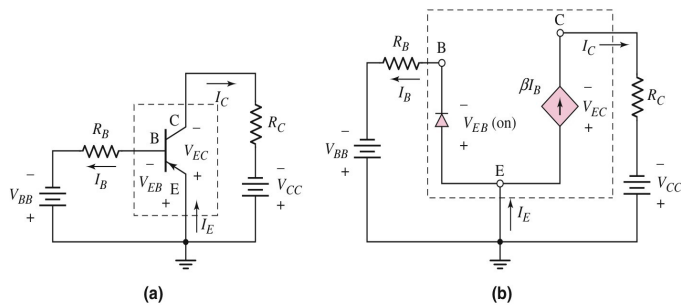DC Equivalent Circuit for pnp Common Emitter




Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 5-15

Load Line

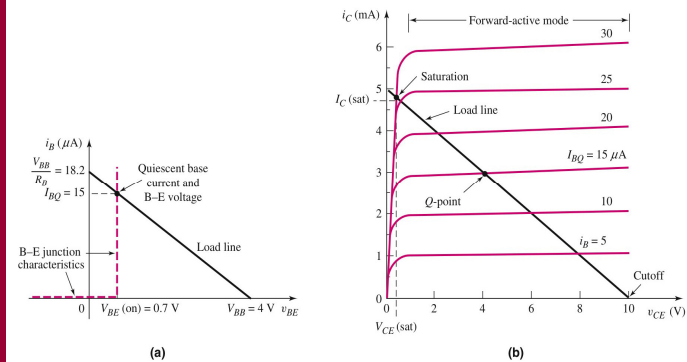

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 5-16

Problem-Solving Technique: Bipolar DC Analysis


1. Assume that the transistor is biased in forward active mode
 - a. $V_{BE} = V_{BE(on)}$, $I_B > 0$, & $I_C = \beta I_B$
2. Analyze 'linear' circuit.
3. Evaluate the resulting state of transistor.
 - a. If $V_{CE} > V_{CE(sat)}$, assumption is correct
 - b. If $I_B < 0$, transistor likely in cutoff
 - c. If $V_{CE} < 0$, transistor likely in saturation
4. If initial assumption is incorrect, make new assumption and return to Step 2.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 5-17

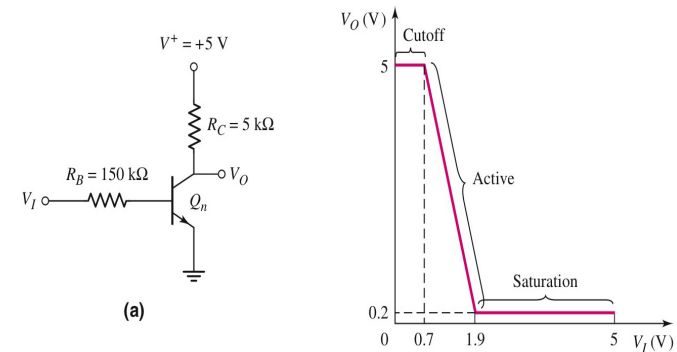Voltage Transfer Characteristic for npn Circuit




Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 5-18

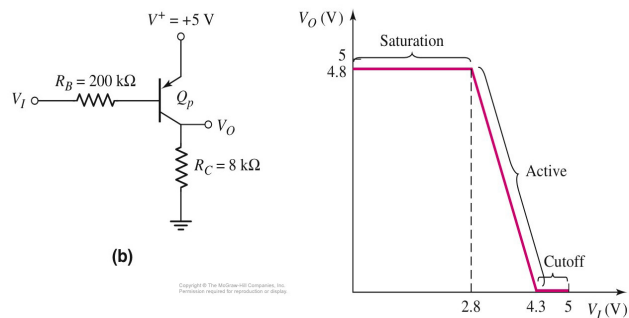Voltage Transfer Characteristic for pnp Circuit




Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 5-19

Digital Logic

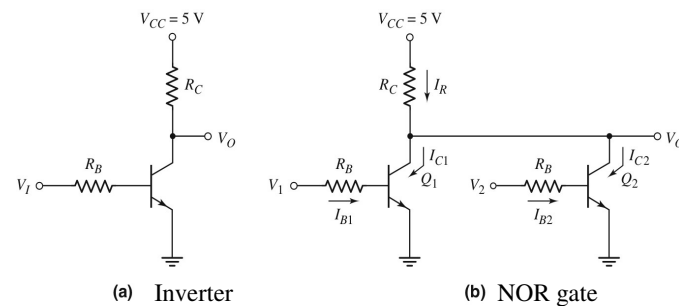


Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 5-20

Bipolar Inverter as Amplifier

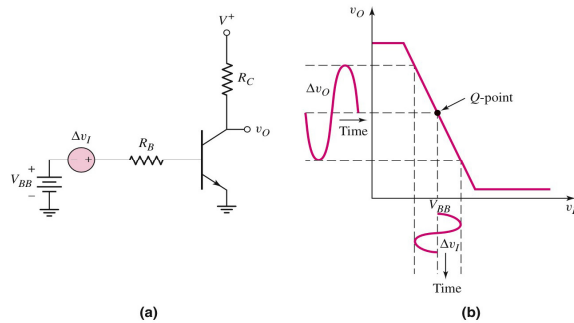


Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 5-21

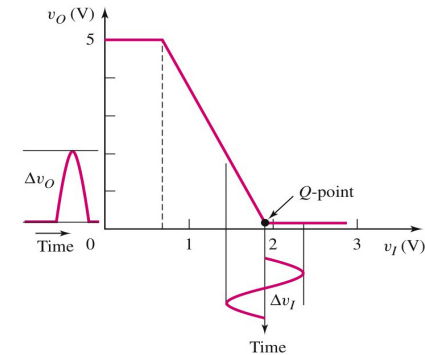Effect of Improper Biasing on Amplified Signal Waveform




Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 5-22

Single Base Resistor Biasing

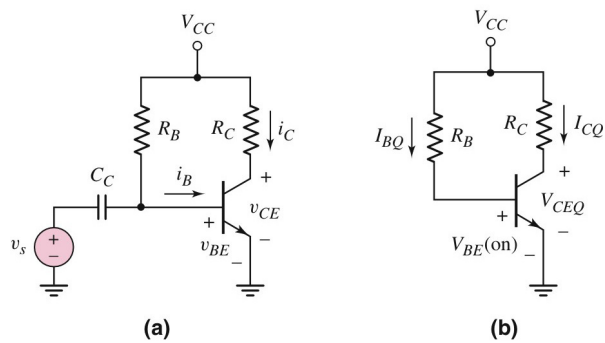


Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 5-23

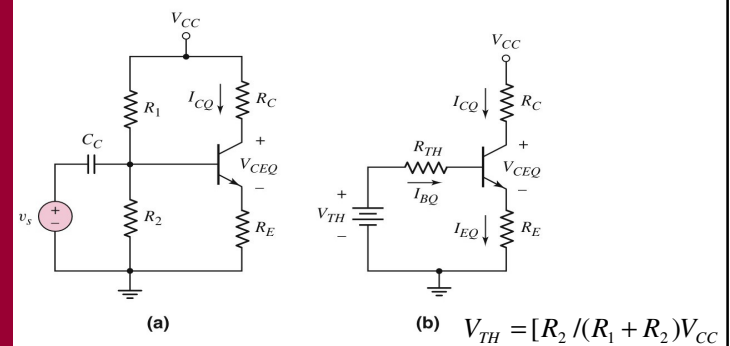Common Emitter with Voltage Divider Biasing and Emitter Resistor



Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 5-24