

Microelectronics Circuit Analysis and Design

Donald A. Neamen

Chapter 3

The Field Effect Transistor

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 3-1

In this chapter, we will:


- Study and understand the operation and characteristics of the various types of MOSFETs.
- Understand and become familiar with the dc analysis and design techniques of MOSFET circuits.
- Examine three applications of MOSFET circuits.
- Investigate current source biasing of MOSFET circuits, such as those used in integrated circuits.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 3-2

Basic Structure of MOS Capacitor

 

Copyright © The McGraw-Hill Companies, Inc.
Permission is granted for reproduction in display.

Copyright © The McGraw-Hill Companies, Inc.
Permission is granted for reproduction in display.


Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 3-3

MOS Capacitor Under Bias: Electric Field and Charge

Parallel plate capacitor

 

Negative gate bias:

Holes attracted to gate

Positive gate bias:


Electrons attracted to gate

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 3-4

 Schematic of n-Channel Enhancement Mode MOSFET




Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 3-5

Basic Transistor Operation

 
Before electron
inversion layer is
formedAfter electron
inversion layer is
formed

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 3-6

Basic Transistor Operation

 


Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 3-7

 Current Versus Voltage Characteristics: Enhancement-Mode nMOSFET




Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 3-8

 Family of i_D Versus v_{DS} Curves: Enhancement-Mode nMOSFET




Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 3-9

p-Channel Enhancement-Mode MOSFET

 


Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 3-10

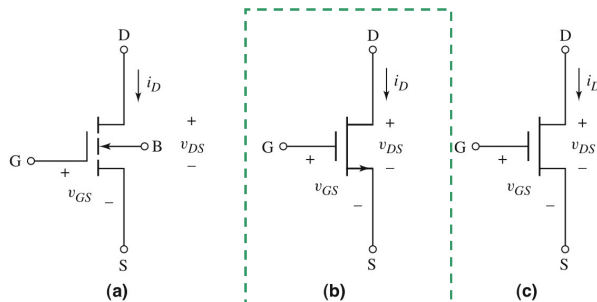Symbols for n-Channel Enhancement-Mode MOSFET




Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 3-11

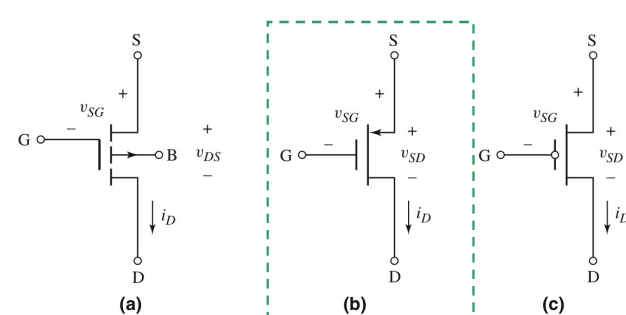Symbols for p-Channel Enhancement-Mode MOSFET




Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 3-12

n-Channel Depletion-Mode MOSFET

 


Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 3-13

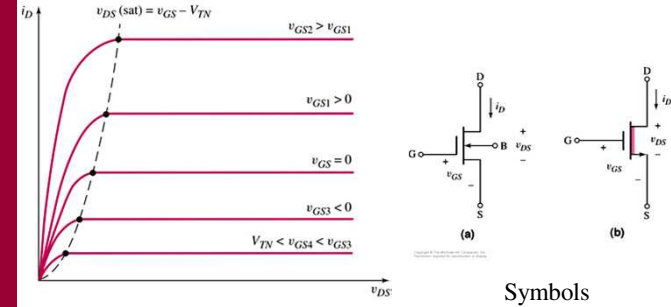Family of i_D Versus v_{DS} Curves: Depletion-Mode nMOSFET




Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 3-14

p-Channel Depletion-Mode MOSFET

 


Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 3-15

Cross-Section of nMOSFET and pMOSFET

 

Both transistors are used in the fabrication of CMOS circuitry.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 3-16

Summary of I-V Relationships

Region	NMOS	PMOS
Nonsaturation	$v_{DS} < v_{DS}(\text{sat})$ $i_D = K_n [2(v_{GS} - V_{TN})v_{DS} - v_{DS}^2]$	$v_{SD} < v_{SD}(\text{sat})$ $i_D = K_p [2(v_{SG} + V_{TP})v_{SD} - v_{SD}^2]$
Saturation	$v_{DS} > v_{DS}(\text{sat})$ $i_D = K_n [v_{GS} - V_{TN}]^2$	$v_{SD} > v_{SD}(\text{sat})$ $i_D = K_p [v_{SG} + V_{TP}]^2$
Transition Pt.	$v_{DS}(\text{sat}) = v_{GS} - V_{TN}$	$v_{SD}(\text{sat}) = v_{SG} + V_{TP}$
Enhancement Mode	$V_{TN} > 0V$	$V_{TP} < 0V$
Depletion Mode	$V_{TN} < 0V$	$V_{TP} > 0V$

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 3-17

Conduction Parameters

NMOSFET

$$K_n = \frac{W\mu_n C_{ox}}{2L} = k'_n \frac{W}{2L}$$

PMOSFET

$$K_p = \frac{W\mu_p C_{ox}}{2L} = k'_p \frac{W}{2L}$$

where:


$$C_{ox} = \epsilon_o / t_{ox}$$

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 3-18

Channel Length Modulation: Early Voltage


 
Copyright © The McGraw-Hill Companies, Inc.
Permission is granted for reproduction or display.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 3-19

Body Effect

  


- Causes an increase in the required threshold voltage
- This is a small effect for a single device and will be ignored

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 3-20

Subthreshold Condition

 

- Small current flows for voltages threshold voltage.
- This is a small effect for a single device and will be ignored.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 3-21

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 3-22

Problem-Solving Technique: NMOSFET DC Analysis


1. Assume the transistor is in saturation.
 - a. $V_{GS} > V_{TN}$, $I_D > 0$, & $V_{DS} \geq V_{DS}(\text{sat})$
2. Analyze circuit using saturation I-V relations.
3. Evaluate resulting bias condition of transistor.
 - a. If $V_{GS} < V_{TN}$, transistor is likely in cutoff
 - b. If $V_{DS} < V_{DS}(\text{sat})$, transistor is likely in nonsaturation region
4. If initial assumption is proven incorrect, make new assumption and repeat Steps 2 and 3.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 3-23

NMOS Common-Source Circuit

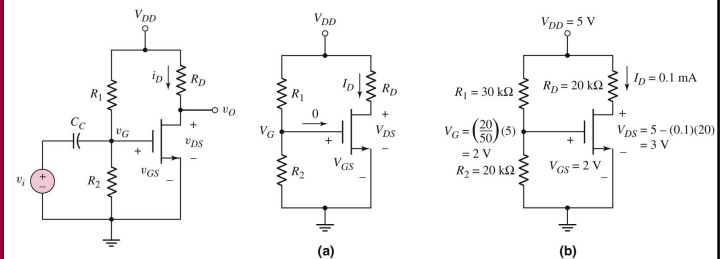


Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 3-24

II MOSFET DC ANALYSIS

A. Common-Source Circuit

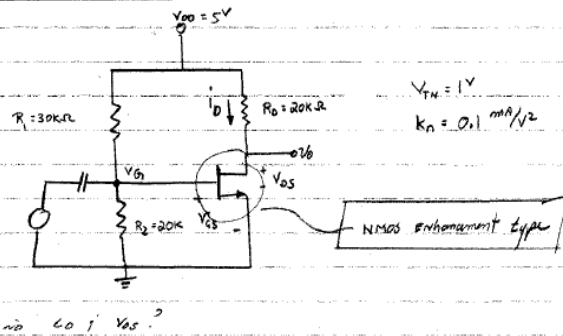

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 3-25

$$\textcircled{1} \quad V_G = V_{GS} = \left(\frac{R_2}{R_1 + R_2} \right) V_{DD} = \left(\frac{20}{20+30} \right) 5 = \textcircled{2V}$$

② Assuming transistor biased in SAT Region:

$$I_D = K_n (V_{GS} - V_{TN})^2 = (0.1)(2-1)^2 = 0.1 \text{ mA}$$

$$V_{DS} = V_{DD} - I_D R_D = 5 - (0.1)(20) = 3V$$


Since: $V_{DS} = 3V > V_{DS(sat)} = V_{GS} - V_{TN} = 2-1 = 1V$, the MOSFET IS INDEED BIASED in SAT REGION.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 3-26

PMOS Common-Source Circuit

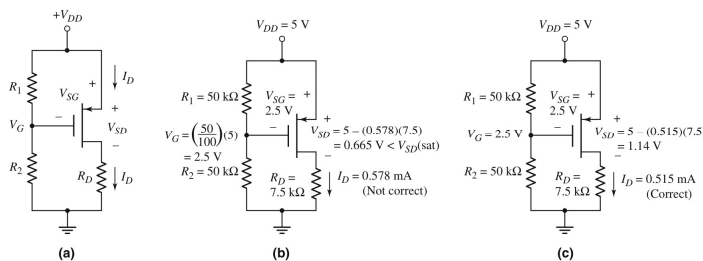


Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 3-27

Ex #2

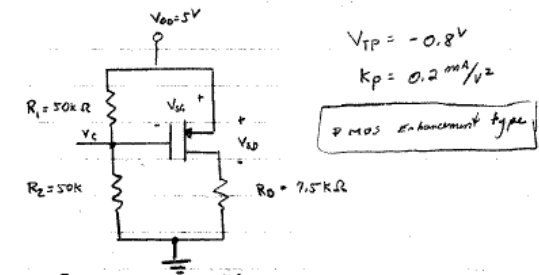

$$V_G = 5 \left(\frac{R_2}{R_1 + R_2} \right) = 5 \left(\frac{50}{100} \right) = 2.5V$$

$$V_{SG} = V_{DD} - V_G = 5 - 2.5 = 2.5V$$

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 3-28

... Assuming SAT: $I_D = K_P (V_{GS} + V_{TP})^2 = 0.2^{mA} (2.5 - 0.8)^2$
 $= 0.578^{mA}$
 ... then: $V_{SD} = V_{DD} - I_D R_D = 5 - (0.578^{mA})(7.5k) = 0.665^V$
 Note: $V_{SD} = 0.665^V < V_{SD(SAT)} = V_{GS} + V_{TP} = 2.5 - 0.8 = 1.7^V$
 ∴ NOT BIASED in SAT Region!

Neamen


Microelectronics, 4e
McGraw-Hill

Chapter 3-29

$I_D = K_P [2(V_{GS} + V_{TP})V_{SD} - V_{SD}^2]$ ← Use Non Sat. EQN.
 $V_{SD} = V_{DD} - I_D R_D$
 $I_D = K_P [2(V_{GS} + V_{TP})(V_{DD} - I_D R_D) - (V_{DD} - I_D R_D)^2]$
 $I_D = 0.2^{mA} [2(2.5 - 0.8)(5 - I_D(7.5k)) - (5 - I_D(7.5k))^2]$
 $= 0.2^{mA} [17 - I_D(25.5k) - (25 + I_D^2(56.25k) - (7.5k)I_D)]$
 $5k I_D = I_D(7.5k - 25.5k) - I_D^2(56.25k) - 8$
 $56.25 \times 10^6 I_D^2 - 44.5k I_D = 8$
 $I_D = 0.515^{mA} \text{ or } 0.276^{mA}$
 ∴ $V_{SD} = 5 - (0.515)7.5 = 1.14^V < V_{SD(SAT)} = 1.7^V$ ← correct solution
 note: $V_{SD} = 5 - (0.276)7.5 = 2.93^V > V_{SD(SAT)}$ ← Not correct solution

McGraw-Hill

 Load Line and Modes of Operation: NMOS Common-Source Circuit



Neamen

Microelectronics, 4e
McGraw-Hill


Chapter 3-31

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 3-32

Enhancement Load Device

 


Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 3-33

2-Input NMOS NOR Logic Gate

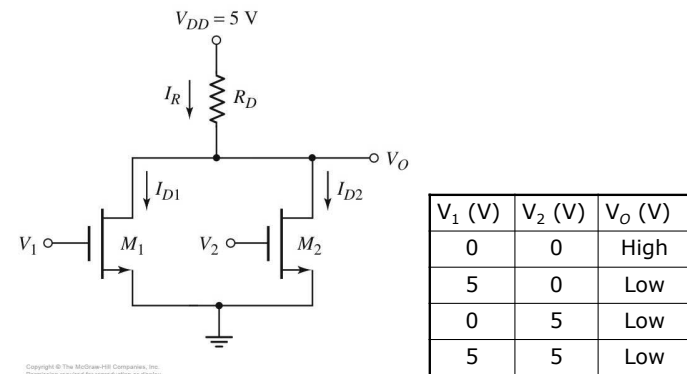


Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 3-34

MOS Small-Signal Amplifier

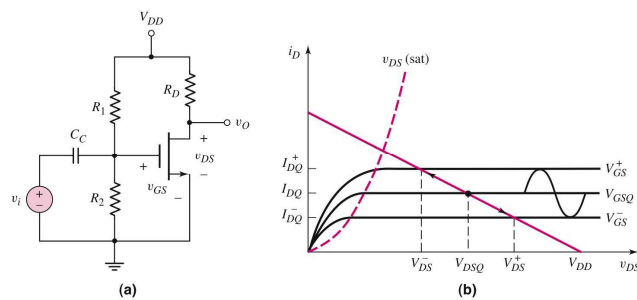


Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 3-35

 Cross Section of n-Channel Junction Field Effect Transistor (JFET)



Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 3-36