

ELEC-313  
Lab 3: Diode Circuits

September 27, 2013

Date Performed: September 25, 2013  
Partners: Charles Pittman  
Stephen Wilson

## Contents

<b>1</b>	<b>Objective</b>	<b>3</b>
<b>2</b>	<b>Equipment</b>	<b>3</b>
<b>3</b>	<b>Schematics</b>	<b>3</b>
<b>4</b>	<b>Procedure</b>	<b>3</b>
4.1	Rectifier . . . . .	3
4.2	Voltage Regulator . . . . .	3
<b>5</b>	<b>Results</b>	<b>3</b>
<b>6</b>	<b>Conclusion</b>	<b>4</b>
<b>7</b>	<b>Equations</b>	<b>4</b>

## List of Figures

1	Circuits used in this lab. . . . .	3
2	Diode characteristics measured in Parts A and B. . . . .	3

## List of Tables

1	Comparison of nominal and measured resistance in Part A. . . .	3
2	Diode characteristics measured in Part B. . . . .	4
3	Diode characteristics measured in Part C. . . . .	4
4	Results from data analysis. . . . .	4

## 1 Objective

The objective is to observe the basic operation of a diode. In addition, the Shockley equation (Eq 2) is used to find the diode's reverse saturation current ( $I_S$ ) and thermal voltage ( $V_T$ ) using values measured in the lab.

## 2 Equipment

Diode: 1N4007	Power supply: HP E3631A
Zener diode: 1N5231	Function generator: HP 33120A
Resistors: $47\ \Omega$	Multimeter: Fluke 8010A
Capacitor: $1\ \mu\text{F}$	Oscilloscope: Agilent 54622D
Resistive decade box: HeathKit IN-3117	

## 3 Schematics

(a) Circuit used for Parts A and Part B.

(b) Circuit used for Part C.

Figure 1: Circuits used in this lab.

## 4 Procedure

### 4.1 Rectifier

### 4.2 Voltage Regulator

## 5 Results

	Nominal ( $\Omega$ )	Measured ( $\Omega$ )	% Difference
$R_1$	470	465.3	1.00

Table 1: Comparison of nominal and measured resistance in Part A.

Figure 2: Diode characteristics measured in Parts A and B.

$R$ ( $\Omega$ )	$V_d$ (V)	$I_d$ (mA)
200	0.751	46.00
500	0.713	18.60
1k	0.682	9.30
2k	0.650	4.70
5k	0.605	1.85
10k	0.571	0.94
20k	0.538	0.47
50k	0.494	0.19
100k	0.464	0.10

Table 2: Diode characteristics measured in Part B.

$V_d$ (V)	$I_d$ (mA)	$V_{OC}$ (V)
0.712	27.2	6.70

Table 3: Diode characteristics measured in Part C.

$m$	$V_T$ (V)	$V_d$ (V)	$I_d$ (mA)	$I_s$ ( $\mu$ A)
21.772	0.046	0.687	10.18	0.325

Table 4: Results from data analysis.

## 6 Conclusion

## 7 Equations

$$\%_{diff} = \frac{|nominal - measured|}{nominal} 100\% \quad (1)$$

$$I_D = I_S \left( e^{\frac{V_D}{V_T}} - 1 \right) \quad (2)$$

$$m = \frac{\ln(I_2) - \ln(I_1)}{V_2 - V_1} = \frac{1}{V_T} \quad (3)$$