

ELEC-313
Lab 2: Diode Characterization

September 23, 2013

Date Performed: September 18, 2013
Partners: Charles Pittman
Stephen Wilson

1 Objective

The objective is to observe the basic operation of a diode. In addition, the Shockley equation (Eq 1) is used to find the diode's reverse saturation current (I_S) and thermal voltage (V_T) using measured values in the lab.

2 Equipment

Diode: 1N4002

Resistors: $330\ \Omega$, $470\ \Omega$, $680\ \Omega$

Resistive decade box: HeathKit IN-3117

Power supply: HP E3631A

Multimeter: Fluke 8010A

3 Schematics

3.1 Circuits Tested

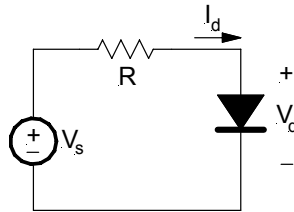


Figure 1: Circuit used for Part A and Part B.

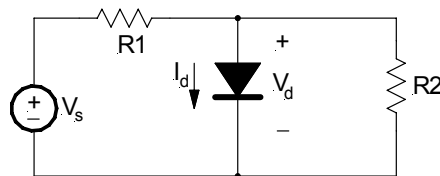


Figure 2: Circuit used for Part C.

4 Procedure

4.1 Part A

The circuit in Figure 1 with $R = 470\ \Omega$ and the power supply as V_S .

4.2 Part B

Lorem ipsum dolor sit amet, consectetur adipiscing elit. Donec hendrerit tempor tellus. Donec pretium posuere tellus. Proin quam nisl, tincidunt et, mattis eget, convallis nec, purus. Cum sociis natoque penatibus et magnis dis parturient montes, nascetur ridiculus mus. Nulla posuere. Donec vitae dolor. Nullam tristique diam non turpis. Cras placerat accumsan nulla. Nullam rutrum. Nam vestibulum accumsan nisl.

4.3 Part C

Lorem ipsum dolor sit amet, consectetur adipiscing elit. Donec hendrerit tempor tellus. Donec pretium posuere tellus. Proin quam nisl, tincidunt et, mattis eget, convallis nec, purus. Cum sociis natoque penatibus et magnis dis parturient montes, nascetur ridiculus mus. Nulla posuere. Donec vitae dolor. Nullam tristique diam non turpis. Cras placerat accumsan nulla. Nullam rutrum. Nam vestibulum accumsan nisl.

5 Results

5.1 Part A

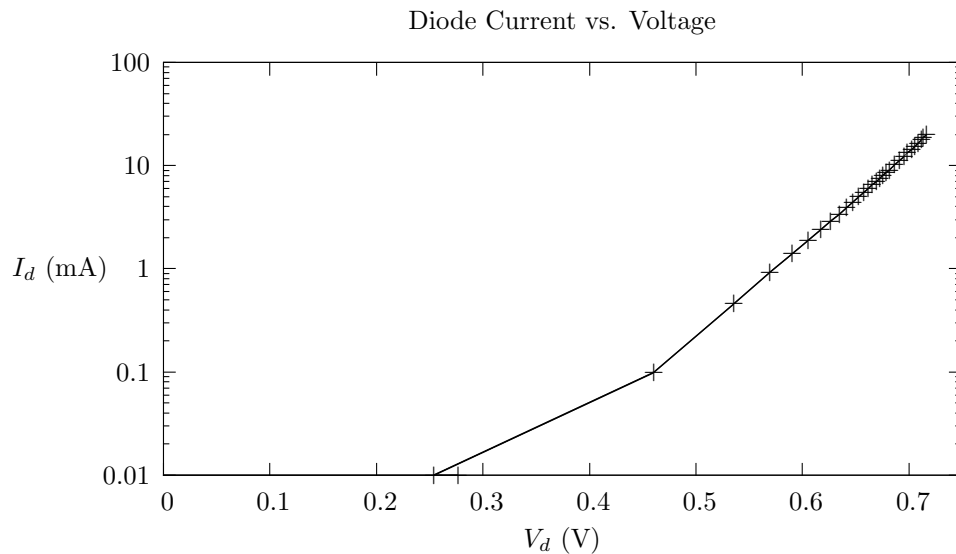


Figure 3: Diode characteristics measured in Part A.

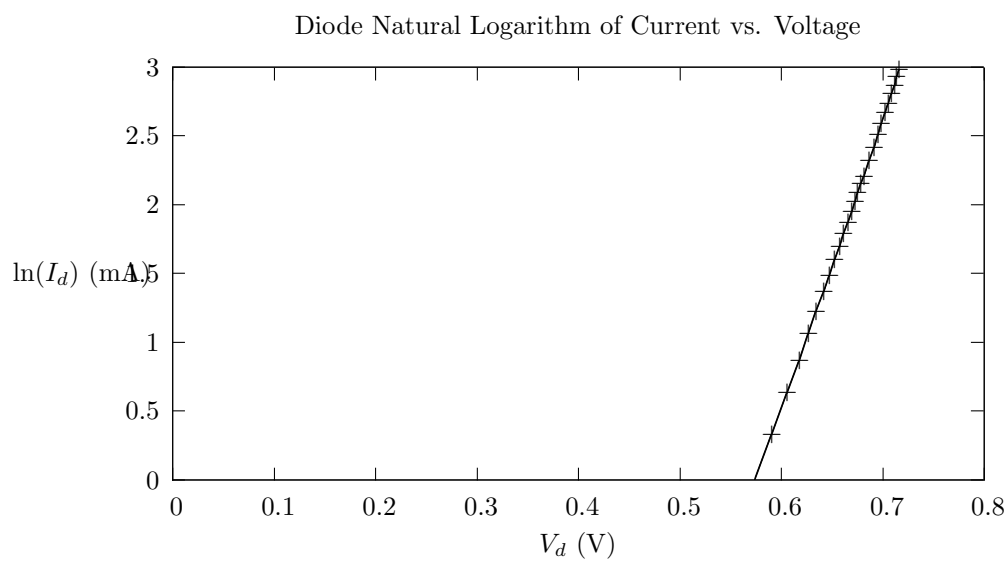


Figure 4: $\ln(I_d)$ vs. V_d .

5.2 Part B

R (Ω)	V_d (V)	I_d (mA)
200	0.751	46.00
500	0.713	18.60
1k	0.682	9.30
2k	0.650	4.70
5k	0.605	1.85
10k	0.571	0.94
20k	0.538	0.47
50k	0.494	0.19
100k	0.464	0.10

Table 1: Diode characteristics measured in Part B.

V_d (V)	I_d (mA)	V_{OC} (V)
0.712	27.2	6.70

Table 2: Diode characteristics measured in Part C.

5.3 Part C

6 Conclusion

7 Equations

$$I_D = I_S \left(e^{\frac{V_D}{V_T}} - 1 \right) \quad (1)$$