ELEC-313 Lab 9: Common-Emitter Transistor Amplifier

November 29, 2013

Date Performed: November 20, 2013 Partners: Charles Pittman

Stephen Wilson

1 Objective

2 Equipment

Transistor: 2N2222A Power supply: HP E3631A

Resistors: $22 \,\mathrm{k}\Omega$, $33 \,\mathrm{k}\Omega$, $220 \,\Omega$ (x2) Capacitor: $0.1 \,\mu\mathrm{F}$

Multimeters: HP 34401A, Fluke 8010A (x2)

- 3 Schematics
- 4 Procedure
- 5 Results

- 6 Conclusion
- 7 Equations