

ELEC-313
Lab 3: Diode Circuits

September 28, 2013

Date Performed: September 25, 2013
Partners: Charles Pittman
Stephen Wilson

Contents

1	Objective	3
2	Equipment	3
3	Schematics	3
4	Procedure	3
4.1	Rectifier	3
4.2	Voltage Regulator	3
5	Results	3
6	Conclusion	3
7	Equations	3

List of Figures

1	Circuits used in this lab.	3
2	AC input vs. DC output of circuit, where $R_L = 10\text{ k}\Omega$	4

List of Tables

1	Comparison of nominal and measured resistance in Part A. . . .	3
2	Diode characteristics measured in Part B.	4
3	Diode characteristics measured in Part C.	4
4	Results from data analysis.	5

1 Objective

The objective is to observe the basic operation of a diode. In addition, the Shockley equation (Eq 2) is used to find the diode's reverse saturation current (I_S) and thermal voltage (V_T) using values measured in the lab.

2 Equipment

Diode: 1N4007

Zener diode: 1N5231

Resistors: 47 Ω

Capacitor: 1 μ F

Resistive decade box: HeathKit IN-3117

Power supply: HP E3631A

Function generator: HP 33120A

Multimeter: Fluke 8010A

Oscilloscope: Agilent 54622D

3 Schematics

(a) Circuit used for Parts A and Part B.

(b) Circuit used for Part C.

Figure 1: Circuits used in this lab.

4 Procedure

4.1 Rectifier

4.2 Voltage Regulator

5 Results

	Nominal (Ω)	Measured (Ω)	% Difference
R_1	470	465.3	1.00

Table 1: Comparison of nominal and measured resistance in Part A.

6 Conclusion

7 Equations

$$\%_{diff} = \frac{|nominal - measured|}{nominal} 100\% \quad (1)$$

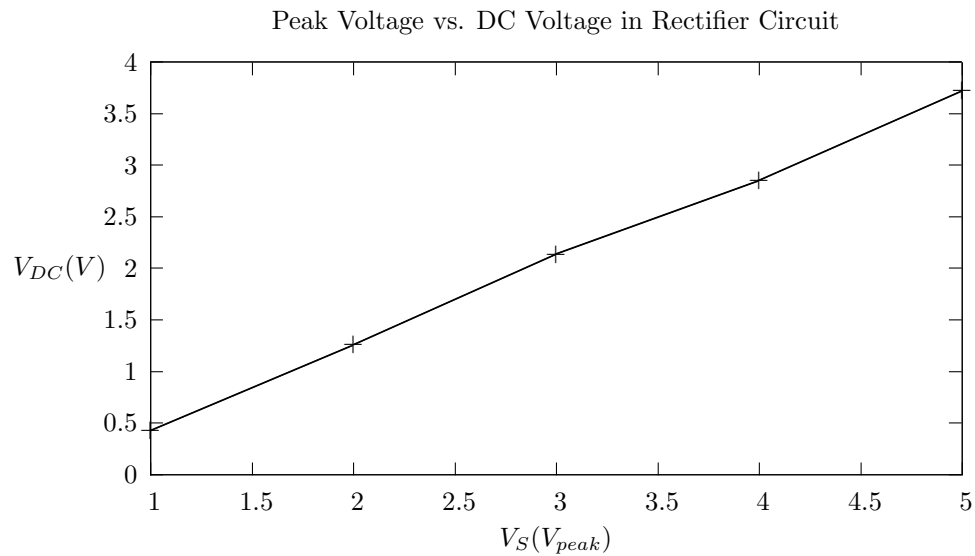


Figure 2: AC input vs. DC output of circuit, where $R_L = 10\text{ k}\Omega$

$R\ (\Omega)$	$V_d\ (V)$	$I_d\ (mA)$
200	0.751	46.00
500	0.713	18.60
1k	0.682	9.30
2k	0.650	4.70
5k	0.605	1.85
10k	0.571	0.94
20k	0.538	0.47
50k	0.494	0.19
100k	0.464	0.10

Table 2: Diode characteristics measured in Part B.

$V_d\ (V)$	$I_d\ (mA)$	$V_{OC}\ (V)$
0.712	27.2	6.70

Table 3: Diode characteristics measured in Part C.

m	V_T (V)	V_d (V)	I_d (mA)	I_s (μ A)
21.772	0.046	0.687	10.18	0.325

Table 4: Results from data analysis.

$$I_D = I_S \left(e^{\frac{V_D}{V_T}} - 1 \right) \quad (2)$$

$$m = \frac{\ln(I_2) - \ln(I_1)}{V_2 - V_1} = \frac{1}{V_T} \quad (3)$$