

1. Find the Q pt.

$$I_{BQ} = \frac{V_{BB} - V_{BE(on)}}{R_B} = \frac{1.2 - 0.7}{5k} = 10 \mu A$$

$$I_{CQ} = \beta I_{BQ} = (100)(10 \mu A) = 1 mA$$

$$V_{CEQ} = V_{CC} - I_{CQ} R_C = 12 - (1)(6) = 6V$$


∴ Q is in forward active mode.

2. Small Signal Hybrid parameters

$$r_{\pi} = \frac{\beta V_T}{I_{CQ}} = \frac{(100)(0.026)}{1 mA} = 2.6 k\Omega$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{1 mA}{0.026} = 38.5 mA/V$$
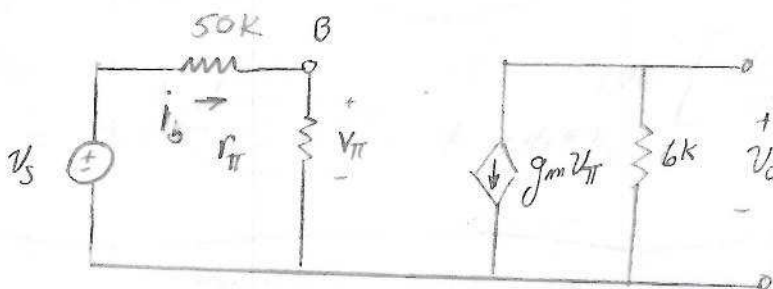
$$A_v = \frac{V_O}{V_S} = - (g_m R_C) \left(\frac{r_{\pi}}{r_{\pi} + R_B} \right) = \underline{\underline{-11.4}}$$



$$V_O = -g_m V_{\pi} R_C$$


$$V_{\pi} = \left(\frac{r_{\pi}}{r_{\pi} + R_B} \right) V_S$$

3. Let $v_s = 0.25 \sin \omega t$ V

then: $i_b = \frac{v_s}{R_B + r_{\pi}} = 4.75 \sin \omega t \mu A$

$i_c = \beta i_b = 0.475 \sin \omega t$ mA

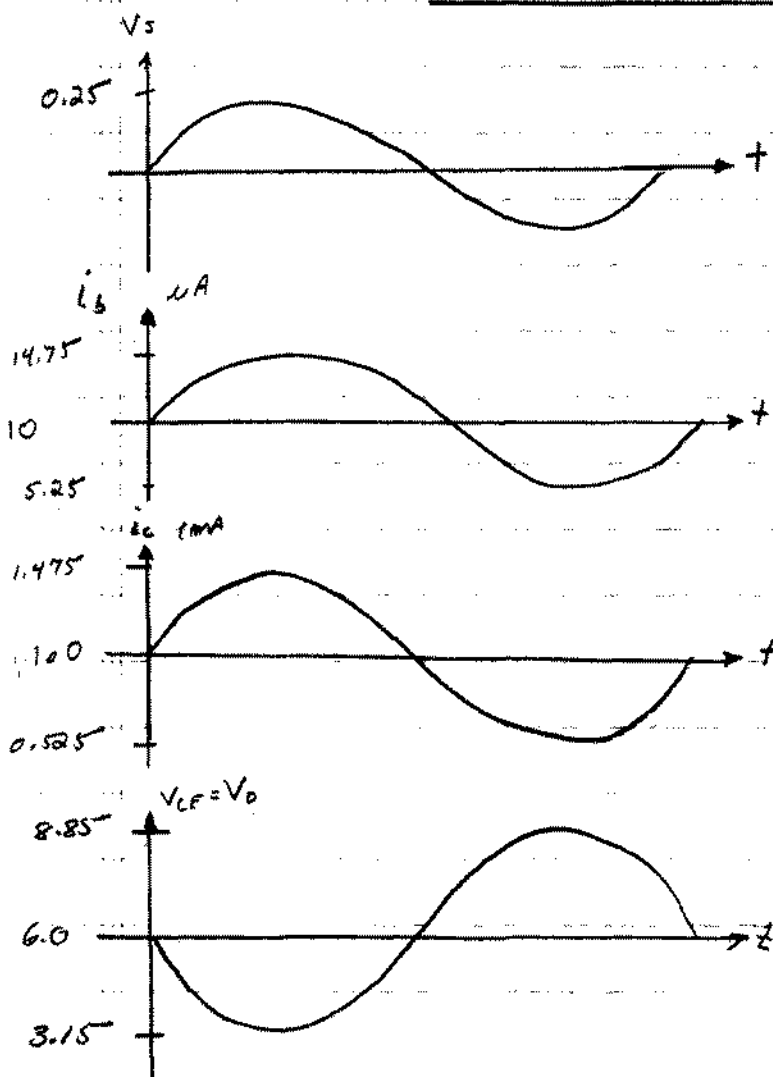$v_{ce} = -i_c R_C = -(0.475) 6 \sin \omega t = \underline{\underline{-2.85 \sin \omega t}} V$



Ex. Using last example: $V_A = 50V$

FIND r_o & A_v

$$r_o = \frac{V_A}{I_{CQ}} = \frac{50}{1 \text{ mA}} = 50 \text{ k}\Omega$$

$$61150 = 5.36$$

$$A_v = \frac{V_o}{V_s} = -g_m (R_C \parallel r_o) \left(\frac{r_\pi}{r_\pi + R_B} \right)$$


$$= -(38.5 \text{ mS}) (5.36 \text{ k}) \left(\frac{2.6}{2.6 + 50} \right) = \underline{\underline{-10.2}}$$

The output resistance r_o reduces the magnitude of A_v . Typically $r_o \gg R_C$, and in many cases can be neglected.

V. Common Emitter Amplifiers

A1

Examp 1

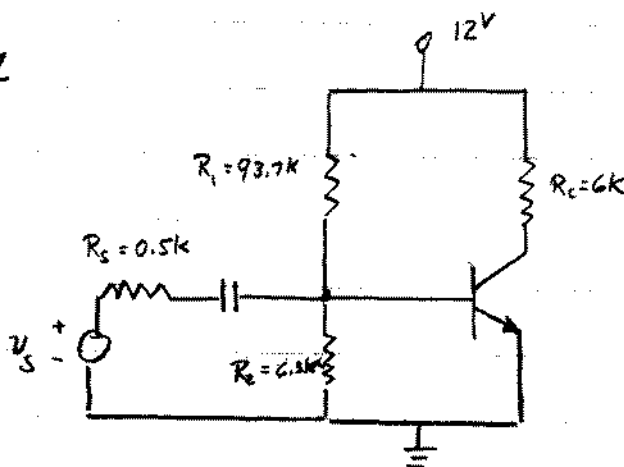

$$V_{BE(on)} = 0.7V$$

$$V_A = 100V$$

$$\beta = 100$$

FIND: Small signal voltage gain.

DC Solution:

$$V_{TH} = \left(\frac{6.3K}{6.3K + 93.7K} \right) 12 = 0.756V$$

$$R_{TH} = R_1 \parallel R_2 = 5.9K \Omega$$

$$I_{BQ} = \frac{0.756 - 0.7}{5.9K} = 9.5 \mu A$$

$$I_{CQ} = \beta I_{BQ} = 0.95 mA$$

$$V_{CEQ} = 12 - (6)(0.95) = 6.31V$$


FWD-ACTIVE ✓

AC Solution:

$$r_{\pi} = \frac{V_T}{I_{BQ}} = \frac{0.026}{9.5 \mu A} = 2.74K \Omega$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{0.95 mA}{0.026V} = 36.5 mA/V$$
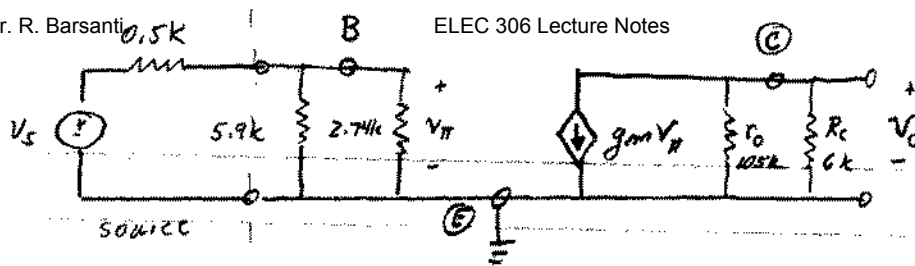
$$r_o = \frac{V_A}{I_{CQ}} = \frac{100}{0.95 mA} = 105K \Omega$$



$$V_o = (-g_m V_{\pi})(r_o \parallel R_L) = -(0.0365)(V_{\pi}) 5.68k = -207 V_{\pi}$$

$$V_{\pi} = V_s \left(\frac{R_{TH}/r_{\pi}}{R_{TH}/r_{\pi} + R_s} \right) = V_s \left(\frac{1.87}{2.37} \right) = 0.79 V_s$$

$$V_o = (0.79)(-207) V_s = -163 V_s \Rightarrow \boxed{A_v = \frac{V_o}{V_s} = -163}$$


Notes: ① $R_i = R_1 \parallel R_2 \parallel r_{\pi} = 1.87k\Omega$, this is relatively small compared to the source resist. $R_s = 0.5k$ and therefore put an appreciable load on the source.

$$\text{e.g. } V_{\pi} \approx 80\% V_s \quad (\text{vice } 99\%)$$

② $R_o = r_o \parallel R_L = 5.68k$ which is relatively high for many loads.

B. Circuit w/ Emitter Resistor

Exerc. 2

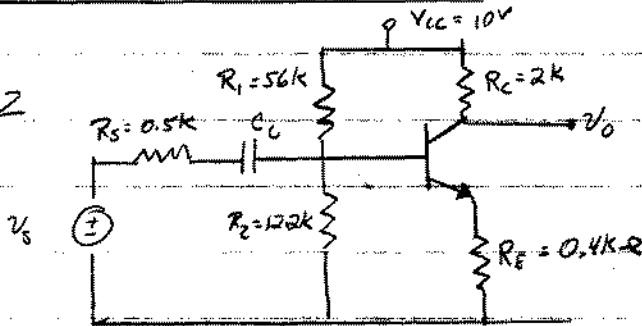

$$\beta = 100$$

$$V_A = \infty$$

$$V_{BE(on)} = 0.7V$$

DC Solution: $V_{TH} = 10 \left(\frac{12.2}{12.2 + 56} \right) = 1.79V$

$$R_{TH} = 12.2 // 56 = 10K$$

KVL: BASE LOOP $\Rightarrow -1.79 + I_B 10K + 0.7 + (\beta + 1) I_B (0.4K) = 0$

$$I_{BQ} = \frac{1.79 - 0.7}{10K + (100 + 1)0.4K} = 21.6 \mu A$$

$$I_{CQ} = \beta I_{BQ} = 2.16 mA$$

KVL: OUTPUT LOOP: $-10 + I_{CQ} 2k + V_{CE} + (\beta + 1) (21.6 \mu A) 0.4K = 0$


$$V_{CE} = 10 - 4.32 - 0.87 = 4.81V$$

Q is in FWD ACTIVE MODE.

Small Signal Solution

$$r_{\pi} = \frac{V_T}{I_{BQ}} = \frac{0.026}{21.6 \mu A} = 1.20 k\Omega$$
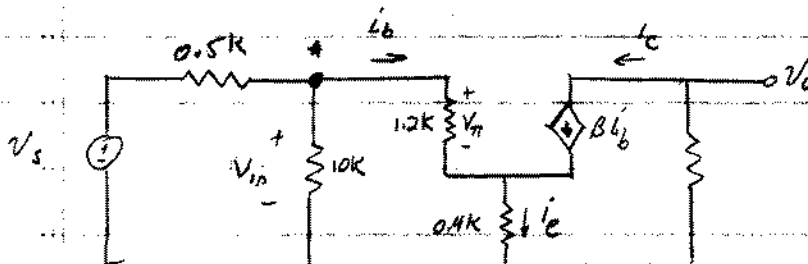
$$g_m = \frac{I_{CQ}}{V_T} = \frac{2.16}{26} = 83.1 \text{ mA/V}, \quad r_o = \frac{V_A}{I_{CQ}} = \infty$$



$$V_O = -\beta i_b R_C$$

Node A: $\frac{V_s - V_O}{0.5k} = \frac{V_{in}}{10k} + \frac{V_{in}}{1.2k + (\beta + 1)0.4k}$

$$V_O \left[\frac{1}{0.5} + \frac{1}{10} + \frac{1}{1.2 + 40.4} \right] = \frac{V_s}{0.5} \Rightarrow V_O = 0.94 V_s$$

$$L_b = \frac{V_{in}}{41.6k} = \frac{V_{in}}{1.2k \times (\beta+1) R_E}$$

$$\therefore A_v = \frac{V_o}{V_s} = \frac{-\beta L_b R_c}{V_{in}/0.94} = \frac{-(100 \times \frac{V_{in}}{41.6k})(2k)}{V_{in}/0.94} = \underline{\underline{-4.52}}$$

Notes: ① $A_v \approx -\frac{R_c}{R_E} = -\frac{2}{0.4} = -5$

② Can you show that for $A_v = \frac{-\beta L_b R_c}{V_{in} R_s + R_s + R_{in} \parallel R_c}$

β	A_v
50	-4.41

100	-4.53
-----	-------

150	-4.57
-----	-------

?

∴ A_v is nearly independent of β due to addition of R_E .


③ The input resistance of the amplifier is also increased so that $V_{in} \approx V_s$. The source is not heavily loaded.

C. Emitter bypass Capacitor

• There are times that the emitter resistor must be large for the purpose of dc design, but the large value degrades the small-signal voltage gain too severely.

• In such a case, an emitter bypass capacitor is used to short out all or part of R_E as seen by the ac signal.

Ex. Test Your Understanding 4.9

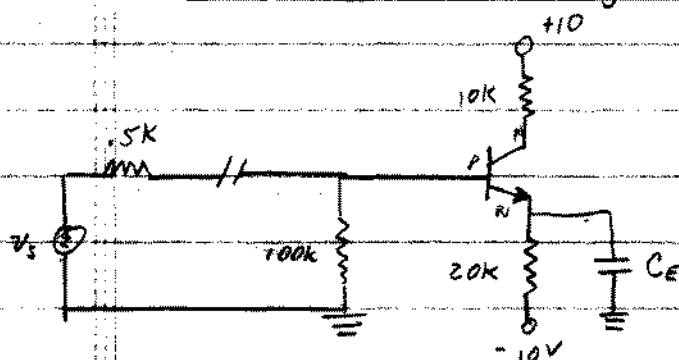

Given: $\beta = 100$

$V_{BE(on)} = 0.7V$

$V_A = 100V$

- a) A_v ? b) R_i seen by source? c) R_o looking back into Amp.

a) DC Analysis

$$\text{B-E Loop: } I_B(100k) + 0.7 + (\beta+1)I_B 20k - 10V = 0$$


$$I_B = \frac{9.3}{100k + 2020k} = 4.4\mu A \Rightarrow I_{CQ} = 0.44mA$$

$$\text{C-E Loop: } -20 + I_{CQ}10k + V_{CEQ} + 20k I_{EQ} = 0$$

$$V_{CEQ} = 20 - 4.4 - 8.8 = 6.8V \Rightarrow \text{FND Active}$$

AC Parameters: $r_{\pi} = \frac{V_T}{I_{BQ}} = 5.9k$, $g_m = \frac{I_{CQ}}{V_T} = 16.9mA/V$

$$r_o = \frac{V_A}{I_{CQ}} = 227k\Omega$$

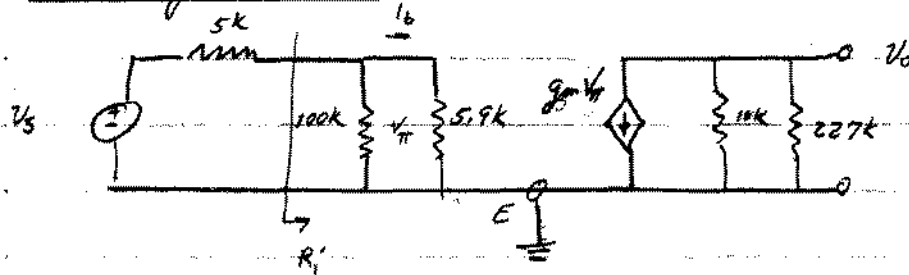Small Signal Model

$$v_o = -g_m v_{\pi} (10k \parallel 227k) = (0.0169)(0.918)v_s (9.58k) = \underline{-148 v_s}$$


$$v_{\pi} = v_s \left(\frac{100k \parallel 5.9k}{100k \parallel 5.9k + 0.5k} \right) = 0.918 v_s$$

$$a) A_v = v_o / v_s = \boxed{-148}$$

$$b) R_{in} = 100k \parallel 5.9k = \boxed{5.58k}$$

$$c) R_o = 10k \parallel 227k = \boxed{9.58k}$$


V. AC LOAD LINE: MAX. Symmetrical Swing

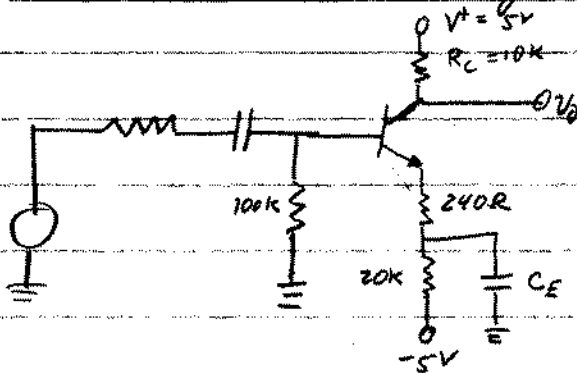

DC LOAD LINE : $-V^+ + I_C R_C + V_{CE} + I_E (R_{E1} + R_{E2}) - V^- = 0$

$$V_{CE} = (V^+ + V^-) - I_C \left[R_C + \left(\frac{1+\beta}{\beta} \right) (R_{E1} + R_{E2}) \right]$$

$$= 10 - I_C (30.24k)$$

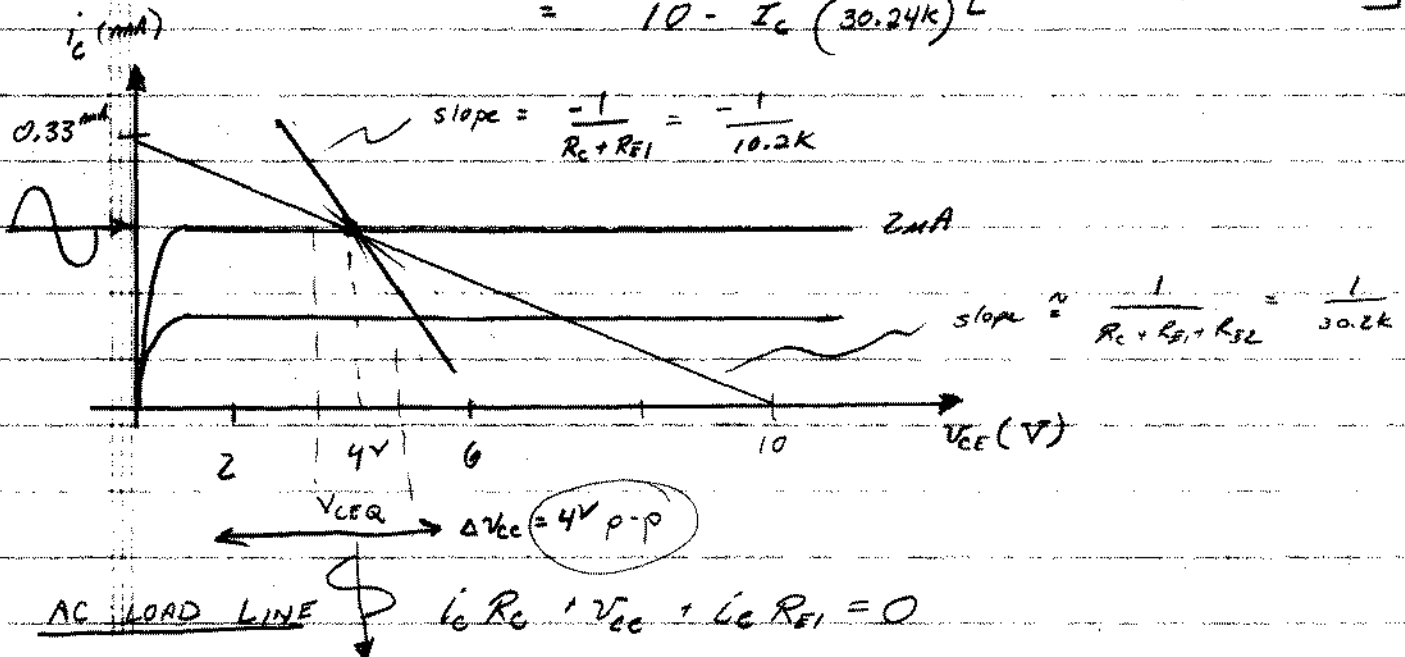

$$I_C = -\frac{V_{CE}}{R_C + R_{E1}} \quad \text{assuming } I_C = I_E$$


note : when $V_{CE} = I_C = 0$ we are at the Q' pte.

MAX Symmetrical Swing $I_{CQ} = \frac{10 - V_{CEQ}}{30.24} = \underline{\underline{0.2 \text{ mA}}}$

$\Delta I_C(\text{max}) = 2(0.2 \text{ mA}) = 0.4 \text{ mA}$ peak-peak

$\Delta V_{CE}(\text{max}) = \Delta I_C(\text{max}) [R_C + R_{E1}] = 4 \text{ V}$ peak-peak
 see load line eg 2 → 6 V

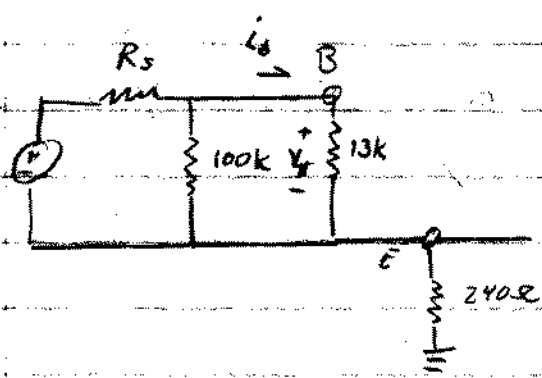
Note: $r_{\pi} = \frac{V_T}{I_{BQ}} = \frac{26 \text{ mV}}{2 \mu\text{A}} = \underline{13 \text{ k}\Omega}$



$V_{BE} = 13 \text{ k}\Omega I_B$
 $\Delta V_{BE(\text{max})} = 13 \text{ k}\Omega \left(\frac{0.4 \text{ mA}}{100} \right)$
 $= \underline{52 \text{ mV}}$

This exceeds the small signal model assumption of $\pm 10 \text{ mV}$ or 20 mV p-p !

Emitter Follower

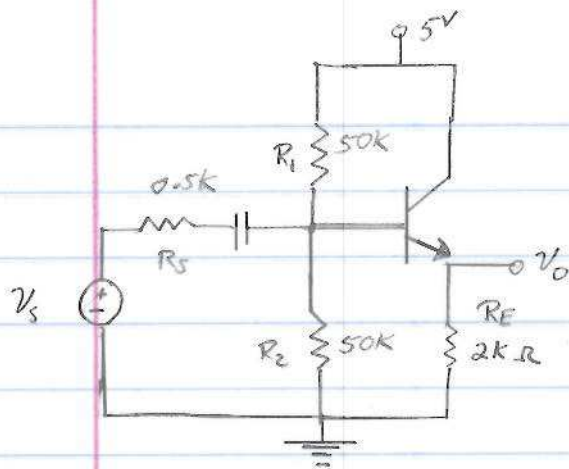

$$\beta = 100$$

$$V_{BE(on)} = 0.7V$$

$$V_A = 80V$$

DC ANALYSIS : $V_{TH} = 5 \left(\frac{50}{50+50} \right) = 2.5V$

$$R_{TH} = 50k \parallel 50k = 25k\Omega$$

$$I_B = \frac{2.5 - 0.7}{25k + (100)2k} = 7.93\mu A$$


$$I_{CQ} = 100 I_B = \boxed{0.793mA}, \quad V_{CEQ} = 5 - 7.93\mu A (100)2k = \boxed{3.4V}$$


AC Parameters: $r_{\pi} = \frac{V_T \beta}{I_{CQ}} = \frac{(0.026)(100)}{0.793mA} = 3.28k\Omega$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{0.793mA}{0.026} = 30.5 \frac{mA}{V}$$

$$r_o = \frac{V_A}{I_{CQ}} = \frac{80}{0.793mA} \cong 100k\Omega$$

AC MODEL

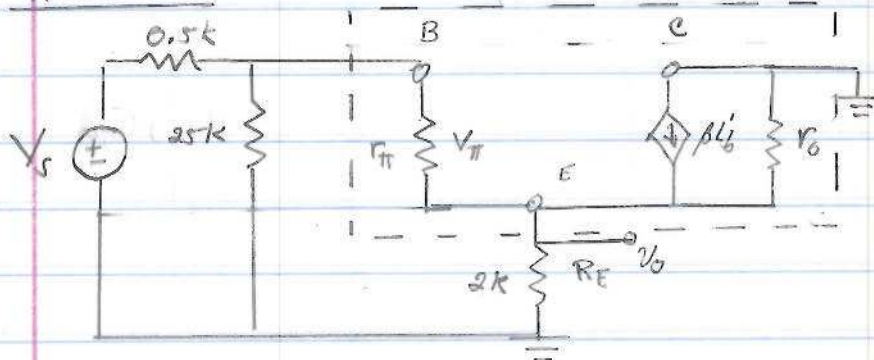

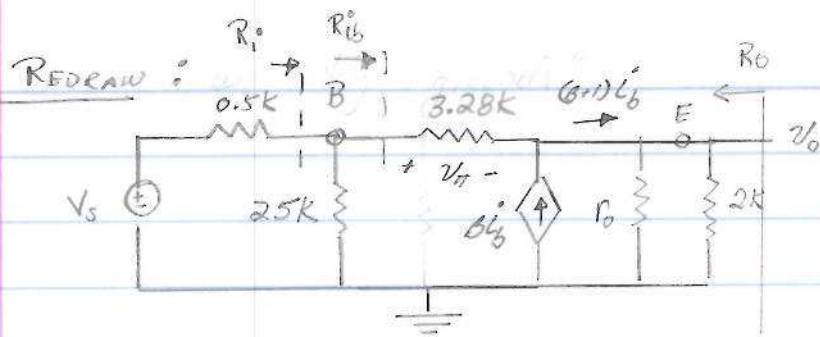

$$R_{ib} = 3.28k + (101)(100k \parallel 2k) = 201k\Omega$$

$$R_i = 25k \parallel R_{ib} = 25k \parallel 201k = 22.2k\Omega$$

$$R_o = \left(\frac{r_{\pi}}{\beta + 1} \right) \parallel r_o \parallel R_E = \frac{3.28k}{101} \parallel 100k \parallel 2k = 32\Omega$$

$$A_v = \frac{v_o}{v_i} = \frac{(1 + \beta)(r_o \parallel R_E)}{r_{\pi} + (1 + \beta)(r_o \parallel R_E)} \cdot \left(\frac{R_i}{R_i + R_s} \right)$$

$$= \frac{(101)(100/2)k}{3.28k + (101)(100/2)k} \left(\frac{22.2}{22.2 + 0.5} \right) = \boxed{0.962}$$

$$A_v^o = (1 + \beta) \left(\frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_{ib}} \right) \left(\frac{r_o}{r_o + R_E} \right)$$

$$= (101) \left(\frac{25k}{25k + 201k} \right) \left(\frac{100k}{100k + 2k} \right) = \boxed{10.9}$$