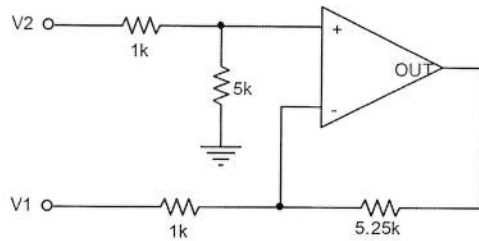


1. For the difference amplifier shown below, determine the CMRR in dB.



By superposition:
$$V_o = \left(\frac{5}{6}\right)\left(1 + \frac{5.25}{1}\right)V_2 + \left(-\frac{5.25}{1}\right)V_1$$

$$= \left(\frac{5}{6}\right)\left(\frac{6.25}{1}\right)V_2 - \left(\frac{5.25}{1}\right)V_1$$

$$= 5.208V_2 - 5.25V_1$$

$$V_{cm} = \frac{V_2 + V_1}{2} \quad V_{cm} = \frac{V_2}{2} + \frac{V_1}{2} \quad \left. \begin{array}{l} \text{By Addition: } V_{cm} + \frac{V_d}{2} = V_2 \\ \text{By Subtraction: } V_{cm} - \frac{V_d}{2} = V_1 \end{array} \right\}$$

$$V_d = V_2 - V_1 \quad \frac{V_d}{2} = \frac{V_2}{2} - \frac{V_1}{2}$$

$$V_o = 5.208\left(V_{cm} + \frac{1}{2}V_d\right) - 5.25\left(V_{cm} - \frac{1}{2}V_d\right)$$


$$= -0.0417V_{cm} + 5.23V_d$$

$$\therefore |A_{cm}| = 0.0417 \quad |A_d| = 5.23$$

$$\therefore CMRR = 20 \log \left(\frac{5.23}{0.0417} \right) = \underline{\underline{42 \text{ dB}}}$$

2. Design an inverting amplifier to provide a nominal closed-loop voltage gain of $A_v=100$ with no more than a 0.5% variance in the gain. The voltage source has an output resistance of $10k\Omega \pm 10\%$. If the rail voltages are $\pm 10V$, determine the range of acceptable input voltages.

$$A_v = -\frac{R_2}{R_1 + R_s}$$

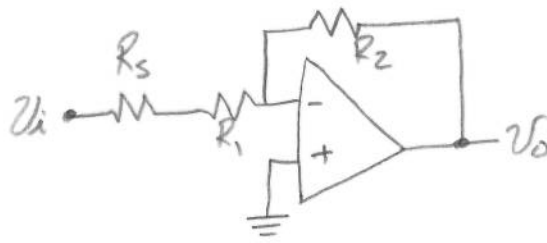

$$R_s = 10k\Omega \pm 10\%$$

$$10\% \text{ of } 10k\Omega = 100\Omega$$

$$\therefore 9.9k < R_s < 10.1k$$

Max gain with $R_s = 9.9k\Omega$

$$0.5\% \text{ of } 100 = 0.5 \Rightarrow 99.5 < A_v < 100.5$$

$$100.5 = \frac{R_2}{R_1 + 9.9} \quad ; \quad 99.5 = \frac{R_2}{R_1 + 10.1}$$

$$100.5(R_1 + 9.9) = 99.5(R_1 + 10.1) \Rightarrow R_1 = \underline{10k\Omega}$$

$$\therefore \underline{R_2 = 2M\Omega}$$

For $V_{o,max} = 10V$ @ largest gain (100.5)

$$V_{i,max} = 99.5mV$$

$$\therefore \underline{-99.5mV < V_{i,max} < 99.5mV}$$