

Designing with FPGAs

ELEC 418

Advanced Digital Systems

Dr. Ron Hayne


Images Courtesy of Thomson Engineering




FPGA Logic Blocks

FIGURE 6-1:

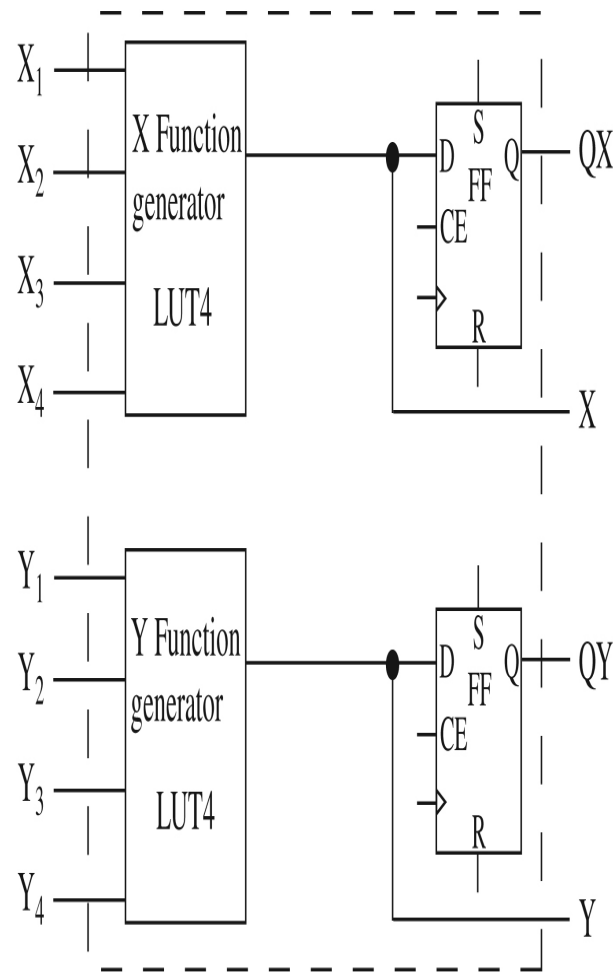(a) Example Building Block for an FPGA; (b) 4-to-1 Multiplexer Using 2-to-1 Multiplexers



(a)
418_06

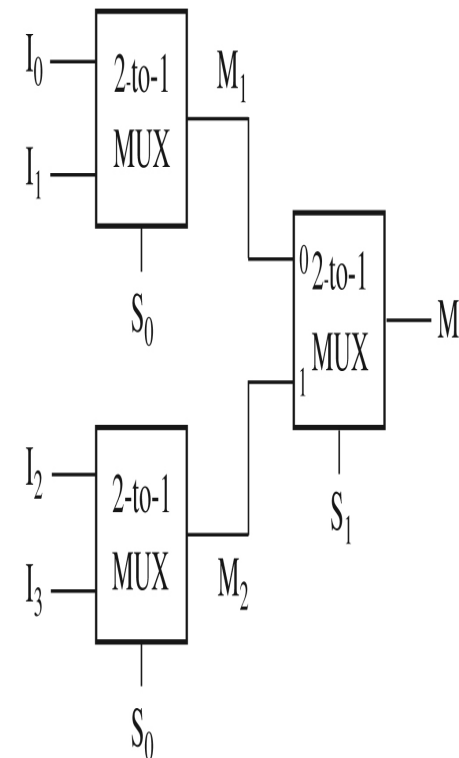

(b)

Implementing Functions

- ◆ **4-to-1 Multiplexer**

- $M = S_1'S_0'I_0 + S_1'S_0I_1 + S_1S_0'I_2 + S_1S_0I_3$


- ◆ **Decomposition into 2-to-1 Multiplexers**

- $M_1 = S_0'I_0 + S_0I_1$


- $M_2 = S_0'I_2 + S_0I_3$

- $M = S_1'M_1 + S_1M_2$

FIGURE 6-1:
(a) Example
Building Block for
an FPGA; (b) 4-to-1
Multiplexer Using
2-to-1 Multiplexers

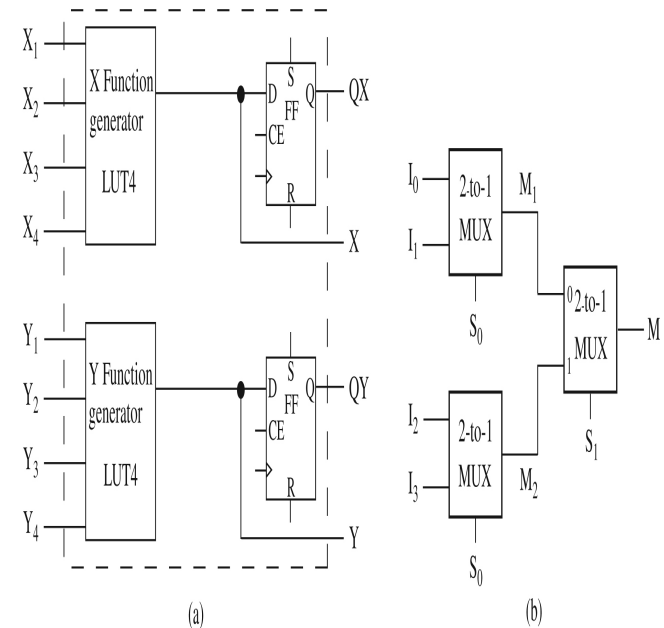

Mapping to Logic Blocks

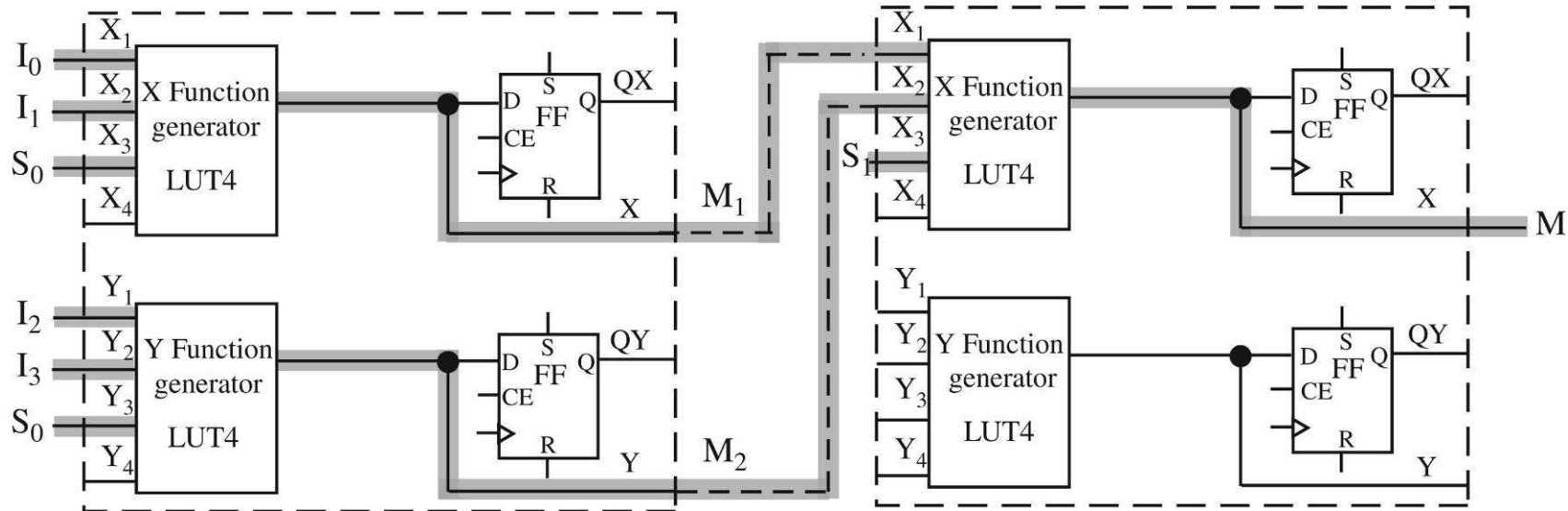

LUT Contents



Inputs				Output
X_4	$X_3 (S_0)$	$X_2 (I_1)$	$X_1 (I_0)$	$X (M_1)$
X	0	0	0	0
X	0	0	1	1
X	0	1	0	0
X	0	1	1	1
X	1	0	0	0
X	1	0	1	0
X	1	1	0	1
X	1	1	1	1

LUT-M1 = 0, 1, 0, 1, 0, 0, 1, 1, 0, 1, 0, 1, 0, 0, 1, 1

Another Example



◆ Ring Counter

FIGURE 6-5:
(a) Circular Shift Register;
(b) Implementation
Using Simple FPGA
Building Block

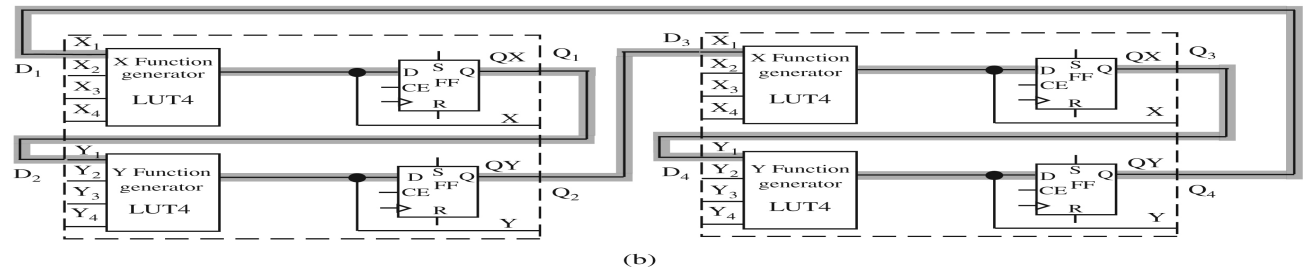 


FPGA Implementation


FIGURE 6-5:
(a) Circular Shift Register;
(b) Implementation
Using Simple FPGA
Building Block

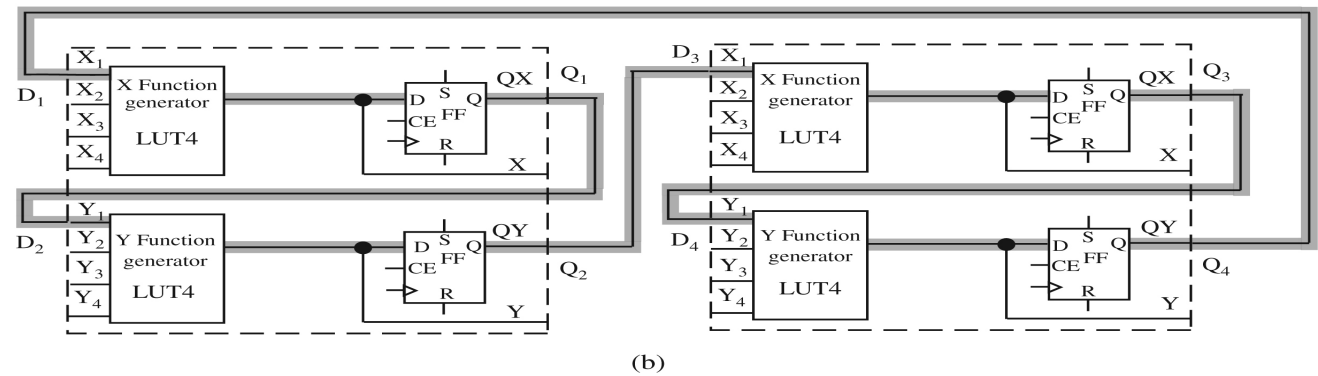 

Xilinx Configurable Logic Block

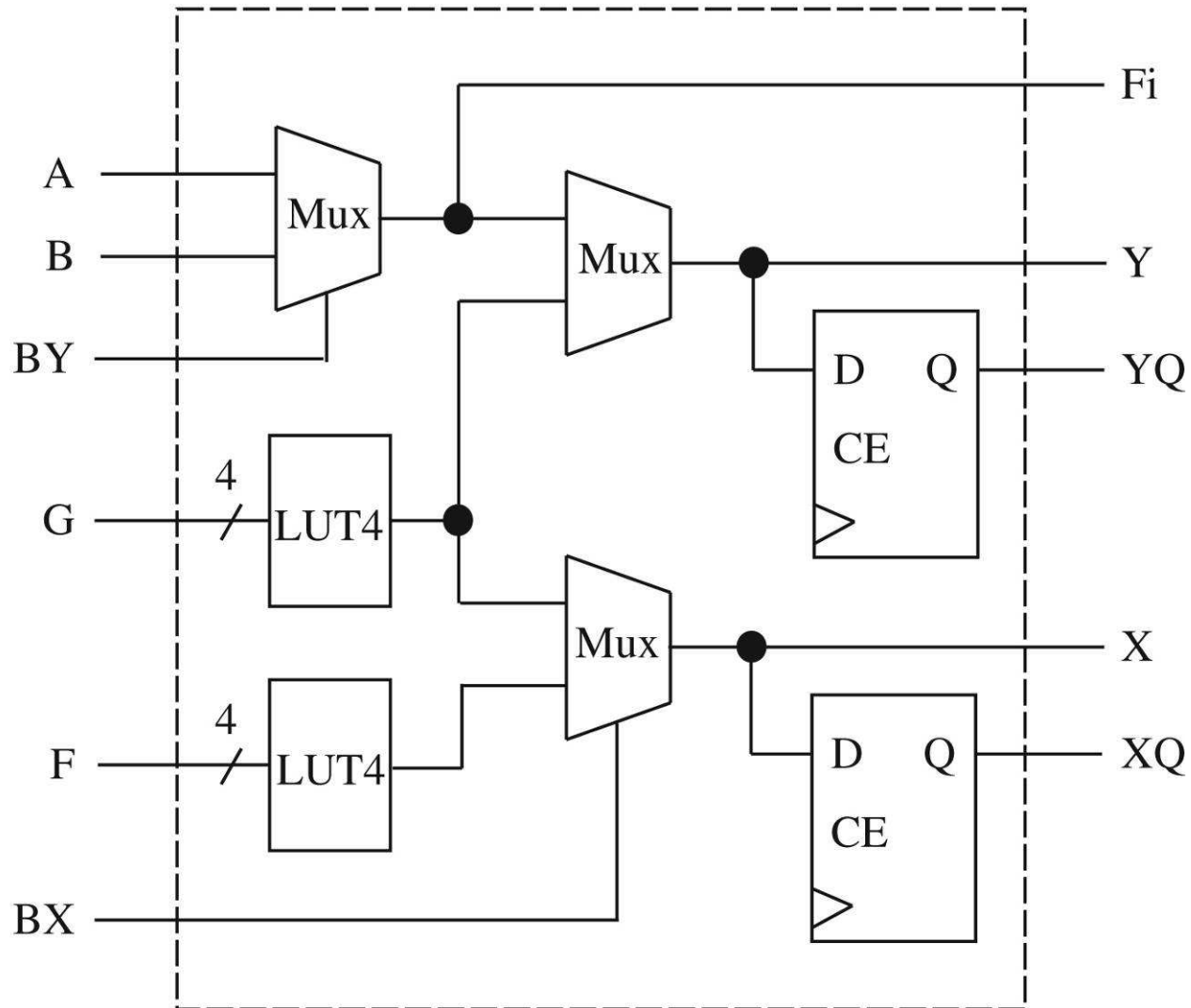


Dedicated Memory in FPGAs

 

Example RAM Sizes

FPGA Family	Dedicated RAM Size (Kb)	Organization
Xilinx Virtex 5	1152–10368	64–576 18Kb blocks
Xilinx Virtex 4	864–9936	48–552 18Kb blocks
Xilinx Virtex-II	72–3024	4–168 18Kb blocks
Xilinx Spartan 3E	72–648	4–36 18Kb blocks
Altera Stratix II	409–9163	104–930 512b blocks 78–768 4Kb blocks 0–9 512Kb blocks
Altera Cyclone II	117–1125	26–250 4Kb blocks
Lattice SC	1054–7987	56–424 18Kb blocks
Actel Fusion	27–270	6–60 4Kb blocks

Memory From LUTs

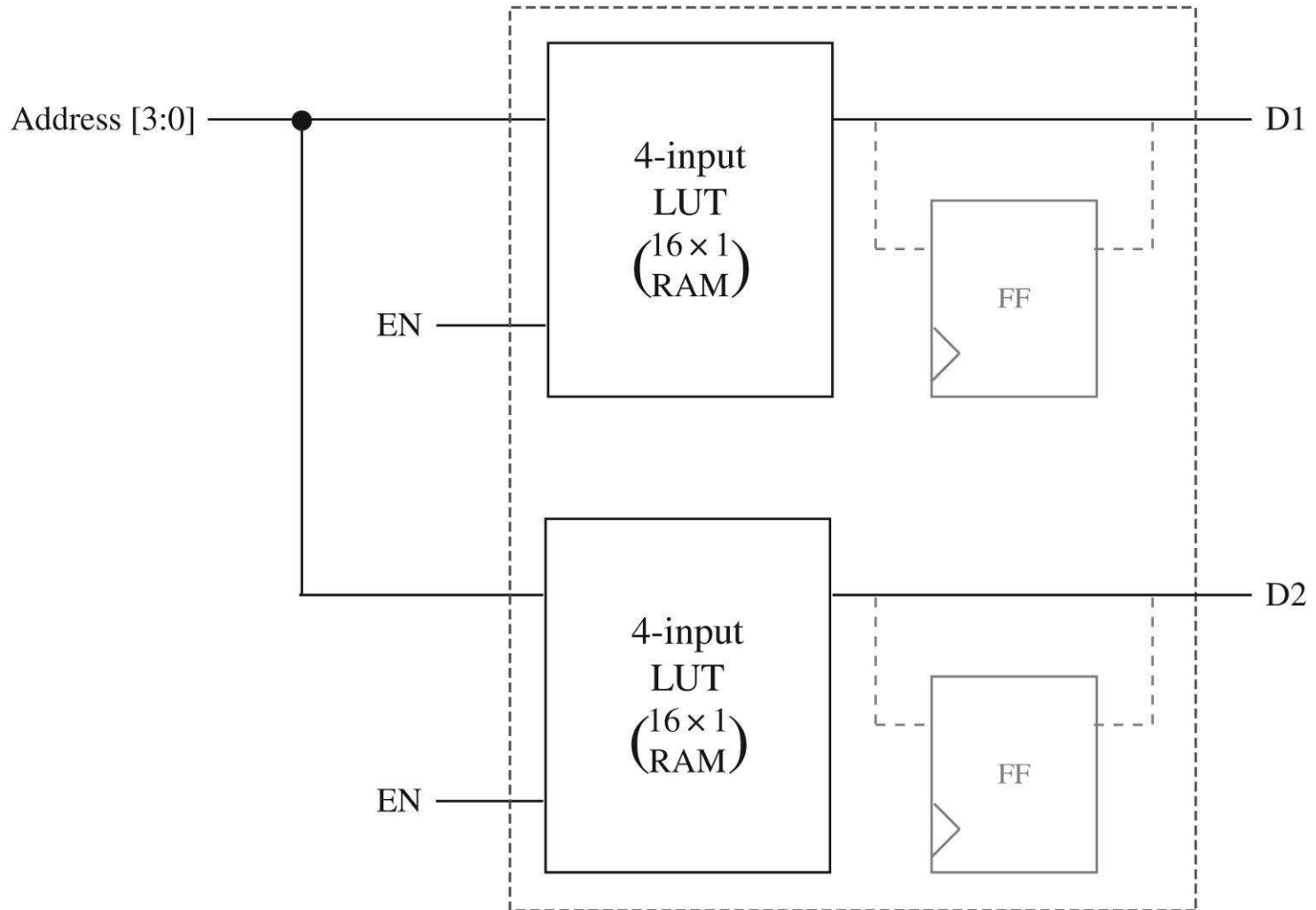

VHDL Models for Memory

- ♦ Synchronous or Asynchronous
- ♦ Synchronous-Write, Asynchronous-Read
 - LUT-Based Memory
- ♦ Synchronous-Write, Synchronous-Read
 - Dedicated (Block) Memory

VHDL Models for Memory

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity Memory is
  port(Address: in  STD_LOGIC_VECTOR(6 downto 0);
        Clk, MemWrite: in  STD_LOGIC;
        Data_In: in  STD_LOGIC_VECTOR(31 downto 0);
        Data_out: out  STD_LOGIC_VECTOR(31 downto 0));
end Memory;
```

LUT-Based Memory

```
architecture LUT of Memory is
    type RAM is array (0 to 127) of
        std_logic_vector(31 downto 0);
    signal DataMEM: RAM;
begin
    process(CLK)
    begin
        if rising_edge(CLK) then
            if MemWrite = '1' then
                DataMEM(conv_integer(Address)) <= Data_In;
            end if;
        end if;
    end process;
    Data_Out <= DataMEM(conv_integer(Address));
end LUT;
```

Dedicated Memory

architecture Dedicated of Memory is

```
    type RAM is array (0 to 127) of
        std_logic_vector(31 downto 0);


    signal DataMEM: RAM;
begin
    process (CLK)
    begin
        if rising_edge(CLK) then
            if MemWrite = '1' then
                DataMEM(conv_integer(Address)) <= Data_In;
            end if;

            Data_Out <= DataMEM(conv_integer(Address));
        end if;
    end process;
end Dedicated;
```

CAD Design Flow

- ♦ **Synthesis (Translation)**
 - **Logic Optimization**
- ♦ **Mapping**
- ♦ **Placement**
- ♦ **Routing**

Self-Correcting Ring Counter

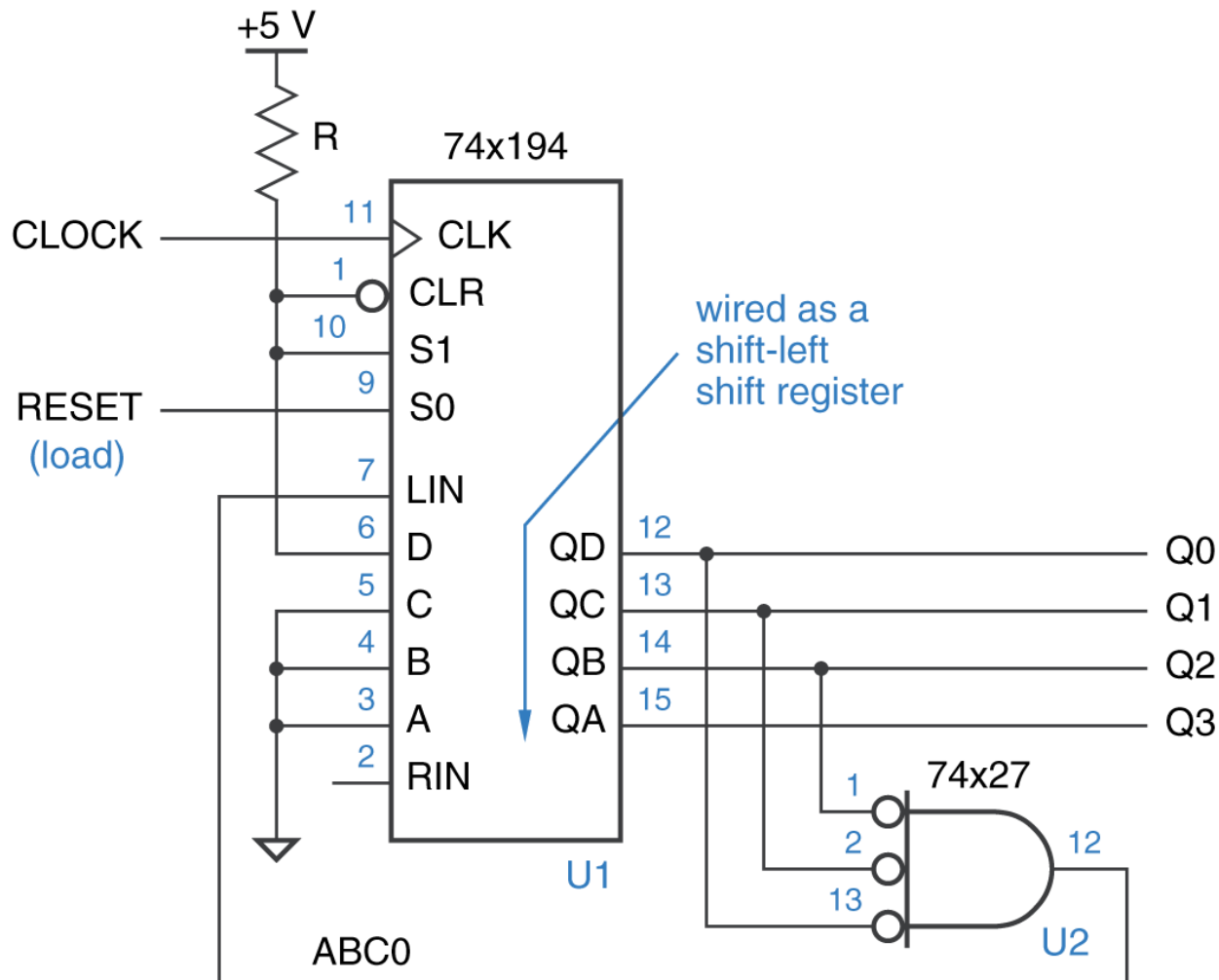

Synthesis Example

```
-- 4-std_logic Self-Correcting Ring Counter
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity RING_COUNT is
    port (CLK, RESET: in std_logic;
          Q : out std_logic_vector(3 downto 0));
end RING_COUNT;

architecture BEHAVE of RING_COUNT is
    signal IQ : std_logic_vector(3 downto 0);
    signal LIN : std_logic;
```

Synthesis Example

```
begin
  LIN <= not IQ(2) and not IQ(1) and not IQ(0);
  process (CLK)
  begin
    if rising_edge(CLK) then
      if RESET = '1' then
        IQ <= "0001";
      else
        IQ <= IQ(2 downto 0) & LIN;
      end if;
    end if;
  end process;
  Q <= IQ;
end BEHAVE;
```

Design Flow Continued

- ◆ **Mapping**

- Process of binding technology-dependent circuits of target technology to technology-independent circuits in the design
 - MUX, ROM, LUT, NAND, NOR


- ◆ **Placement**

- Process of taking defined logic and I/O blocks and assigning them to physical locations


- ◆ **Routing**

- Process of interconnecting the sub-blocks


Mapping

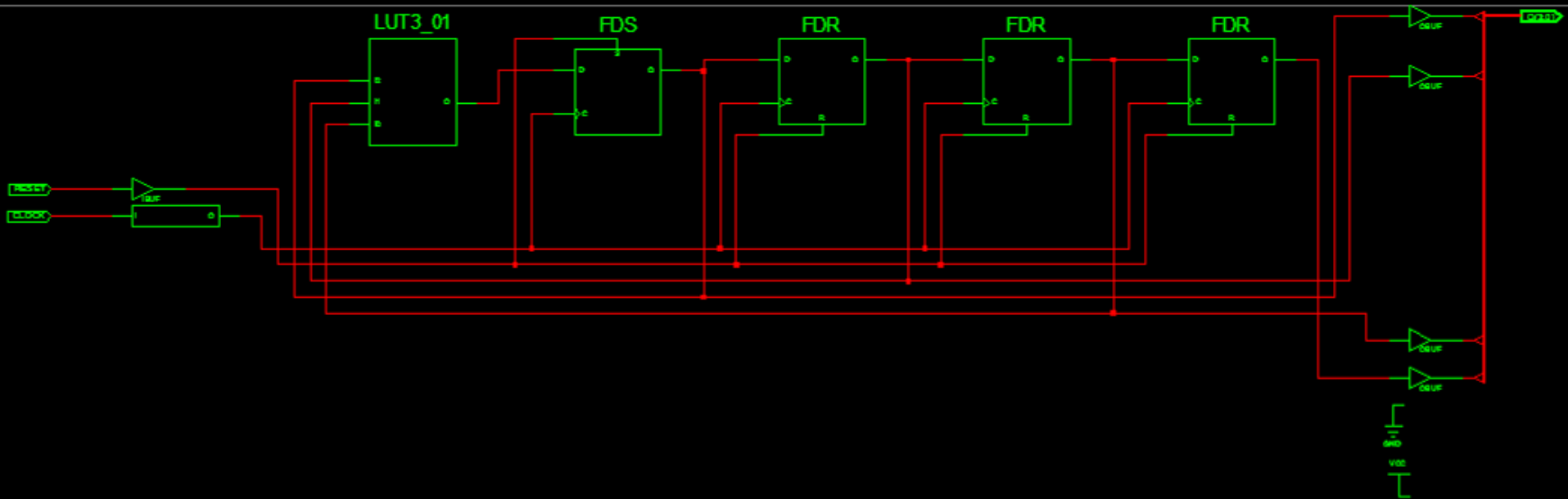

Placement

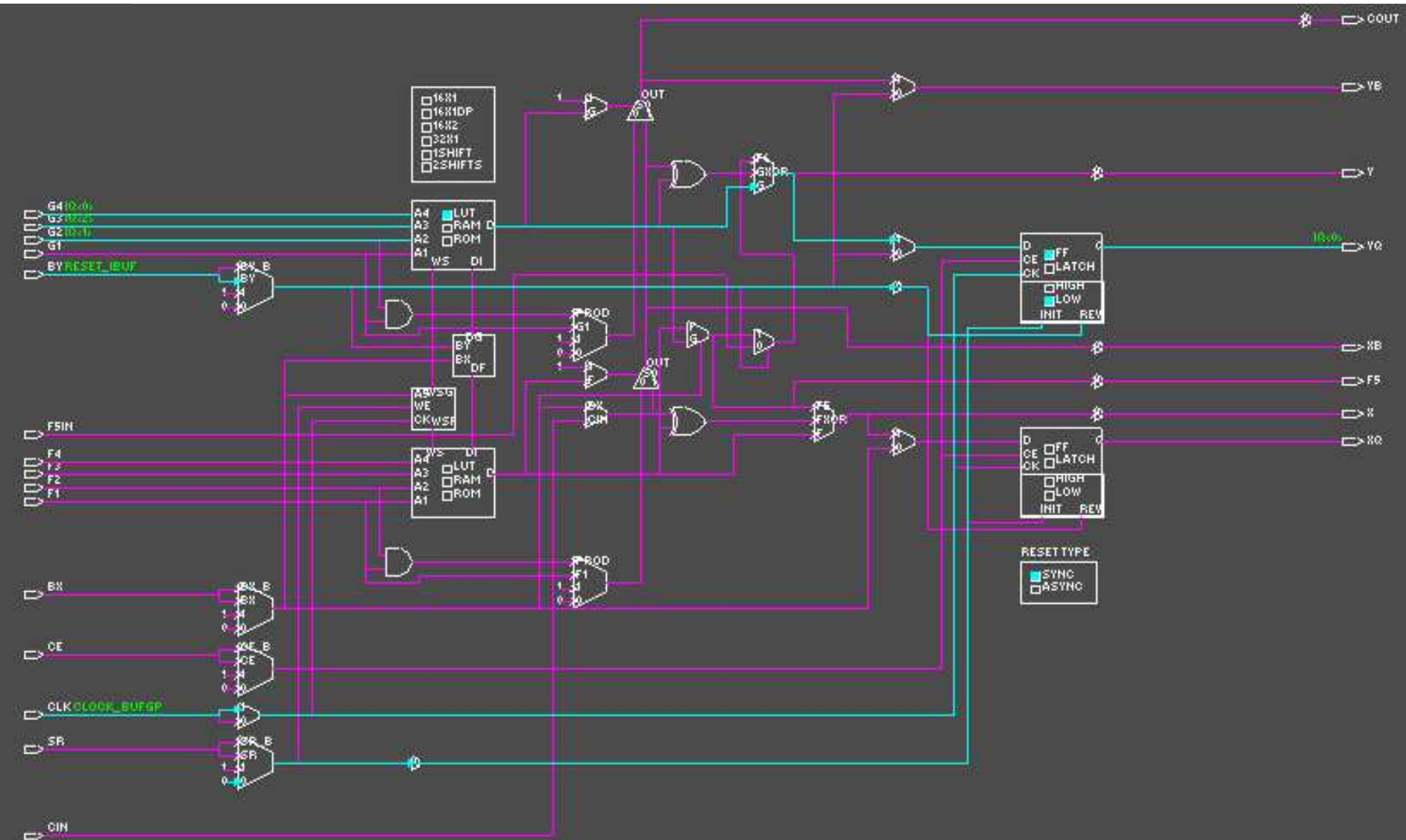

Routing

 

Summary

- ♦ Designing with FPGAs
 - Implementing Functions
 - Memory
 - CAD Design Flow