

ELEC-313  
Lab 2: Diode Characterization

September 18, 2013

Date Performed: September 18, 2013  
Partners: Charles Pittman  
Stephen Wilson

# 1 Objective

## 2 Schematics

Circuit Tested

Test Configuration

## 3 Procedure

## 4 Results

### 4.1 Part A

|       |        |       |
|-------|--------|-------|
| -5.00 | -5.000 | 0.01  |
| -4.50 | -4.500 | 0.01  |
| -4.00 | -4.000 | 0.01  |
| -3.50 | -3.500 | 0.01  |
| -3.00 | -3.000 | 0.01  |
| -2.50 | -2.500 | 0.01  |
| -2.00 | -2.000 | 0.01  |
| -1.50 | -1.500 | 0.01  |
| -1.00 | -1.000 | 0.01  |
| -0.50 | -0.500 | 0.01  |
| 0.00  | 0.277  | 0.01  |
| 0.25  | 0.254  | 0.01  |
| 0.50  | 0.461  | 0.10  |
| 0.75  | 0.536  | 0.46  |
| 1.00  | 0.570  | 0.92  |
| 1.25  | 0.591  | 1.40  |
| 1.50  | 0.606  | 1.89  |
| 1.75  | 0.618  | 2.39  |
| 2.00  | 0.627  | 2.90  |
| 2.25  | 0.635  | 3.41  |
| 2.50  | 0.642  | 3.92  |
| 2.75  | 0.648  | 4.44  |
| 3.00  | 0.653  | 4.95  |
| 3.25  | 0.658  | 5.47  |
| 3.50  | 0.662  | 5.99  |
| 3.75  | 0.666  | 6.51  |
| 4.00  | 0.670  | 7.03  |
| 4.25  | 0.673  | 7.55  |
| 4.50  | 0.676  | 8.08  |
| 4.75  | 0.679  | 8.60  |
| 5.00  | 0.682  | 9.13  |
| 5.50  | 0.687  | 10.18 |
| 6.00  | 0.692  | 11.23 |
| 6.50  | 0.696  | 12.30 |
| 7.00  | 0.699  | 13.36 |
| 7.50  | 0.703  | 14.42 |
| 8.00  | 0.706  | 15.49 |
| 8.50  | 0.709  | 16.56 |
| 9.00  | 0.712  | 17.66 |
| 9.50  | 0.714  | 18.75 |
| 10.00 | 0.717  | 19.84 |

## 5 Conclusion

As shown in Table ??, the amplifier models do closely represent the amplifier used in the experiment. The greatest difference occurred in the current gain ( $A_i$ ), largely due to  $R_o$  being nearly zero. This also causes  $G_m$  to be very large.

## 6 Appendix

### Equations

$$\%_{error} = \frac{|measured - nominal|}{nominal} \times 100\% \quad (1)$$

$$R_o = \frac{V_{noload} - V_{load}}{I_{load}} \quad (2)$$

$$R_i = \frac{V_i}{I_i} \quad (3)$$

$$A_v = \frac{V_o}{V_i} \quad (4)$$

$$A_i = A_v \left( \frac{R_i}{R_o} \right) \quad (5)$$

$$G_m = \frac{A_v}{R_o} \quad (6)$$

$$R_m = A_v R_i \quad (7)$$