

ELEC 302-81
Lab 3
Non-Ideal Transformer Properties

February 6, 2013

Date Performed:	February 4, 2013
Partners:	Rawley Dent Charles Pittman
Instructor:	Dr. Weatherford

1 Purpose of Experiment

In this experiment, the basic characteristics of transformers were studied. Various transformer circuits with different unknown turns ratios were constructed in order to study the different voltage ratios at each particular turns ratio. Other transformer circuits were constructed to observe the similarity between the current ratio and turns ratio, and to observe the saturation curve of a magnetic circuit.

2 Procedure

2.1 EMS Workstation Set-up

At the Lab-Volt EMS workstation, a Fluke multi-meter was used to measure the DC resistance of each transformer winding. These values are recorded in Table 1. The DAI 24V supply was turned on, and the DAI USB connector was connected between the EMS workstation and the PC. On the LVDAM EMS application software, the metering windows for E_1 , E_2 , E_3 , I_1 , and I_2 were opened. The metering windows were set to continuous refresh.

2.2 Transformer Performance

With the main power switch to OFF and the voltage control knob fully counterclockwise (CCW), the voltmeter selector switch was set to position 4-N. The circuit shown in Figure 1 was then constructed. The main power switch was turned to ON and the voltage supply voltage was set to 120V. The primary voltage was recorded from E_1 and the secondary voltage was recorded from E_2 . The values for E_1 and E_2 were then measured and recorded for each winding number listed in Table 2. The main power switch was set to OFF and the voltage control knob was set fully CCW before rewiring the circuit for each winding number. The respective turns ratio for each set of winding number, primary, and secondary voltages was calculated and also listed in Table 2. After completing the requisite measurements, the main power switch was set OFF and the voltage control to fully CCW.

2.3 Open Circuit Test

The circuit shown in Figure 2 was then constructed. The main power switch was set ON and the voltage control knob was slowly adjusted to read 0.4A from I_2 . It was noted that the ammeter I_2 shorted the windings 5-6. Hence, extreme care was given to not exceed the secondary winding current rating of 0.5A. The values for primary voltage E_1 , primary current I_1 , and secondary current I_2 were then measured and recorded, as shown in Table 4. The main power switch was set OFF and the voltage control knob fully CCW.

2.4 Short Circuit Test

The circuit shown in Figure 3 was then constructed. The voltage supply connection was set from 4-N to 4-5. Since the exciting current was small the 300Ω resistor was included and thus the voltage E_3 across the resistor was used to show the current variation. On the PC, the Data Table application was opened and set to record settings from the Options tab. E_1 , E_2 , and E_3 appeared as the columns in the data table. The main power switch was set ON and the supply voltage was then increased in 10V increments from 0–180 volts. At each increment, the Record Data tab was clicked to instantly enter the voltage measurements in the data table. After reaching 180V, the main power switch was set to OFF and the voltage supply control knob was fully CCW. On the PC, the Graph application was opened. E_3 (the exciting current) was set as the x-axis, and E_1 (the applied voltage) as the y-axis. The Line Graph tab was clicked to display the saturation curve of the transformer core.

3 Results

3.1 Transformer Performance

Winding	Resistance
#	Ω
1-2	7.9
5-6	7.9

Table 1: Winding Resistances

Load $Z_L \Omega$	Primary		Input	Secondary		Output
	Voltage $E_1 \text{ V}$	Current $I_1 \text{ A}$	Power $P_1 \text{ W}$	Voltage $E_2 \text{ V}$	Current $I_2 \text{ A}$	Power $P_2 \text{ W}$
∞	119.9	0.027	2.453	119.0	0.003	0
300	119.3	0.388	46.01	112.4	0.368	41.35
$300 + j300$	119.5	0.270	23.63	112.4	0.244	20.20
$300 - j300$	119.5	0.281	27.30	120.0	0.276	23.52

Table 2: Primary and secondary voltages and currents

3.2 Open Circuit Test

Primary Voltage	Current	Input Power
E ₁ V	I ₁ A	P ₂ W
119.7	0.027	2.44

Table 3: Open Circuit

3.3 Short Circuit Test

Primary Voltage	Current	Input Power	Secondary Current
E ₁ V	I ₁ A	P ₁ W	I ₂ A
11.7	0.403	2.607	0.398

Table 4: Data for Fig 3

4 Conclusions

By measuring the resistance of each transformer winding and not getting any extremely high resistance readings similar to an open circuit, it was determined that the transformer windings had no faults and the integrity of the windings were intact.

By measuring the voltage ratios for each particular transformer winding, the turns ratio for that winding was calculated by taking the primary voltage over the secondary voltage. This was one method to determine the turns ratio of an unspecified transformer.

By measuring the current ratio for one set of transformer windings, another method to determine the turns ratio was implemented. By referring to the text *Electric Machinery Fundamentals*, the current ratio of a transformer is inversely proportional to the turns ratio. The relationship states: $\frac{I_p}{I_s} = \frac{N_s}{N_p}$, where I_p is the primary current, I_s the secondary current, N_p the primary winding, and N_s the secondary winding. The ratio of secondary current I_2 over primary current I_1 was the same as the turns ratio calculated and recorded in row 2 of Table 2 pertaining to winding number 5–6. Therefore, the additional method of determining a transformer turns ratio was verified.

By analyzing the saturation curve, it was determined that the transformer core did indeed become saturated. From an applied voltage of 10V to approximately 110V, the saturation curve was linear and the transformer core was unsaturated at this time. A small increase in the magneto-motive force (represented as E_3) resulted in a very large increase in the flux produced (represented as E_1). Then the saturation curve started to level off after an applied voltage of 110V (termed the *knee* of the curve), and therefore the core started to become

saturated. In the saturated region, increases in magneto-motive force produce smaller and smaller increases in flux.

Circuits Tested

Transformer Performance

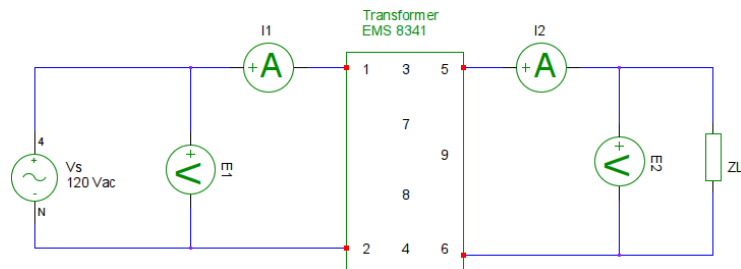


Figure 1: Single Phase Transformer Circuit for part one

Open Circuit Test

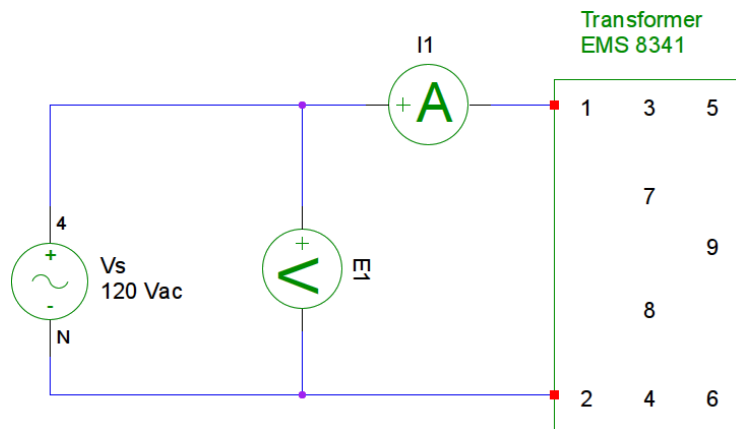


Figure 2: Single Phase Transformer Circuit for part two (open circuit test)

Short Circuit Test

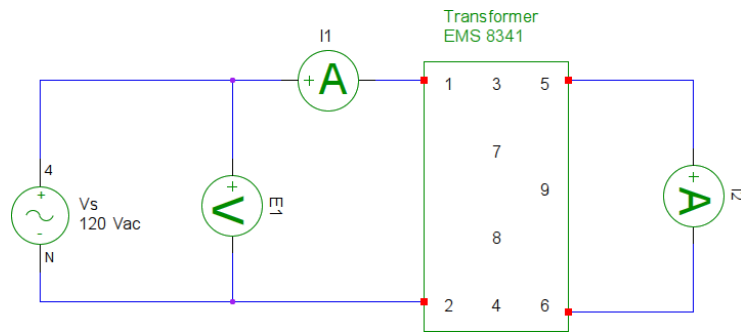


Figure 3: Single Phase Transformer Circuit for part two (short circuit test)