

VHDL for Sequential Logic

ELEC 311


Digital Logic and Circuits

Dr. Ron Hayne

Images Courtesy of Cengage Learning



D Flip-Flop

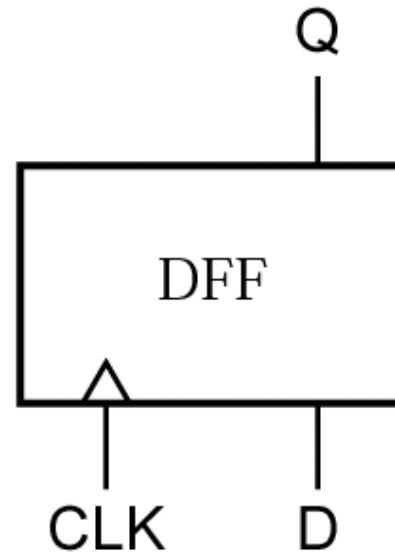

```
process (CLK)
begin
    if CLK'event and CLK = '1' -- rising edge of CLK
        then Q <= D;
    end if;
end process;
```

Asynchronous Clear

```
process (CLK, ClrN)
begin
    if ClrN = '0' then Q <= '0';
        else if CLK'event and CLK = '1'
            then Q <= D;
            end if;
    end if;
end process;
```

Shift Register

```
process (CLK)
begin
    if CLK'event and CLK = '1' then
        if CLR = '1' then Q <= "0000";
        elsif Ld = '1' then Q <= D;
        elsif LS = '1' then Q <= Q(2 downto 0)& Rin;
    end if;
end if;
end process;
```


Counter

```
signal Q: std_logic_vector(3 downto 0);  
-----  
process (CLK)  
begin  
    if CLK'event and CLK = '1' then  
        if ClrN = '0' then Q <= "0000";  
            elsif En = '1' then Q <= Q + 1;  
        end if;  
    end if;  
end process;
```


Design Example

◆ T-bird Tail Lights

- Left Turn
- Right Turn
- Hazard

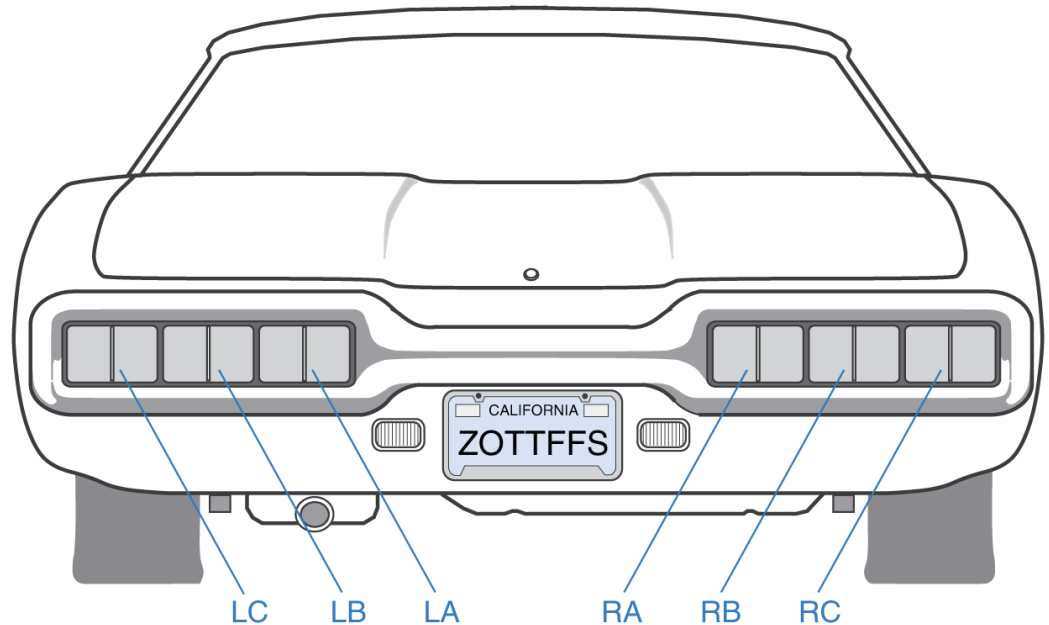


Flashing Sequence

 


Flashing Sequence

◆ Left Turn

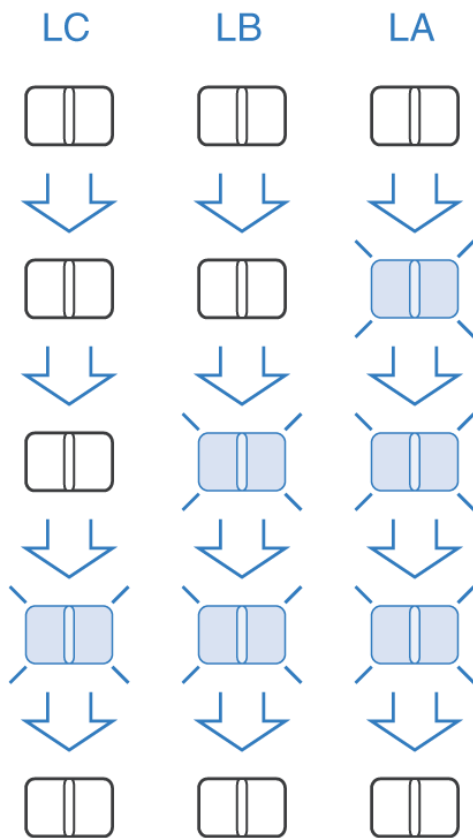

◆ Right Turn

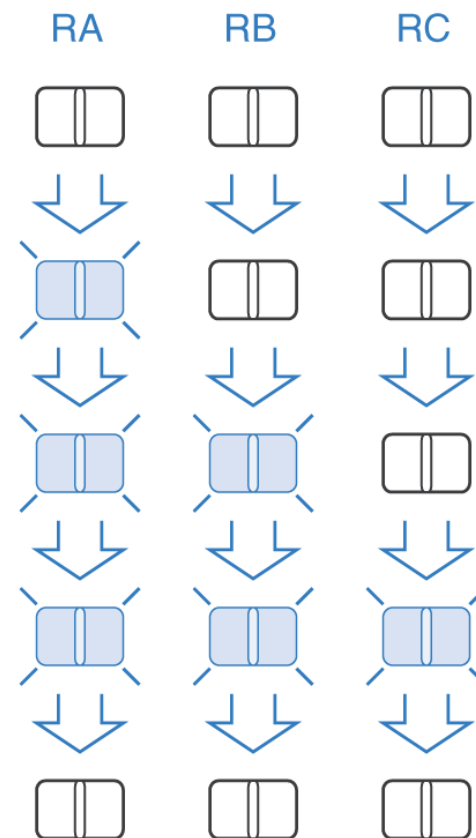


Initial State Graph

- ◆ Mutual Exclusion?
- ◆ All Inclusion?

Output Table

State	LC	LB	LA	RA	RB	RC
IDLE	0	0	0	0	0	0
L1	0	0	1	0	0	0
L2	0	1	1	0	0	0
L3	1	1	1	0	0	0
R1	0	0	0	1	0	0
R2	0	0	0	1	1	0
R3	0	0	0	1	1	1
LR3	1	1	1	1	1	1

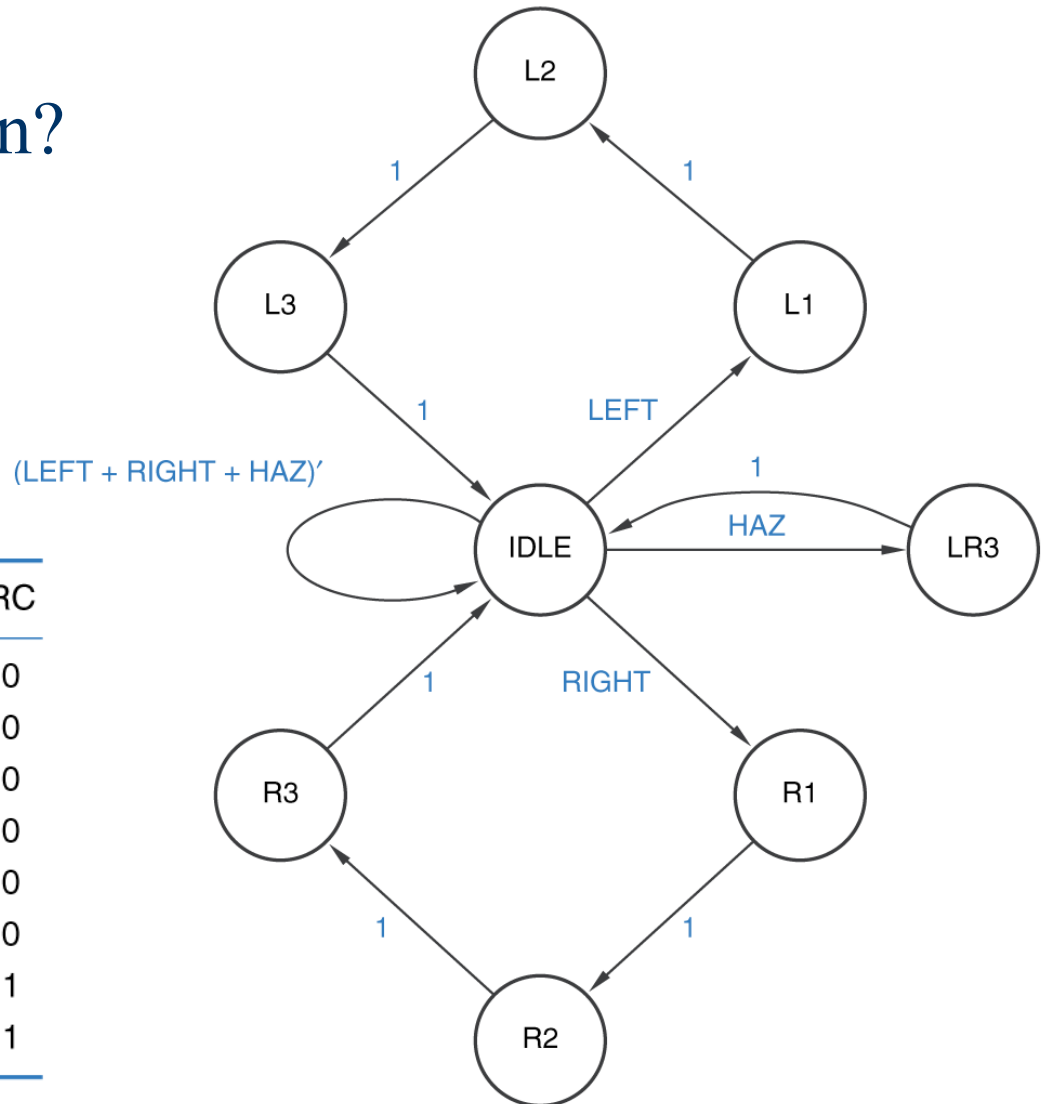


Corrected State Graph

- ◆ Handles multiple inputs asserted simultaneously

Output Table

State	LC	LB	LA	RA	RB	RC
IDLE	0	0	0	0	0	0
L1	0	0	1	0	0	0
L2	0	1	1	0	0	0
L3	1	1	1	0	0	0
R1	0	0	0	1	0	0
R2	0	0	0	1	1	0
R3	0	0	0	1	1	1
LR3	1	1	1	1	1	1

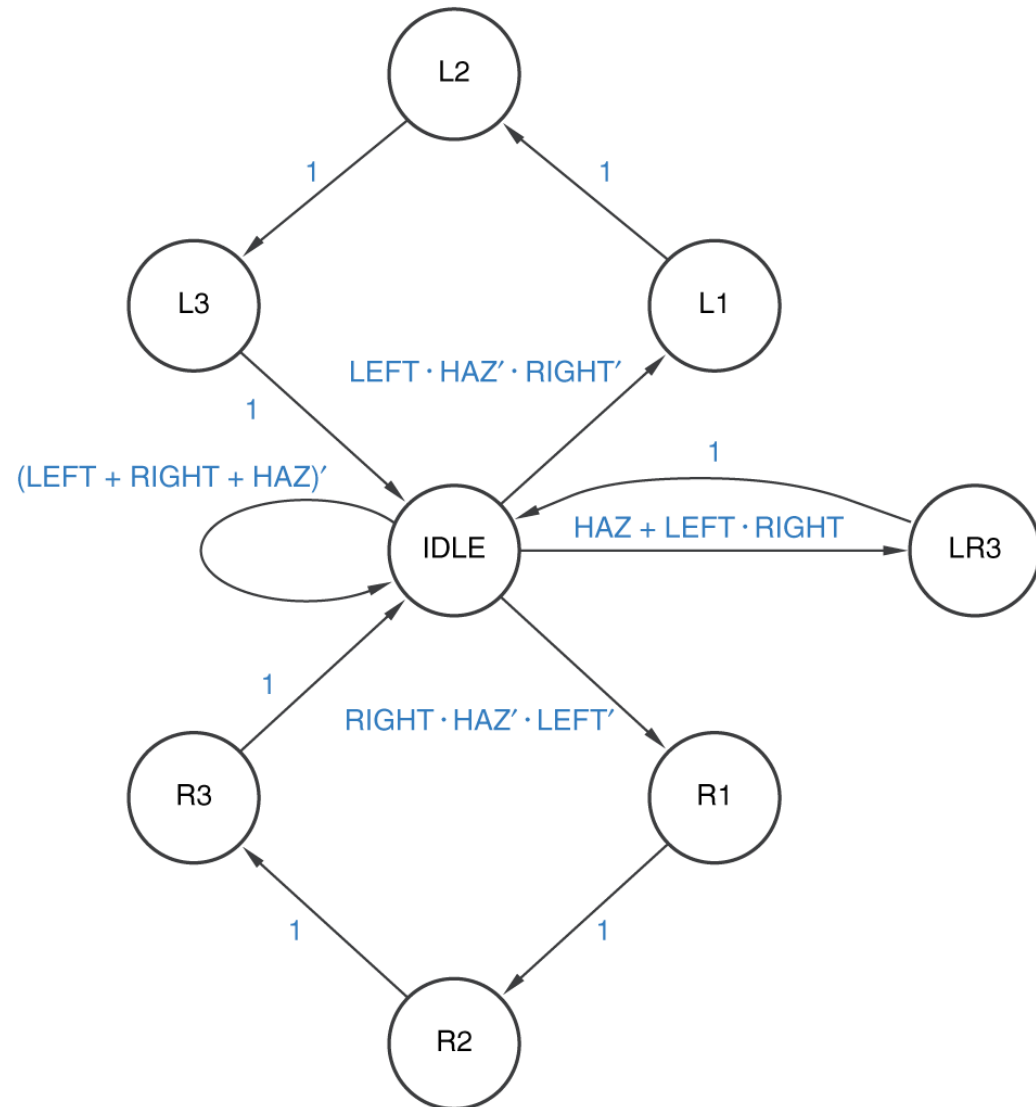


Enhanced State Graph

- ◆ Goes into hazard mode as soon as possible

Output Table

State	LC	LB	LA	RA	RB	RC
IDLE	0	0	0	0	0	0
L1	0	0	1	0	0	0
L2	0	1	1	0	0	0
L3	1	1	1	0	0	0
R1	0	0	0	1	0	0
R2	0	0	0	1	1	0
R3	0	0	0	1	1	1
LR3	1	1	1	1	1	1

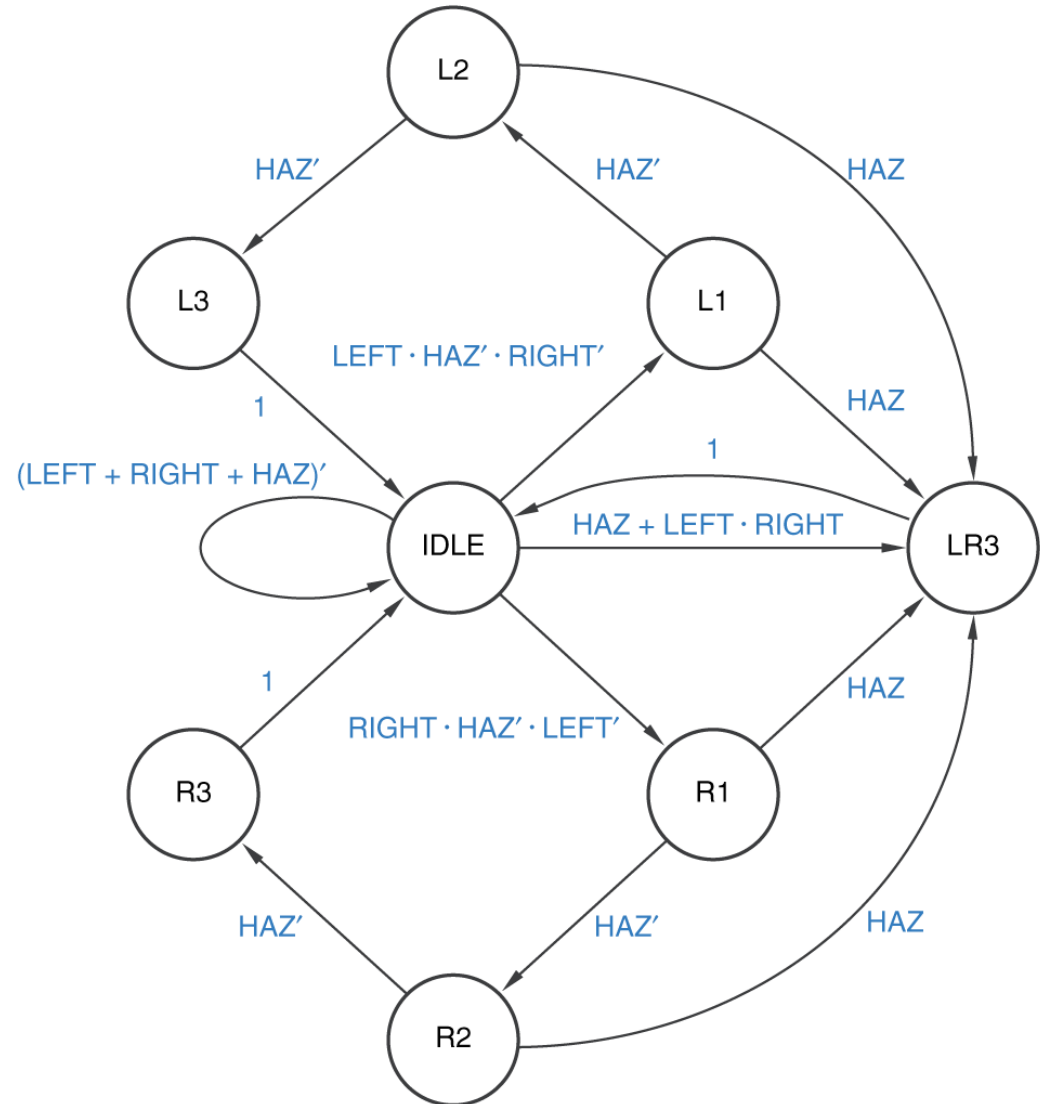

VHDL Model

```
entity TBIRD is
    port (clock, left, right, haz : in  std_logic;
          tail : out  std_logic_vector (1 to 6));
end TBIRD;

architecture BEHAVE of TBIRD is
    type State_type is (IDLE,L1,L2,L3,R1,R2,R3,LR3) ;
    signal State, Next_State: State_type;
    signal input: std_logic_vector(1 to 3);

begin
    input <= left & right & haz;
```

VHDL Outputs

```
with State select
    tail <= "000000" when IDLE,
            "001000" when L1,
            "011000" when L2,
            "111000" when L3,
            "000100" when R1,
            "000110" when R2,
            "000111" when R3,
            "111111" when LR3;
```

VHDL Sequential Machine

```
process (input, State)
begin
    case State is
        when IDLE =>
            case input is
                when "010" => Next_State <= R1;
                when "100" => Next_State <= L1;
                when "--1" => Next_State <= LR3;
                when others => Next_State <= IDLE;
            end case;
        when L1 =>
            case input is
                when "--1" => Next_State <= LR3;
                when others => Next_State <= L2;
```

VHDL Sequential Machine

```
process (SLOW_CLK)
begin
    if SLOW_CLK'event and SLOW_CLK = '1' then
        State <= Next_State;
    end if;
end process;
```

Summary

- ◆ Sequential VHDL
 - process
 - if-then-else
 - case
- ◆ Design Example